

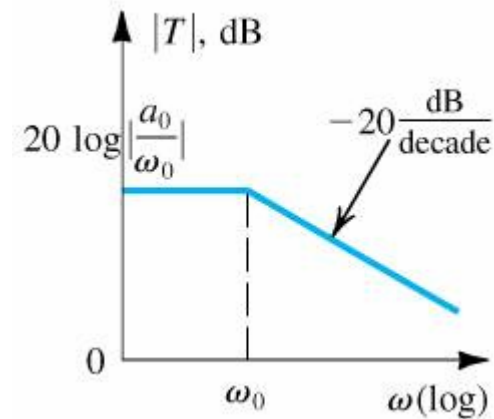
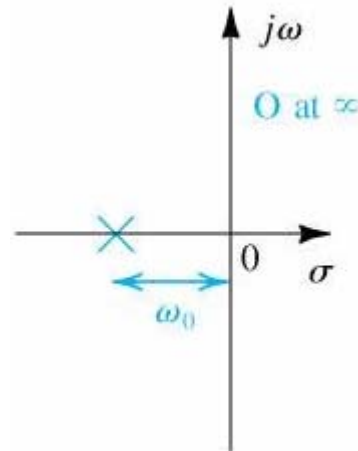


Lect. 17: Higher-Order Filters (S&S 12.1-3)

First-Order LP Filter

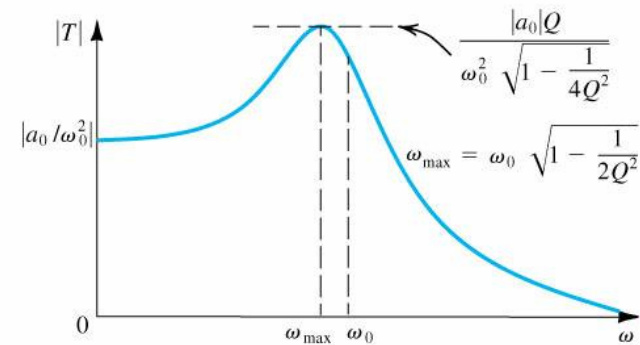


Second-Order LP Filter

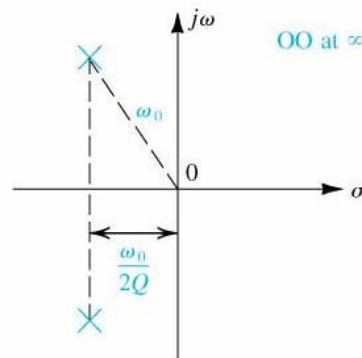


Lect. 17: Higher-Order Filters

Examples of
Fifth-Order LP Filter



(many other possibilities)

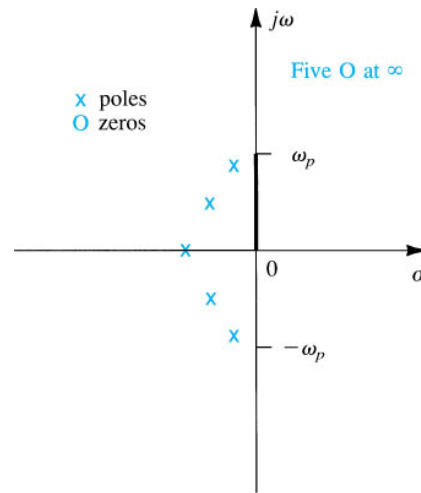

(b)

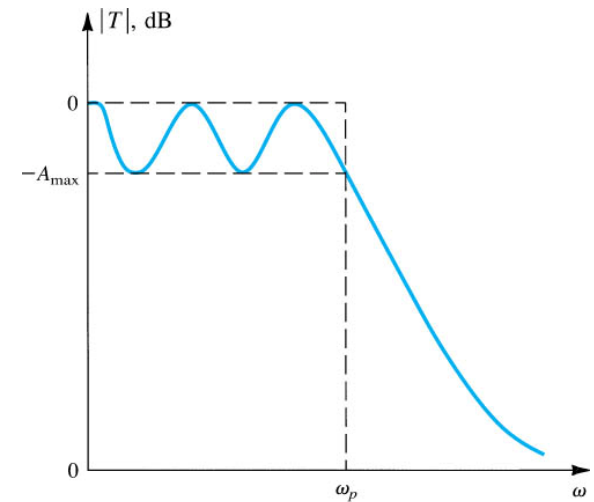


(a)

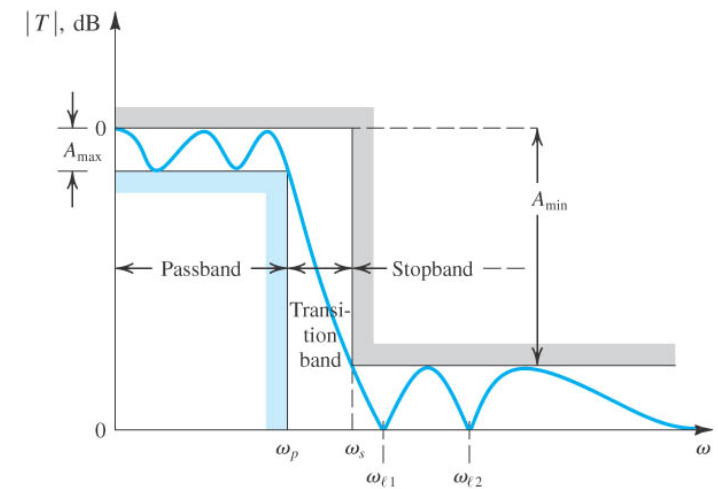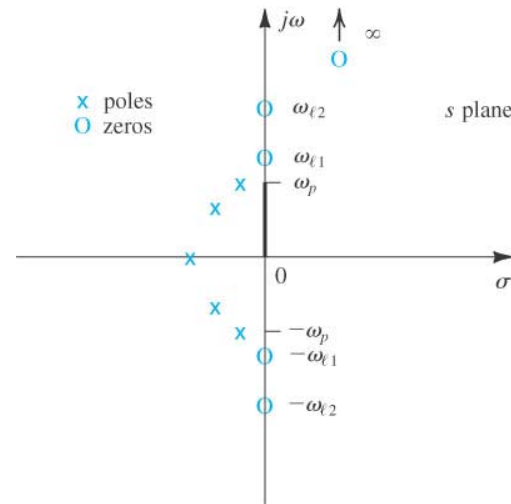


Lect. 17: Higher-Order Filters

Example of Sixth-Order BP Filter
(many other possibilities)

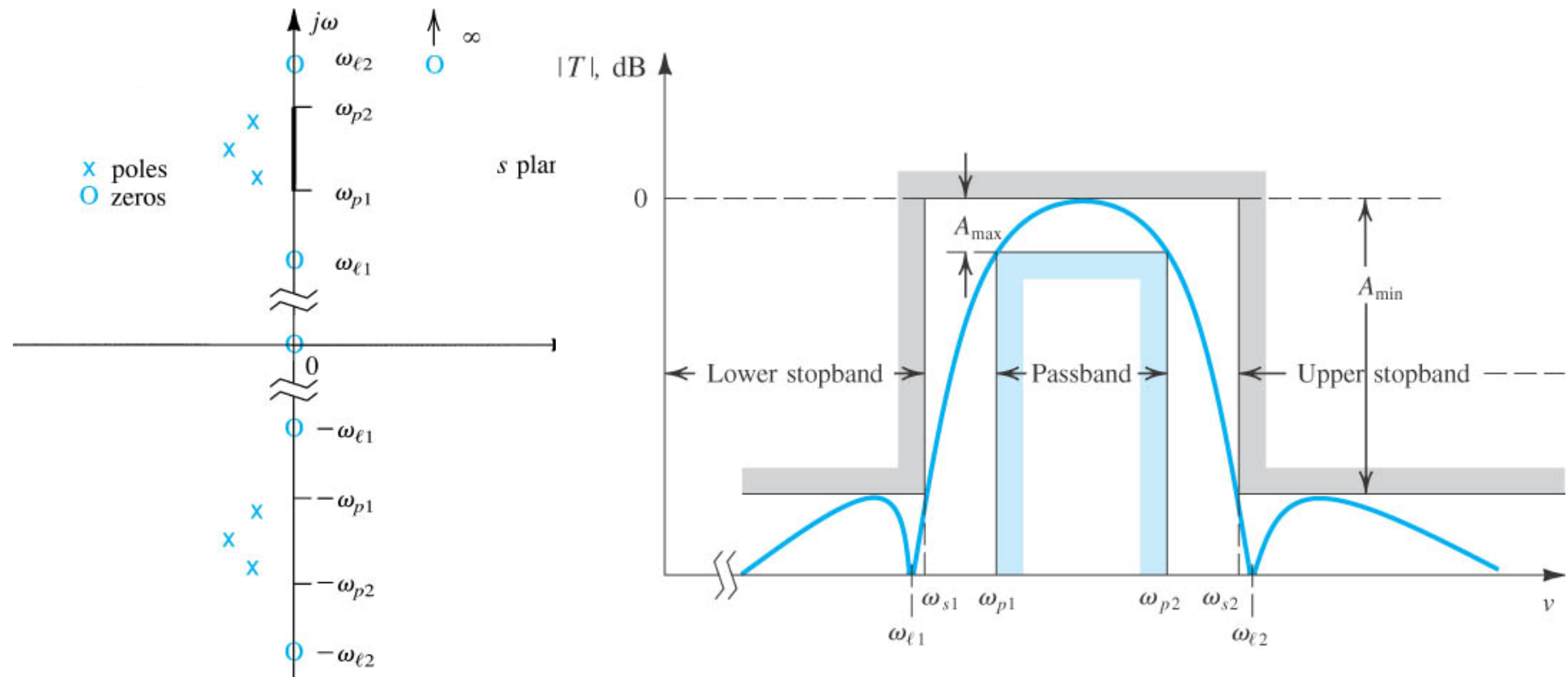

Lect. 17: Higher-Order Filters


Different types of LP filters

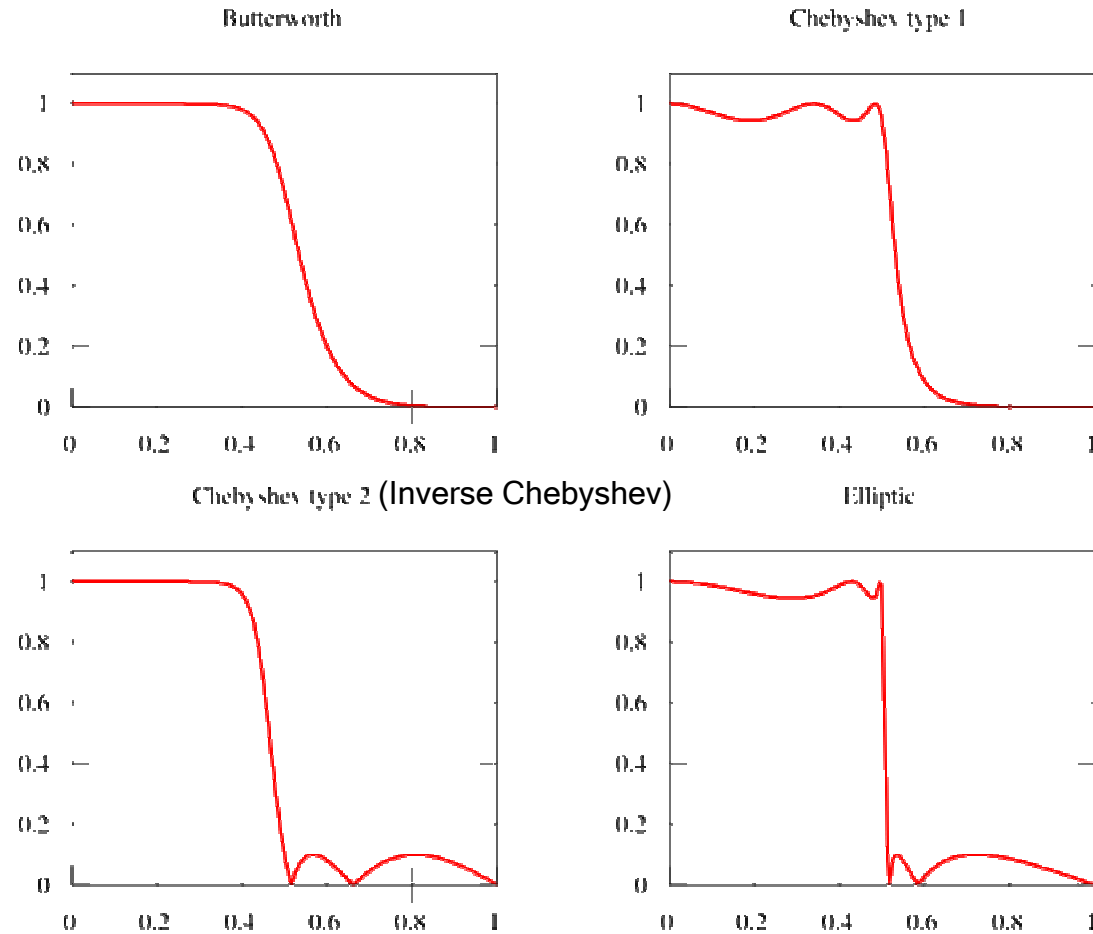

Lect. 17: Higher-Order Filters

Butterworth LP Filter

$$|T(j\omega)| = \frac{1}{\sqrt{1 + \varepsilon^2 \left(\frac{\omega}{\omega_p}\right)^{2N}}}$$

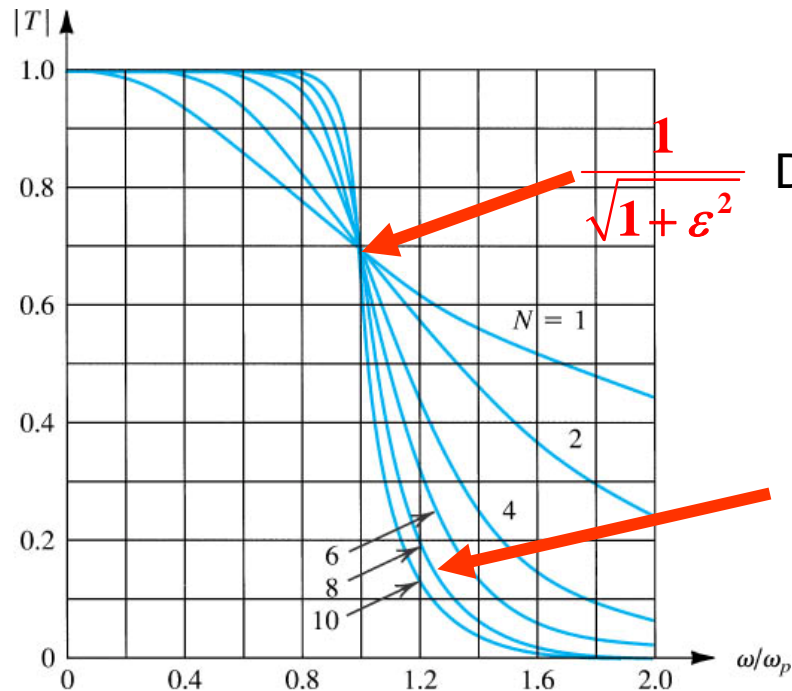




Determine ε so that A_{\max} is satisfied

$$A_{\max} = 20 \log \sqrt{1 + \varepsilon^2}$$

Determine N for the required stop-band attenuation


Lect. 17: Higher-Order Filters

Pole-Zero diagrams for Butterworth Filter

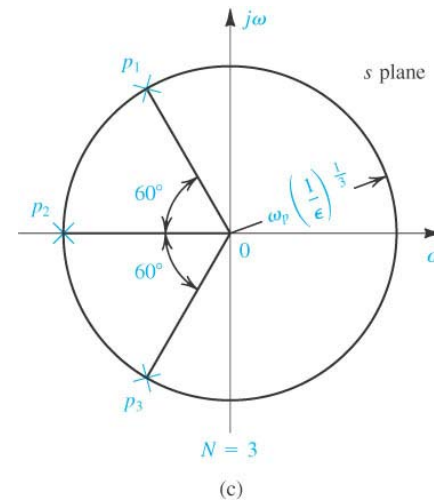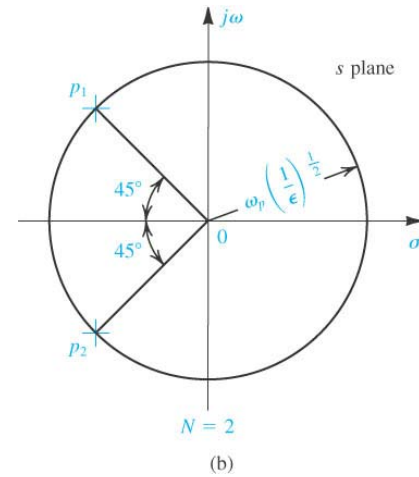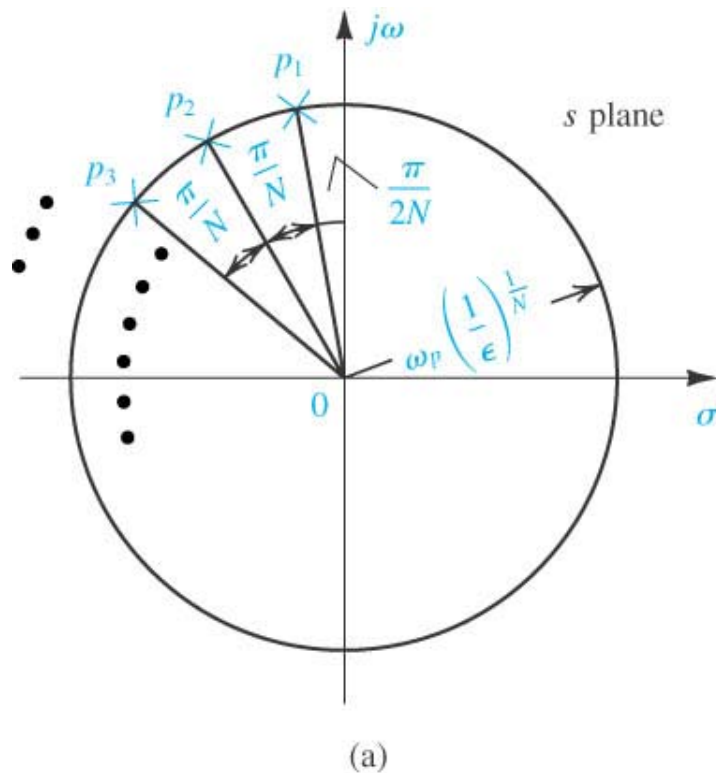

Lect. 17: Higher-Order Filters

Butterworth Filter

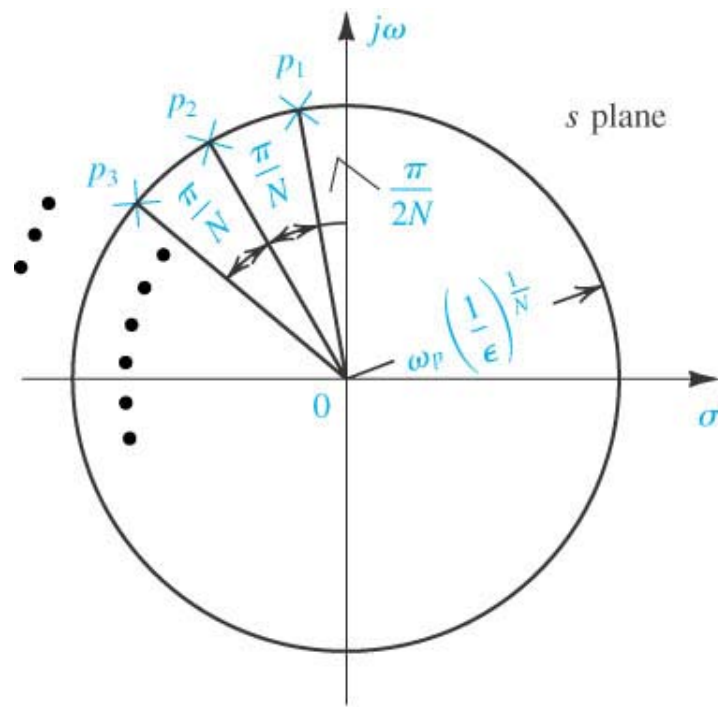

(a)

$$T(s) = K \frac{\omega_0^N}{(s - p_1)(s - p_2) \cdots (s - p_N)}$$

$$\omega_0 = \omega_p \left(\frac{1}{\epsilon} \right)^{\frac{1}{N}}$$

Lect. 17: Higher-Order Filters

How to design higher-order filters with electronic circuits

1. Select the filter type with desired filter specifications. → System specifications
2. Obtain the required transfer function. → Previous lecture materials for Butterworth
Or use the software package (MATLAB)
3. Derive the corresponding block diagram
4. Design the circuit for the given block diagram

→ Project #3