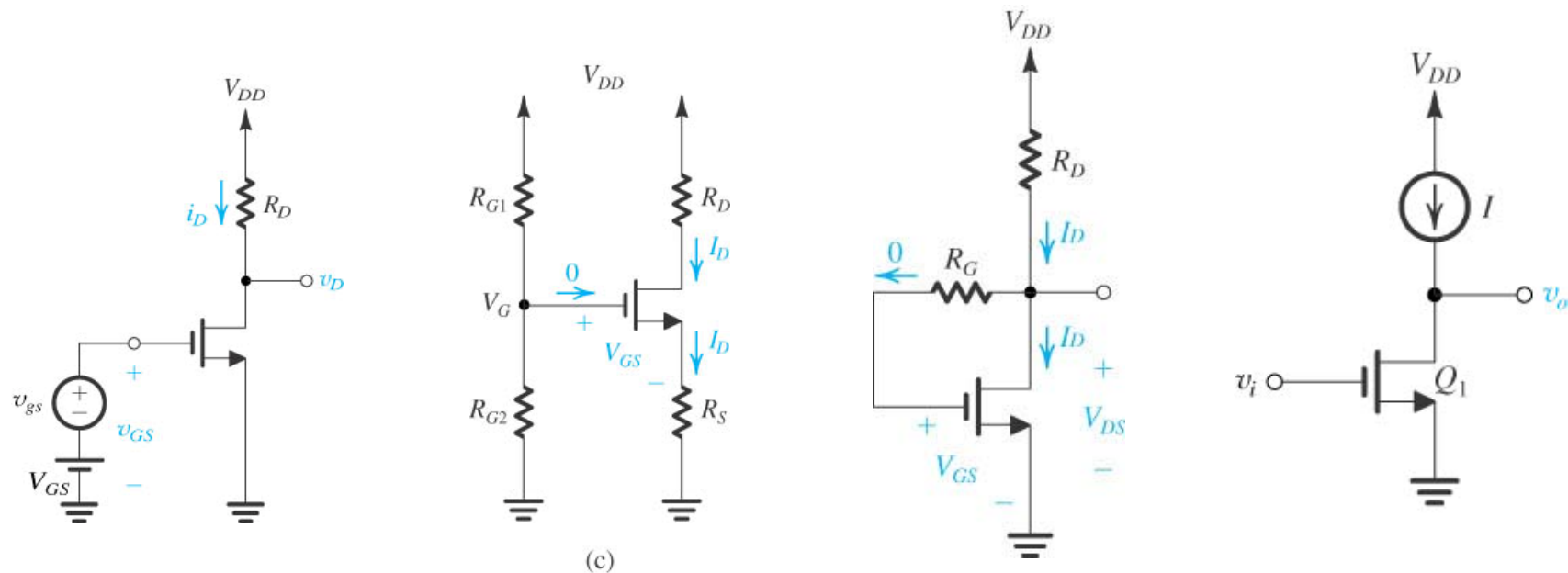


Lect. 22: MOSFET Current Mirror and CS Amplifier


Various bias techniques for MOSFET circuits



How do we make
a constant current source
with MOSFETs?

Lect. 22: MOSFET Current Mirror and CS Amplifier

Constant current source:

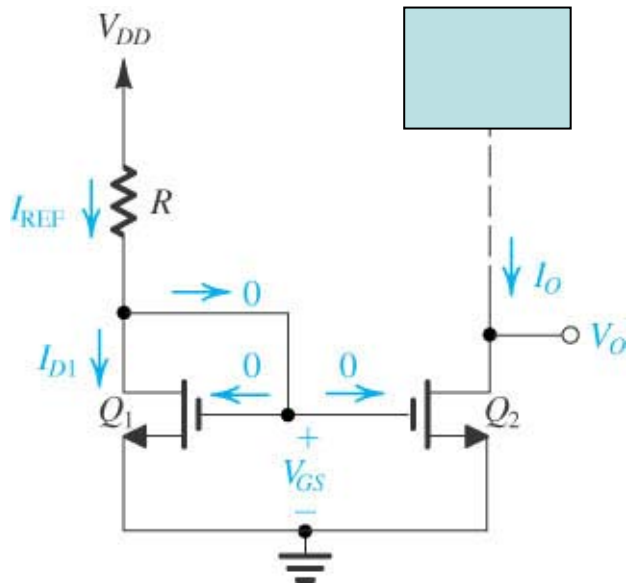

(R can be outside the IC chip)

→ Current mirror

$$I_{D1} = \frac{1}{2} k'_n \left(\frac{W}{L} \right)_1 (V_{GS} - V_{tn})^2$$

$$I_{D1} = I_{REF} = \frac{V_{DD} - V_{GS}}{R}$$

Assuming Q_1, Q_2 have same properties,


$$I_O = I_{D2} = \frac{1}{2} k'_n \left(\frac{W}{L} \right)_2 (V_{GS} - V_{tn})^2$$

$$\frac{I_O}{I_{REF}} = \frac{(W/L)_2}{(W/L)_1}$$

Limitation on V_o ? $V_o \geq V_{GS} - V_{tn}$

Lect. 22: MOSFET Current Mirror and CS Amplifier

Mismatches between I_{REF} and I_O

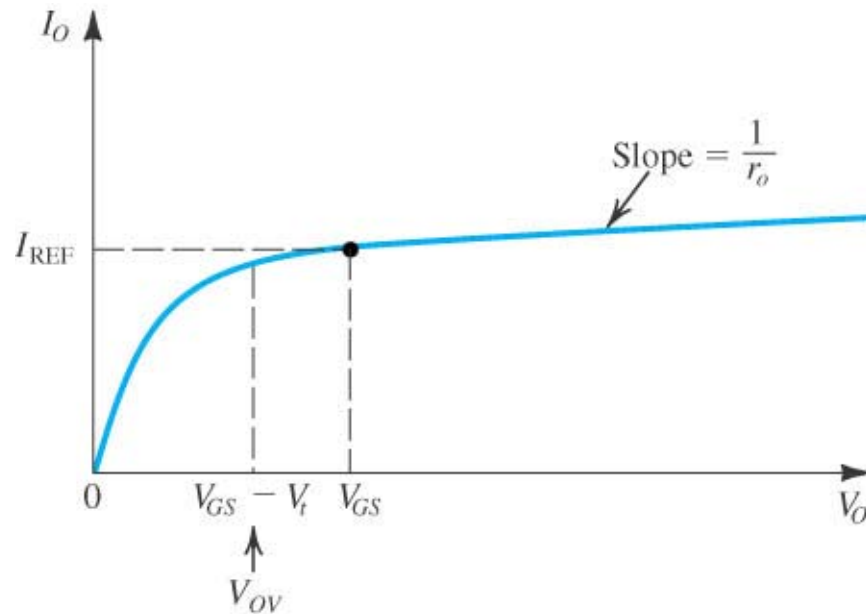

Channel-length modulation

For two identical Q_1 and Q_2

$$I_O = I_{REF} \text{ when } V_O = V_{GS}$$

As V_O increased, I_O increases from I_{REF}

$$I_O = I_{REF} + \frac{V_O - V_{GS}}{r_o}$$

$$\text{Since } r_o \approx \frac{V_A}{I_{REF}}$$


$$I_O = I_{REF} + \frac{V_O - V_{GS}}{V_A} \cdot I_{REF} = I_{REF} \left(1 + \frac{V_O - V_{GS}}{V_A} \right)$$

Lect. 22: MOSFET Current Mirror and CS Amplifier


Example 6.5

$V_{DD}=3V$, Q_1 and Q_2 are identical with
 $L=1\mu\text{m}$, $W=100\mu\text{m}$, $V_t=0.7V$, $k_n'=200\mu\text{A}/V^2$,
 V_A' (Early voltage per L) $=20V/\mu\text{m}$

1. Determine R for $I_O=100\mu\text{A}$.
2. What is the lowest value for V_O ?
3. How much I_O changes when V_O changes 1V?

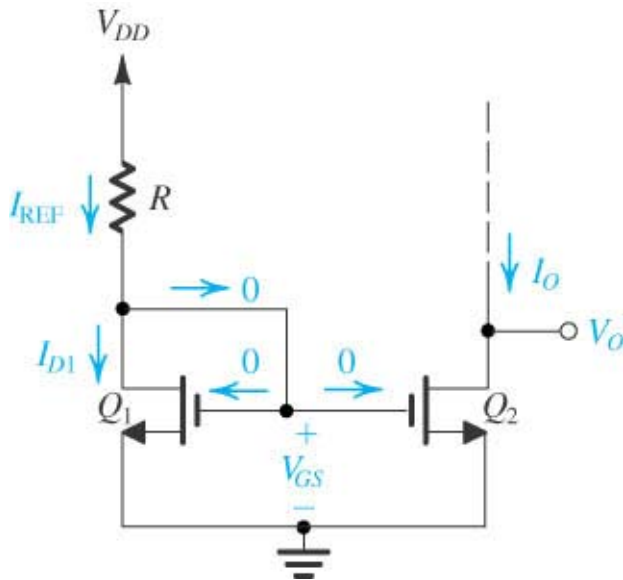

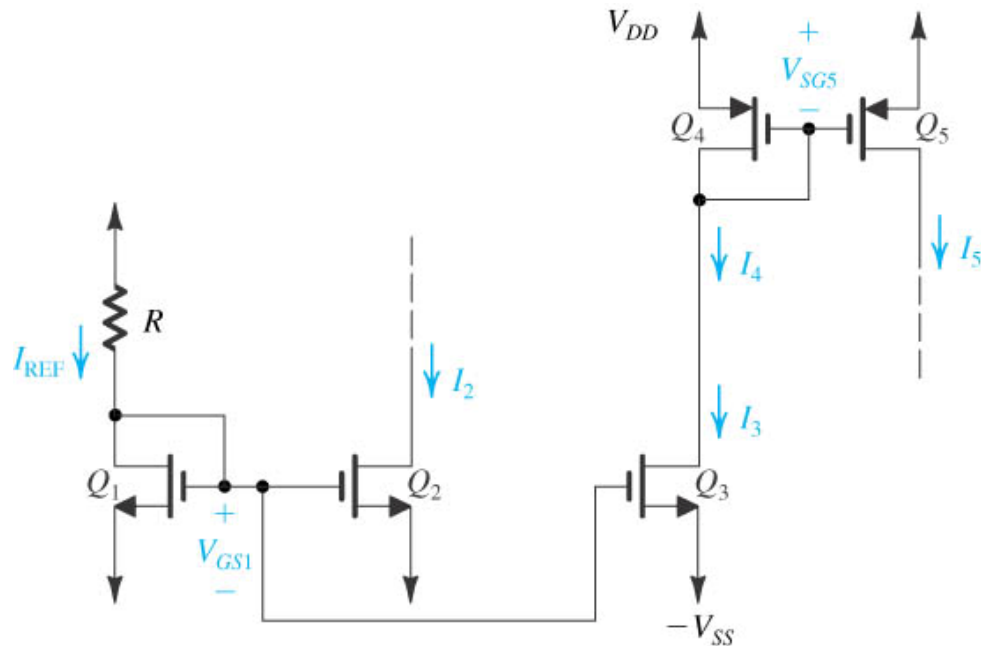Lect. 22: MOSFET Current Mirror and CS Amplifier



$$I_2 = I_{REF} \frac{(W/L)_2}{(W/L)_1}$$


$$I_3 = I_{REF} \frac{(W/L)_3}{(W/L)_1}$$

$$I_3 = I_4$$

$$I_5 = I_4 \frac{(W/L)_5}{(W/L)_4}$$

Current-steering circuits, current source (\$Q_5\$), current sink (\$Q_2\$)

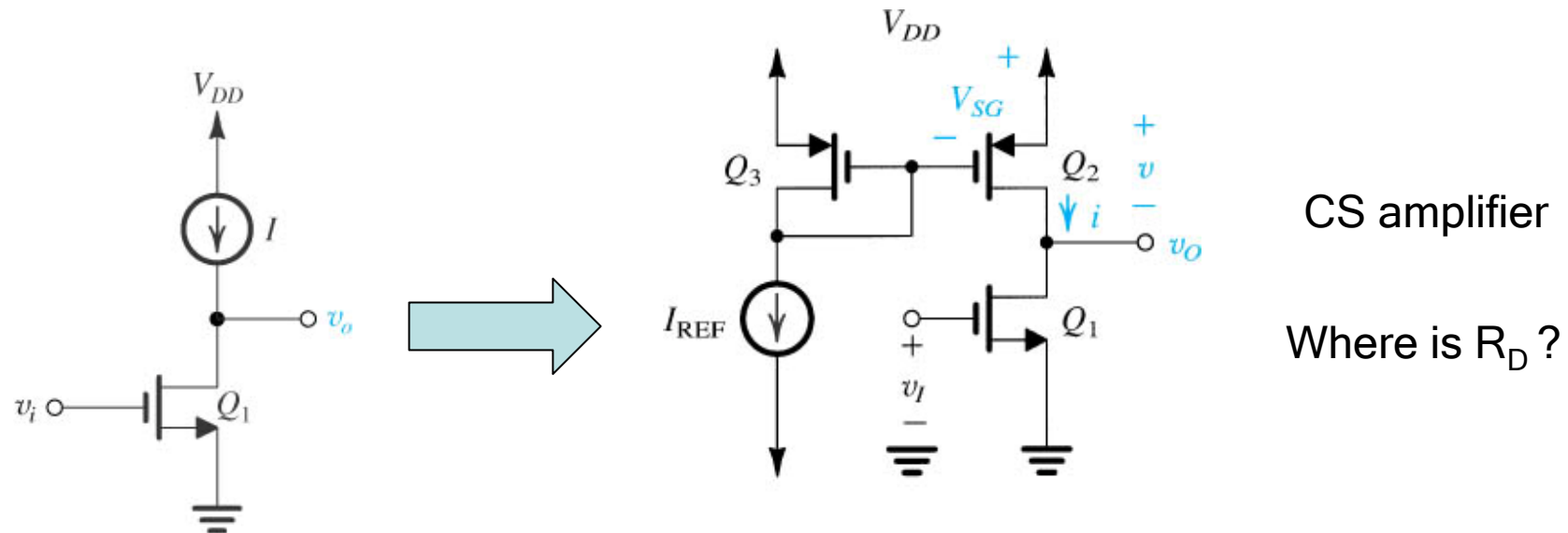Lect. 22: MOSFET Current Mirror and CS Amplifier



CS amplifier

Where is R_D ?



Current mirror as a resistor → Active load

(Remember Q_2 has r_o)


Lect. 22: MOSFET Current Mirror and CS Amplifier

Large change in v_o with v_i change!
 → Large amplifier gain

Load-line analysis

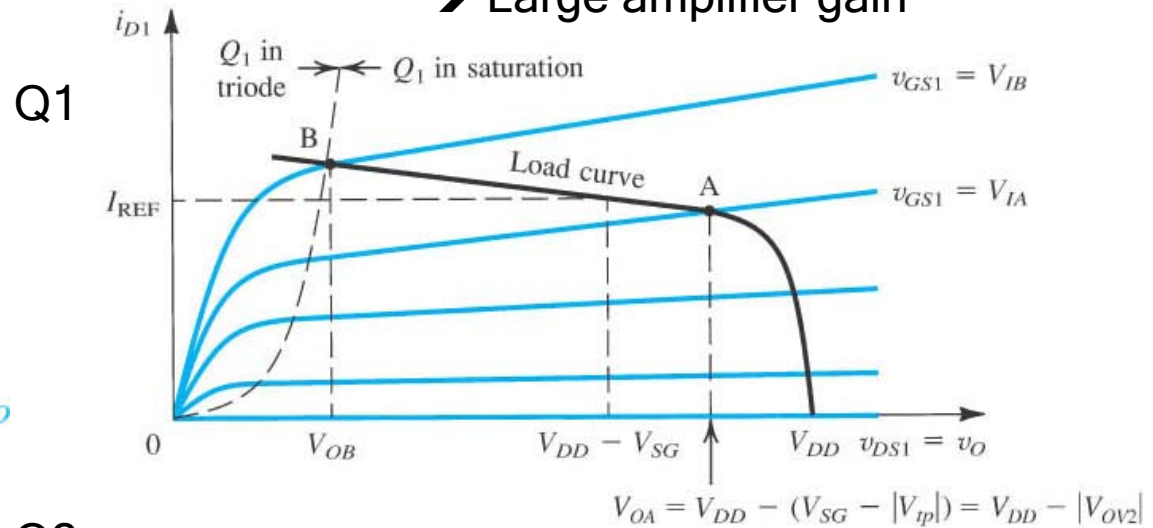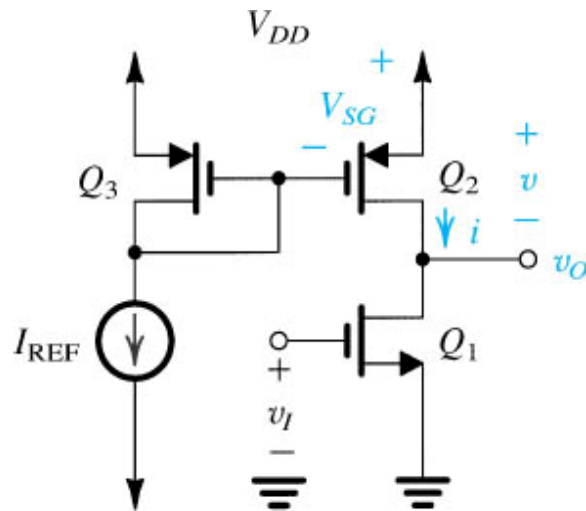


Q2

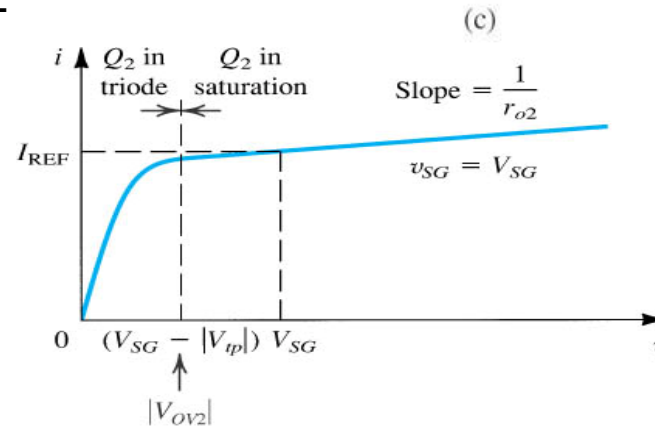


$$v = V_{DD} - v_o$$

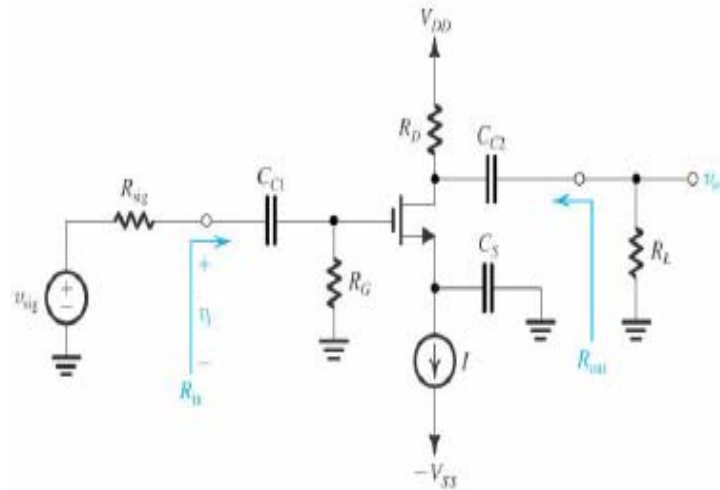Lect. 22: MOSFET Current Mirror and CS Amplifier



Gain for CS amplifier with R_D :
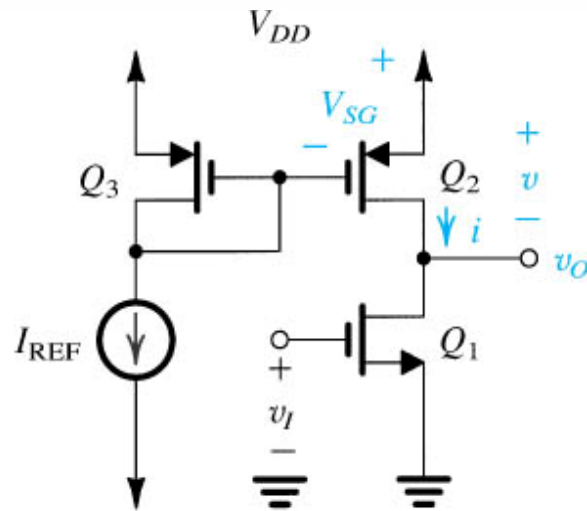
$$-g_m (r_o \parallel R_D \parallel R_L)$$



Gain for CS amplifier with PMOS current mirror

$$-g_m (r_{o1} \parallel r_{o2} \parallel R_L)$$

PMOS current mirror provides large "Drain" resistance (Active Load) as well as bias current!

→ Good for IC!

Lect. 22: MOSFET Current Mirror and CS Amplifier

Homework: Do your design project: Part 1 and 2 (No need to hand it in)

