

Quiz #3


May 28, 2007

Prof. Woo-Young Choi

Electronic Circuits II

 Problem 1 (4)

Consider the following CMOS inverter having $v_{Tn}=1V$, $v_{Tp}= -1V$, $V_{DD} = 2.5V$, $r_{on} = r_{op} = 50K\Omega$, and $k'(W/L)=1mA/V^2$ for both NMOS and PMOS transistors,



Estimate the noise margin for the low logic level.

Problem 2 (3)

Draw the transistor-level circuit configuration for CMOS XOR gate. Assume the input signals are available in A, A, B and B.

Problem 3 (3)

Consider the following block diagram for PLL.

Assume the phase detector has gain of K_{PD} , the VCO has gain of K_{VCO} , and the low pass filter has one pole at ω_p . Derive the close-loop transfer function in s-domain for ϕ_{out}/ϕ_{in} .

