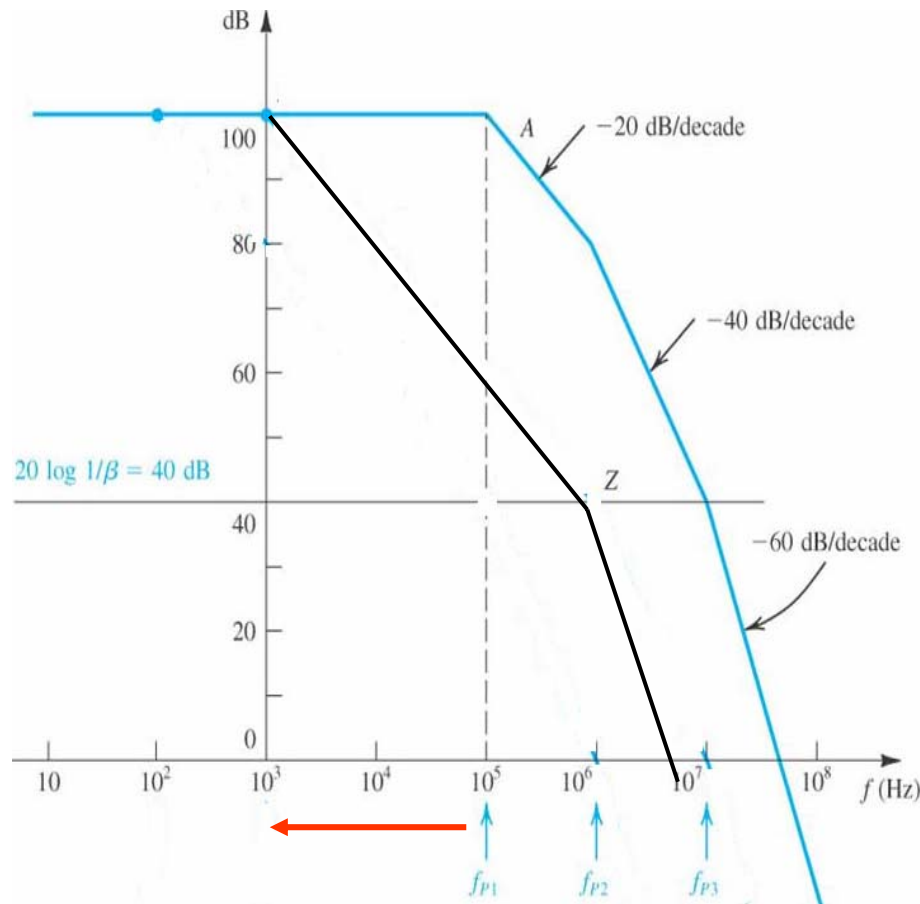


Lect. 10: Frequency Compensation

Bode plots for multi-pole amplifier



Unstable feedback system

Any way of fixing it?

Move f_{p1} to lower frequency
so that $|A|$ intersects $20 \log(1/\beta)$
with -20dB/decade slope,





➔ Frequency Compensation

Lect. 10: Frequency Compensation

How to move a pole?


High-frequency small-signal model

CS amplifier with active load

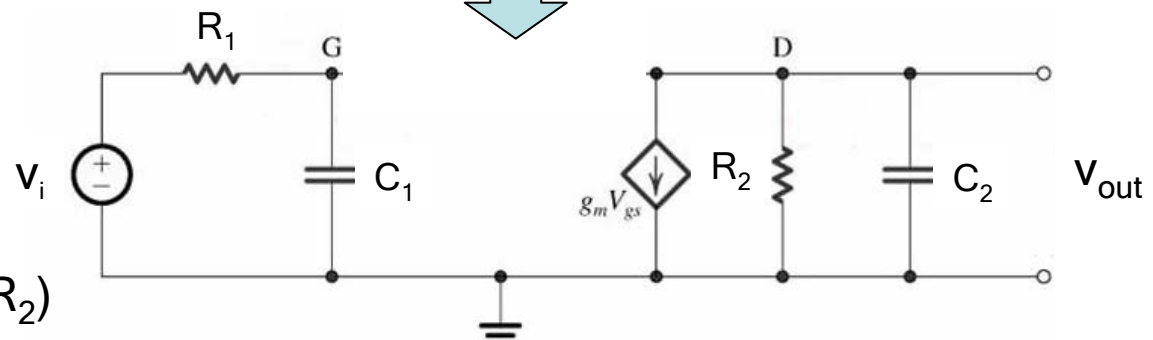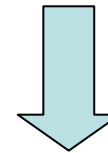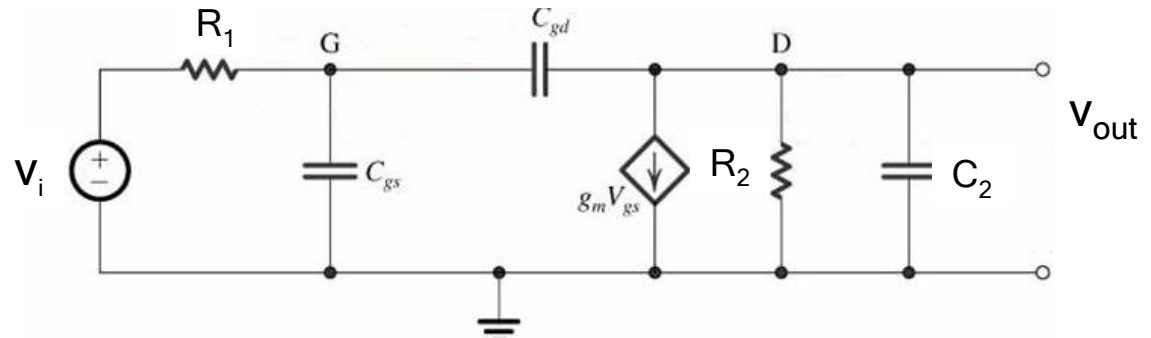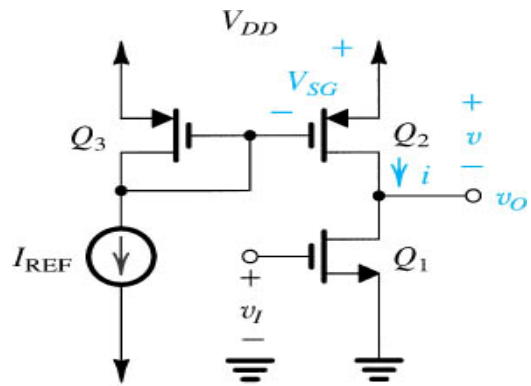

$$C_1 = C_{gs} + C_{gd}(1 + g_m R_2)$$

Lect. 10: Frequency Compensation

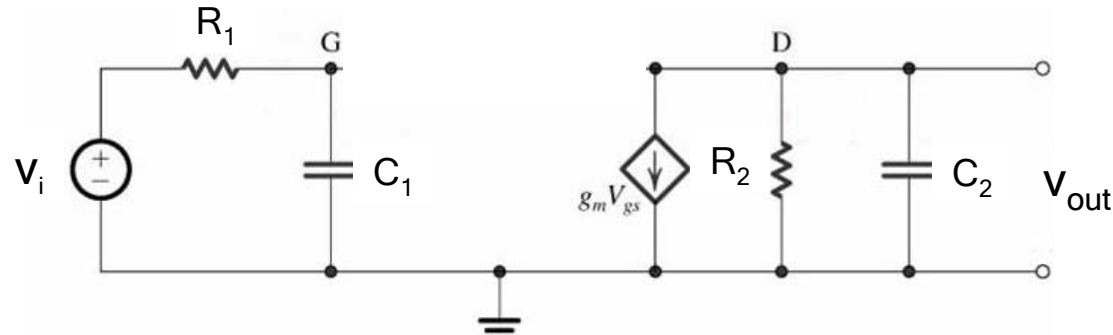

$$V_{out}(\omega) = -g_m V_{gs} \left(R_2 \parallel \frac{1}{j\omega C_2} \right) = -g_m V_i(\omega) \frac{1/j\omega C_1}{(R_1 + 1/j\omega C_1)} \frac{R_2 / j\omega C_2}{(R_2 + 1/j\omega C_2)}$$

$$\frac{V_{out}(\omega)}{V_i(\omega)} = -g_m \frac{1}{(j\omega R_1 C_1 + 1)} \frac{R_2}{(j\omega R_2 C_2 + 1)}$$

$$\omega_{P1} = \frac{1}{C_1 R_1}$$

$$\omega_{P2} = \frac{1}{C_2 R_2}$$


ω_{P1} can be made smaller by large C_1

$$\omega_{P1} < \omega_{P2}$$

→ Large capacitors are not desired

Lect. 10: Frequency Compensation

Use Miller effect

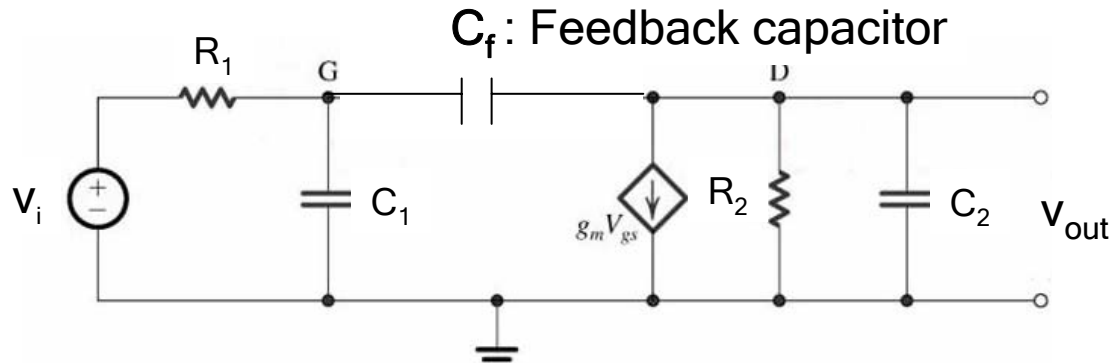


$$\frac{V_o}{V_i} = \frac{(g_m - sC_f)R_2}{1 + s[C_1R_1 + C_2R_2 + C_f(g_mR_1R_2 + R_1 + R_2)] + s^2[C_1C_2 + C_f(C_1 + C_2)]R_1R_2}$$

$$D(s) = \left(1 + \frac{s}{\omega_{P1}'}\right) \left(1 + \frac{s}{\omega_{P2}'}\right) = 1 + s \left(\frac{1}{\omega_{P1}'} + \frac{1}{\omega_{P2}'}\right) + \frac{s^2}{\omega_{P1}'\omega_{P2}'} \approx 1 + \frac{s}{\omega_{P1}'} + \frac{s^2}{\omega_{P1}'\omega_{P2}'} \quad (\omega_{P1}' \ll \omega_{P2}')$$

$$\omega_{P1}' = \frac{1}{C_1R_1 + C_2R_2 + C_f(g_mR_1R_2 + R_1 + R_2)} \approx \frac{1}{C_f g_m R_1 R_2} \ll \omega_{P1} = \frac{1}{C_1 R_1}$$

$$\omega_{P2}' \approx \frac{g_m C_f}{C_1 C_2 + C_f(C_1 + C_2)} > \omega_{P2} = \frac{1}{C_2 R_2}$$

Lect. 10: Frequency Compensation

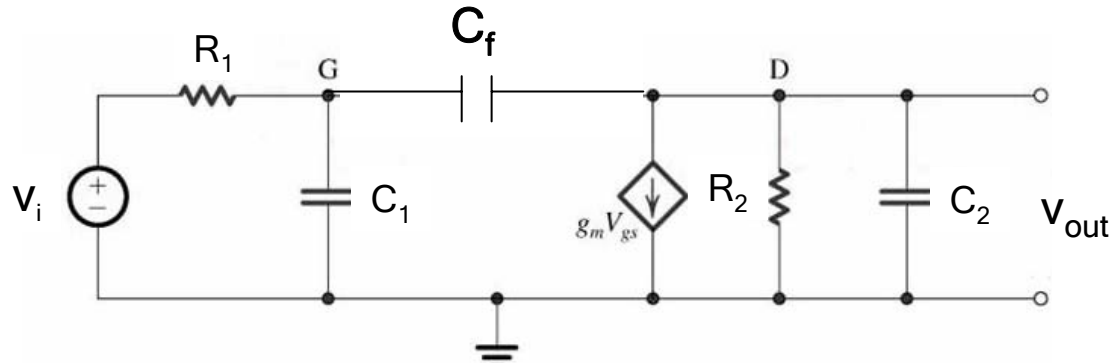


Addition of C_f between G and D → Miller compensation

Move ω_{p1} to lower frequency
 ω_{p2} to higher frequency: Pole splitting

→ More phase margin: Safer for feedback


Lect. 10: Frequency Compensation

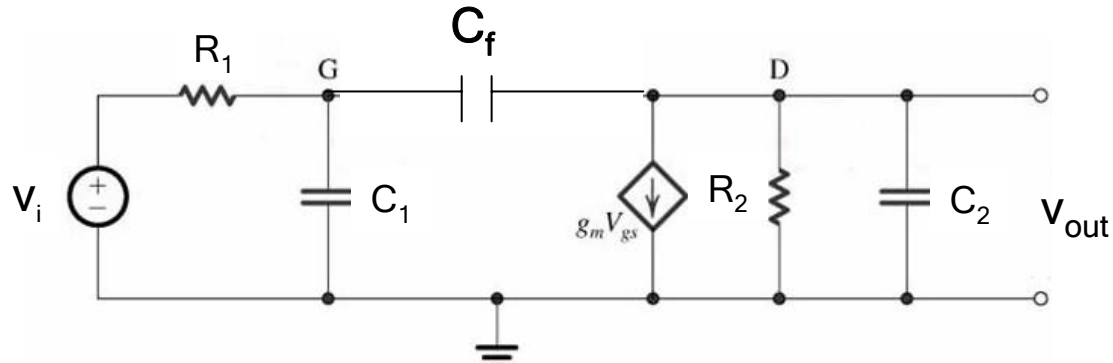

$$\frac{V_o}{V_i} = \frac{(sC_f - g_m)R_2}{1 + s[C_1R_1 + C_2R_2 + C_f(g_mR_1R_2 + R_1 + R_2)] + s^2[C_1C_2 + C_f(C_1 + C_2)]R_1R_2}$$


How about zero at $s = g_m/C_f$?

The positive zero adds phases
 → Bad for phase margin

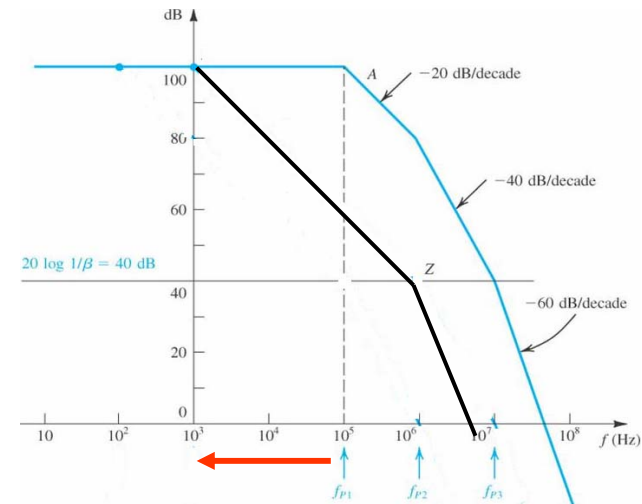

Lect. 10: Frequency Compensation

Solve the problem by adding a resistor

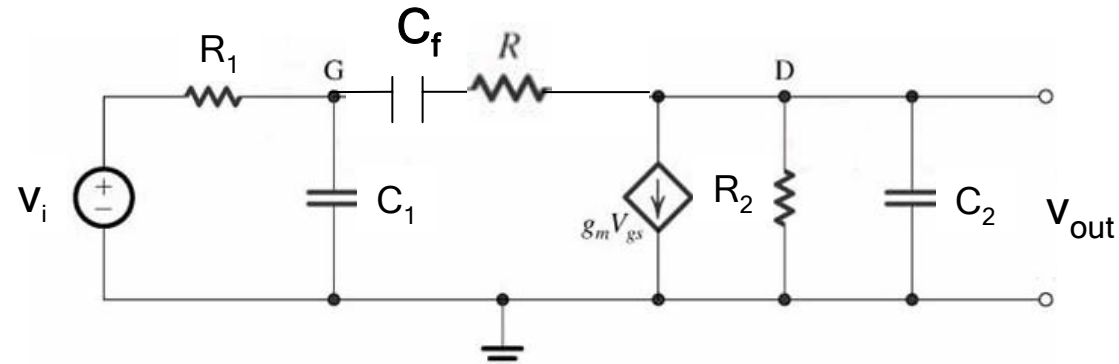

$$\text{For zero, } V_{\text{out}}(s) = 0, \quad \frac{V_{gs}}{R + \frac{1}{sC_f}} = g_m V_{gs} \quad \therefore s = \frac{1}{C_f} \left(\frac{1}{g_m} - R \right)$$

If $R > 1/g_m$, zero will be on the negative real-axis

→ It adds phase margin!