

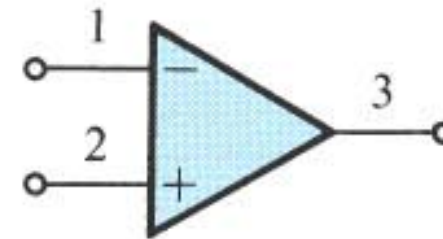


Lect. 13: Operational Amplifiers

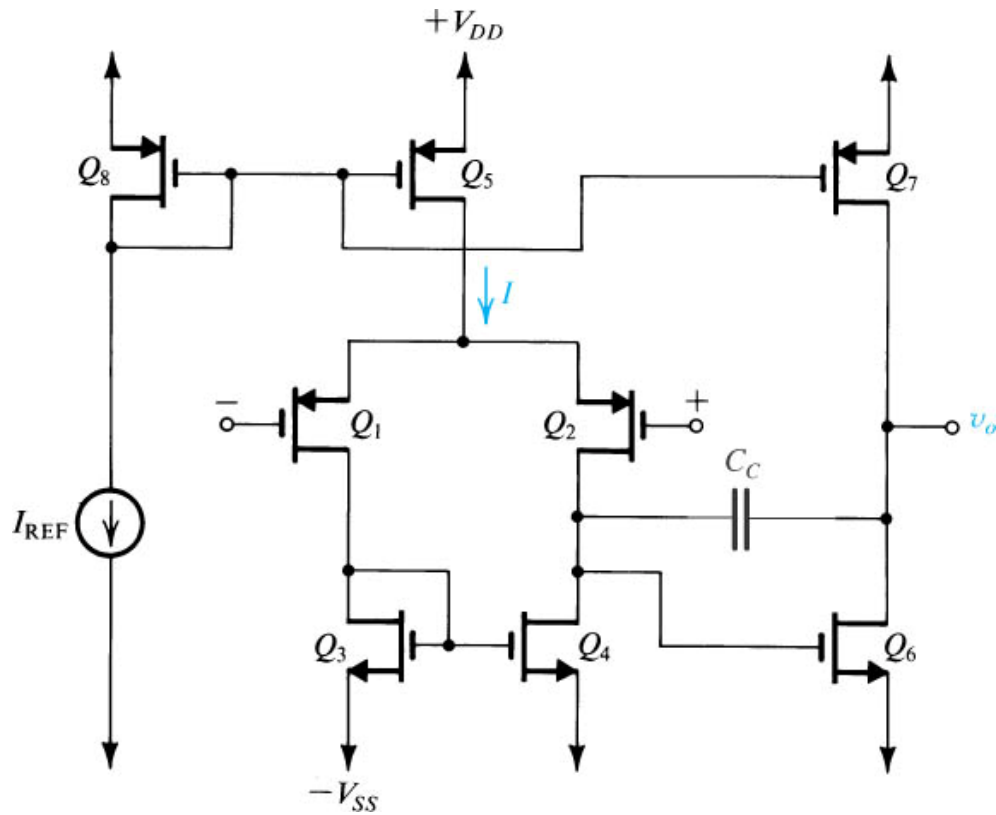

Operational amplifier (Op Amp)

Lect. 13: Operational Amplifiers

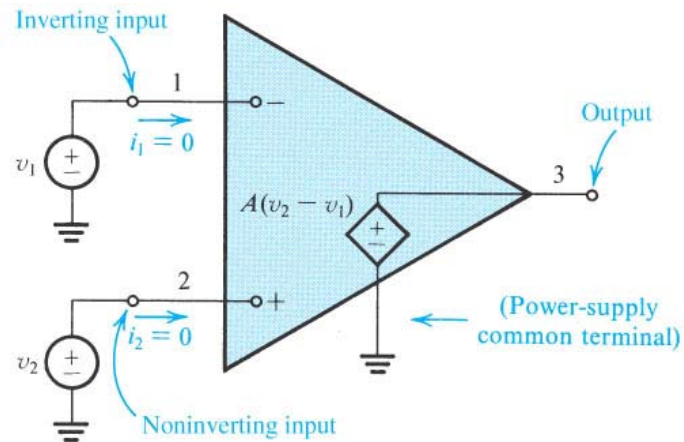

Characteristics of an *ideal* op amp

- Ideal amplifier for voltage difference

R_{in} : Infinite


A_v : Infinite

R_{out} : 0 for voltage output

infinite for current output


→ transconductance amplifier (OTA)

Zero common-mode gain
(or infinite common-mode rejection)

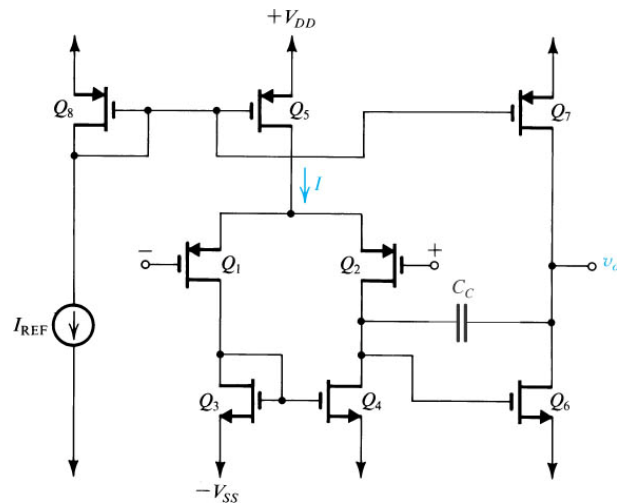

Lect. 13: Operational Amplifiers

Op amp is very often used with feedback

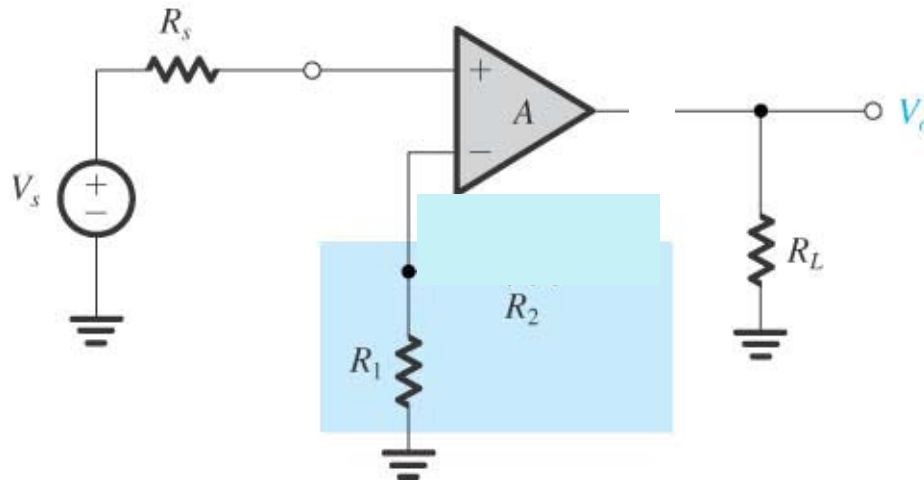

$$V_o = A_v(V_s - 0)$$

→ +/- supply voltage

With feedback

$$V_o = A_v \left(V_s - V_o \cdot \frac{R_1}{R_1 + R_2} \right)$$


$$V_o \left(1 + \frac{A_v R_1}{R_1 + R_2} \right) = A_v V_s$$

$$\therefore \frac{V_o}{V_s} = \frac{A_v}{1 + \frac{A_v R_2}{R_1 + R_2}} \approx \frac{R_1 + R_2}{R_1}$$

Remember $A_f = \frac{x_o}{x_s} = \frac{A}{1 + A\beta} \approx \frac{1}{\beta}$

$$\beta = R_1 / (R_1 + R_2)$$

Lect. 13: Operational Amplifiers

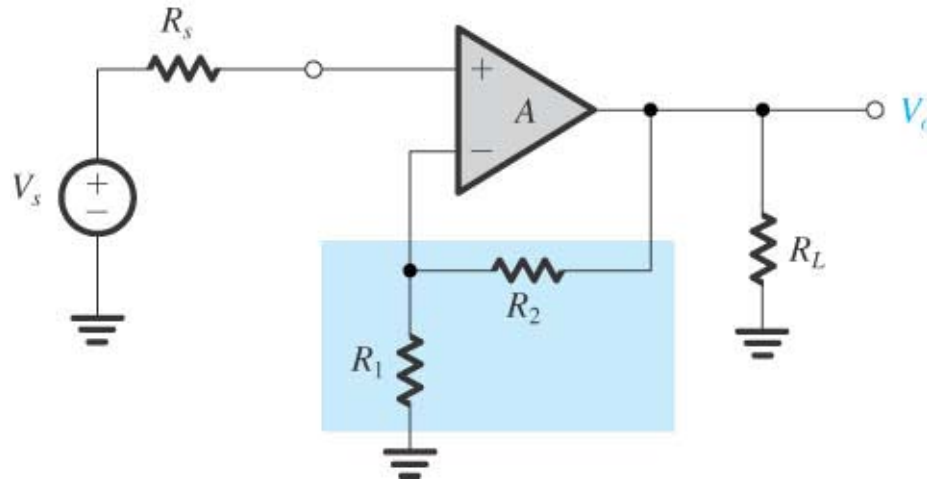


$$\frac{V_o}{V_s} = \frac{A_v}{1 + \frac{A_v R_1}{R_1 + R_2}} \approx \frac{R_1 + R_2}{R_1}$$

The same result can be obtained by assuming $V^+ = V^-$ (virtual short)

$$V_s = V_o \frac{R_1}{R_1 + R_2}$$
$$\therefore \frac{V_o}{V_s} = \frac{R_1 + R_2}{R_1}$$

Lect. 13: Operational Amplifiers


What good is it?

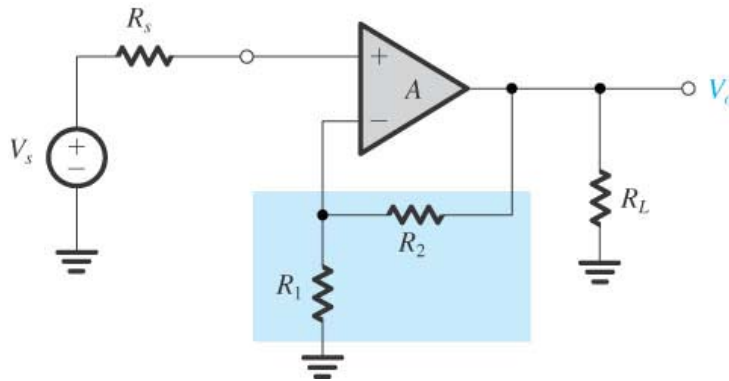

$$\frac{V_o}{V_s} = \frac{R_1 + R_2}{R_2} \quad \text{Voltage amplifier}$$

- Infinite input resistance
- Same gain regardless of R_L
- Gain is stable and can be easily changed


Voltage amplifier with negative gain?

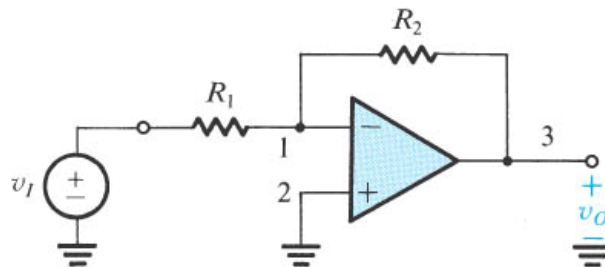

$$V_o = -\frac{R_2}{R_1} V_I$$


Lect. 13: Operational Amplifiers

Current amplifier

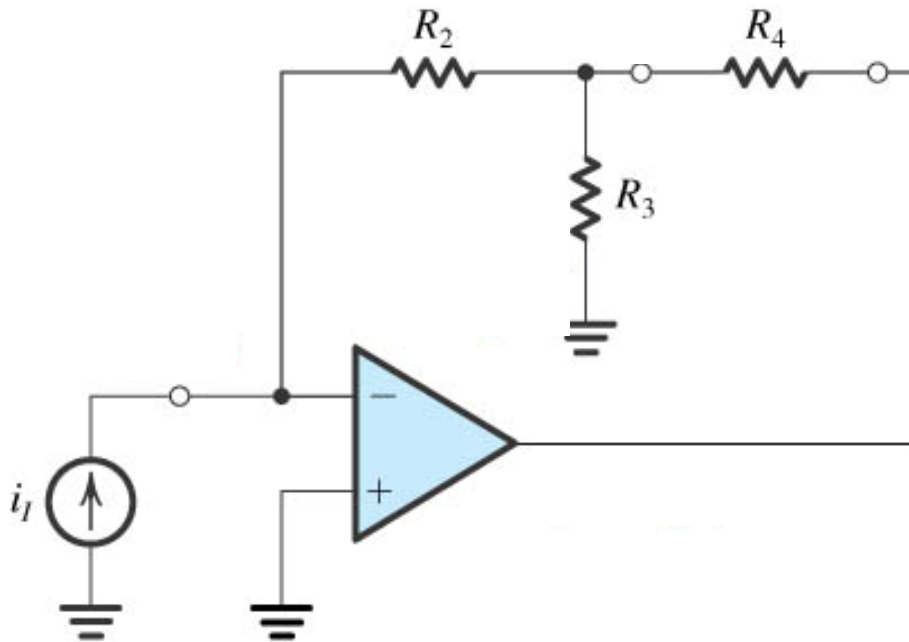


$$A_i = \frac{i_4}{i_i} = \left(1 + \frac{R_2}{R_3}\right)$$

Lect. 13: Operational Amplifiers

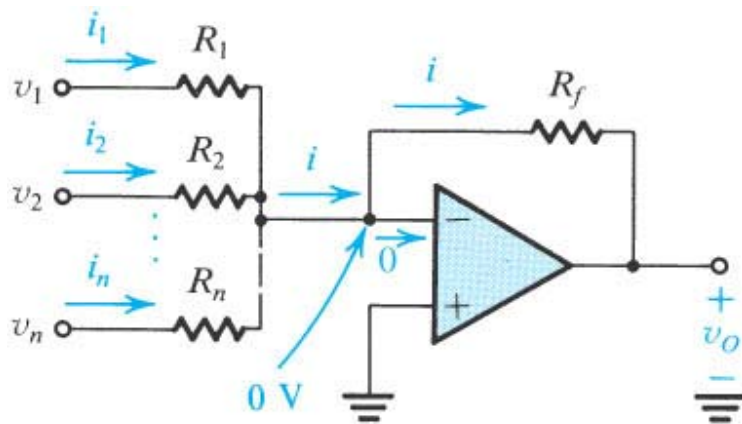

weighted summer (adder)

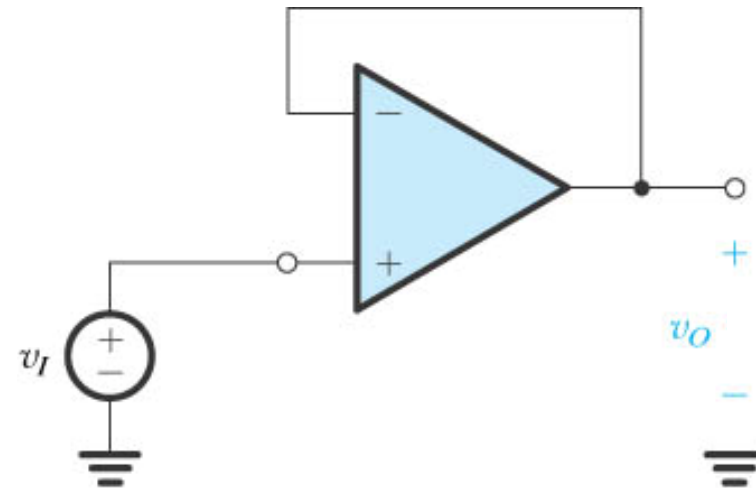


(a)

voltage buffer

Op amp for many analog signal processing applications

Lect. 13: Operational Amplifiers

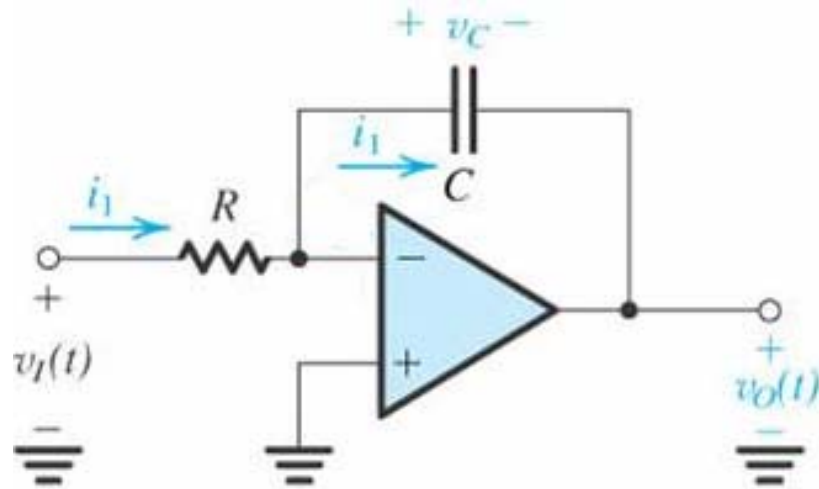

$$C \frac{dv_o(t)}{dt} = -\frac{v_i(t)}{R}$$

$$v_o(t) - v_o(t=0) = -\frac{1}{RC} \int_0^t v_i(t) dt$$



Integrator

Op amp for many useful analog signal processing applications!

Lect. 13: Operational Amplifiers


Real Op Amps are not ideal: Input voltage offset

Ideally, $v_o = 0$ if $v^+ = v^-$ But, often, $v_o = 0$ when $v^+ - v^- = V_{OS}$ (offset voltage)

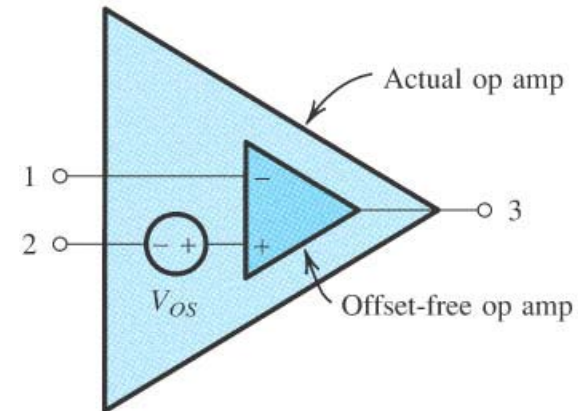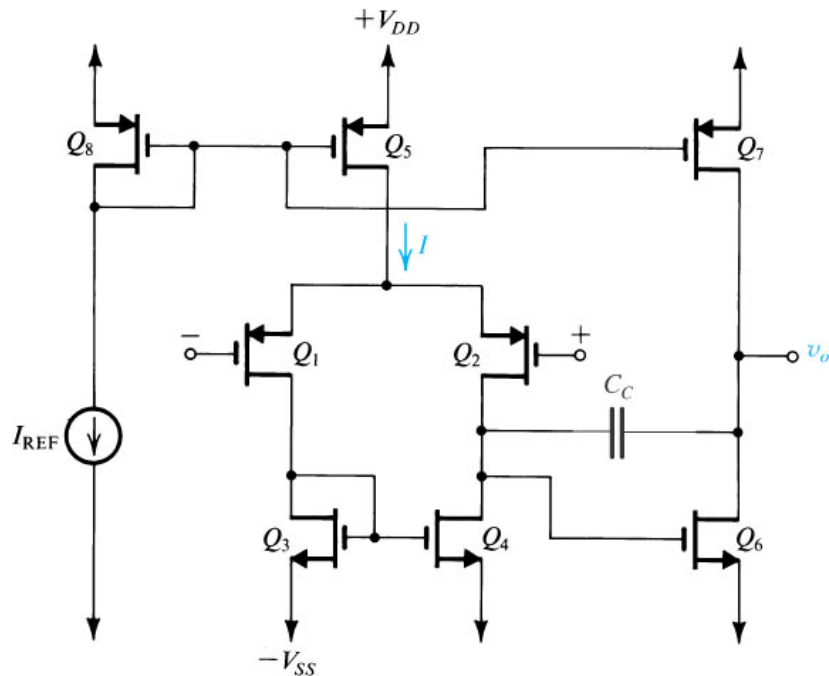


Lect. 13: Operational Amplifiers

What happens to Op Amp integrator?

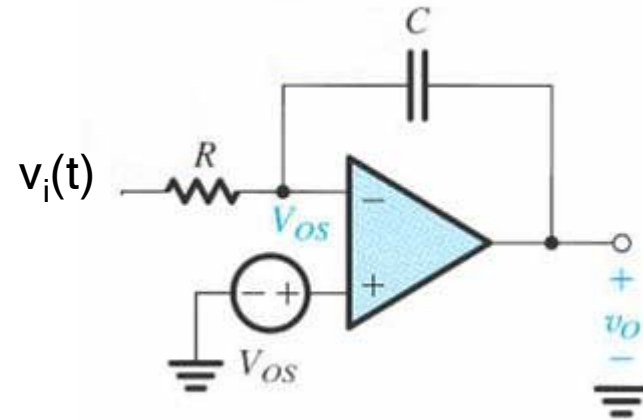


It does not work as an integrator!

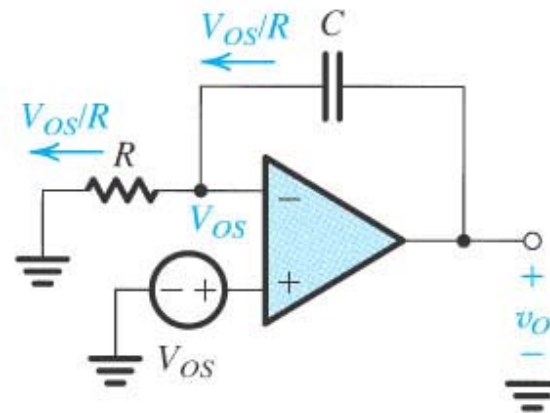

$$v_o = V_{os} + \frac{1}{C} \int_0^t \frac{V_{os}}{R} dt$$
$$= V_{os} + \frac{V_{os}t}{CR}$$

Lect. 13: Operational Amplifiers

Solution: Lossy Integrator

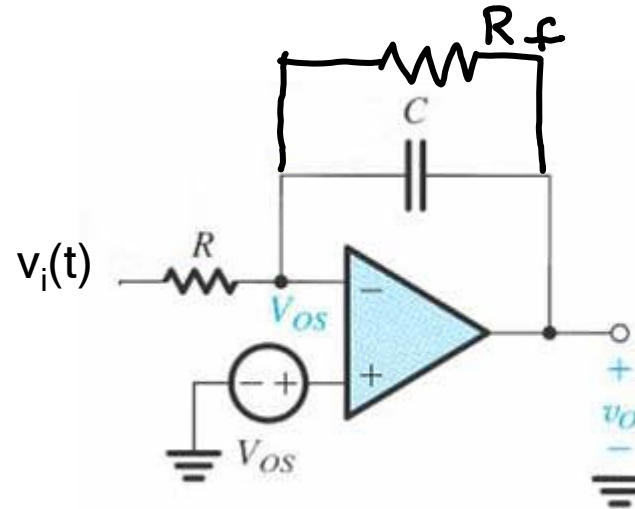


$$\frac{v_i(t) - V_{os}}{R} + \frac{v_o(t) - V_{os}}{R_f} + C \frac{d(v_o(t) - V_{os})}{dt} = 0$$

$$R_f C \frac{dv_o(t)}{dt} + v_o(t) = -\frac{R_f}{R} v_i(t) + \left(1 + \frac{R_f}{R}\right) V_{os}$$

Lect. 13: Operational Amplifiers

Solution: Lossy Integrator

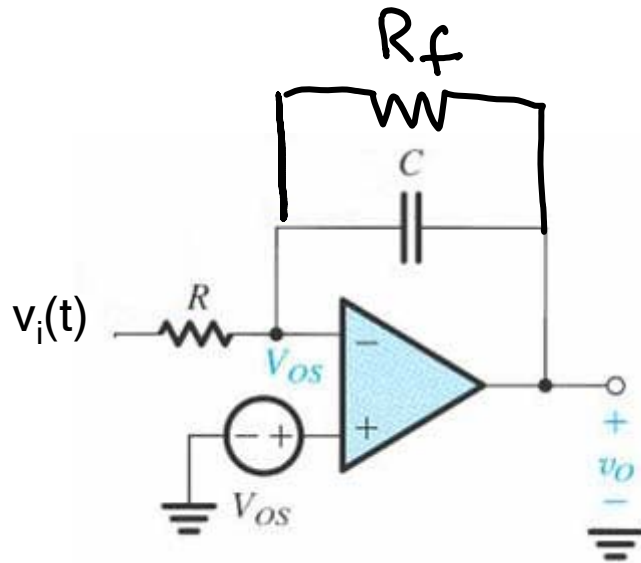

$$R_f C \frac{dv_o(t)}{dt} + v_o(t) = -\frac{R_f}{R} v_i(t) + \left(1 + \frac{R_f}{R}\right) V_{os}$$

Use superposition

$$R_f C \frac{dv_{o1}(t)}{dt} + v_{o1}(t) = \left(1 + \frac{R_f}{R}\right) V_{os}$$

$$R_f C \frac{dv_{o2}(t)}{dt} + v_{o2}(t) = -\frac{R_f}{R} v_i(t)$$

$$v_o(t) = v_{o1}(t) + v_{o2}(t)$$


Lect. 13: Operational Amplifiers

$$R_f C \frac{dv_{o1}(t)}{dt} + v_{o1}(t) = \left(1 + \frac{R_f}{R}\right) V_{os}$$

$$v_{o1}(t) = v_{o1,0} \exp\left(-\frac{1}{R_f C} t\right) + \left(1 + \frac{R_f}{R}\right) V_{os} = \left(1 + \frac{R_f}{R}\right) V_{os} \quad (\text{Assuming } v_{o1,0} = 0)$$

$$R_f C \frac{dv_{o2}(t)}{dt} + v_{o2}(t) = -\frac{R_f}{R} v_i(t)$$

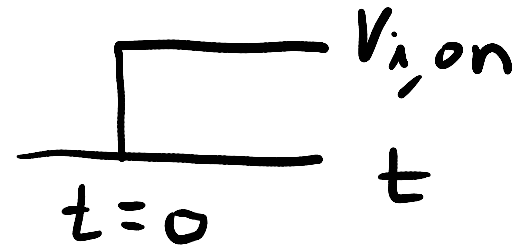Assuming $v_i(t)$ is a step function at $t=$ with $V_{i,on}$





$$v_{o2}(t) = -\frac{R_f}{R} V_{i,on} \left[1 - \exp\left(-\frac{t}{R_f C}\right)\right]$$

Lect. 13: Operational Amplifiers

$$\begin{aligned}\therefore v_o(t) &= v_{o1}(t) + v_{o1}(t) \\ &= \left(1 + \frac{R_f}{R}\right)V_{os} - \frac{R_f}{R}V_{i,on} \left[1 - \exp\left(-\frac{t}{R_f C}\right)\right]\end{aligned}$$

Is this an integrator?

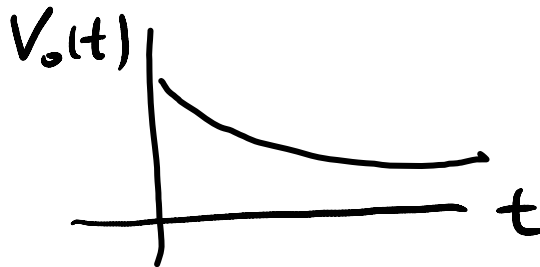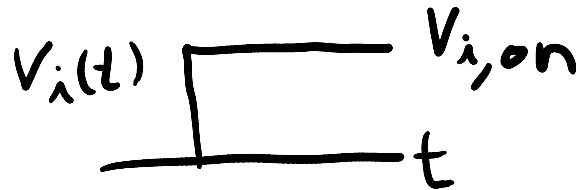

Yes, if $t \ll R_f C$

$\rightarrow f \gg 1/(R_f C)$