

# Lect. 15: Second-Order Passive Filters (S&S 12.5)

2nd-order filter 
$$T(s) = \frac{a_2 S^2 + a_1 S^1 + a_0}{S^2 + b_1 S^1 + b_0} = \frac{a_2 (s - z_1)(s - z_2)}{(s - p_1)(s - p_2)}$$

If  $p_1, p_2$  are real,


→ 2nd-order filters can be easily made by cascading two 1st-order filters

Consider  $T(s)$  with complex poles

$$T(s) = \frac{a_2 s^2 + a_1 s + a_0}{s^2 + (\omega_0 / Q)s + \omega_0^2}$$

$$p_1, p_2 = -\frac{\omega_0}{2Q} \pm j\omega_0 \sqrt{1 - (1/4Q^2)}$$


( $Q > 1/2$ )

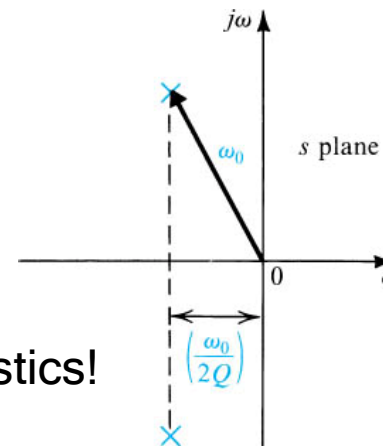



Depending on zero locations, various filter characteristics!

# Lect. 15: Second-Order Passive Filters
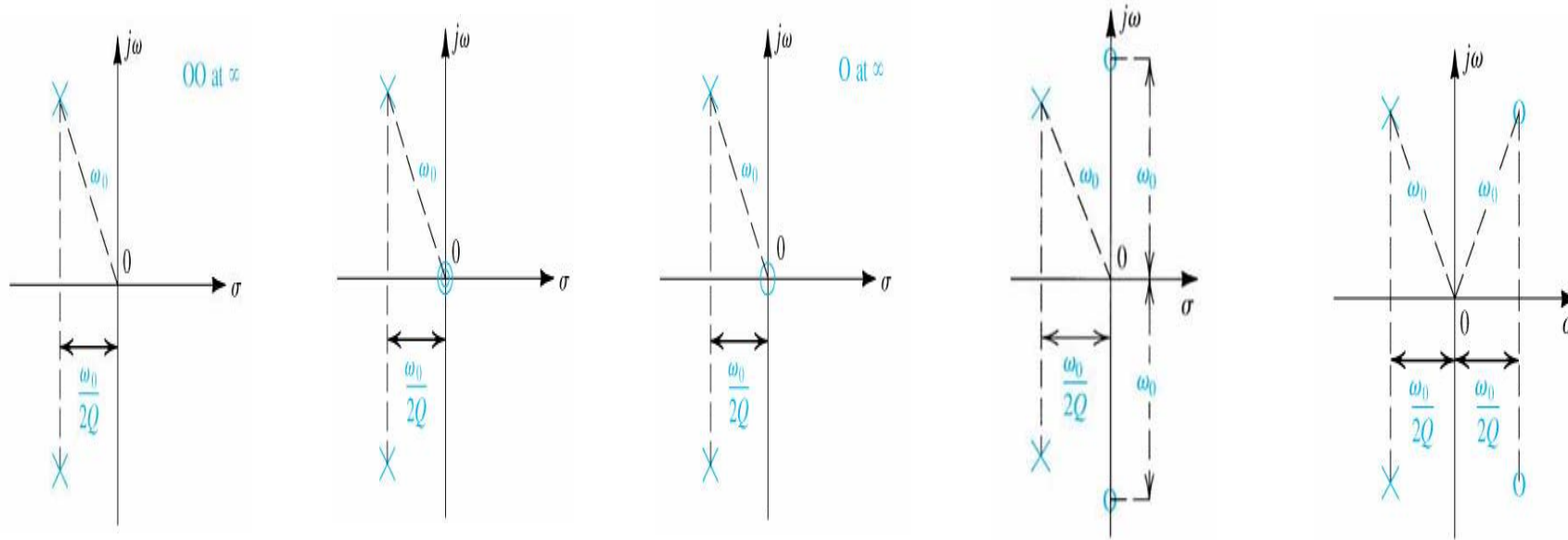
## Second-order filter pole-zero diagrams



# Lect. 15: Second-Order Passive Filters

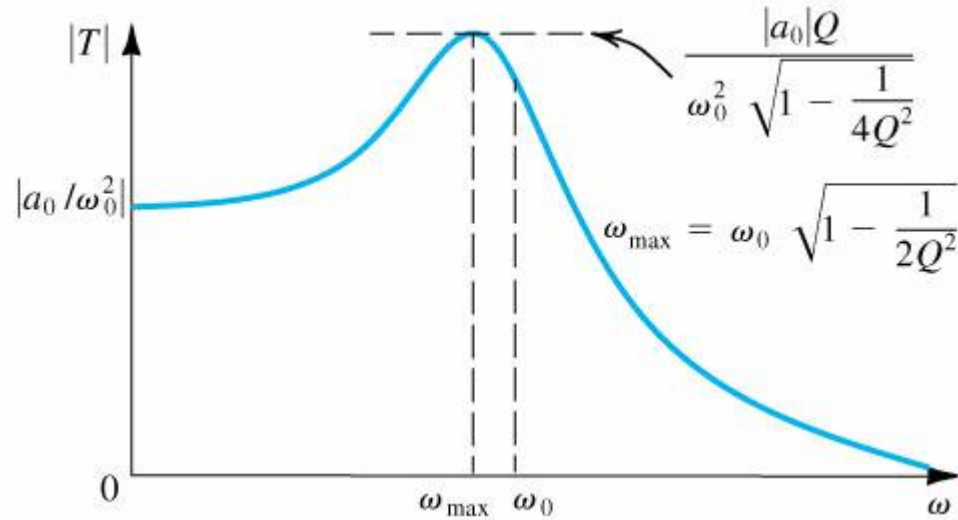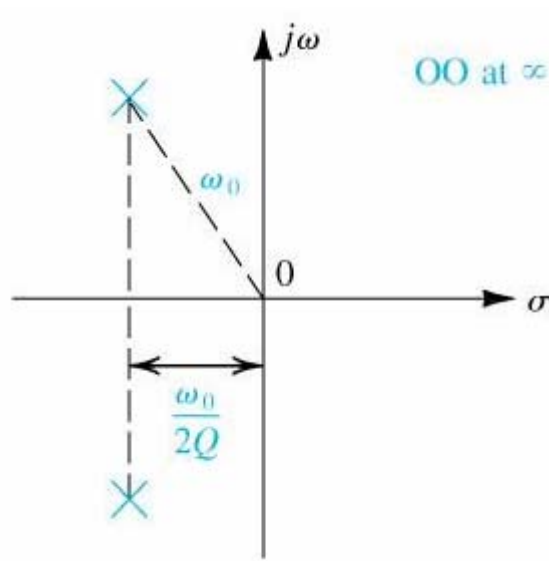


$$T(s) = \frac{a_0}{s^2 + s\frac{\omega_0}{Q} + \omega_0^2}$$

At  $\omega = \omega_0$ ,  $|T| = |a_0/\omega_0^2| Q$

Larger  $Q \rightarrow$  More peaking

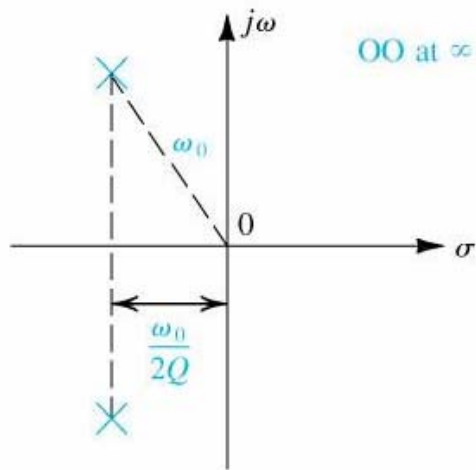
# Lect. 15: Second-Order Passive Filters

How to realize passive second-order LP filter




$$T(s) = \frac{a_0}{s^2 + s\frac{\omega_0}{Q} + \omega_0^2}$$

Use LCR

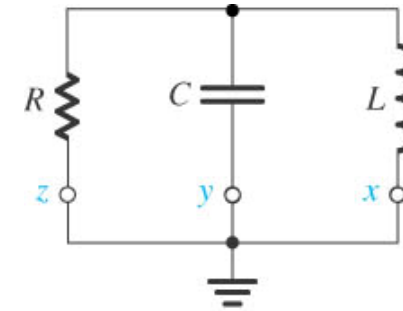

(a)

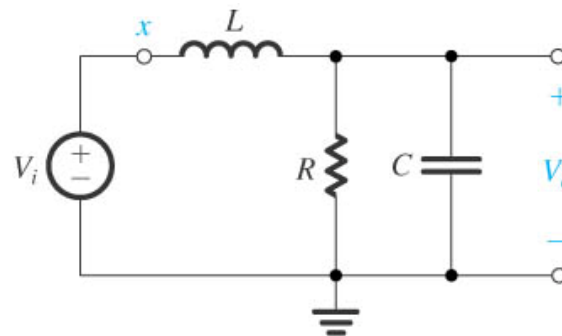


(b) LP


→ Two zeros at s infinity
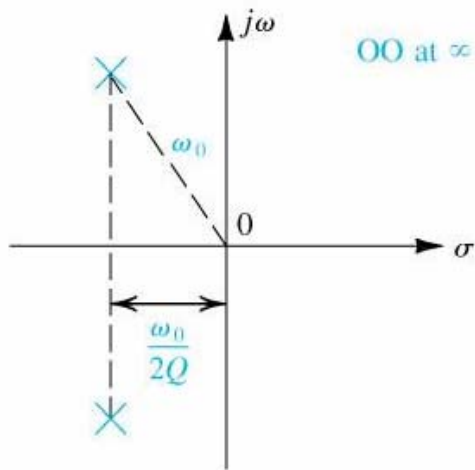
# Lect. 15: Second-Order Passive Filters

How to realize passive second-order LP filter


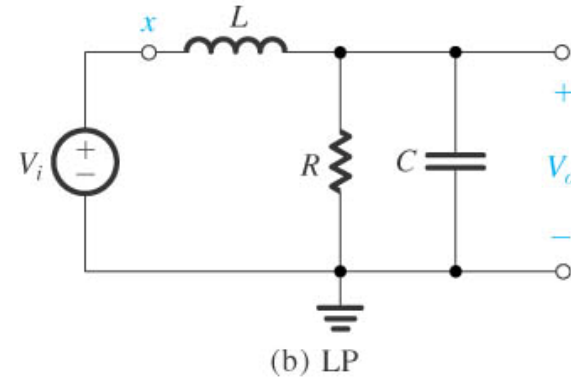
$$T(s) = \frac{a_0}{s^2 + s\frac{\omega_0}{Q} + \omega_0^2}$$




$$T(s) \equiv \frac{V_o}{V_i} = \frac{Z_2}{Z_1 + Z_2} = \frac{Y_1}{Y_1 + Y_2} = \frac{1/sL}{(1/sL) + sC + (1/R)}$$


$$= \frac{1/LC}{s^2 + s(1/CR) + (1/LC)} = \frac{\omega_0^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \frac{\omega_0}{Q} = \frac{1}{CR} \quad Q = \omega_0 CR = \sqrt{\frac{C}{L}} R$$

# Lect. 15: Second-Order Passive Filters

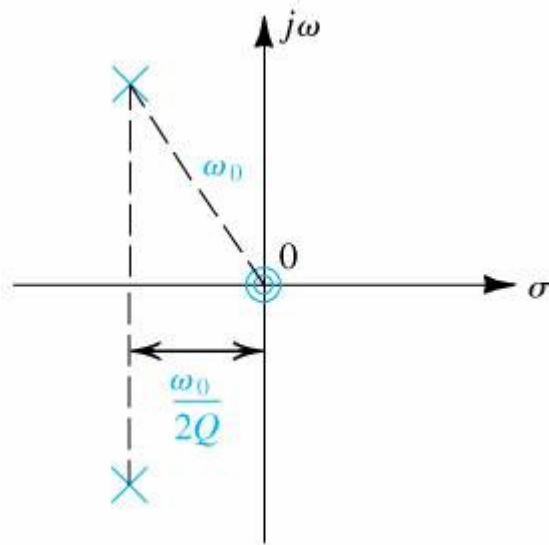

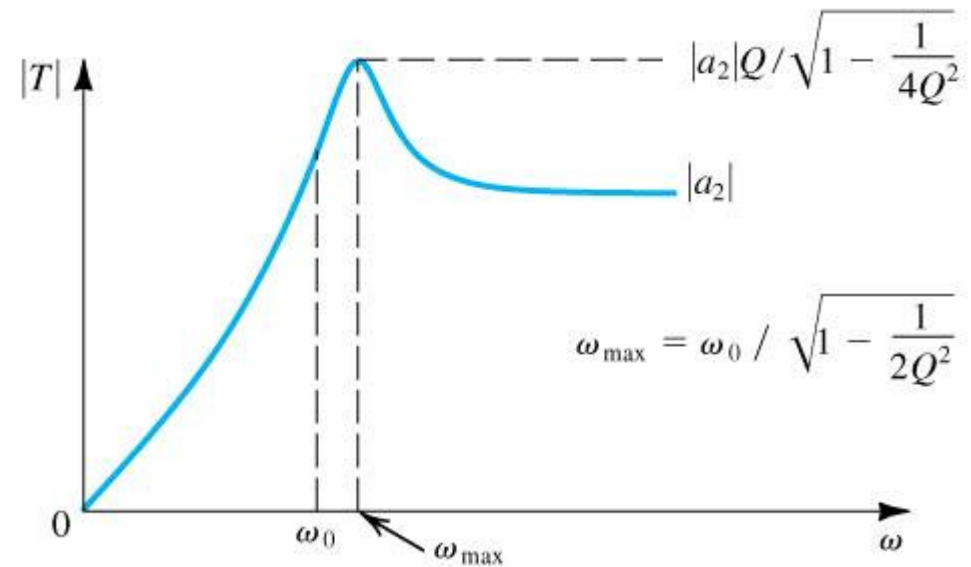
$$T(s) = \frac{a_2 s^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$





HP Filter

# Lect. 15: Second-Order Passive Filters

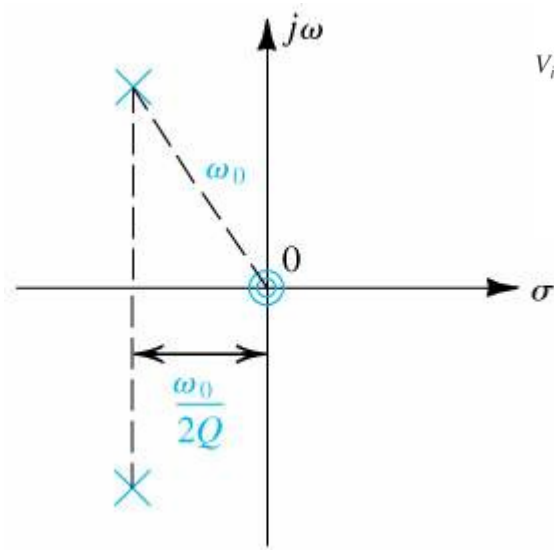
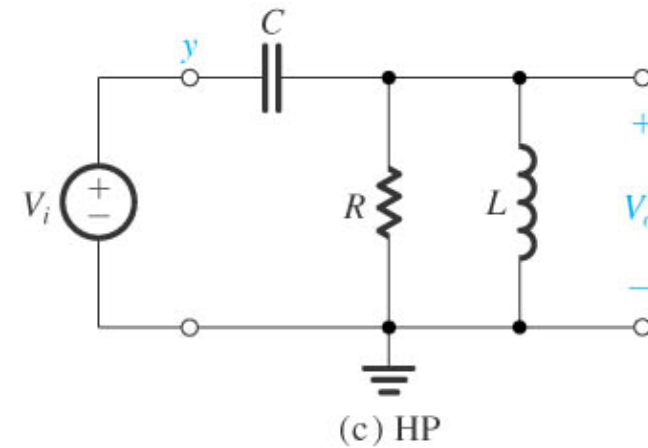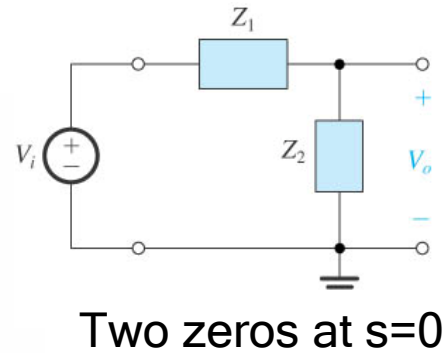
$$T(s) = \frac{a_2 s^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$




$$T(s) \equiv \frac{V_o}{V_i} = \frac{Z_2}{Z_1 + Z_2} = \frac{Y_1}{Y_1 + Y_2} = \frac{sC}{sC + (1/R) + (1/sL)}$$

$$= \frac{s^2}{s^2 + s(1/CR) + (1/LC)}$$


Same pole characteristics as LP filter:  $\omega_0$   $Q$  identical

# Lect. 15: Second-Order Passive Filters

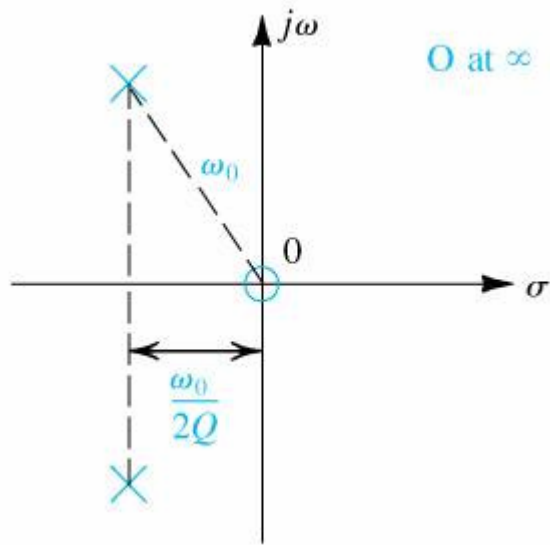

$$T(s) = \frac{a_1 s}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$
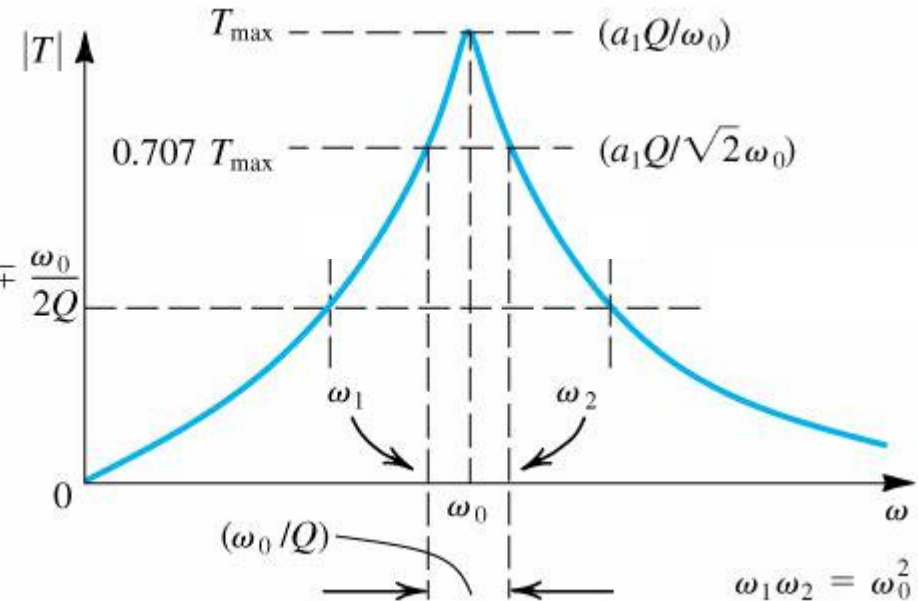
$$\omega_1, \omega_2 = \omega_0 \sqrt{1 + \frac{1}{4Q^2}} \pm \frac{\omega_0}{2Q}$$




3dB bandwidth

BP Filter



Large  $Q \rightarrow$  Sharper response



# Lect. 15: Second-Order Passive Filters

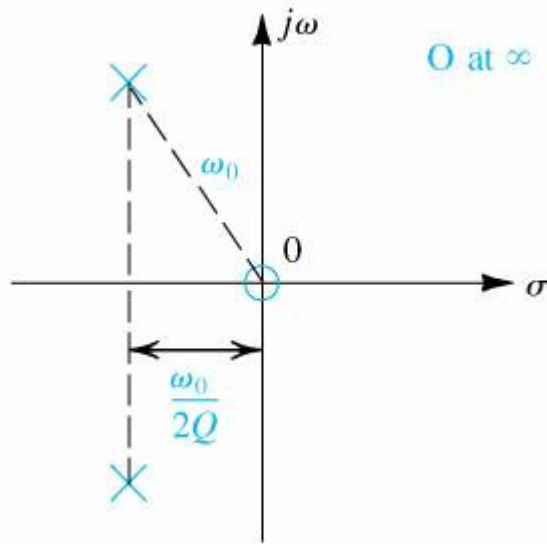
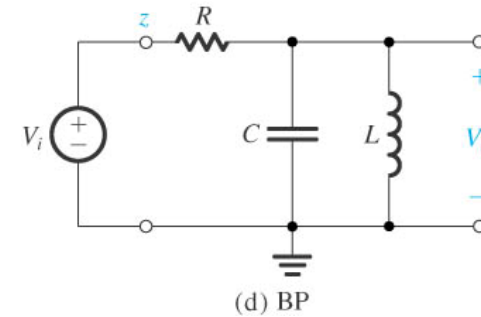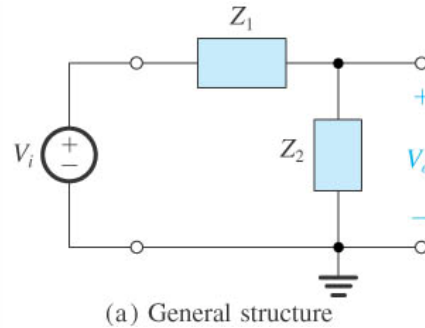
$$T(s) = \frac{a_1 s}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$





$$T(s) = \frac{V_o}{V_i} = \frac{Y_1}{Y_1 + Y_2} = \frac{1/R}{(1/R) + sC + (1/sL)}$$

$$= \frac{s(1/RC)}{s^2 + s(1/RC) + (1/LC)}$$

$$Q = \omega_0 CR = \sqrt{\frac{C}{L}} R$$



# Lect. 15: Second-Order Passive Filters

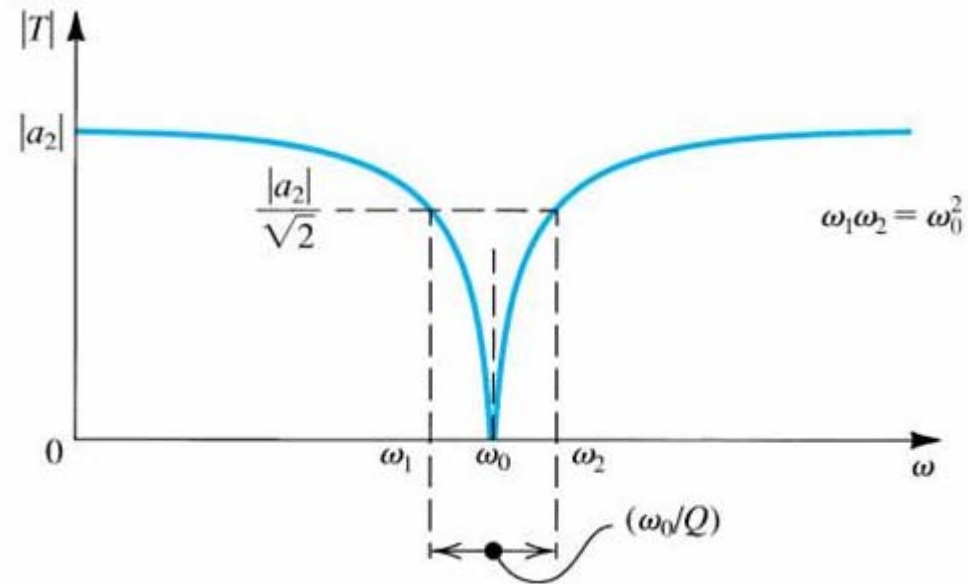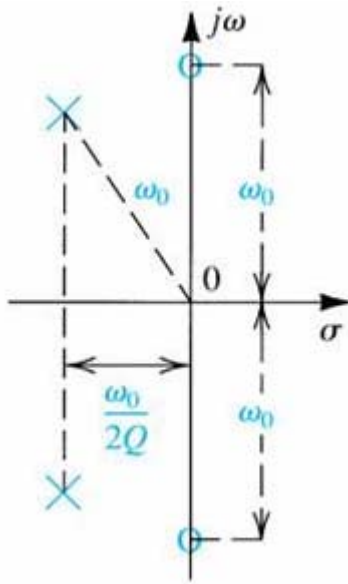

$$T(s) = a_2 \frac{s^2 + \omega_0^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

Band-Rejection or Notch Filter

# Lect. 15: Second-Order Passive Filters

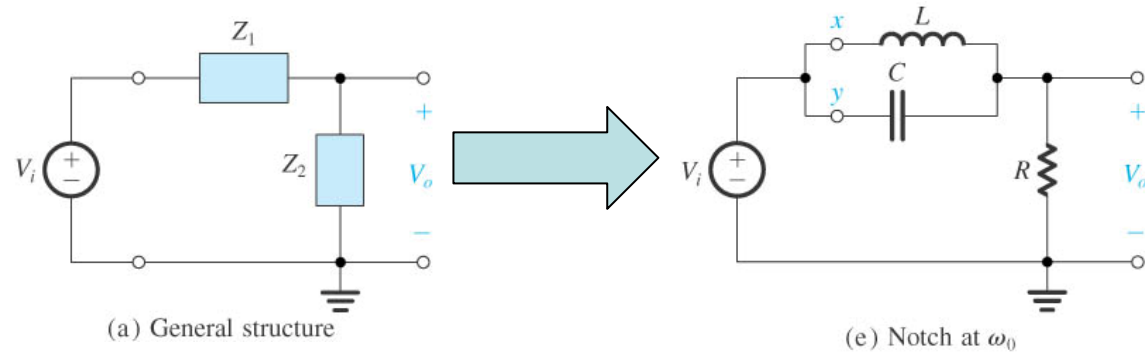
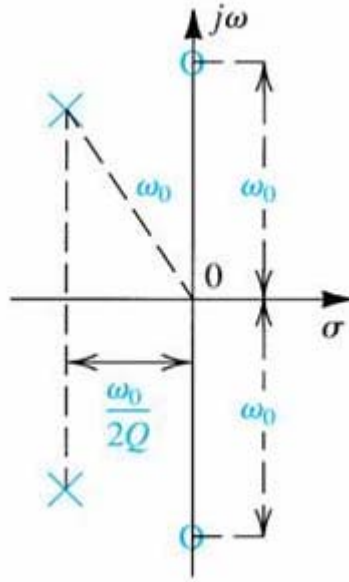


$$Z_1 = \frac{sL \cdot \frac{1}{sC}}{sL + \frac{1}{sC}} = \frac{sL}{1 + s^2LC}$$

$$T(s) = a_2 \frac{s^2 + \omega_0^2}{s^2 + s\frac{\omega_0}{Q} + \omega_0^2}$$

$$T(s) = \frac{V_o}{V_i} = \frac{Z_2}{Z_1 + Z_2} = \frac{R}{\frac{sL}{1 + s^2LC} + R} = \frac{s^2 + (1/LC)}{s^2 + s(1/RC) + (1/LC)}$$

# Lect. 15: Second-Order Passive Filters

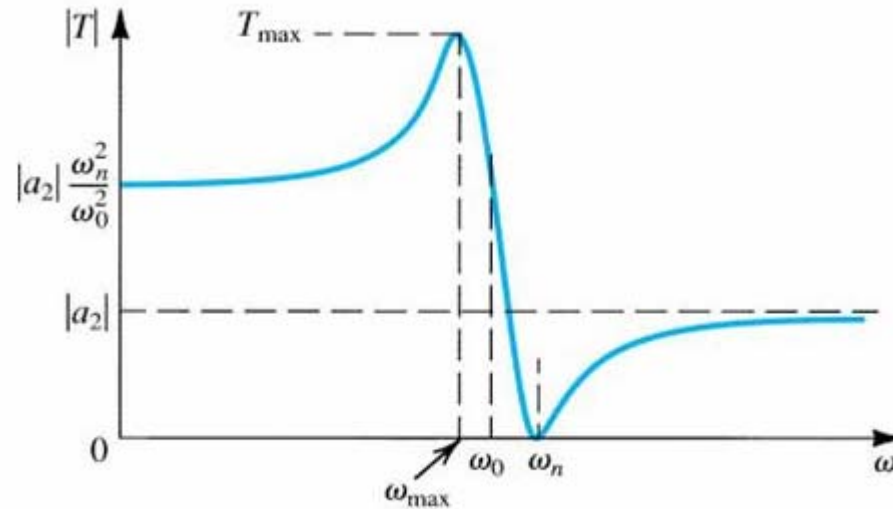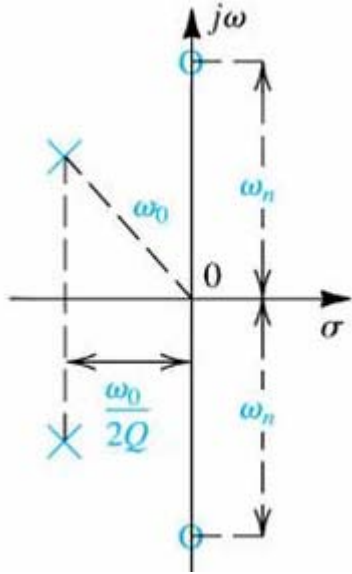


Low-Pass Notch Filter

$$T(s) = a_2 \frac{s^2 + \omega_n^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

$\omega_n \geq \omega_0$

DC gain =  $a_2 \frac{\omega_n^2}{\omega_0^2}$



High-frequency gain =  $a_2$

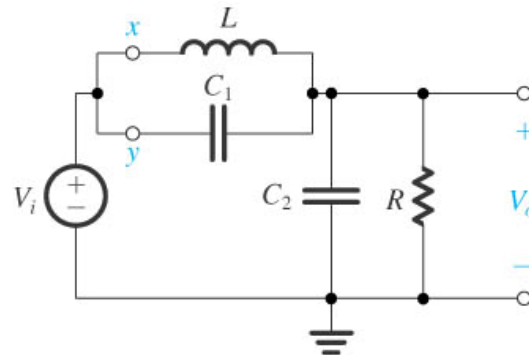

(g) LPN ( $\omega_n > \omega_0$ )

$$T(s) = \frac{s^2 + (1/LC_1)}{s^2 + s \frac{1}{(C_1 + C_2)R} + \frac{1}{L(C_1 + C_2)}}$$

# Lect. 15: Second-Order Passive Filters

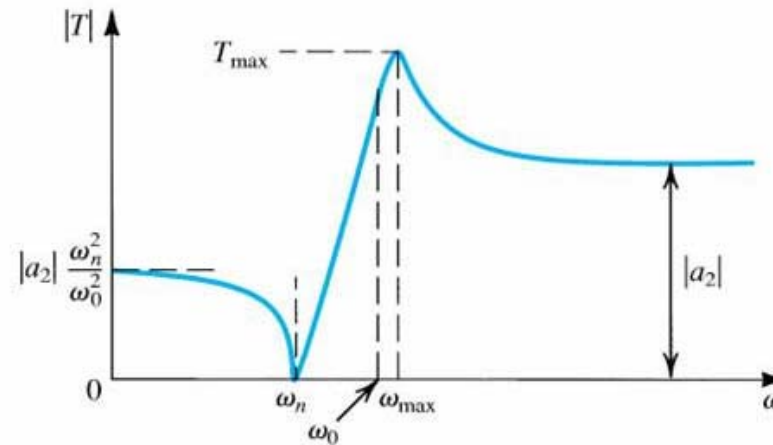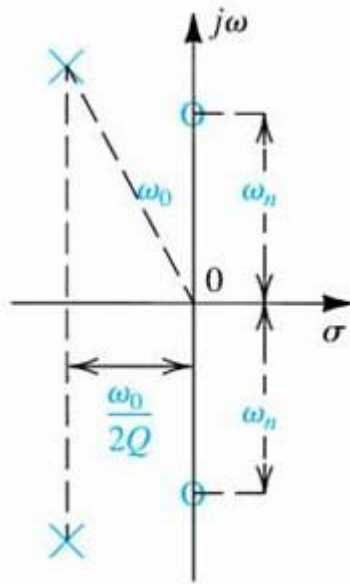


High-Pass Notch Filter

$$T(s) = a_2 \frac{s^2 + \omega_n^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

$$\omega_n \leq \omega_0$$

$$\text{DC gain} = a_2 \frac{\omega_n^2}{\omega_0^2}$$


$$\text{High-frequency gain} = a_2$$

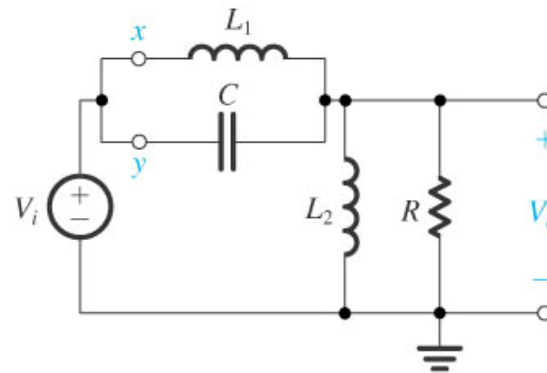


(i) HPN ( $\omega_n < \omega_0$ )

$$T(s) = \frac{s^2 + (1/L_1 C)}{s^2 + s(1/CR) + [1/(L_1 \parallel L_2)C]}$$


# Lect. 15: Second-Order Passive Filters

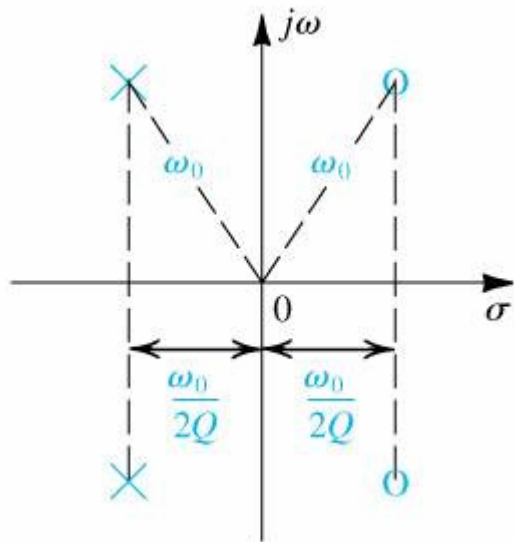
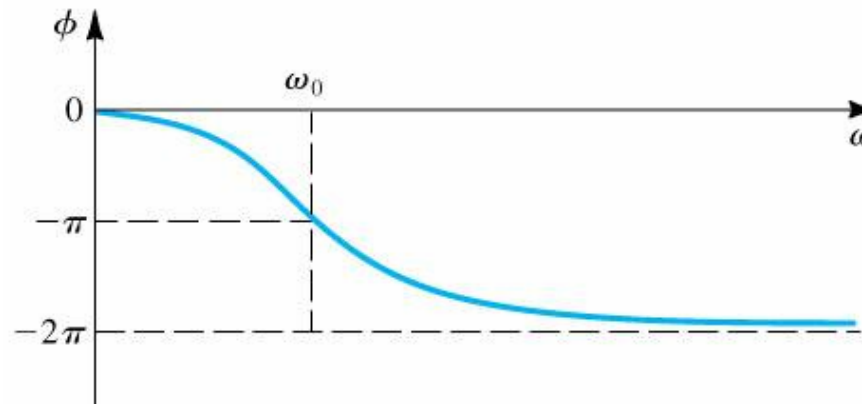
$$T(s) = a_2 \frac{s^2 - s \frac{\omega_0}{Q} + \omega_0^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$



# Lect. 15: Second-Order Passive Filters

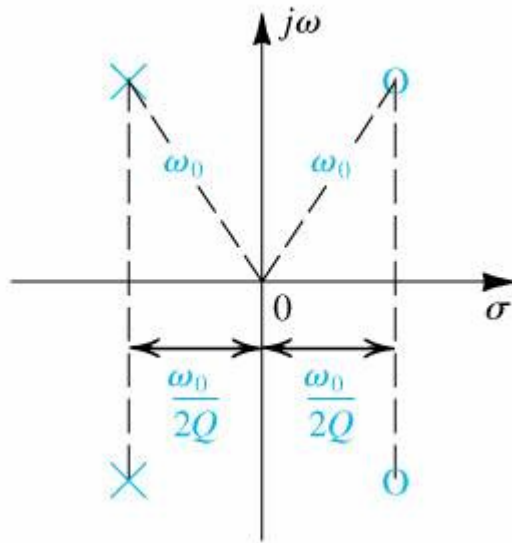

$$T(s) = a_2 \frac{s^2 - s \frac{\omega_0}{Q} + \omega_0^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

$$T(s) = \frac{s^2 - s(\omega_0/Q) + \omega_0^2}{s^2 + s(\omega_0/Q) + \omega_0^2} = 1 - \frac{s2(\omega_0/Q)}{s^2 + s(\omega_0/Q) + \omega_0^2}$$

$$= 2 \left( \frac{1}{2} - \frac{s(\omega_0/Q)}{s^2 + s(\omega_0/Q) + \omega_0^2} \right)$$

