
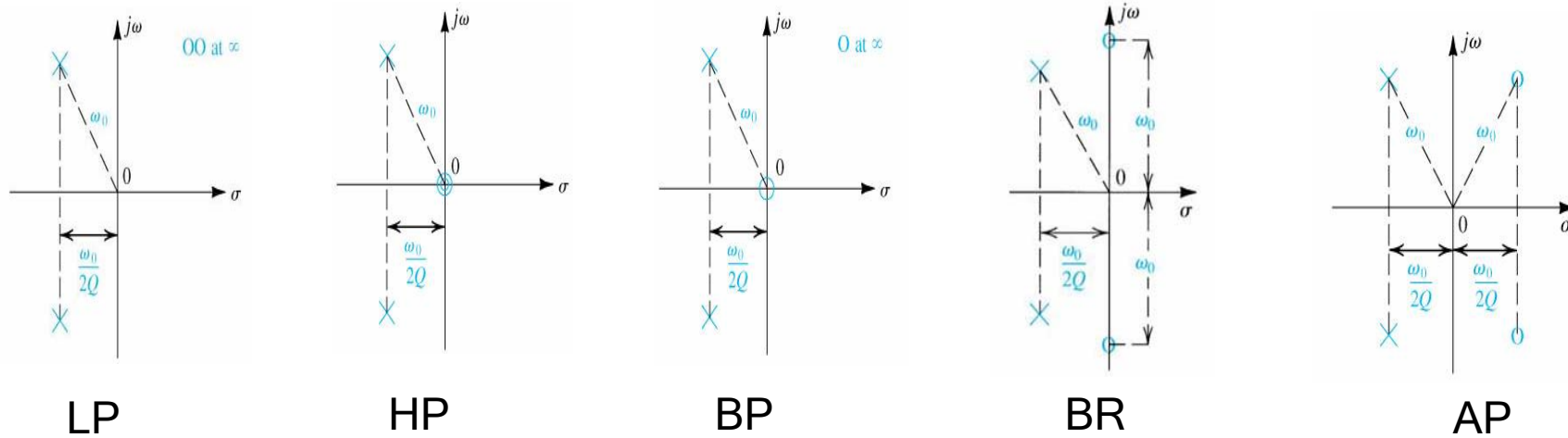


# Lect. 16: Second-Order Active Filters (S&S 12.6)

## 2nd-order filters

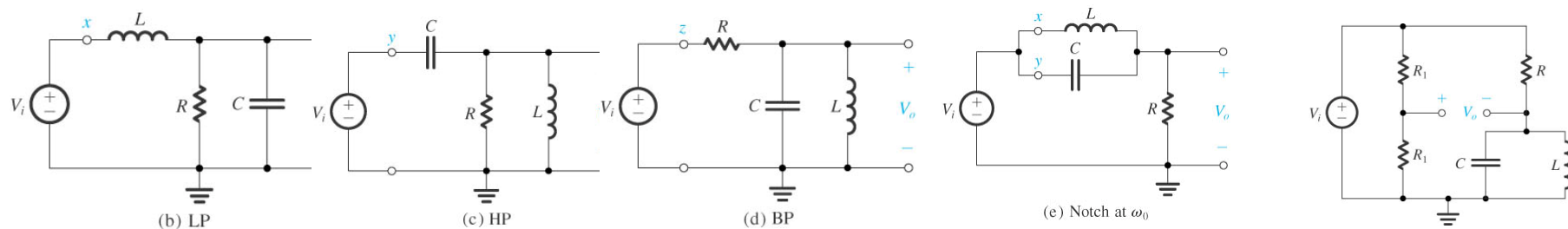

## Passive Realization




## Active Realization?

Replace inductor with op-amp circuit


# Lect. 16: Second-Order Active Filters
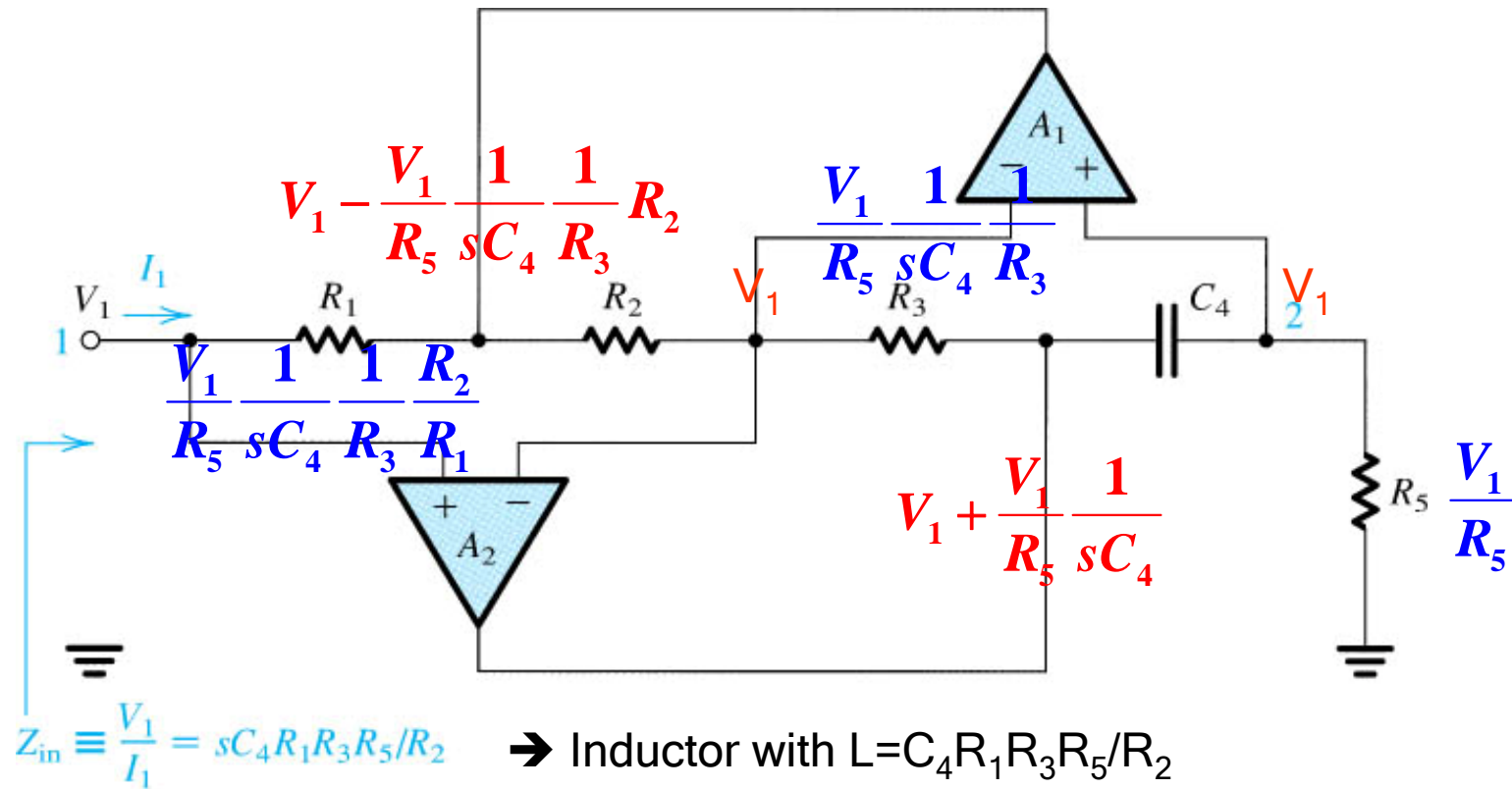
## Antoniou Inductance-Simulation Circuit





(a)

# Lect. 16: Second-Order Active Filters

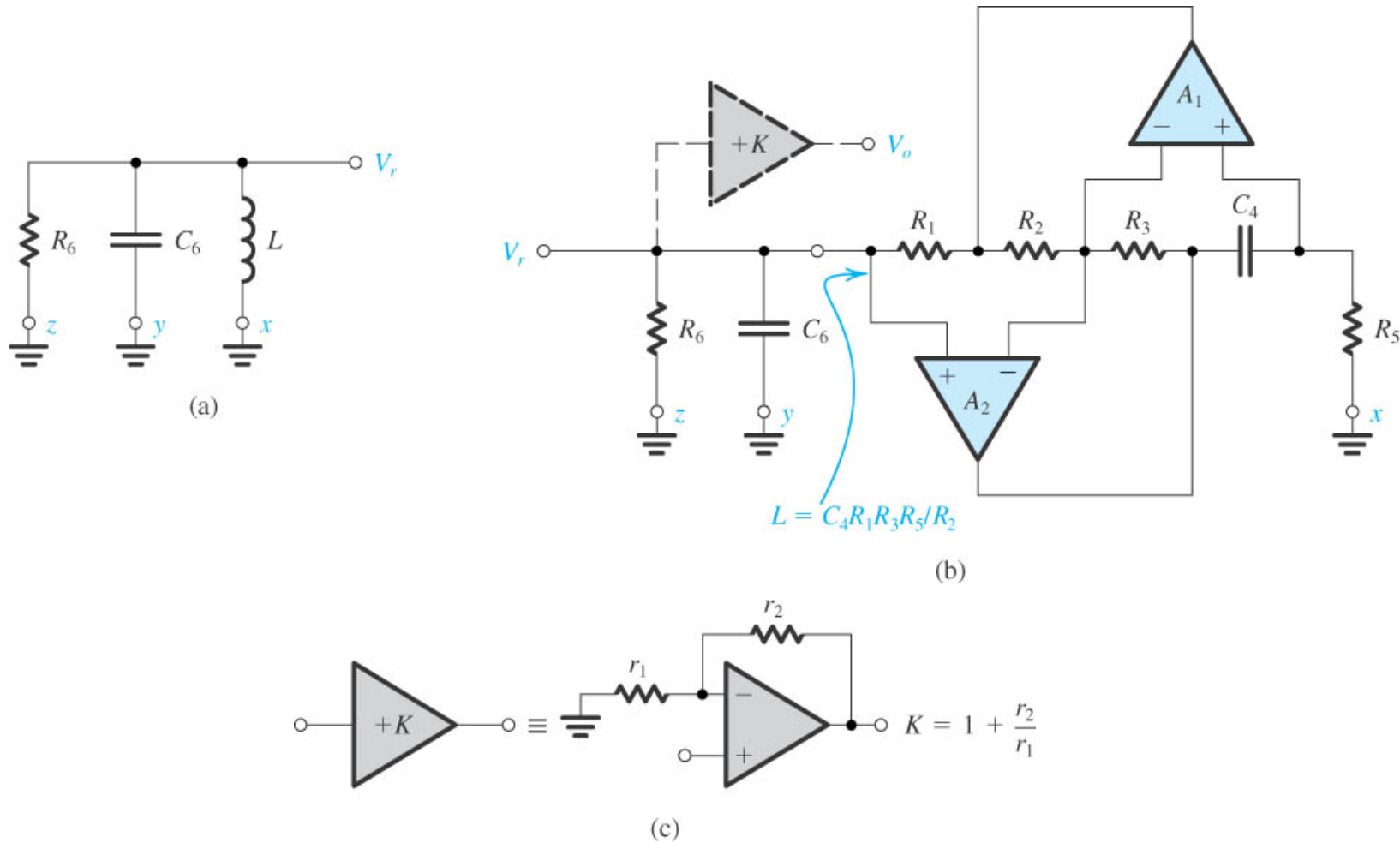

# Lect. 16: Second-Order Active Filters

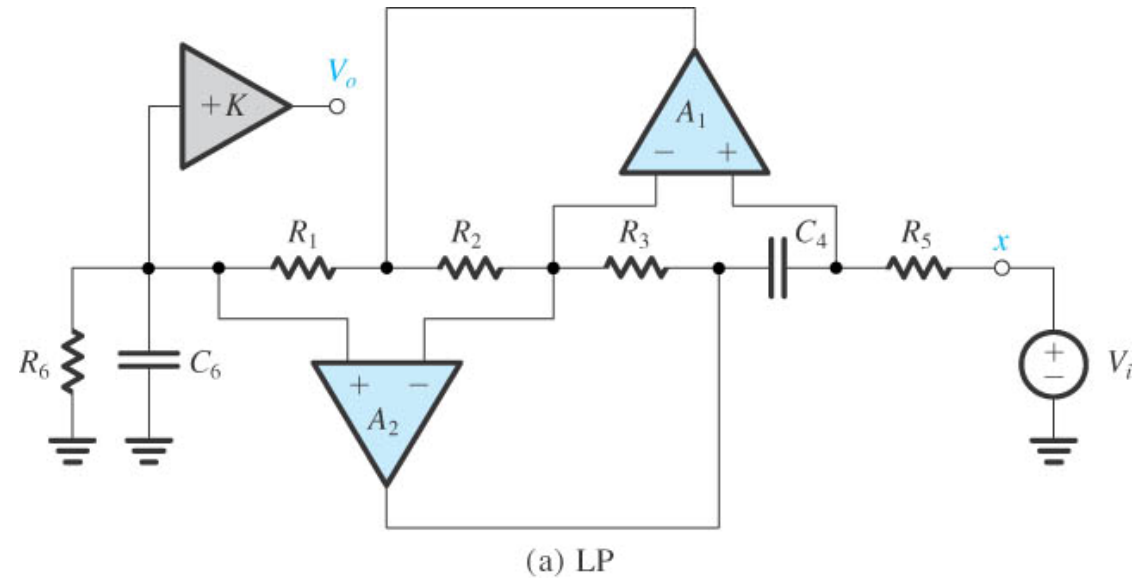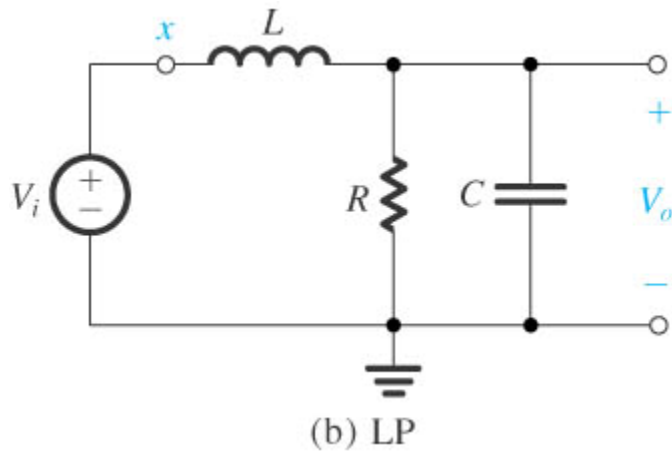


$$T(s) = \frac{\omega_0^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad Q = \sqrt{\frac{C}{L}}R$$


→ Replace L with  $C_4 R_1 R_3 R_5 / R_2$

Multiply K

# Lect. 15: Second-Order Active Filters

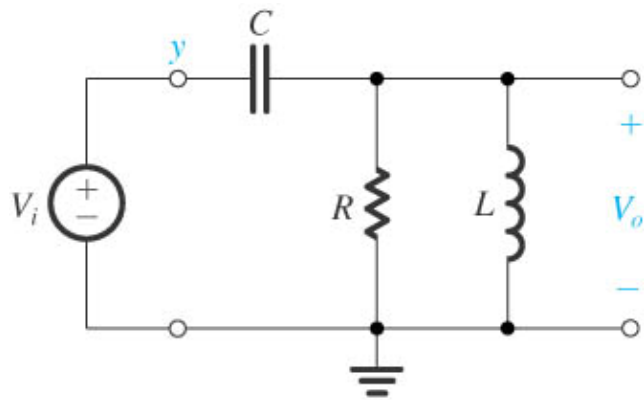


HP Filter

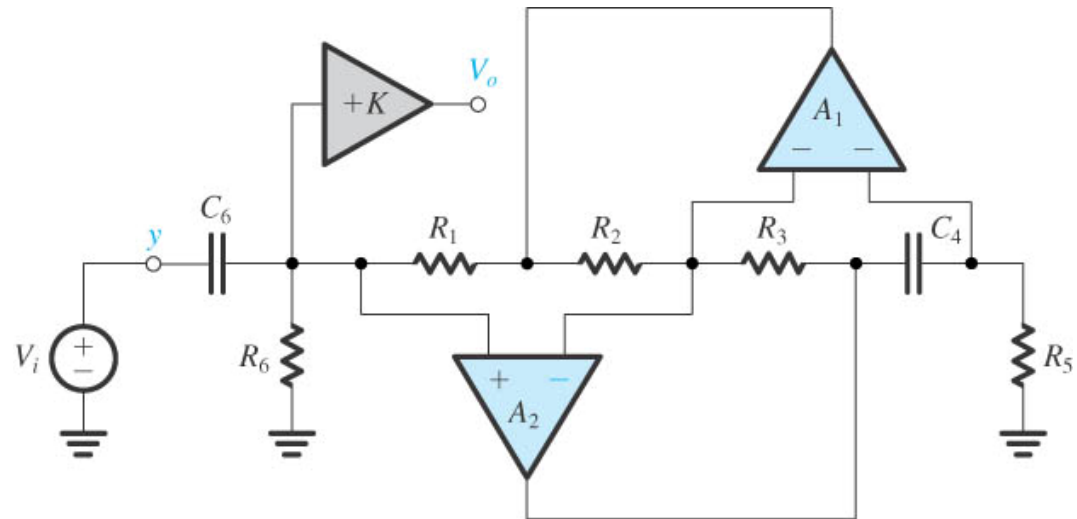


→ Replace  $L$  with  $C_4 R_1 R_3 R_5 / R_2$

Multiply  $K$


# Lect. 15: Second-Order Active Filters

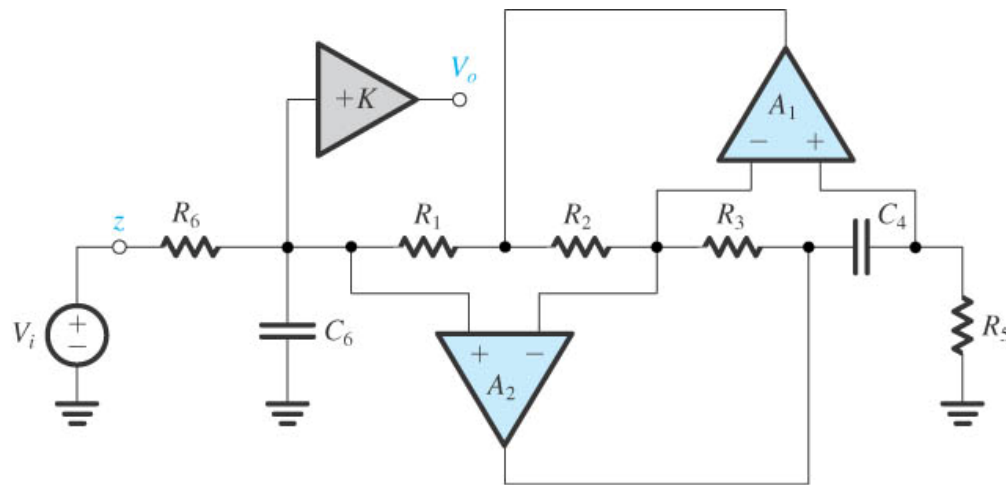


# Lect. 16: Second-Order Active Filters

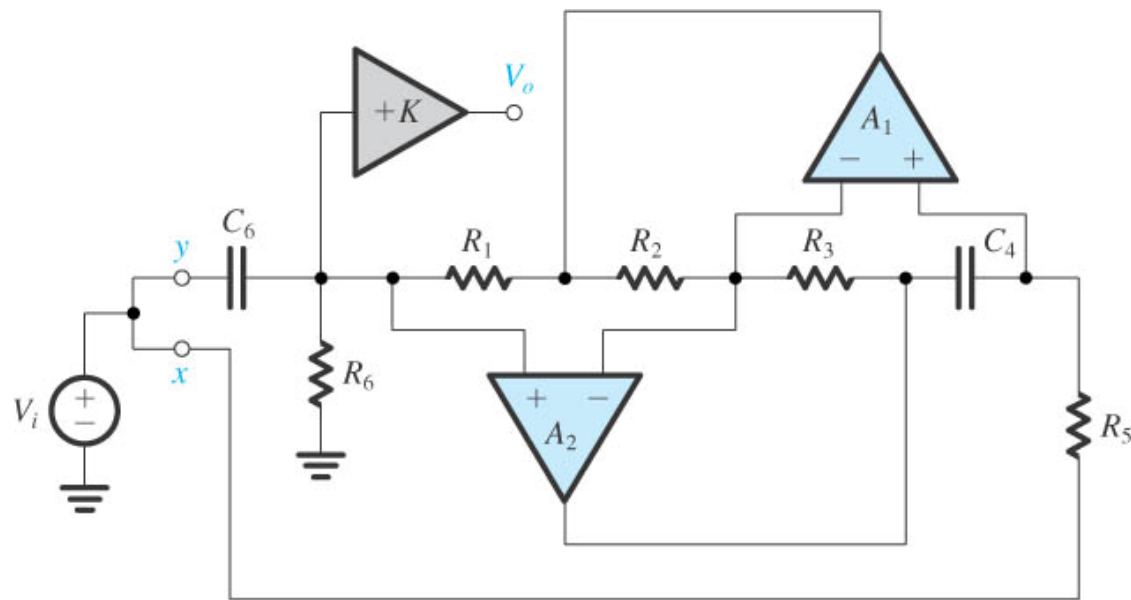

# Lect. 16: Second-Order Active Filters

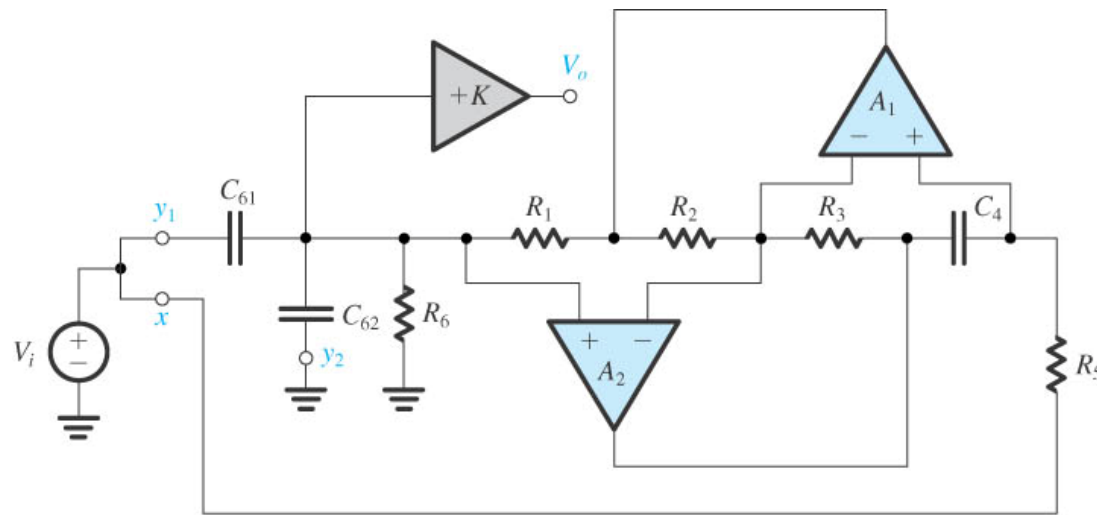


(e) LPN,  $\omega_n \geq \omega_0$

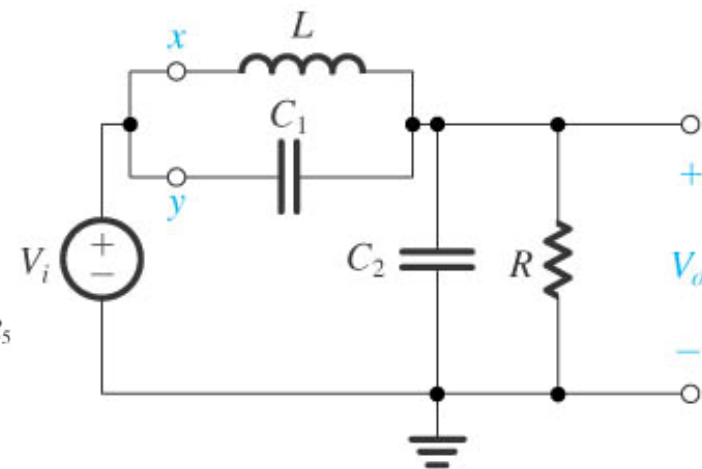


(g) LPN ( $\omega_n > \omega_0$ )



# Lect. 16: Second-Order Active Filters

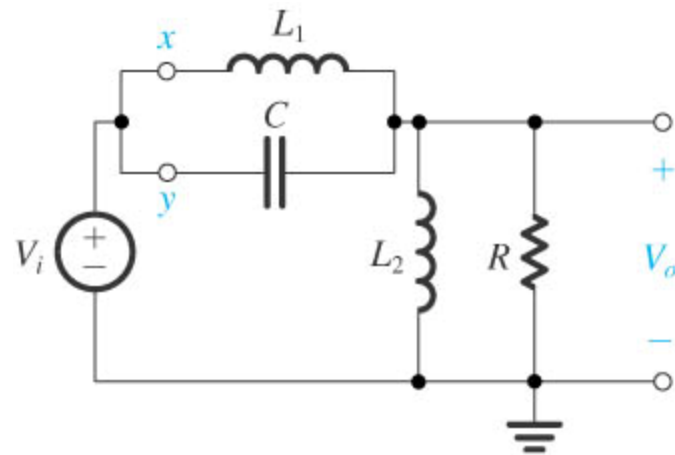

(i) HPN ( $\omega_n < \omega_0$ )

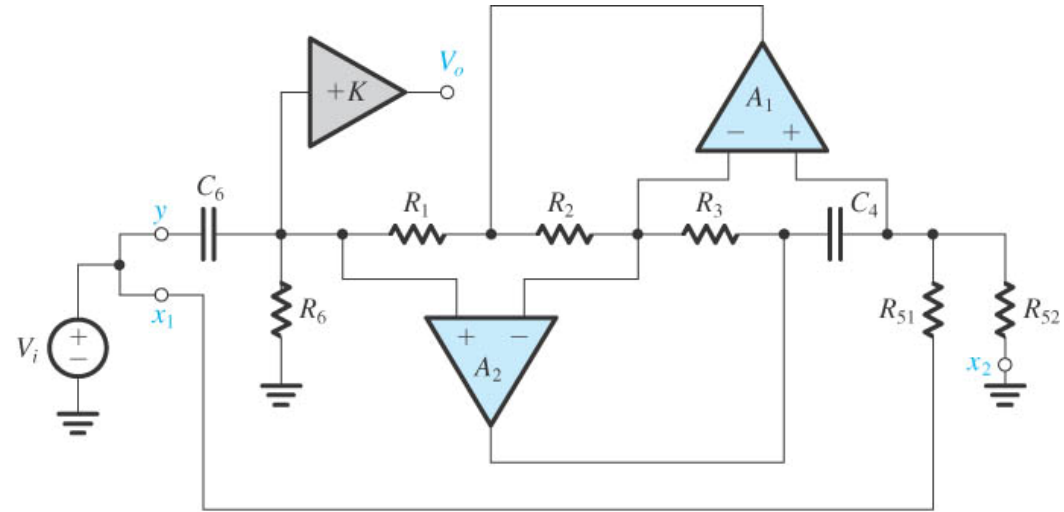

(f) HPN,  $\omega_n \leq \omega_0$


$$L_1 = C_4 R_1 R_3 R_{51} / R_2$$

$$L_2 = C_4 R_1 R_3 R_{52} / R_2$$


# Lect. 16: Second-Order Active Filters

## First-Order All-Pass Filter

Remember

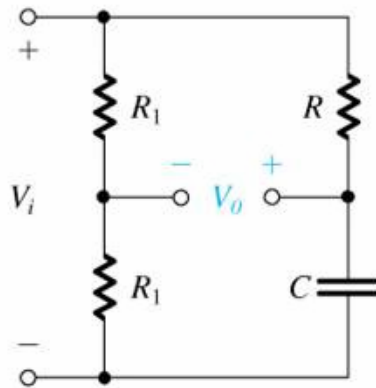

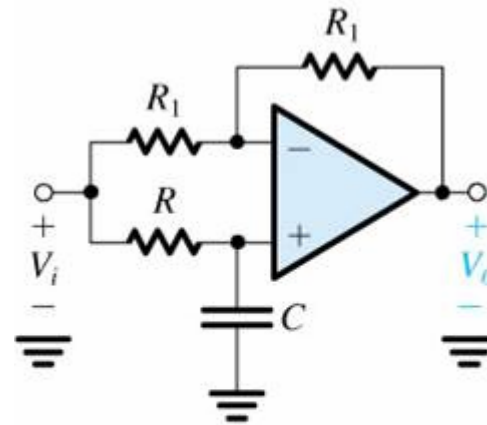$CR = 1/\omega_0$   
Flat gain ( $a_1$ ) = 0.5



$CR = 1/\omega_0$   
Flat gain ( $a_1$ ) = 1

$$V^+ = V_i \frac{1/sC}{1/sC + R}$$

$$V^- = \frac{V_i + V_o}{2}$$



$$V_i \frac{2}{1 + sRC} = V_i + V_o$$

$$V_o = 2V_i \left( \frac{1}{1 + sRC} - \frac{1}{2} \right)$$

$$\frac{V_o}{V_i} = -\frac{sRC - 1}{sRC + 1}$$


# Lect. 16: Second-Order Active Filters

## Second-Order All-Pass Filter

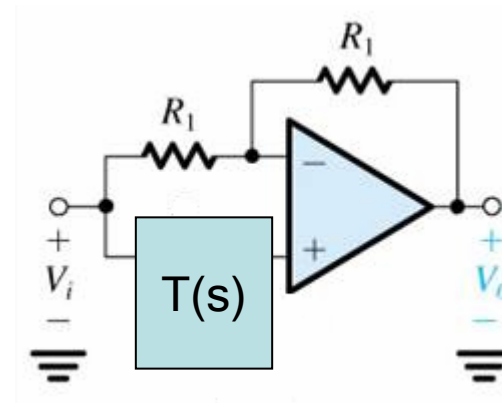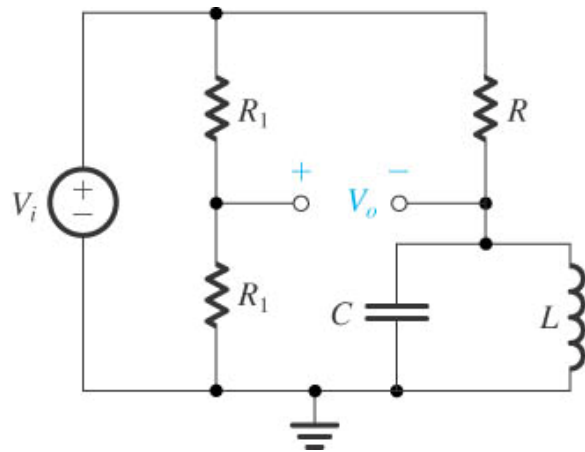

$T(s)$ : Bandpass Filter

# Lect. 16: Second-Order Active Filters

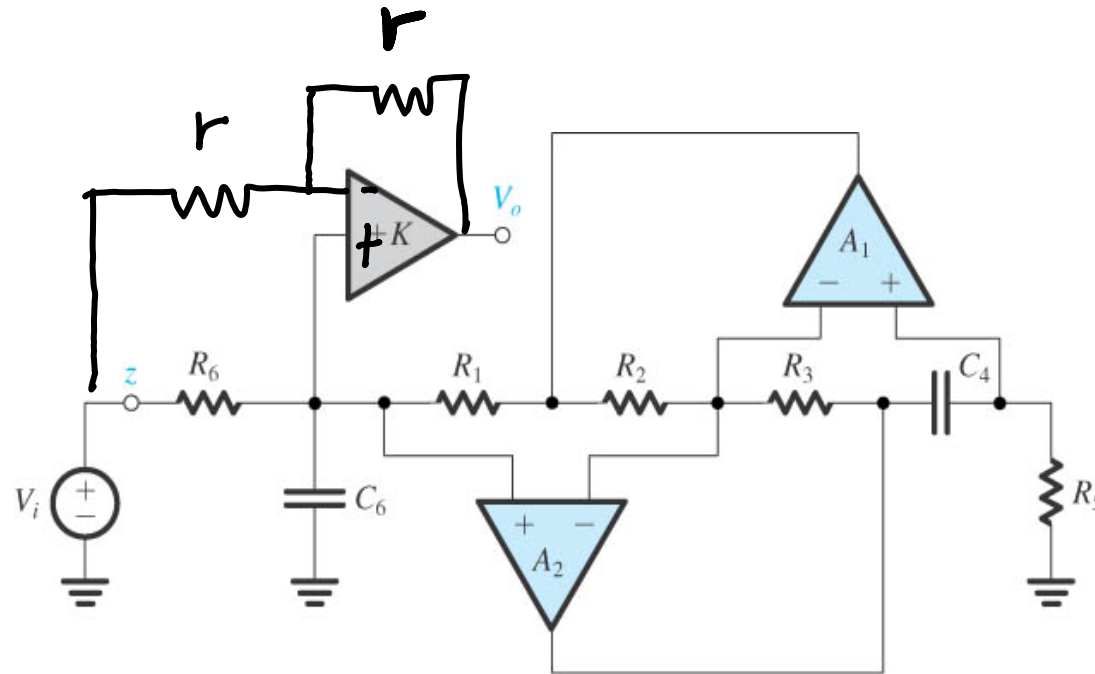

Second-order Bandpass Filter

→ Second-Order All-Pass Filter