
 
 


Lect. 21: CMOS Logic Gates (S&S 10.3)


CMOS inverter

 

Different transistor acting for pull-down and pull-up operation
(NMOS) (PMOS)


Lect. 21: CMOS Logic Gates

CMOS Logic Gates

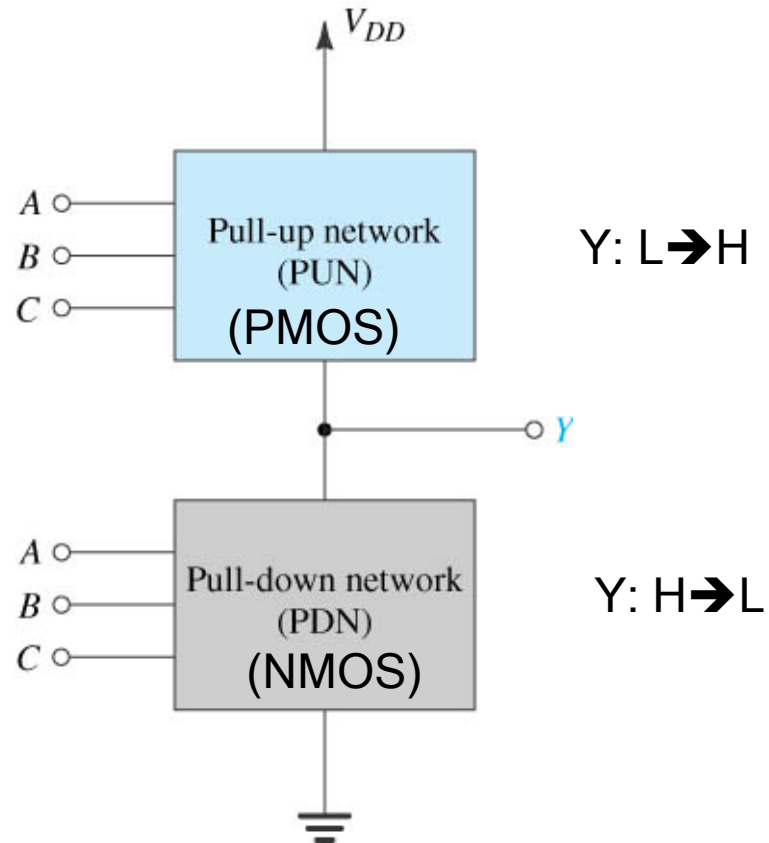

Lect. 21: CMOS Logic Gates

Examples of pull-down networks

 

Y pull-down, if A high OR B high
→ Q_A or Q_B ON


For Y pull-up, A low AND B low
→ Q_A and Q_B OFF

Logic Operation: $\bar{Y} = A + B$

→ NOR Gate

Lect. 21: CMOS Logic Gates

Examples of pull-down networks

 

Y pull-down, if A high AND B high

→ Q_A and Q_B ON

For Y pull-up, A low OR B low


→ Q_A or Q_B OFF

Logic Operation: $\bar{Y} = AB$

→ NAND Gate

Lect. 21: CMOS Logic Gates


Examples of pull-down networks

 

$$\bar{Y} = A + BC$$

Lect. 21: CMOS Logic Gates

Examples of pull-up networks

 

Y pull-up, if A low OR B low
→ Q_A or Q_B ON


For Y pull-down, A high AND B high
→ Q_A and Q_B OFF

Logic Operation: $Y = \bar{A} + \bar{B}$

→ NAND Gate

Lect. 21: CMOS Logic Gates

Examples of pull-up networks

 

Y pull-up, if A low AND B low
→ Q_A and Q_B ON



For Y pull-down, A high or B high
→ Q_A or Q_B OFF

Logic Operation: $Y = \overline{A\overline{B}}$

→ NOR Gate

Lect. 21: CMOS Logic Gates

CMOS NOR Gate

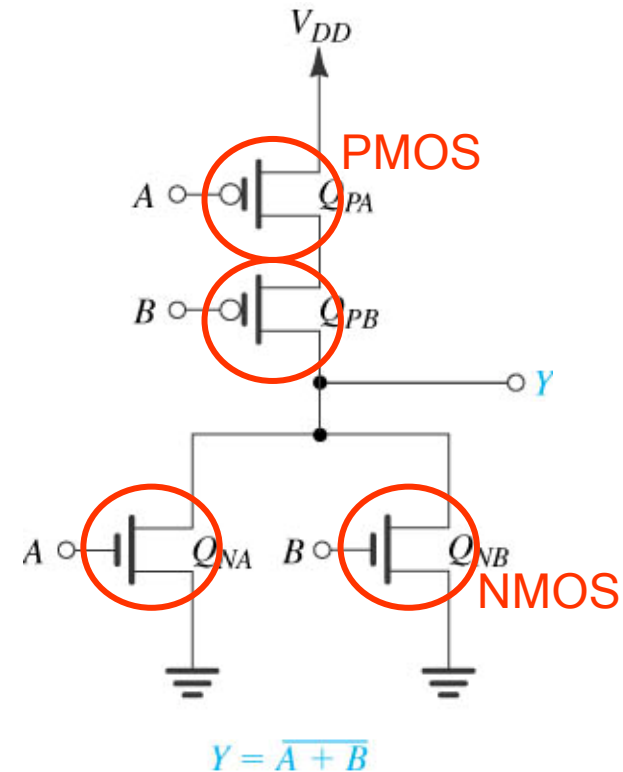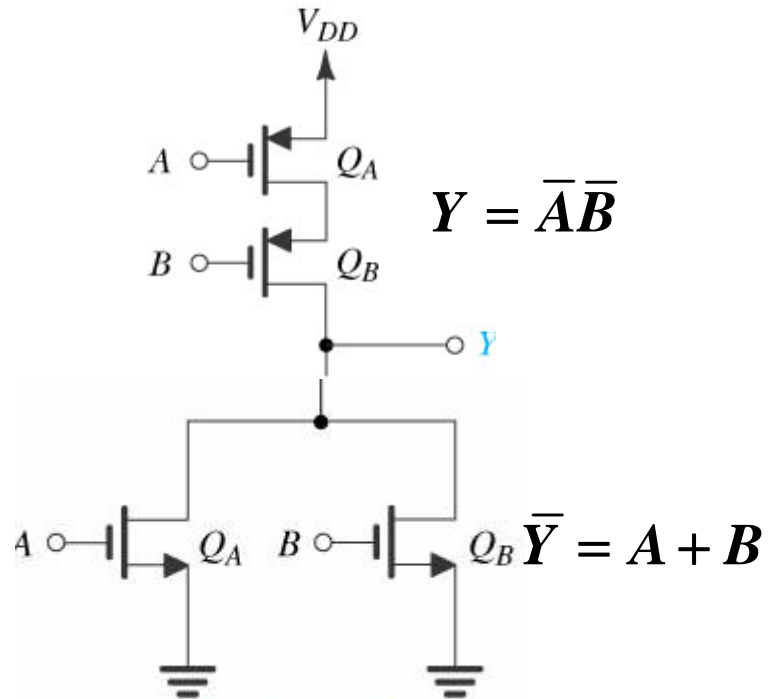


PUN: complemented input

PDN: complemented output

Structures of PUN and PDN have the duality property

Lect. 21: CMOS Logic Gates

 

CMOS NAND Gate

Lect. 21: CMOS Logic Gates

CMOS XOR (Exclusive OR)

A: 0 1 0 1

B: 0 0 1 1

XOR: 0 1 1 0

$$Y = A\bar{B} + \bar{A}B \rightarrow \text{PUN}$$

$$\bar{Y} = AB + \bar{A}\bar{B} \rightarrow \text{PDN}$$

