
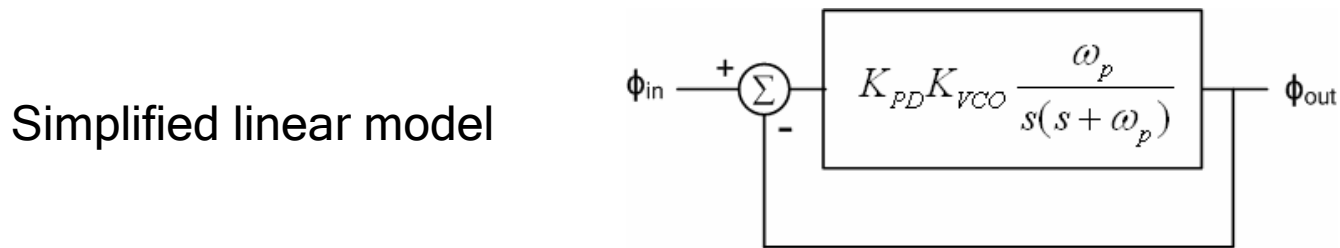
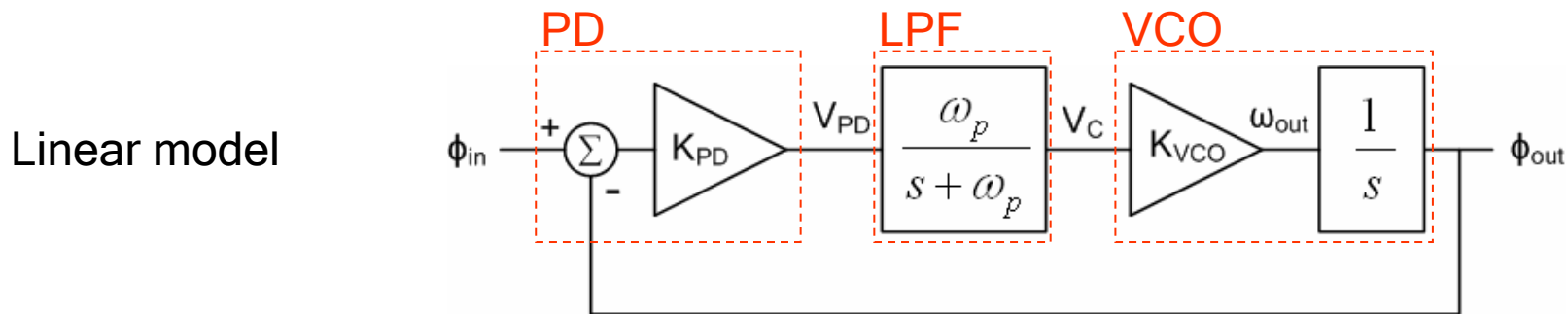


Lect. 23: PLL(2)


Linear PLL model:

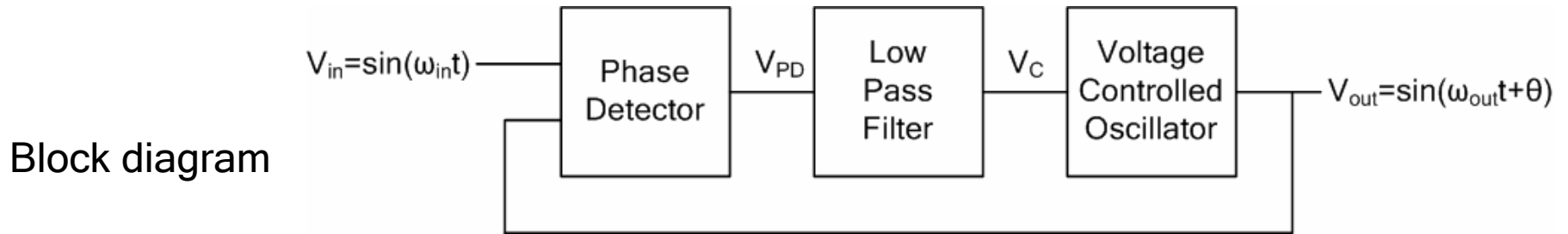

Lect. 23: PLL(2)

Open loop gain:
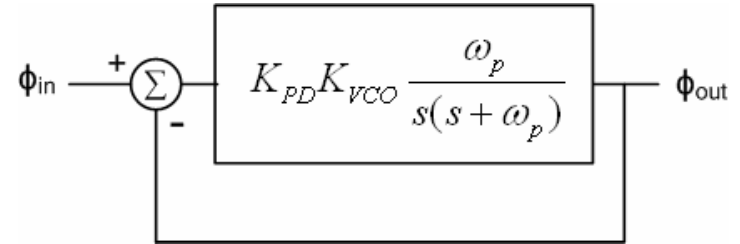
$$G(s) = K_{PD} K_{VCO} \frac{\omega_p}{s(s + \omega_p)}$$




Closed loop gain (transfer function): 2nd order low-pass filter

$$\begin{aligned} H(s) &= \frac{\phi_{out}}{\phi_{in}} = \frac{G(s)}{1 + G(s)} = \frac{K_{PD} K_{VCO} \frac{\omega_p}{s(s + \omega_p)}}{1 + K_{PD} K_{VCO} \frac{\omega_p}{s(s + \omega_p)}} \\ &= \frac{K_{PD} K_{VCO} \omega_p}{s^2 + \omega_p s + K_{PD} K_{VCO} \omega_p} \end{aligned}$$

Lect. 23: PLL(2)

Transfer function of PLL
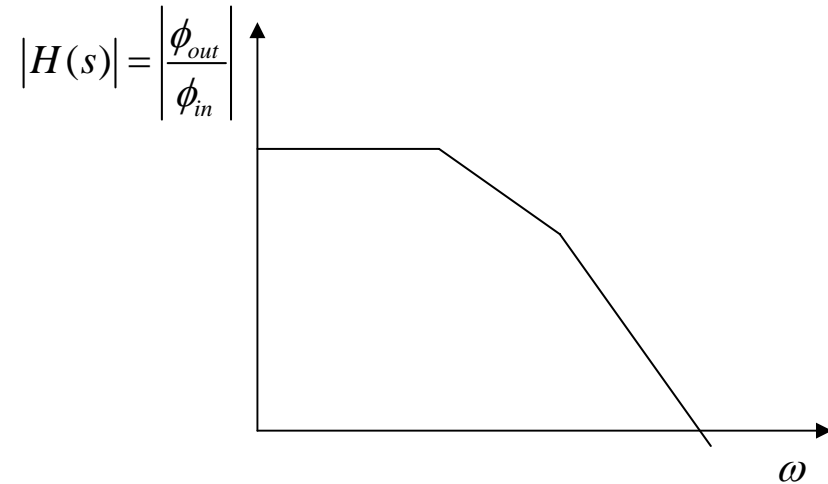
$$H(s) = \frac{\phi_{out}}{\phi_{in}} = \frac{K_{PD}K_{VCO}\omega_p}{s^2 + \omega_p s + K_{PD}K_{VCO}\omega_p}$$





Note that input and output of PLL model are '*phase*'.

What does ω mean in x-axis?

Lect. 23: PLL(2)

In LPF,



$$|H(s)| = \left| \frac{V_{out}}{V_{in}} \right|$$

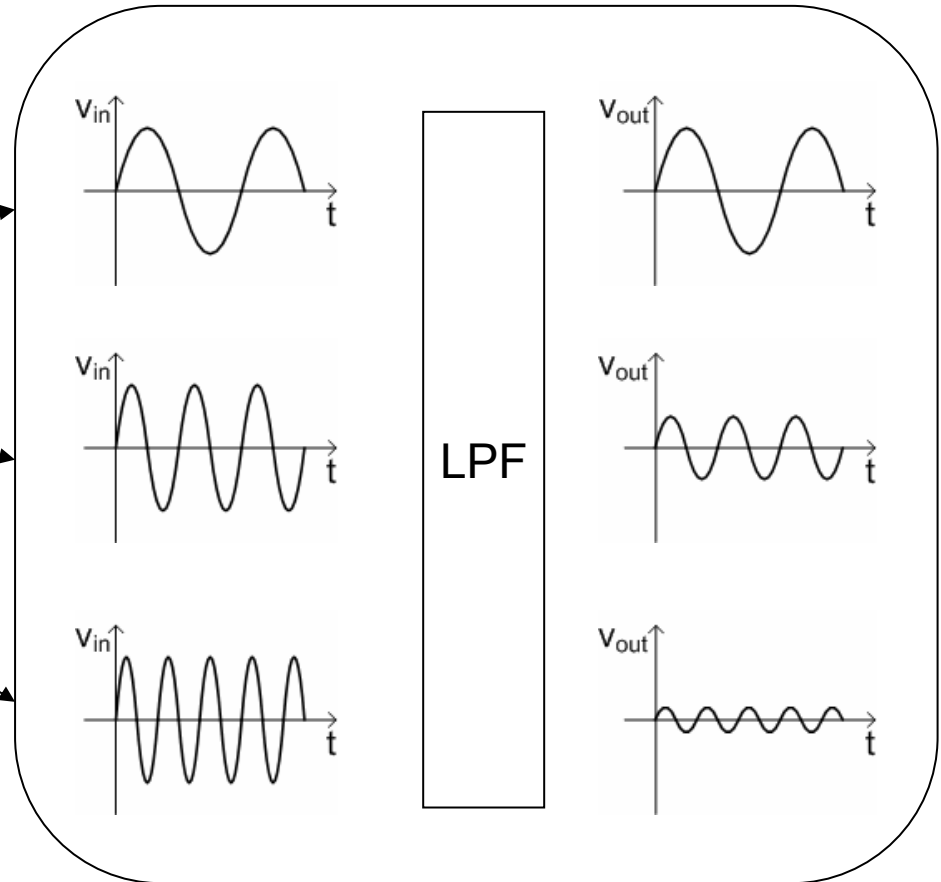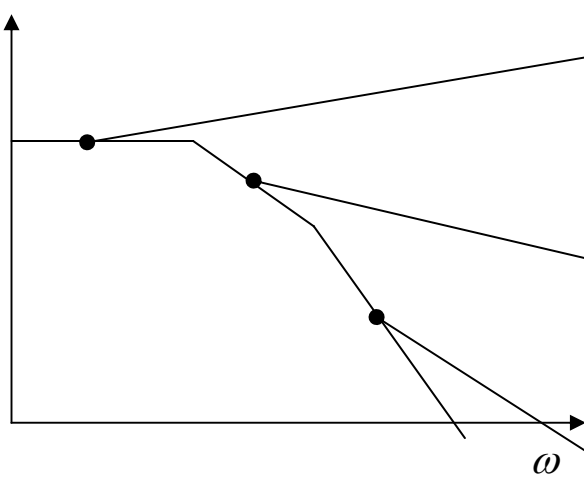

Lect. 23: PLL(2)

In PLL,

$$|H(s)| = \left| \frac{\phi_{out}}{\phi_{in}} \right|$$

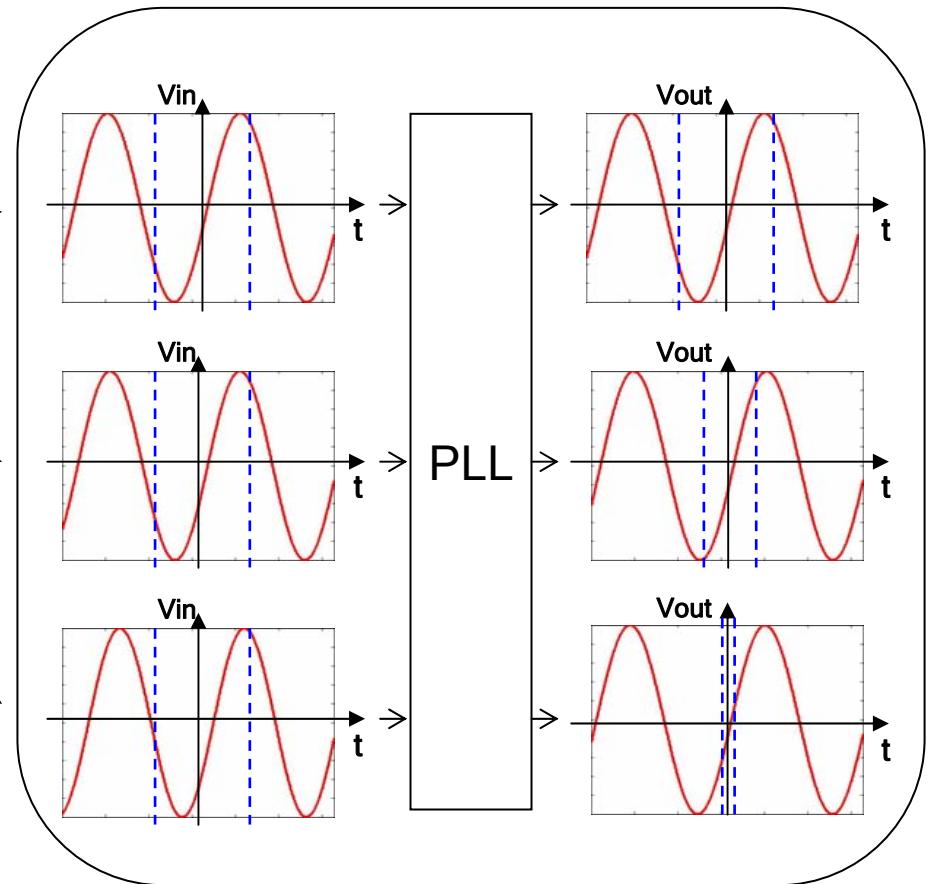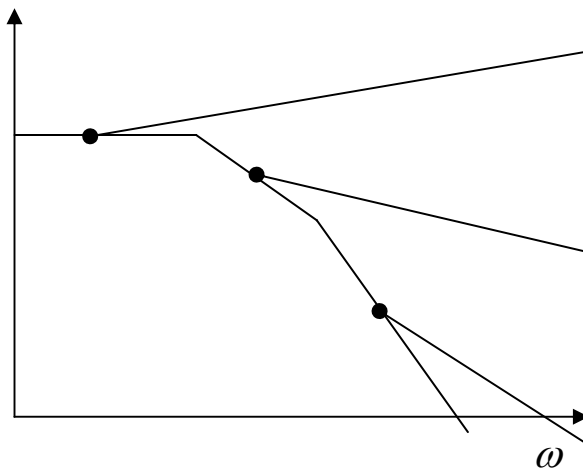

Lect. 23: PLL(2)

$$H(s) = \frac{\phi_{out}}{\phi_{in}} = \frac{K_{PD}K_{VCO}\omega_p}{s^2 + \omega_p s + K_{PD}K_{VCO}\omega_p}$$

In general 2nd order form,

$$H(s) = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

Natural frequency $\omega_n = \sqrt{\omega_p K_{PD} K_{VCO}}$

Damping ratio $\zeta = \frac{1}{2} \sqrt{\frac{\omega_p}{K_{PD} K_{VCO}}}$

Two poles $s_{1,2} = -\zeta\omega_n \pm \sqrt{(\zeta^2 - 1)\omega_n^2}$

Lect. 23: PLL(2)

Step response


$$H(s) = \frac{\phi_{out}}{\phi_{in}} = \frac{\omega_{out}/s}{\omega_{in}/s} = \frac{\omega_{out}}{\omega_{in}} = \frac{K_{PD}K_{VCO}\omega_p}{s^2 + \omega_p s + K_{PD}K_{VCO}\omega_p}$$

$$\omega_{in}(t) = \Delta\omega \cdot u(t)$$

$$\omega_{out}(t) = \left\{ 1 - e^{-\zeta\omega_n t} \left[\cos(\omega_n \sqrt{1-\zeta^2} \cdot t) + \frac{\zeta}{\sqrt{1-\zeta^2}} \sin(\omega_n \sqrt{1-\zeta^2} \cdot t) \right] \right\} \Delta\omega \cdot u(t)$$

$$= \left[1 - \frac{1}{\sqrt{1-\zeta^2}} e^{-\zeta\omega_n t} \sin(\omega_n \sqrt{1-\zeta^2} \cdot t + \theta) \right] \Delta\omega \cdot u(t)$$




$$\text{where } \theta = \sin^{-1} \sqrt{1-\zeta^2}$$

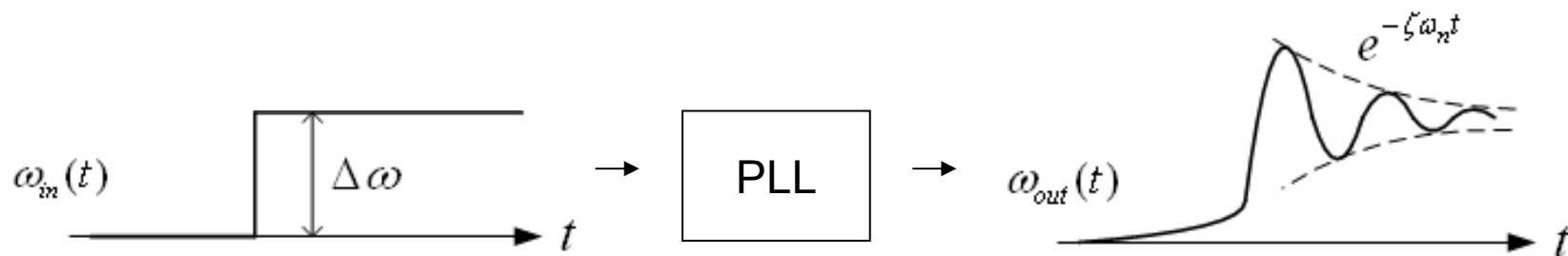

Lect. 23: PLL(2)

Step response simulation using CPPSIM


Simulation setup: $\omega_{in} = 1\text{Hz}$, $\Delta\omega_{in} = 0.01\text{Hz}$, $K_{PD} = 5\text{V/rad}$, $K_{VCO} = 2\pi \times 0.01\text{rad/s/V}$

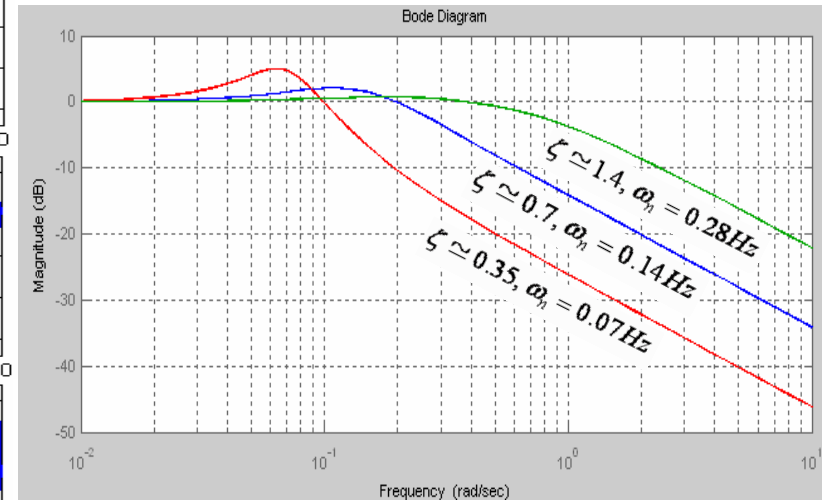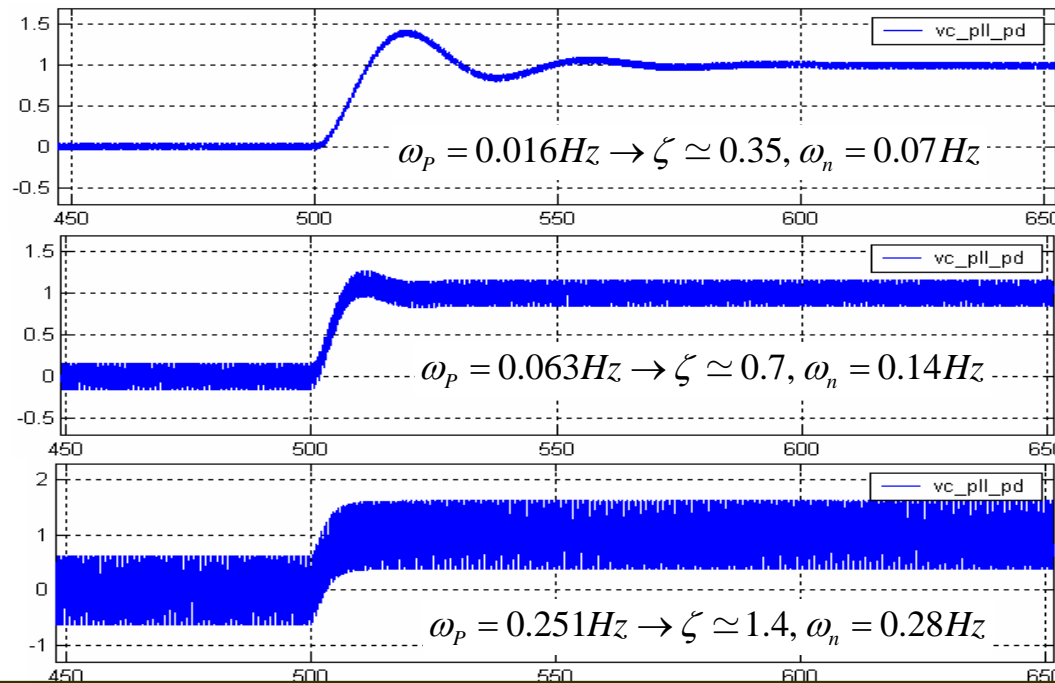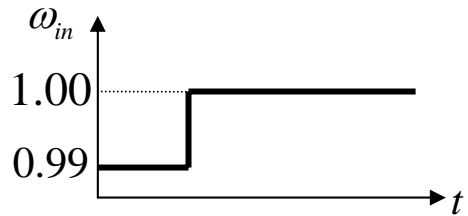



Lect. 23: PLL(2)

Building Blocks: VCO

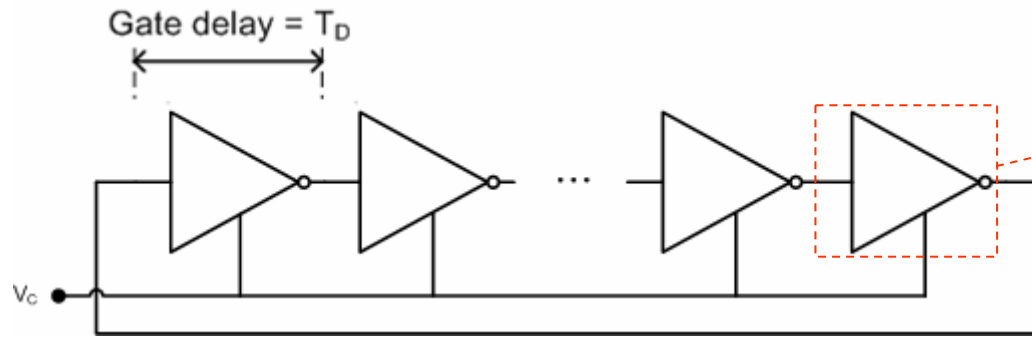→ Ring-oscillator (Odd-stage chain of inverters)



$$T = 2nT_D \quad f = \frac{1}{T} = \frac{1}{2nT_D}$$

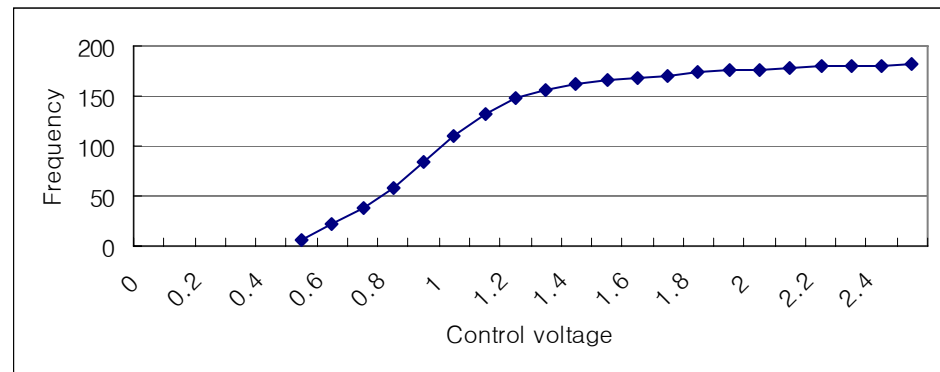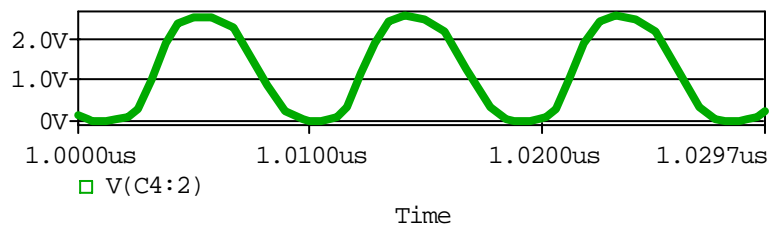


Lect. 23: PLL(2)

Problems of PLL using PD

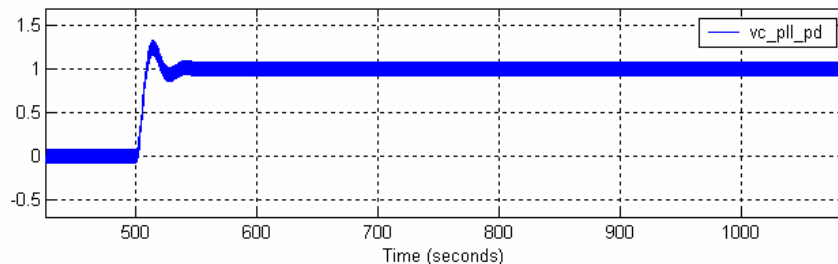
1. Narrow acquisition range \rightarrow PLL acquisition range is roughly on the order of ω_p .

Simulation setup: $\omega_{in} = 1\text{Hz}$, $K_{PD} = 5\text{V} / \text{rad}$, $K_{VCO} = 2\pi \times 0.01\text{rad} / \text{s} / \text{V}$, and $\omega_p = 0.032\text{Hz}$

$\Delta\omega_{in} = 0.01\text{Hz}$ (Locked)



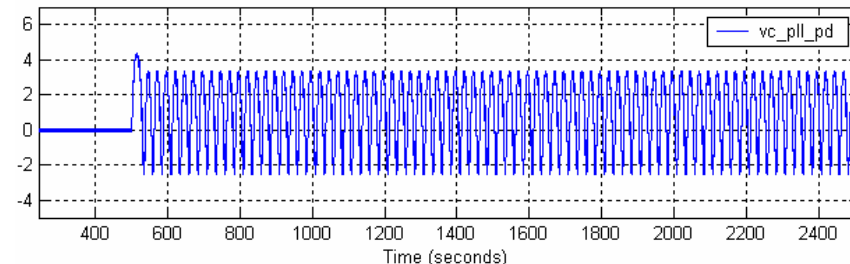$\Delta\omega_{in} = 0.05\text{Hz}$ (Lock failed)






2. ζ and loop bandwidth (1st pole) can not be independently determined.

$$\omega_n = \sqrt{\omega_p K_{PD} K_{VCO}} \quad \zeta = \frac{1}{2} \sqrt{\frac{\omega_p}{K_{PD} K_{VCO}}} \quad s_1 = -\zeta\omega_n + \sqrt{(\zeta^2 - 1)\omega_n^2}$$

Lect. 23: PLL(2)

Solutions!


Phase and Frequency Detector (PFD)

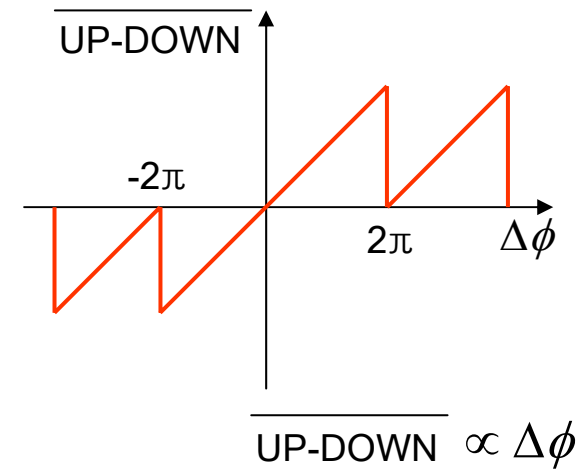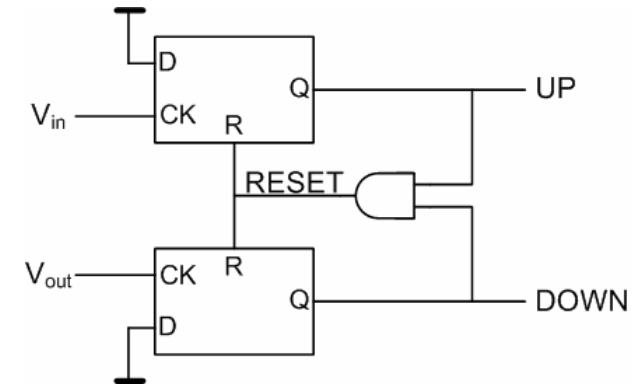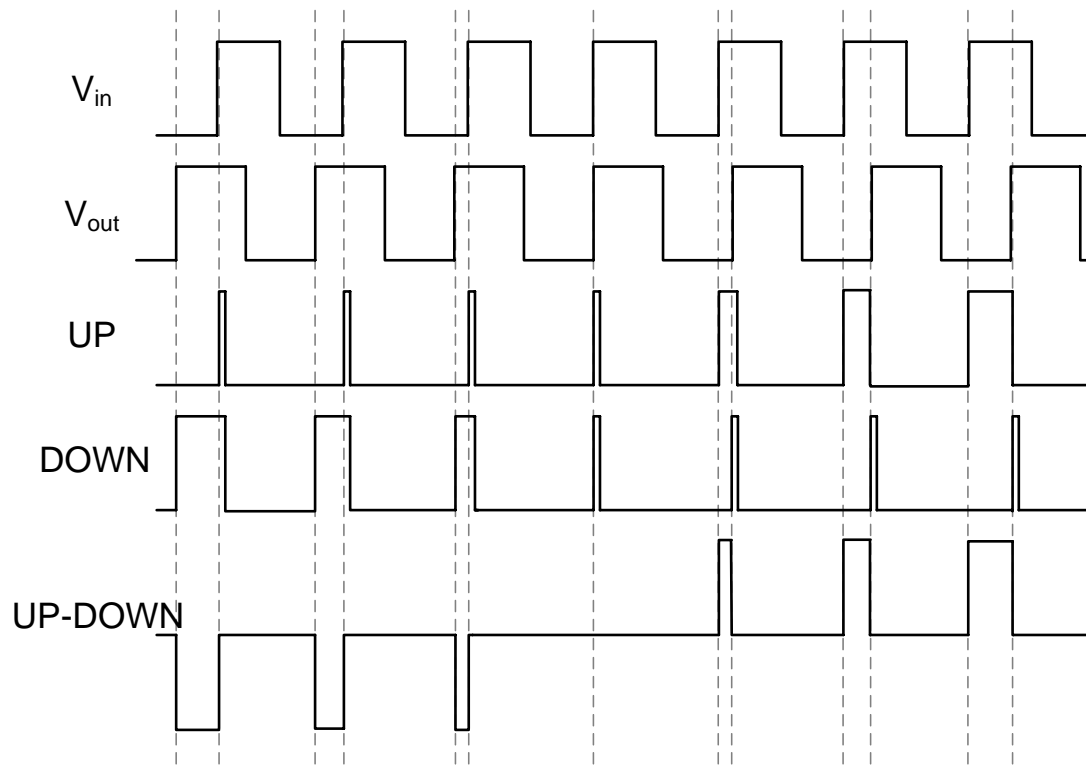


Lect. 23: PLL(2)

Subtraction and integration

Voltage mode
using OP amplifiers

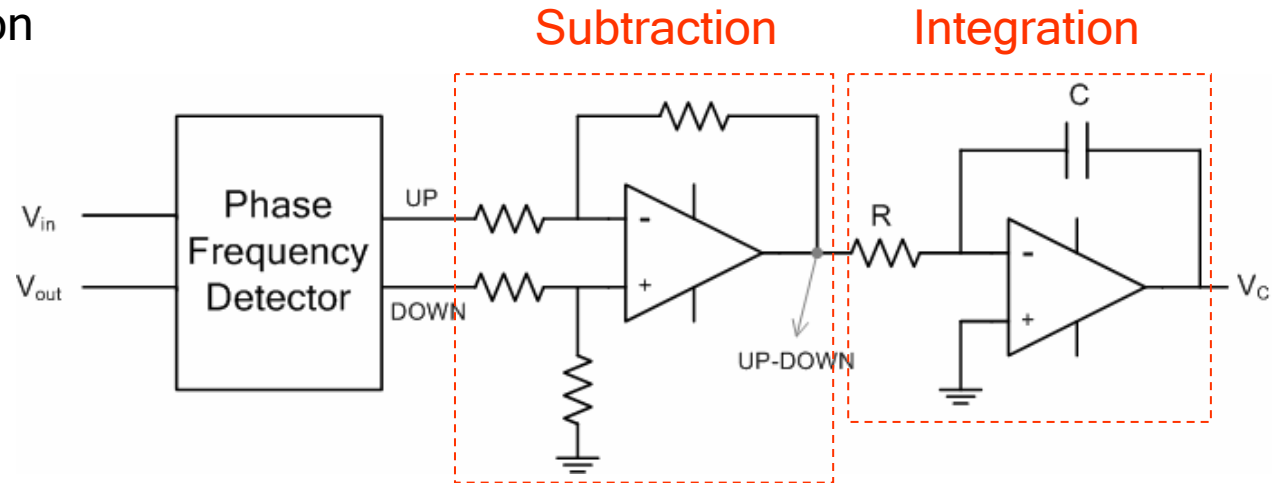


Current mode
using charge pump

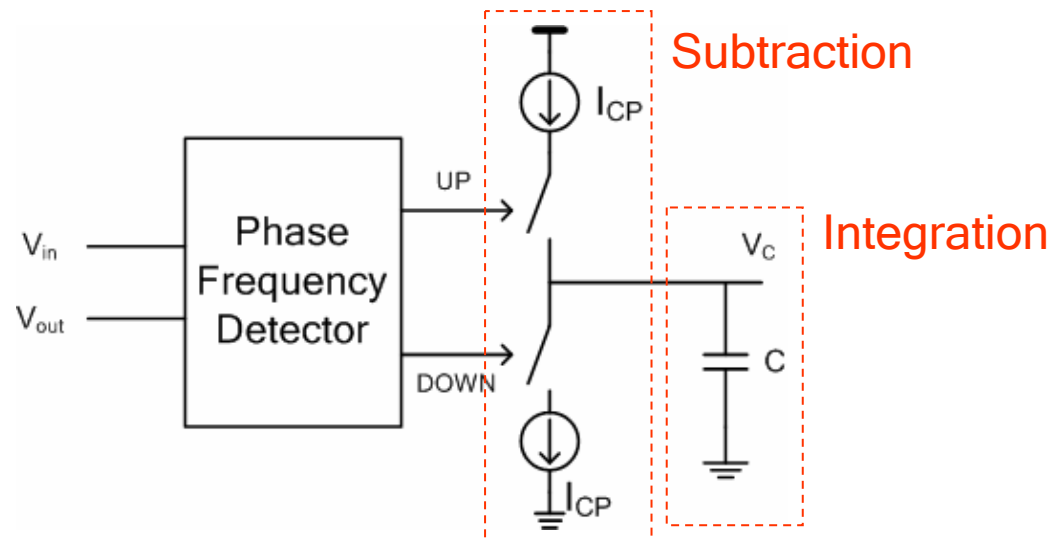


Lect. 23: PLL(2)

Charge Pump PLL

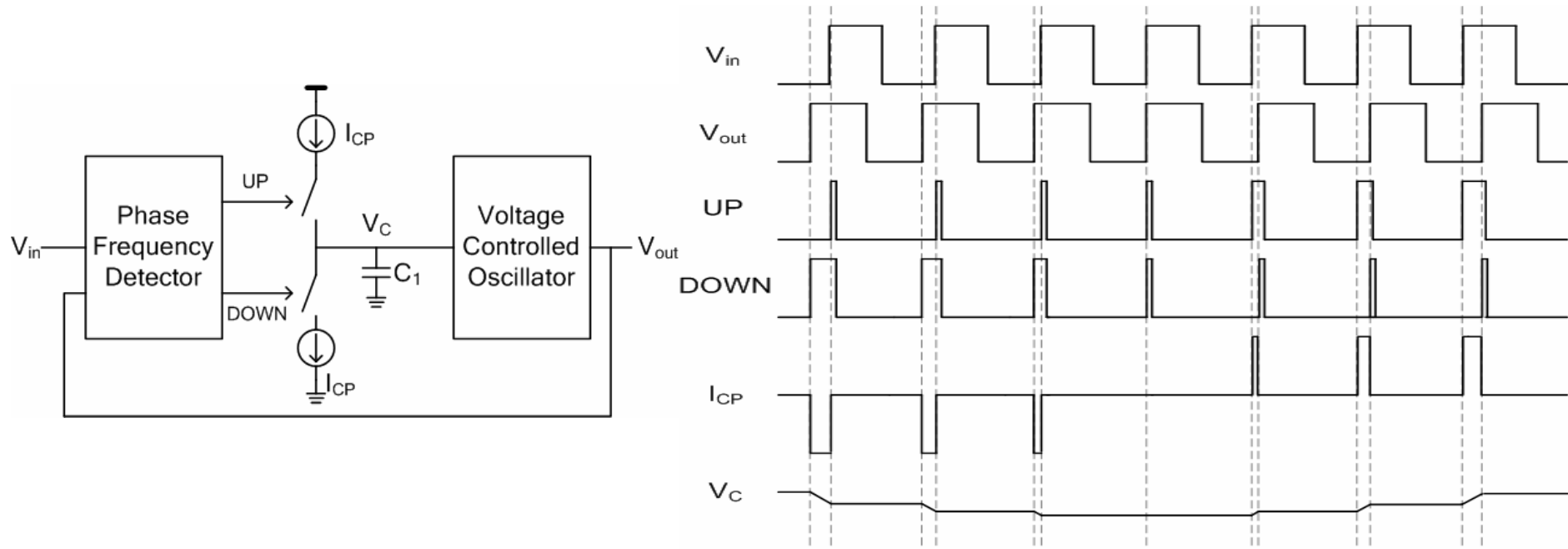


Lect. 23: PLL(2)

Linear model of CPPLL

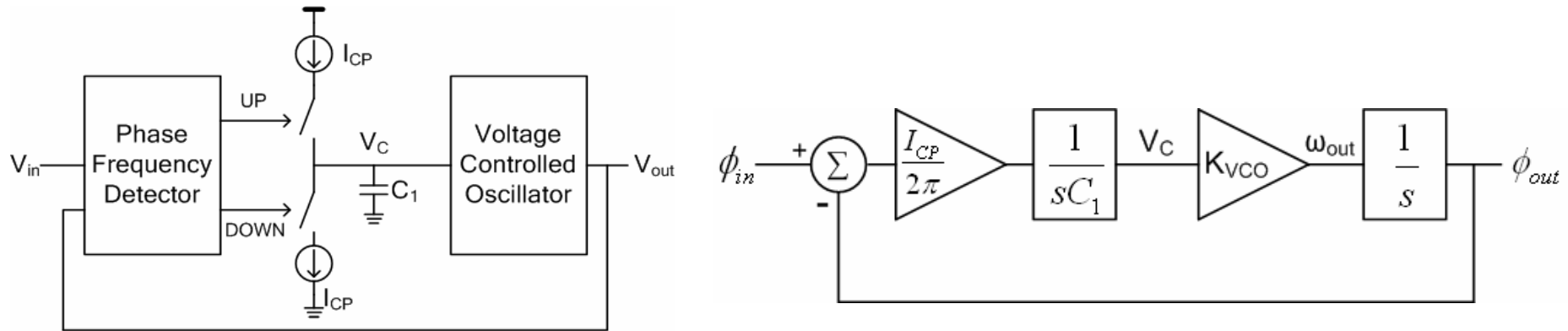


Open loop gain:
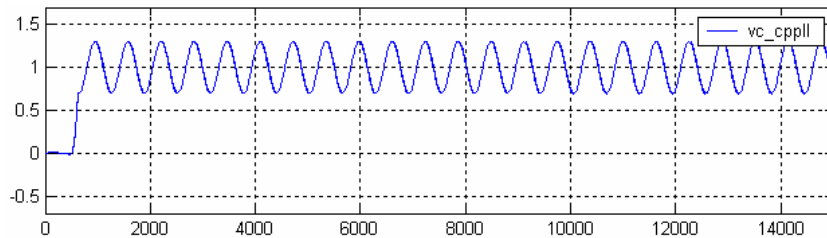
$$G(s) = \frac{1}{2\pi} I_{CP} K_{VCO} \frac{1}{s^2 C_1}$$




No phase margin \rightarrow Unstable

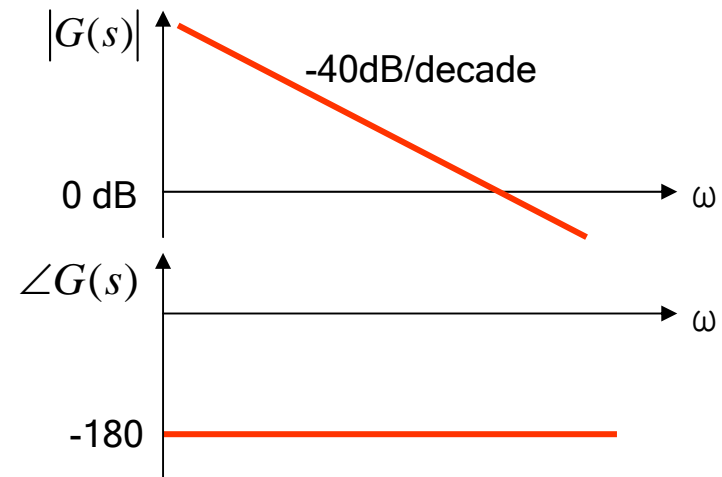



Lect. 23: PLL(2)

Charge Pump PLL

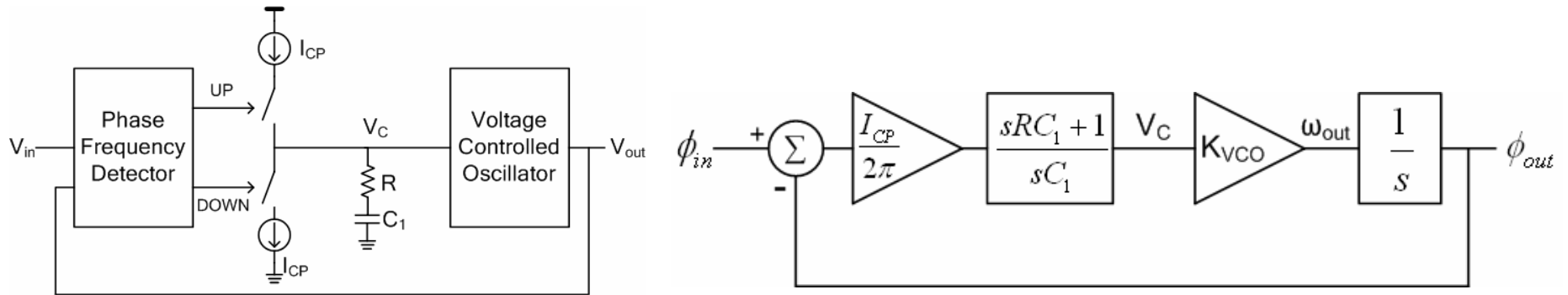


Open loop gain:

$$G(s) = \frac{1}{2\pi} I_{CP} K_{VCO} \frac{sRC_1 + 1}{s^2 C_1}$$

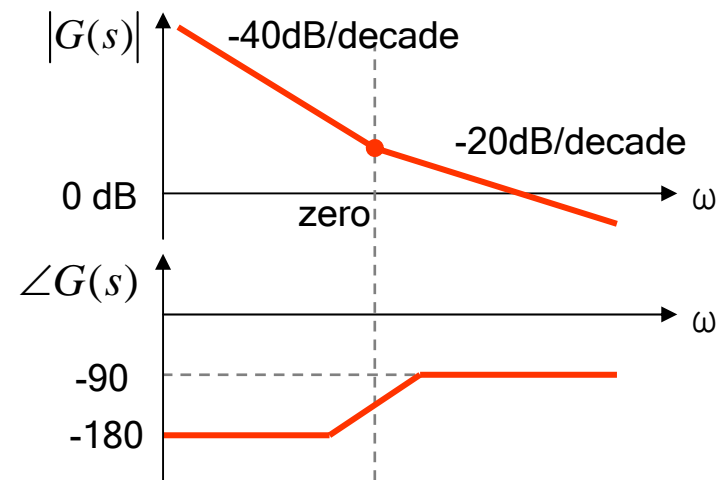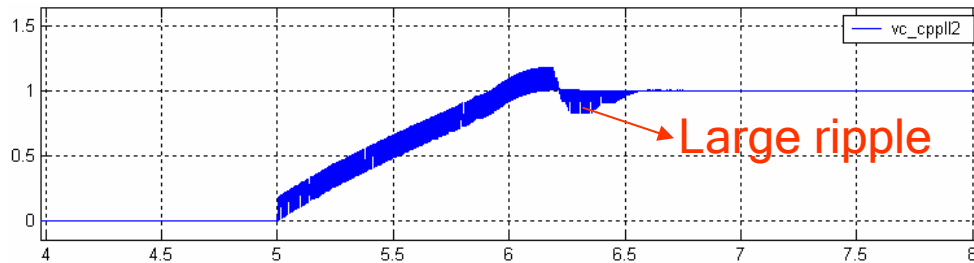

Lect. 23: PLL(2)


Charge Pump PLL

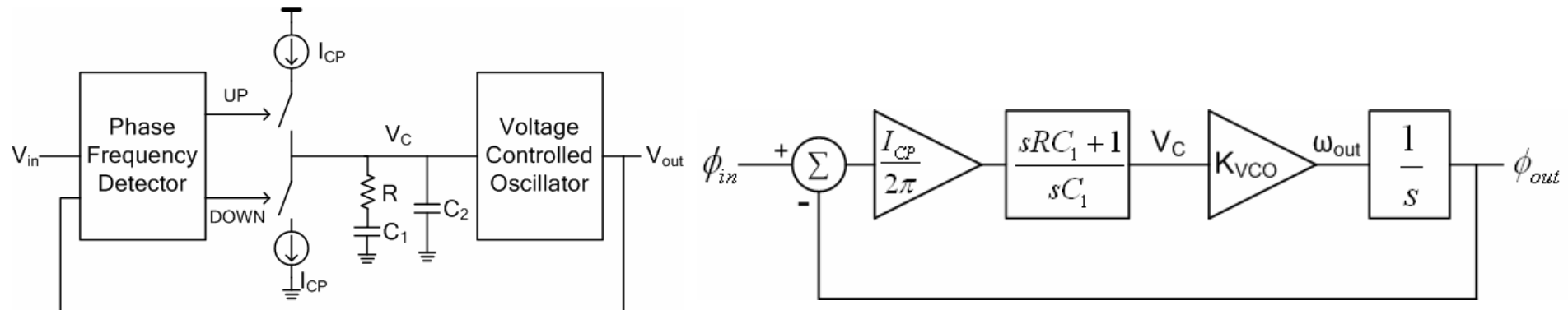

- Ripple reduction with small C_2 ($\approx C_1/10$)
- Simplification as 2nd-order system

Open loop gain:

$$G(s) = \frac{1}{2\pi} I_{CP} K_{VCO} \frac{sRC_1 + 1}{s^2 C_1}$$

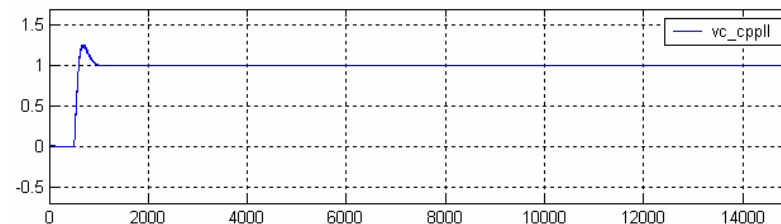

Lect. 23: PLL(2)

Closed loop transfer function

$$H(s) = \frac{\frac{I_{CP}}{2\pi C_1} K_{VCO} (RC_1 s + 1)}{s^2 + \frac{I_{CP}}{2\pi} K_{VCO} R s + \frac{I_{CP}}{2\pi C_1} K_{VCO}}$$

Natural frequency $\omega_n = \sqrt{\frac{I_{CP} K_{VCO}}{2\pi C_1}}$, K_{VCO} in rad/s/V and ω_n in rad/s

Damping ratio $\zeta = \frac{R}{2} \sqrt{I_{CP} C_1 K_{VCO}}$

→ Independent change of natural frequency and damping ratio!

Lect. 23: PLL(2)


Transient simulation for various damping ratio and fixed ω_n

$$\omega_{in} = 200\text{Hz}$$

$$I_{CP} = 100\mu\text{A}$$

$$K_{VCO} = 2\pi \times 100\text{rad} / \text{s} / \text{V}$$

$$\omega_n = 1\text{Hz}$$

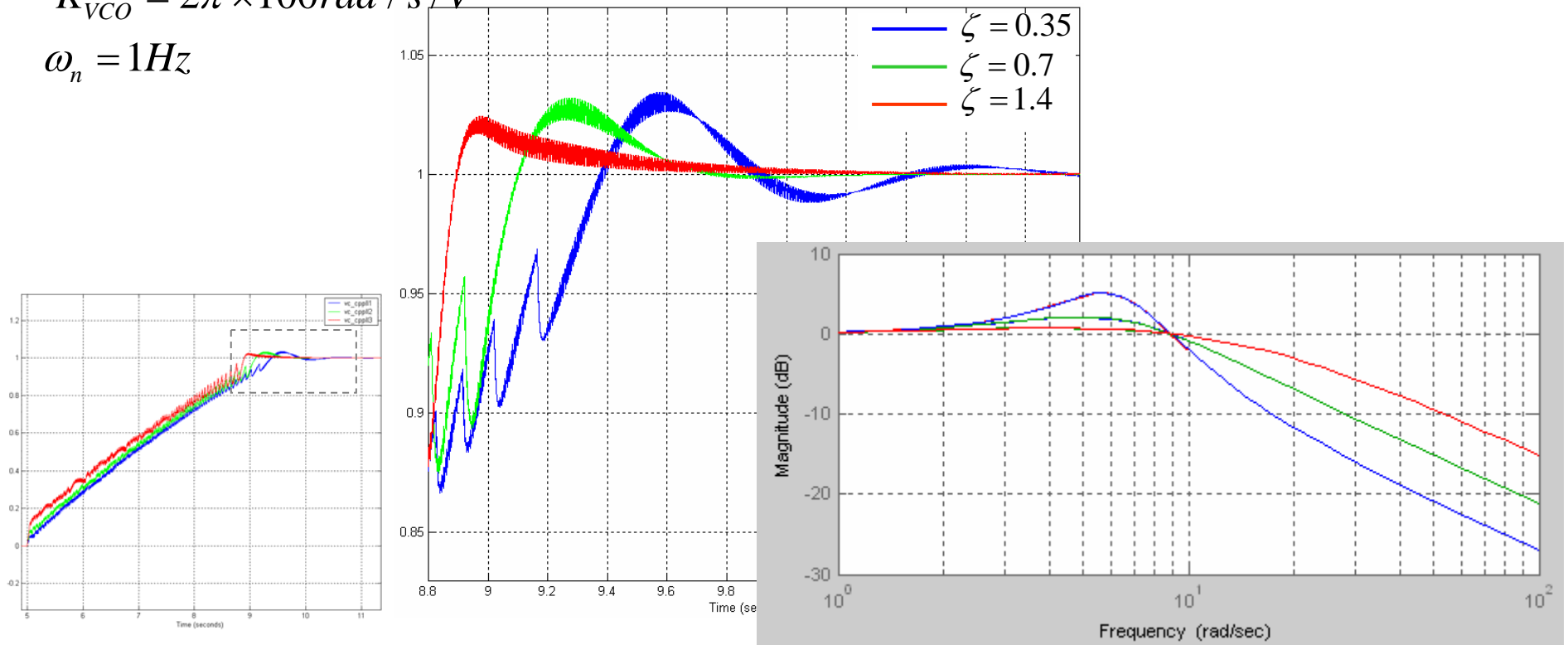

Lect. 23: PLL(2)

Transient simulation for various ω_n and fixed damping ratio

$$\omega_{in} = 200\text{Hz}$$

$$I_{CP} = 100\mu\text{A}$$

$$K_{VCO} = 2\pi \times 100\text{rad} / \text{s} / \text{V}$$

$$\zeta = 0.7$$

→ Optimization for desired performance!

