

Lect. 24: Data Converters


Data Converters

- ADC: Analog to Digital Converter
- DAC: Digital to Analog Converter


Why data conversion?

Digital Signal Processing is very powerful: DSP is better if possible

Real world is made up of analog signals

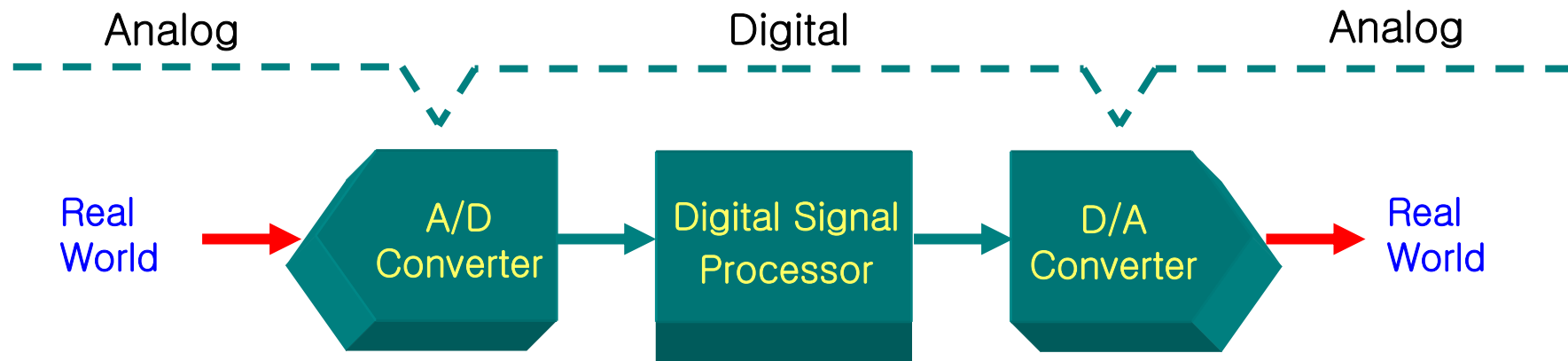


Lect. 24: Data Converters

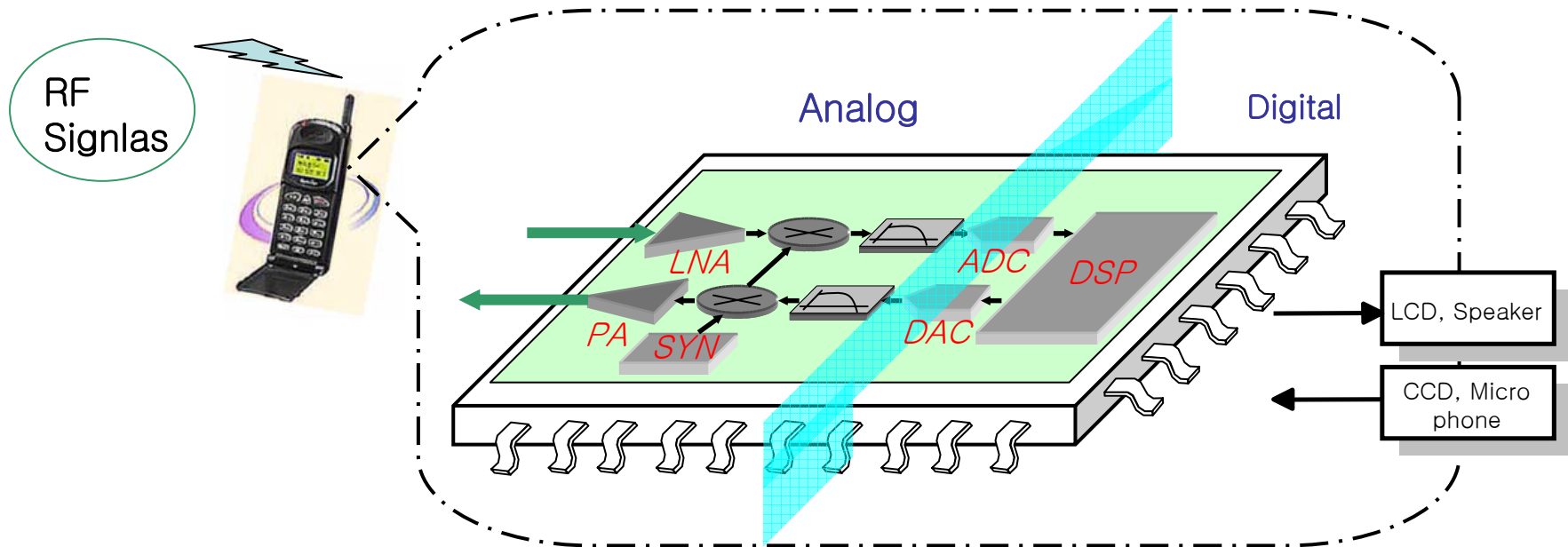


LNA: Low Noise Amplifier
PA: Power Amplifier
SYN: Frequency Synthesizer

Lect. 24: Data Converters


A/D Process

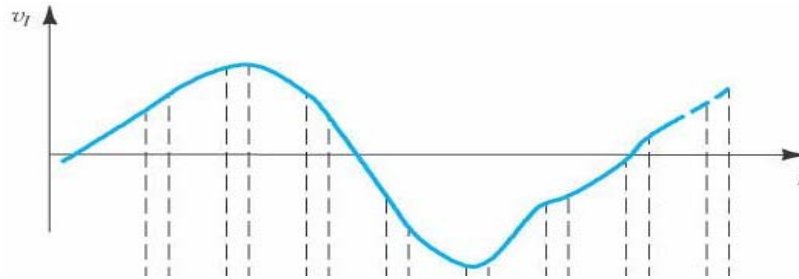

Input analog signal

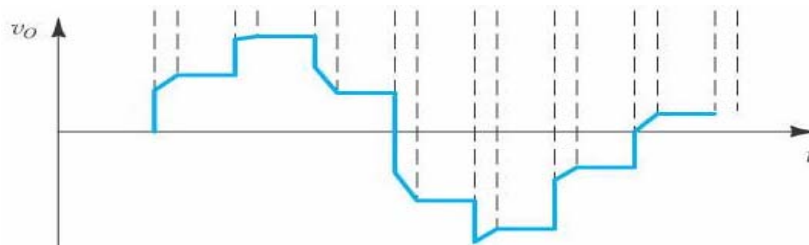


Sampled signal

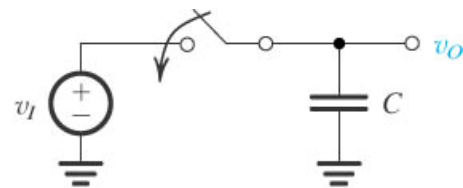

Sample and Hold Circuit

(a)



Lect. 24: Data Converters

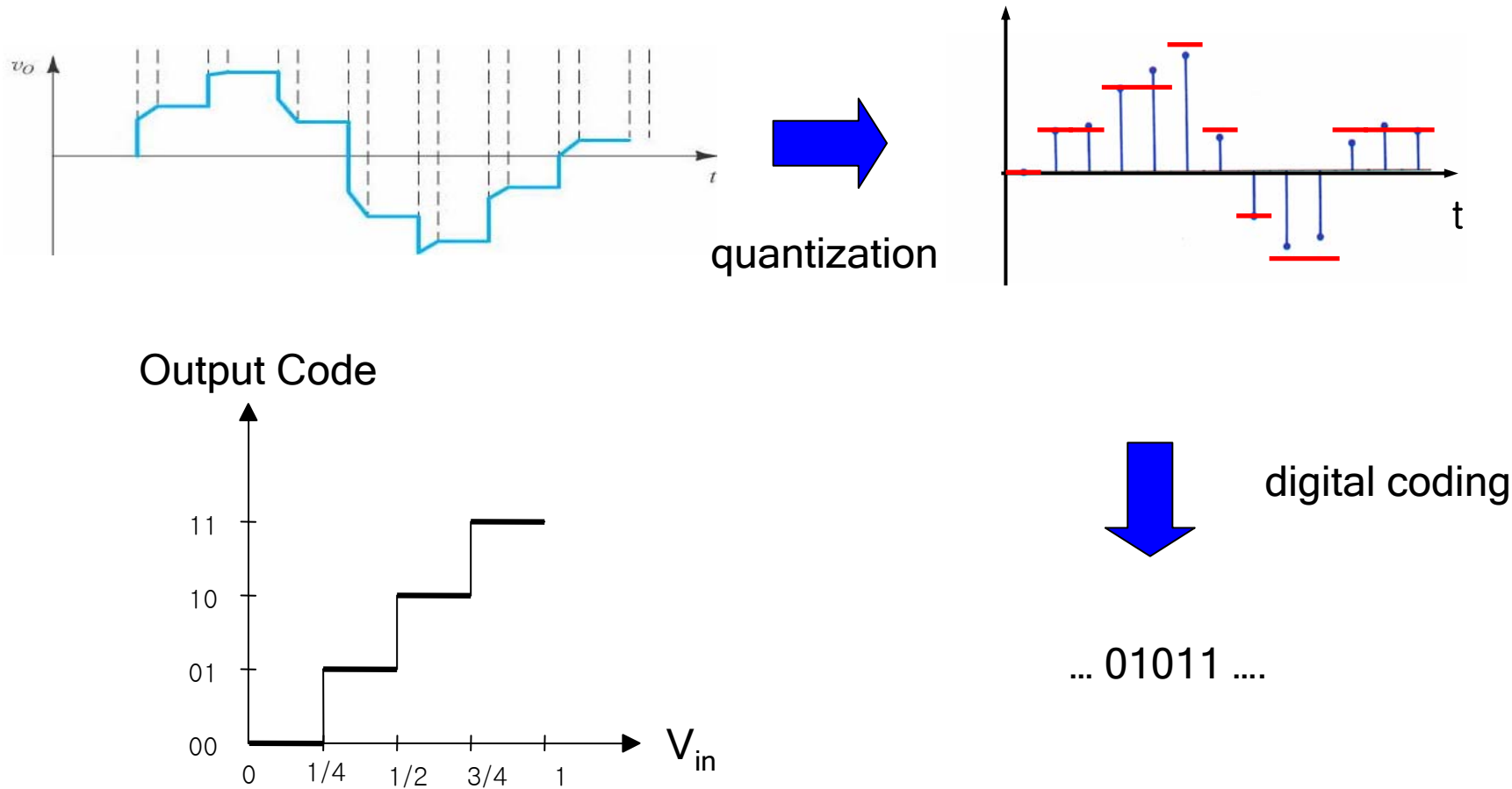

Lect. 24: Data Converters

D/A Process

Digital input: ...01011

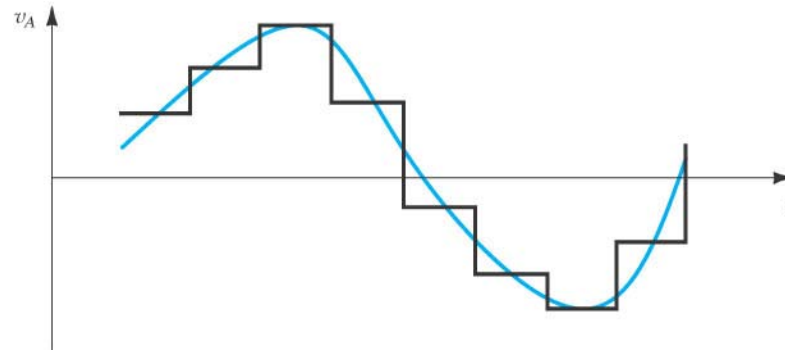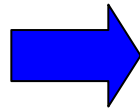


Key parameters: Resolution and bandwidth

Lect. 24: Data Converters

Hardware implementation of D/A Converter

Input: $b_1 b_2 b_3 \dots b_N$ (b_N : Least significant bit)


$$D = \frac{b_1}{2^1} + \frac{b_2}{2^2} + \dots + \frac{b_N}{2^N}$$

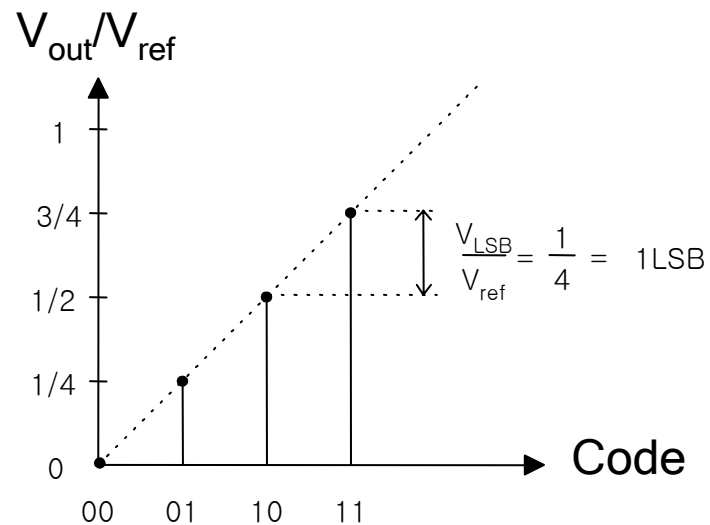

Lect. 24: Data Converters

N-bit D/A Converter
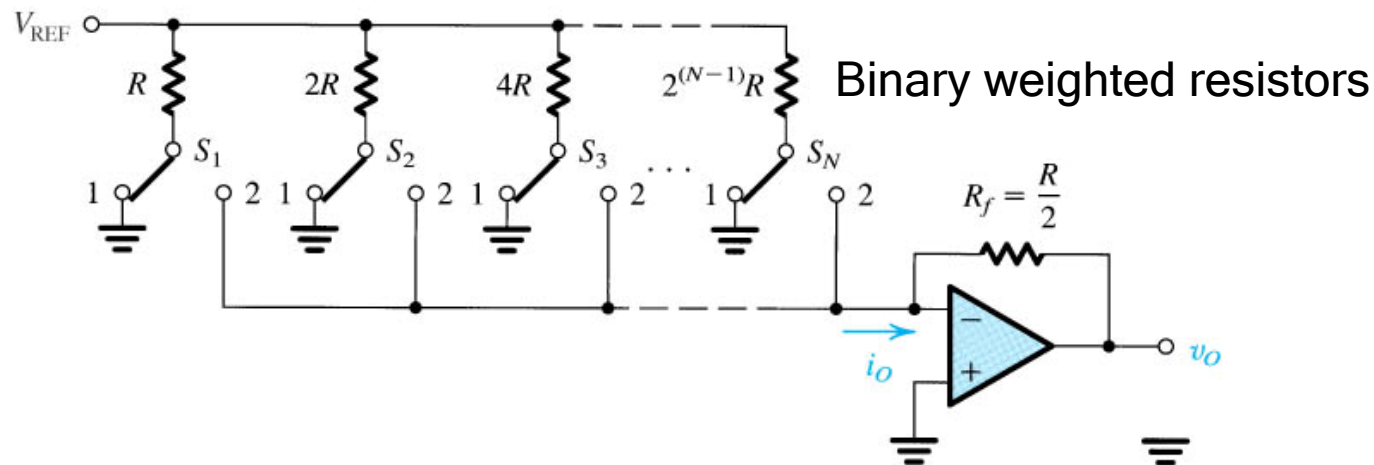
$$D = \frac{b_1}{2^1} + \frac{b_2}{2^2} + \dots + \frac{b_N}{2^N}$$




$$i_o = \frac{V_{REF}}{R} b_1 + \frac{V_{REF}}{2R} b_2 + \dots + \frac{V_{REF}}{2^{N-1}R} b_N = \frac{2V_{REF}}{R} \left(\frac{b_1}{2^1} + \frac{b_2}{2^2} + \dots + \frac{b_N}{2^N} \right) = \frac{2V_{REF}}{R} D$$

$$v_o = -V_{REF} D$$

Lect. 24: Data Converters

N-bit D/A Converter

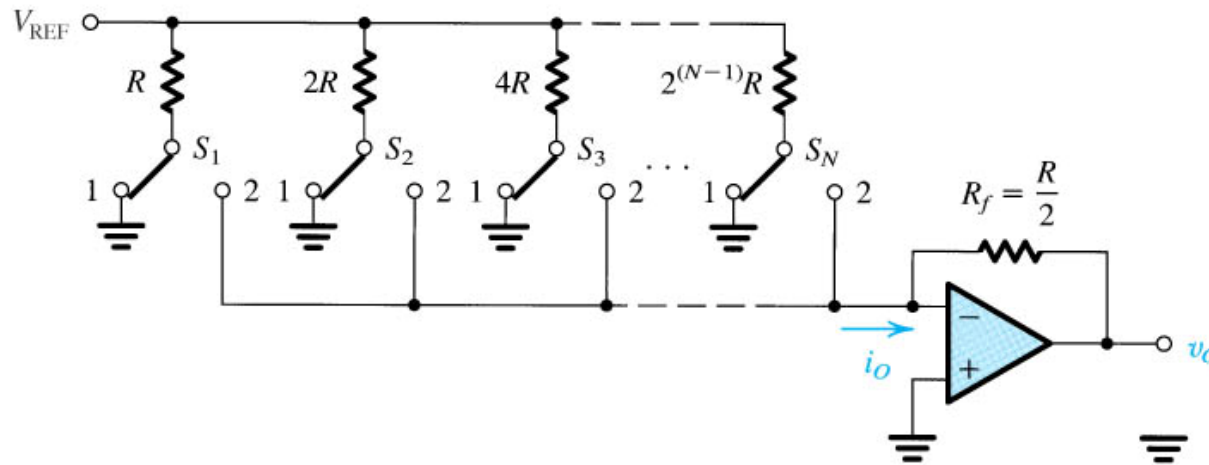

Accuracy of DAC: V_{REF} , precision of binary resistors, switch performance

→ With binary weighted resistors, big differences in R

