
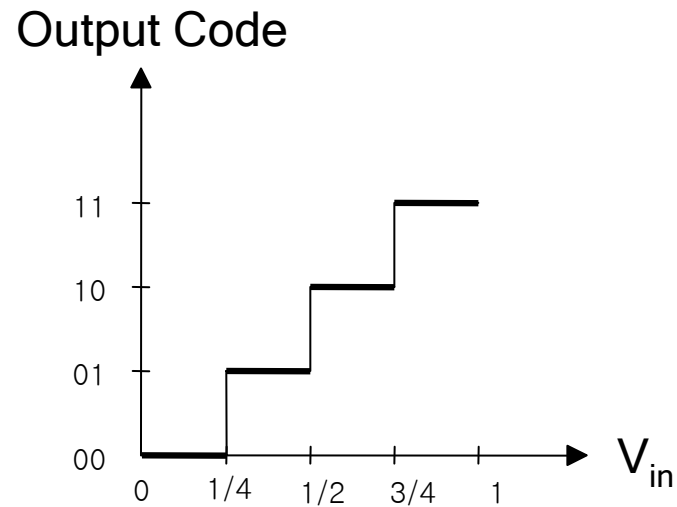


Lect. 25: Analog-to-Digital Converters

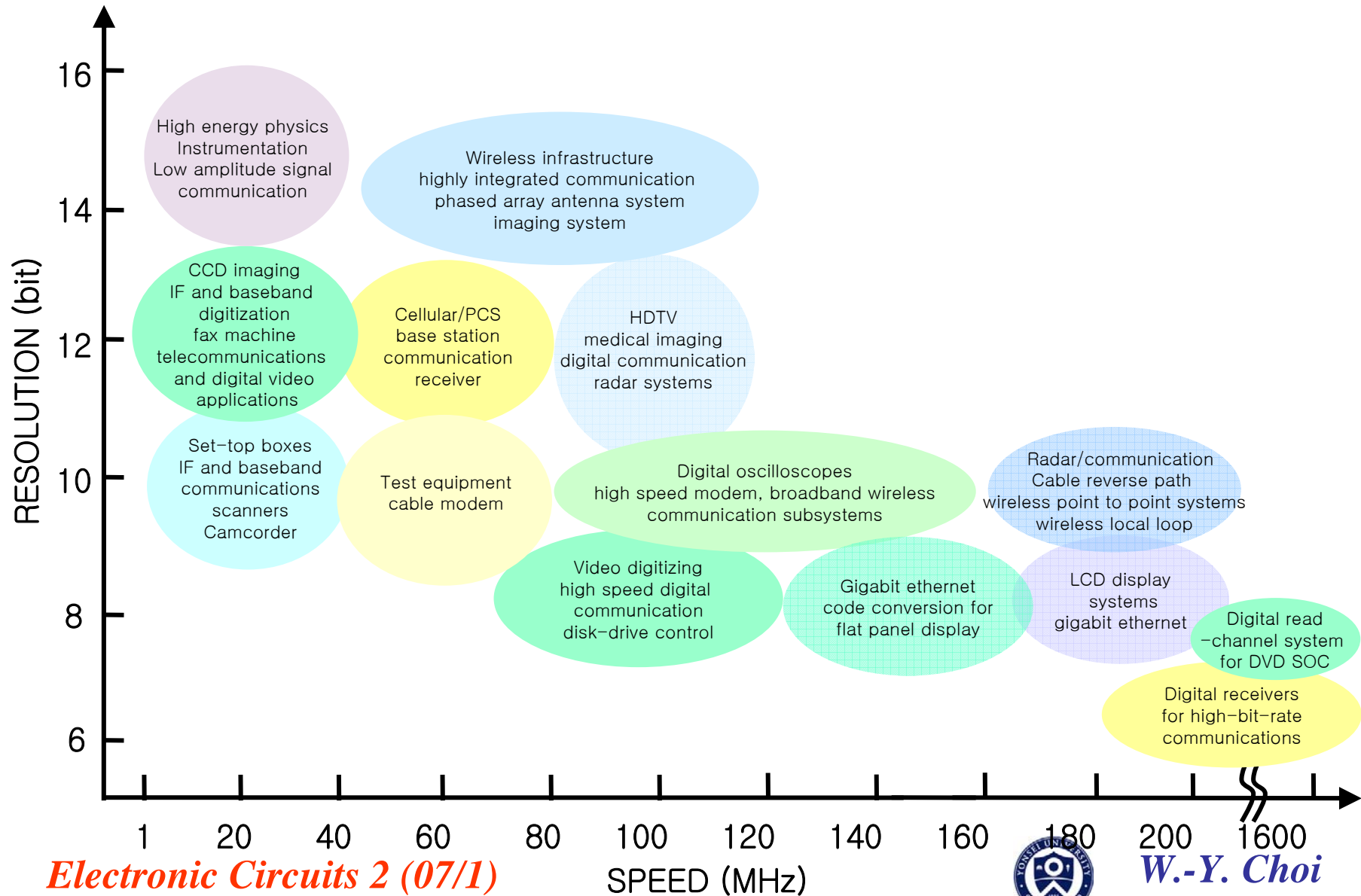

Many ADC architectures are available


Lect. 25: Analog-to-Digital Converters



Lect. 25: Analog-to-Digital Converters

Flash ADC

Ex.) 3-bit Flash ADC


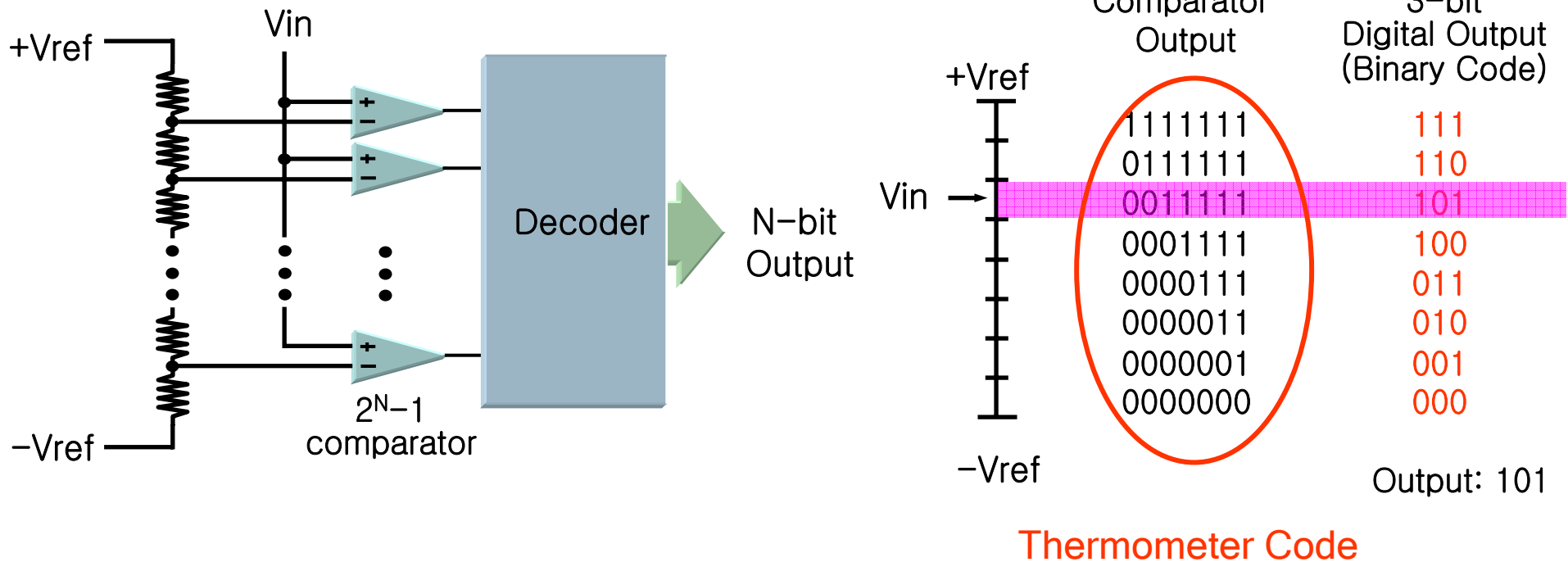


Fast because of parallel processing

R matching problem → Expensive, High-performance applications

Lect. 25: Analog-to-Digital Converters

Feedback-Type ADC

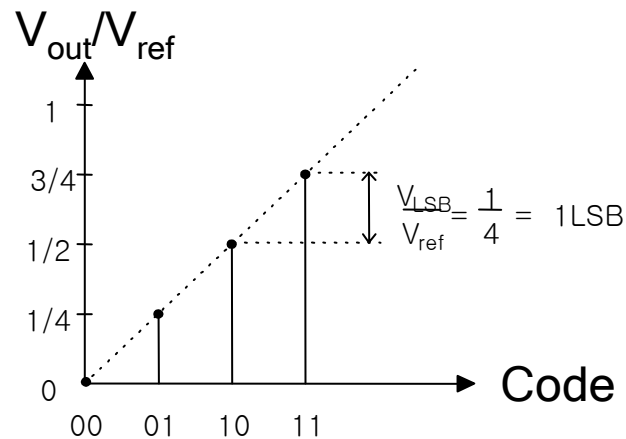
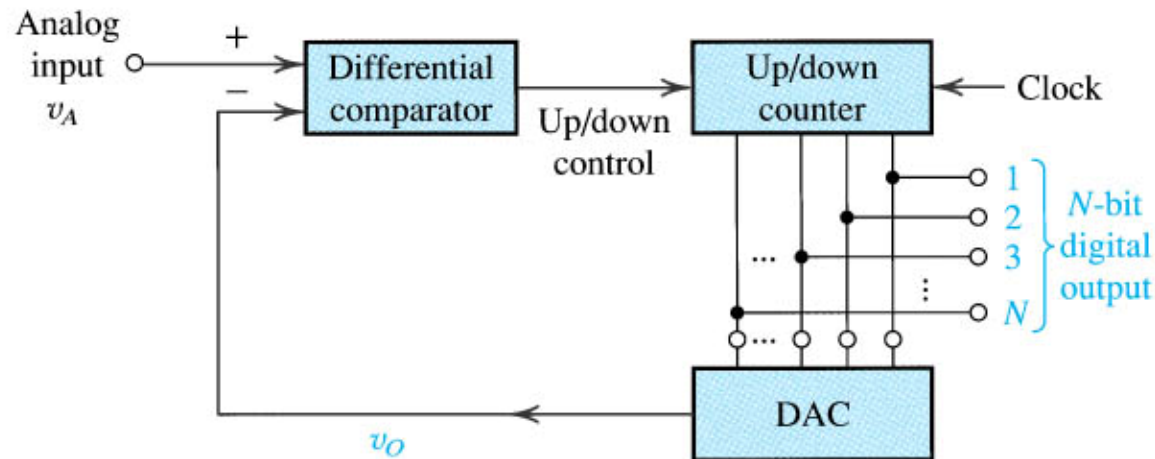


Count up DAC
Until DAC output matches analog input

Very simple but not for high performance

Lect. 25: Analog-to-Digital Converters

Dual-Slope ADC

 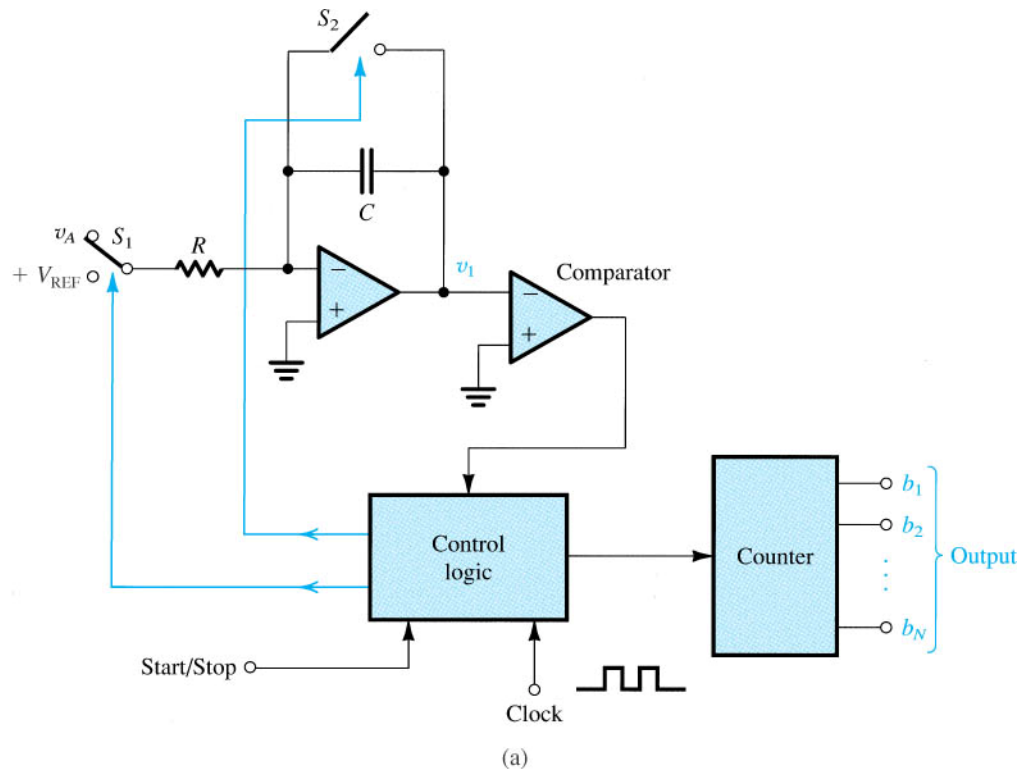



Charge up the integrator for T_1 with v_A

$$V_{PEAK} = \frac{v_A}{RC} \cdot T_1$$

Simultaneously count up the counter to 2^N

Lect. 25: Analog-to-Digital Converters

Dual-Slope ADC

 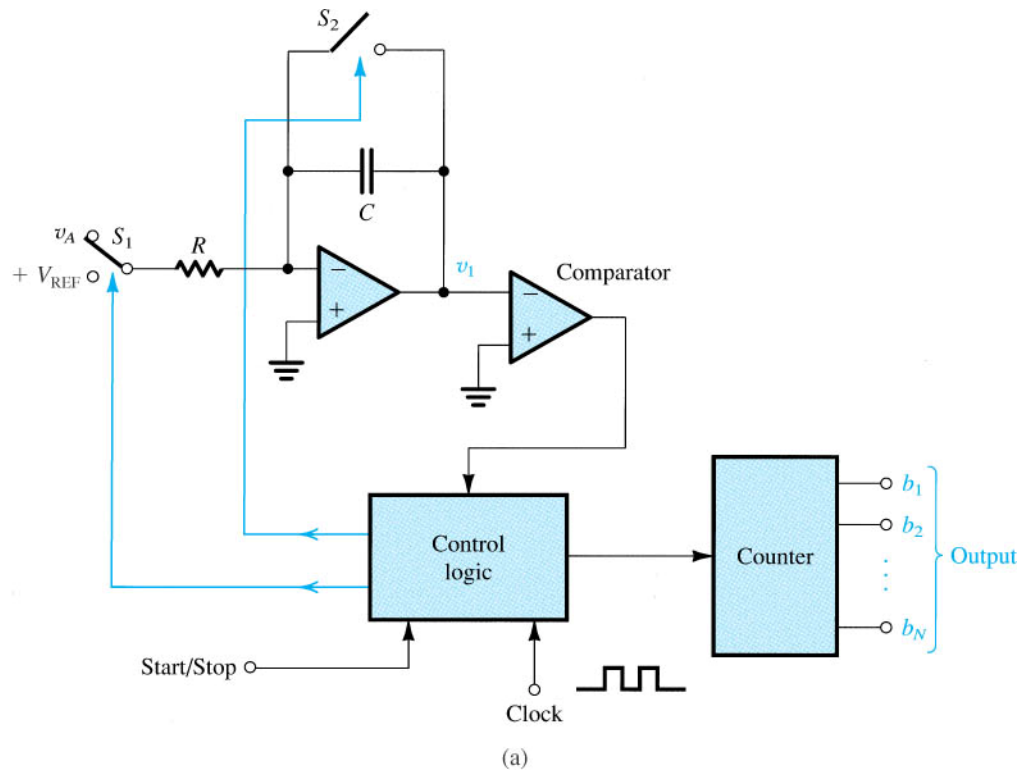

Discharge the integrator with V_{REF}
 Stop counting when v_i reaches 0 at T_2


$$V_{PEAK} = \frac{V_{REF}}{RC} \cdot T_2$$

$$\therefore T_2 = T_1 \left(\frac{v_A}{V_{REF}} \right) \implies n = 2^N \left(\frac{v_A}{V_{REF}} \right)$$

High accuracy: No direct dependence on R, C
 But slow

Lect. 25: Analog-to-Digital Converters

Charge Redistribution ADC

 


Sampling Phase

$$Q_{\text{total}} = 2 C v_A$$

Lect. 25: Analog-to-Digital Converters

Charge Redistribution ADC

 


Hold Phase

$$V_O = -V_A$$

S_A connect to V_{REF}

Lect. 25: Analog-to-Digital Converters

Charge Redistribution ADC

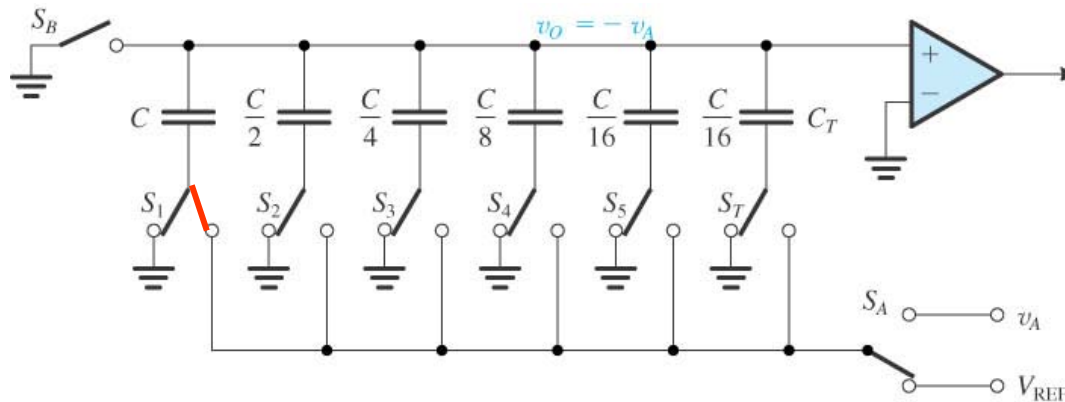

Charge-redistribution phase (b)

With S_1 connected to V_{REF} , $v_O = V_{REF}/2 - v_A$

If $v_O > 0$, connect S_1 to ground and move to S_2

If $v_O < 0$, move to S_2

Repeat above with increasing n

Final switch configuration is the digital output