
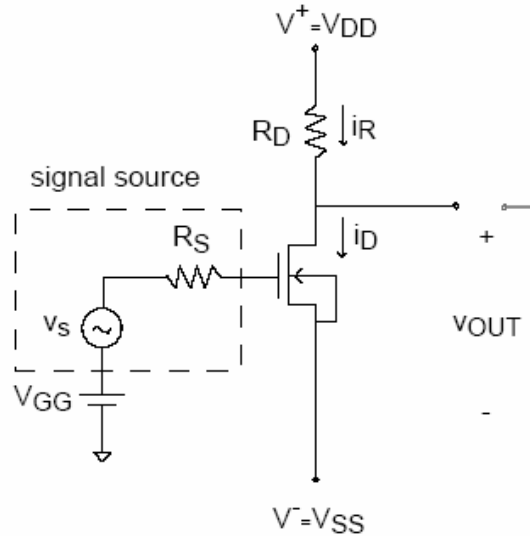


# Lect. 6: Amplifiers (2)


Three basic configurations: CS, CD, CG

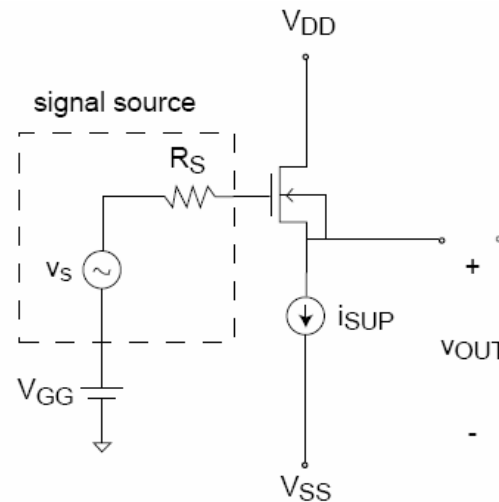

Common Source




Common Drain  
(Source Follower)

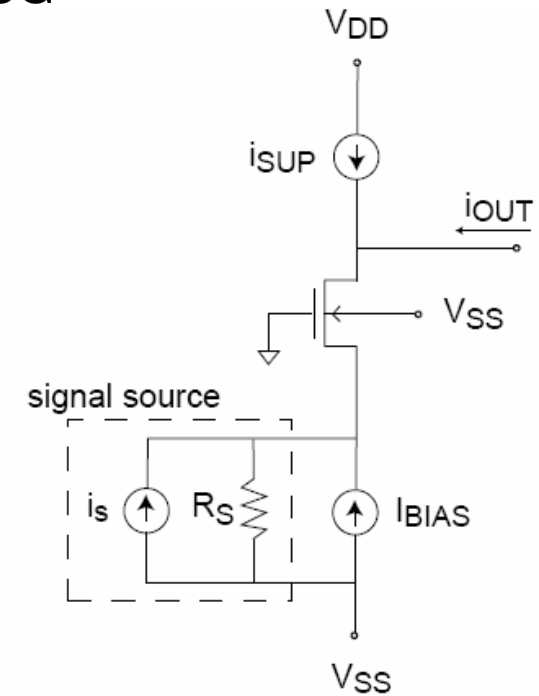

Common Gate
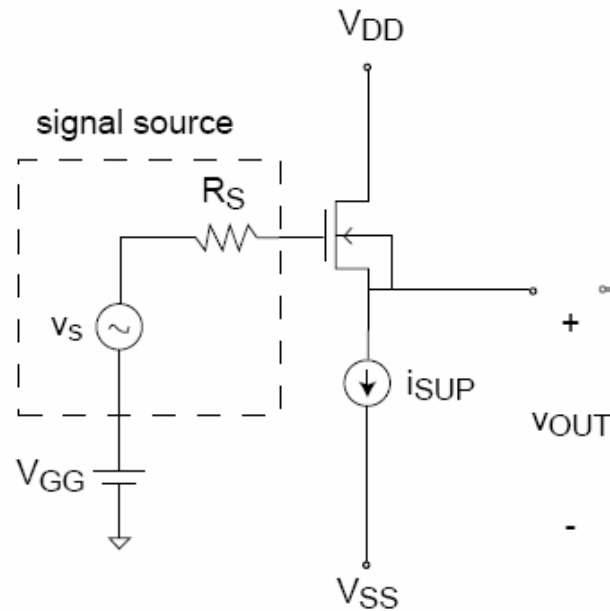
# Lect. 6: Amplifiers (2)



Common-Drain Amplifier  
(Source Follower)



How does it work?



$v_G \uparrow \Rightarrow i_D \text{ can't change} \Rightarrow v_{OUT} \uparrow$   
(source follower)

Small signal circuit  
(No Body Effect)

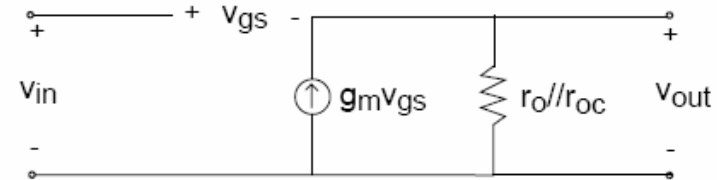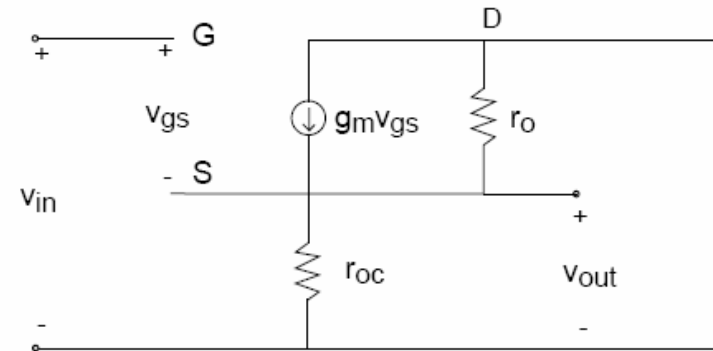

# Lect. 6: Amplifiers (2)
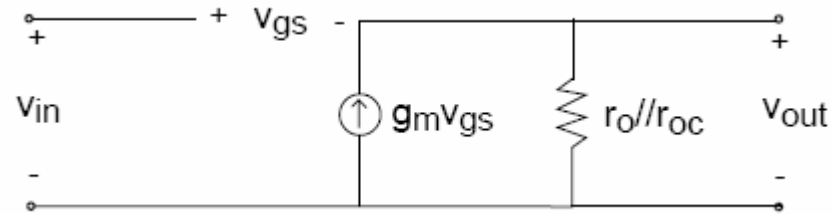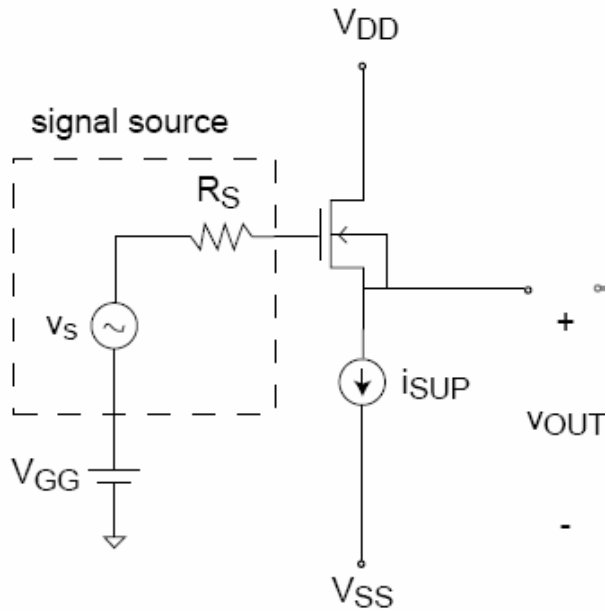
## Common-Drain Amplifier (Source Follower)



$$v_{in} = v_{gs} + v_{out}$$

$$v_{out} = g_m v_{gs} (r_o // r_{oc})$$

$$A_{vo} = \frac{g_m}{g_m + \frac{1}{r_o // r_{oc}}} \simeq 1$$

$$R_{in} = \infty$$

$$R_{out} = \frac{1}{g_m + \frac{1}{r_o // r_{oc}}} \simeq \frac{1}{g_m}$$


Large  $R_{in}$ , Small  $R_{out}$

➔ Voltage amplifier

But (almost) unit voltage gain

➔ Voltage buffer

## Lect. 6: Amplifiers (2)

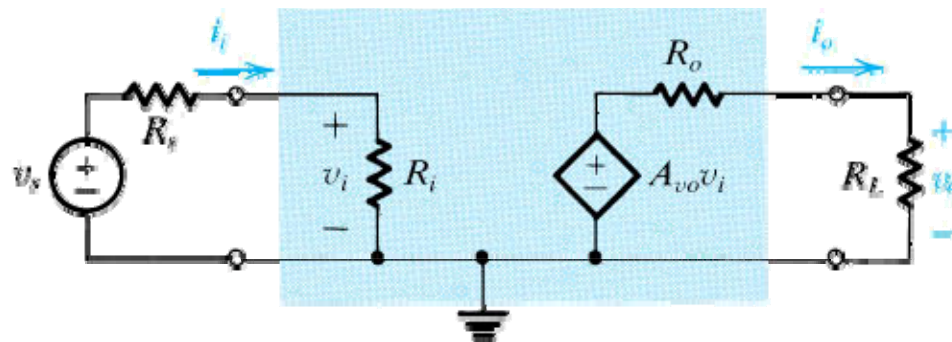


$$v_o = \frac{R_L}{R_L + R_o} A_{vo} v_i = \frac{R_L}{R_L + R_o} A_{vo} \frac{R_i}{R_i + R_s} v_s \approx v_s$$

Source Follower: Large  $R_i$ , Small  $R_o$ ,  $A_{vo}$  close to one


→ Voltage buffer

# Lect. 6: Amplifiers (2)


With Body Effect

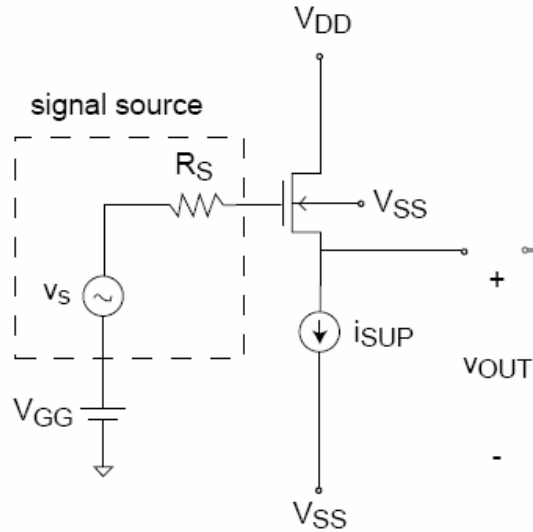
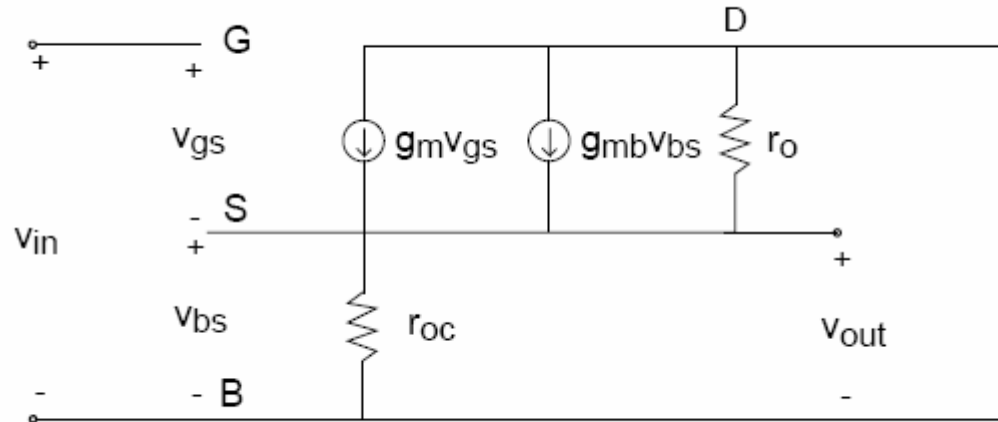
$$g_{mb} = \chi g_m \quad (\chi: 0.1-0.3)$$



$$v_{bs} = -v_{out}$$

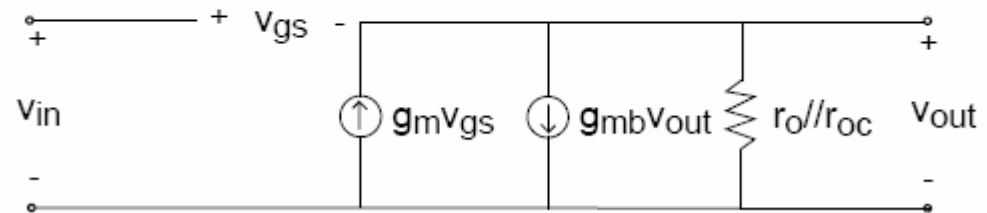


$$A_{vo} = \frac{g_m}{g_m + g_{mb} + \frac{1}{r_o // r_{oc}}} \approx \frac{g_m}{g_m + g_{mb}}$$

$$R_{out} = \frac{1}{g_m + g_{mb} + \frac{1}{r_o // r_{oc}}} \approx \frac{1}{g_m + g_{mb}}$$

$$R_{in} = \infty$$
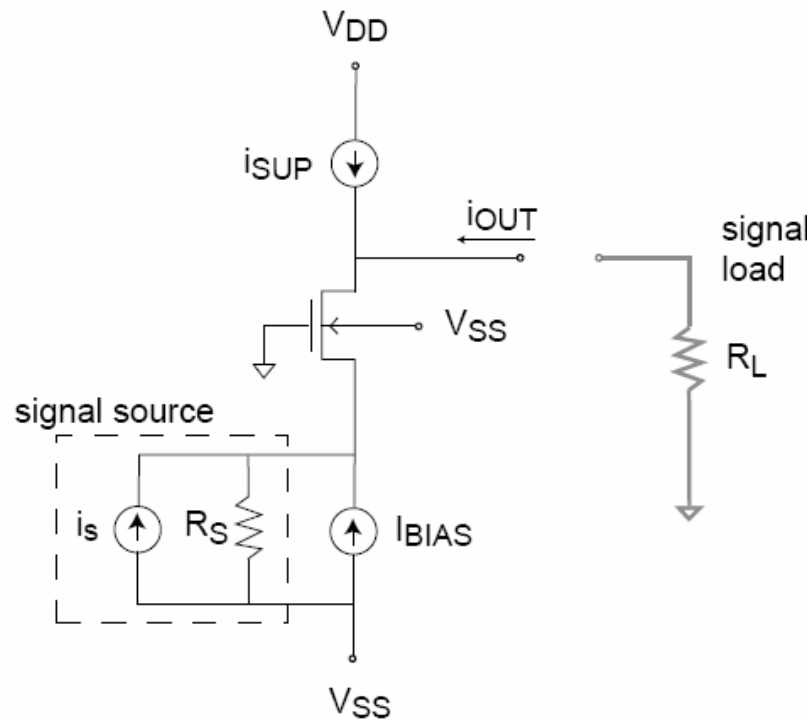
# Lect. 6: Amplifiers (2)

Common-Gate Amplifier (Current Buffer: Unit Current Gain, Low  $R_{in}$ , High  $R_{out}$ )





How does it work?

$$i_s \simeq -i_{out}$$


# Lect. 6: Amplifiers (2)

## Common-Gate Amplifier

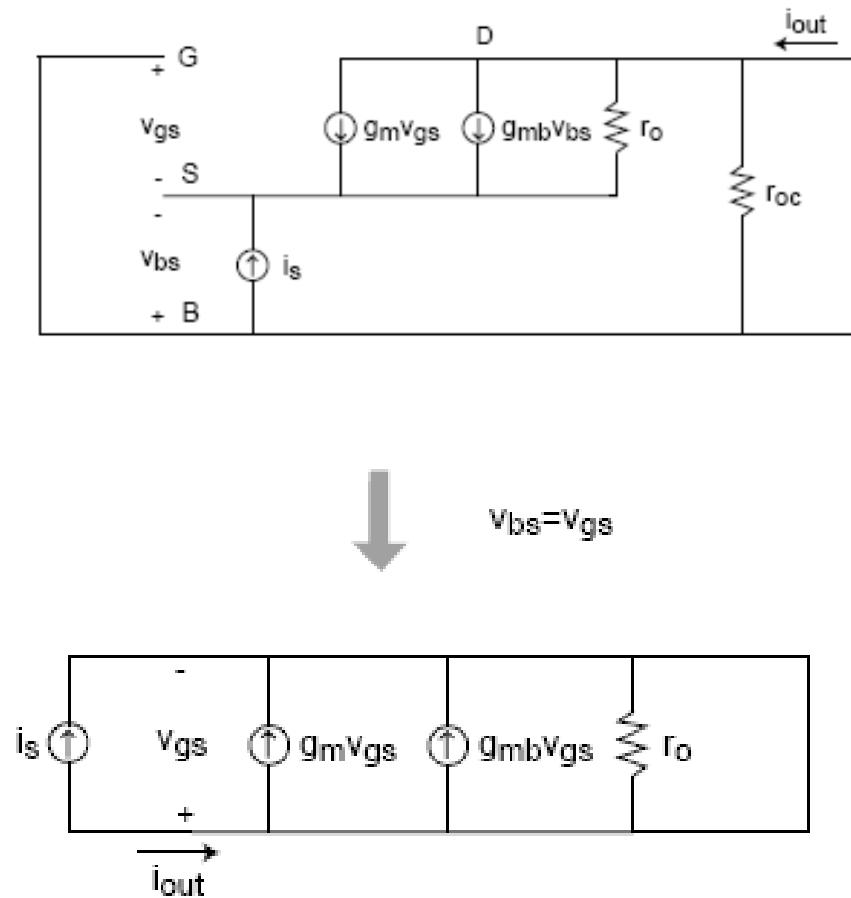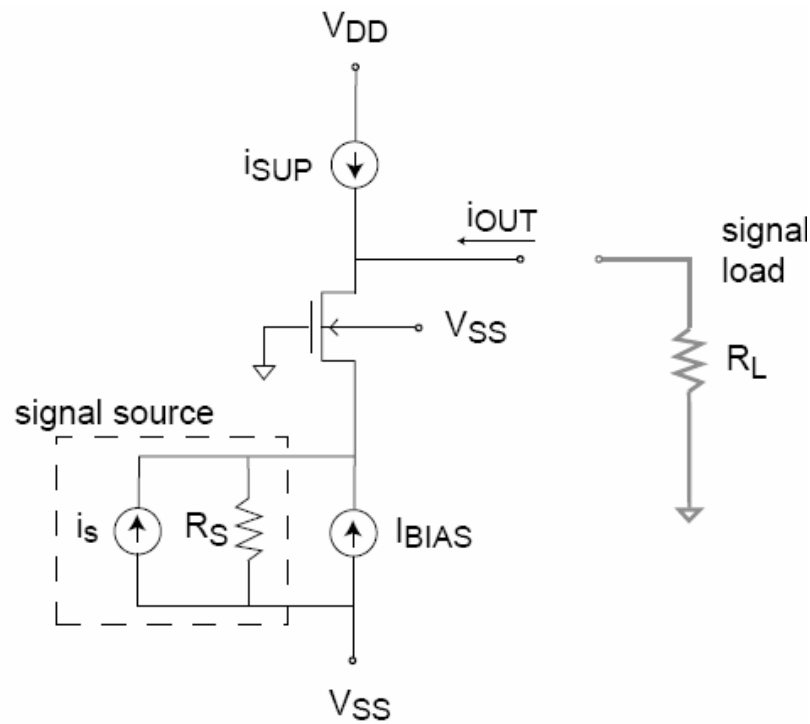


# Lect. 6: Amplifiers (2)

## Common-Gate Amplifier

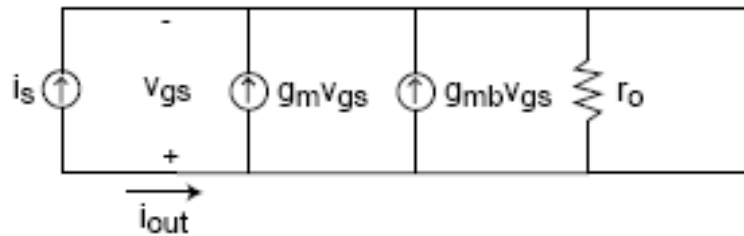

$$i_s = -i_{out}$$

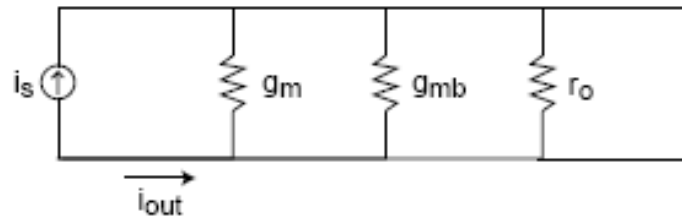




# Lect. 6: Amplifiers (2)

## Common-Gate Amplifier


### Input Resistance

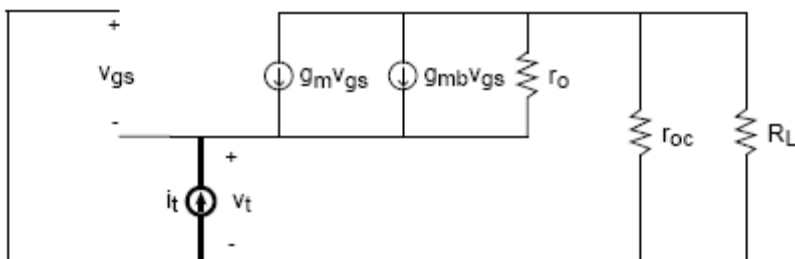

$$R_{in} = \frac{1 + \frac{r_{oc} // R_L}{r_o}}{g_m + g_{mb} + \frac{1}{r_o}}$$

$$\simeq \frac{1}{g_m + g_{mb}}$$

### Output Resistance

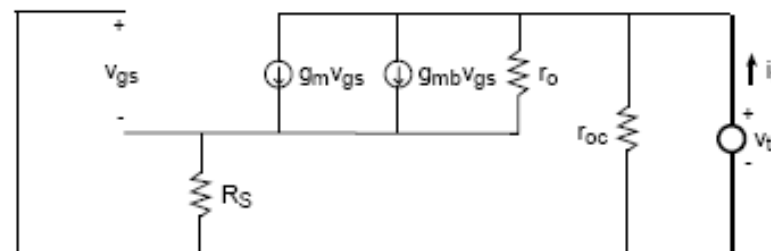

$$R_{out} = r_{oc} // \left\{ r_o \left[ 1 + R_S \left( g_m + g_{mb} + \frac{1}{r_o} \right) \right] \right\}$$

$$\simeq r_{oc} // [r_o (1 + g_m R_S)]$$

## Lect. 6: Amplifiers (2)

stage	$A_{vo}, G_{mo}, A_{io}$	$R_{in}$	$R_{out}$	key function
common source	$G_{mo} = g_m$	$\infty$	$r_o // r_{oc}$	transconductance amp.
common drain	$A_{vo} \simeq \frac{g_m}{g_m + g_{mb}}$	$\infty$	$\frac{1}{g_m + g_{mb}}$	voltage buffer
common gate	$A_{io} \simeq -1$	$\frac{1}{g_m + g_{mb}}$	$r_{oc} // [r_o(1 + g_m R_S)]$	current buffer


Amplifiers with other characteristics?

For example, a voltage amplifier with very high gain.


→ Multistage amplifier

# Lect. 6: Amplifiers (2)

- Start with CS

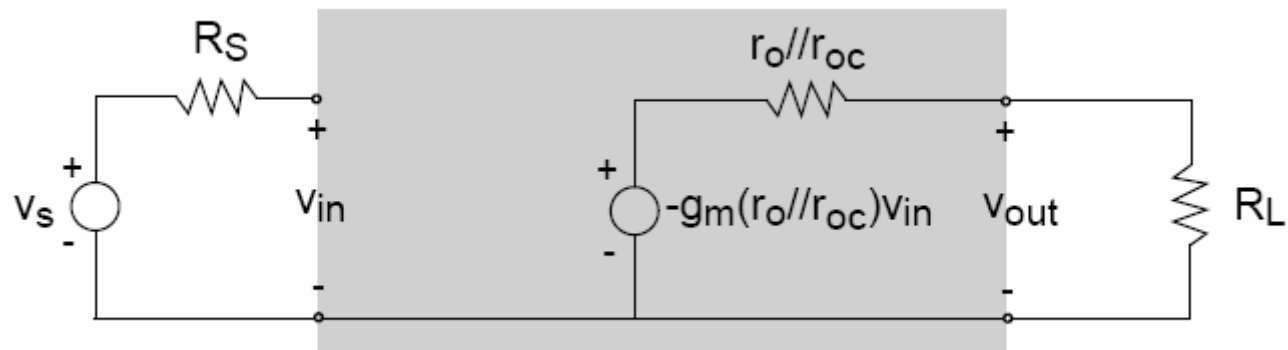


- More gain with another CS

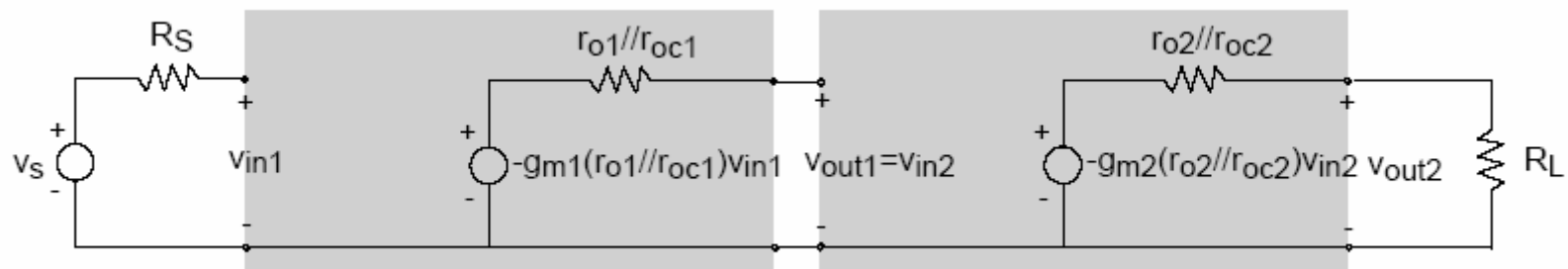

$$R_{in} = \infty \quad A_{vo} = g_{m1}(r_{o1} // r_{oc1})g_{m2}(r_{o2} // r_{oc2}) \quad R_{out} = r_{o2} // r_{oc2},$$

# Lect. 6: Amplifiers (2)

- Add CD at output

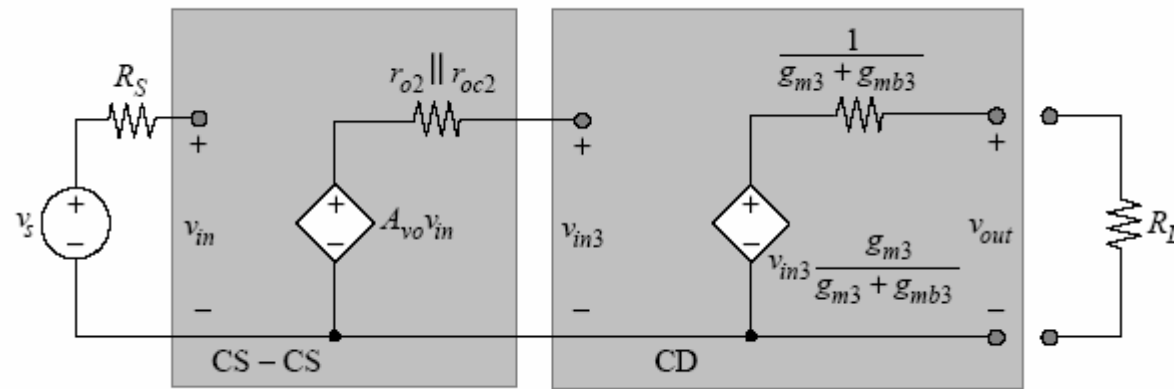

$$R_{in} = \infty$$

$$A_{vo} = g_{m1}(r_{o1} \parallel r_{oc1})g_{m2}(r_{o2} \parallel r_{oc2})\frac{g_{m3}}{g_{m3} + g_{mb3}}$$

$$R_{out} = \frac{1}{g_{m3} + g_{mb3}}$$