
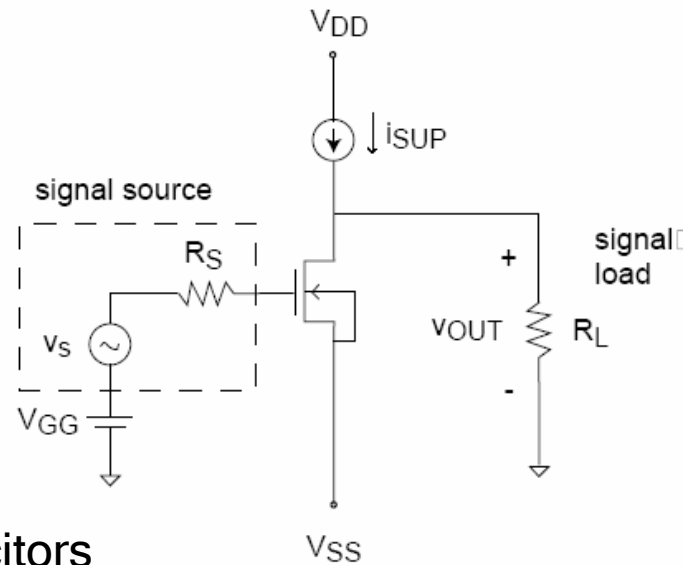


# Lect. 7: Amplifier Frequency Response


Common Source Amplifier

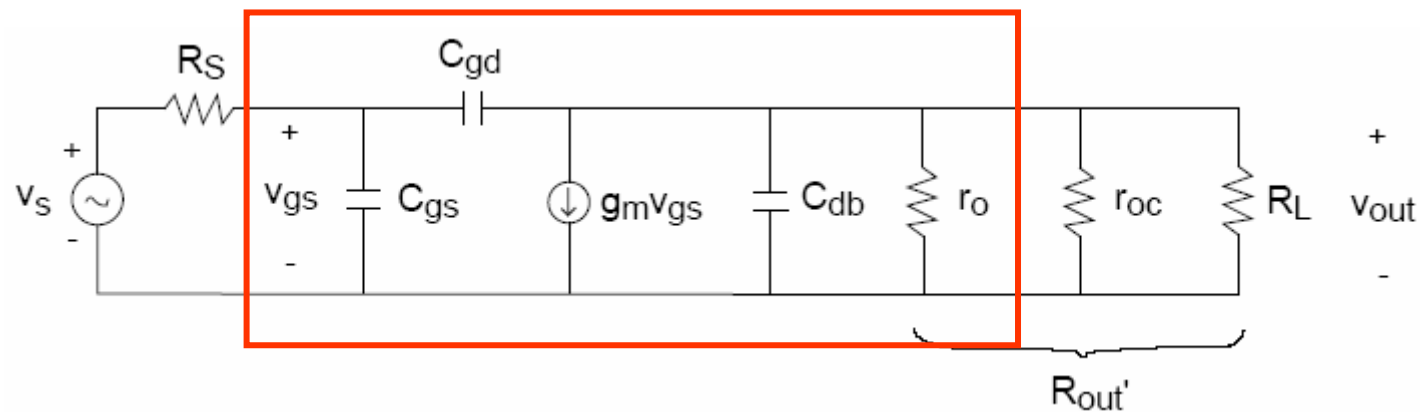

Small-signal model with capacitors




# Lect. 7: Amplifier Frequency Response

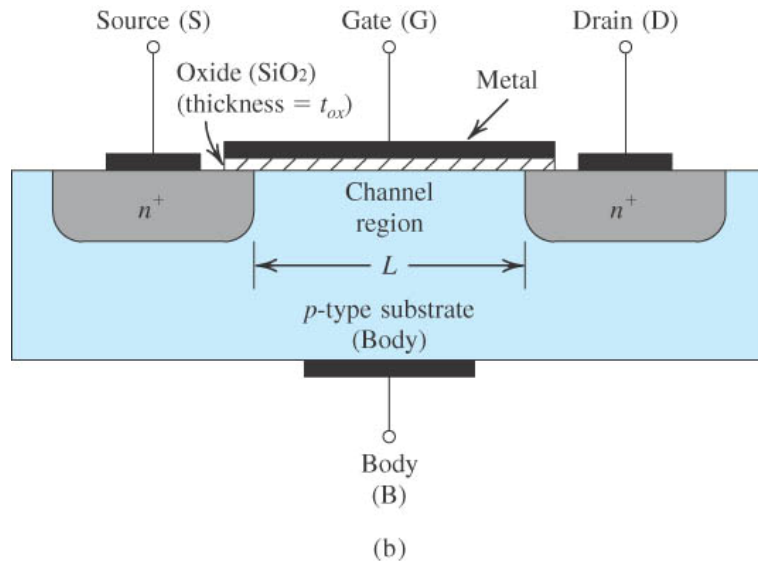

$C_{db}$ :  
Capacitance between drain and body  
Due to depletion-layer between D and B

# Lect. 7: Amplifier Frequency Response

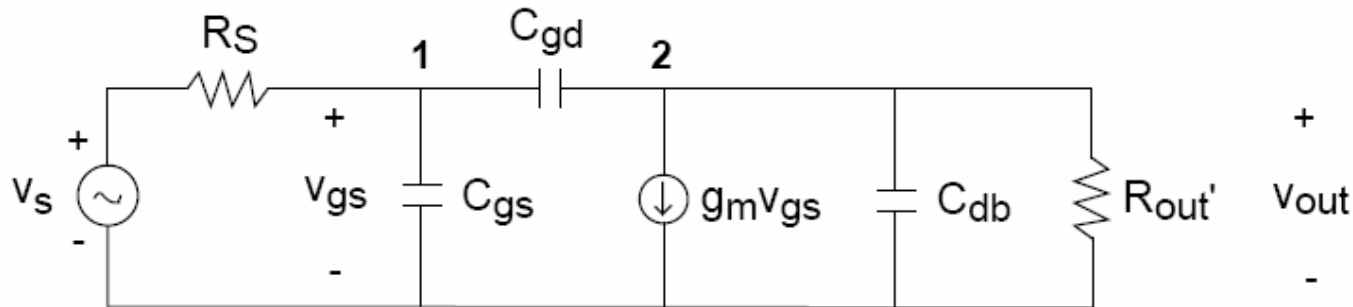

$$A_v = \frac{-(g_m - j\omega C_{gd})R'_{out}}{DEN}$$

$$DEN = 1 + j\omega\{R_S C_{gs} + R_S C_{gd}[1 + R'_{out}(\frac{1}{R_S} + g_m)] + R'_{out} C_{db}\} - \omega^2 R_S R'_{out} C_{gs}(C_{gd} + C_{db})$$


Assumptions for simplification:

$$(1) \omega \ll \omega_T = \frac{g_m}{C_{gs} + C_{gd}} \Rightarrow g_m \gg \omega(C_{gs} + C_{gd}) > \omega C_{gs}, \omega C_{gd}$$

(2): Ignore  $\omega^2$  term

$$(3): \frac{1}{R_S} + g_m \simeq g_m$$

# Lect. 7: Amplifier Frequency Response

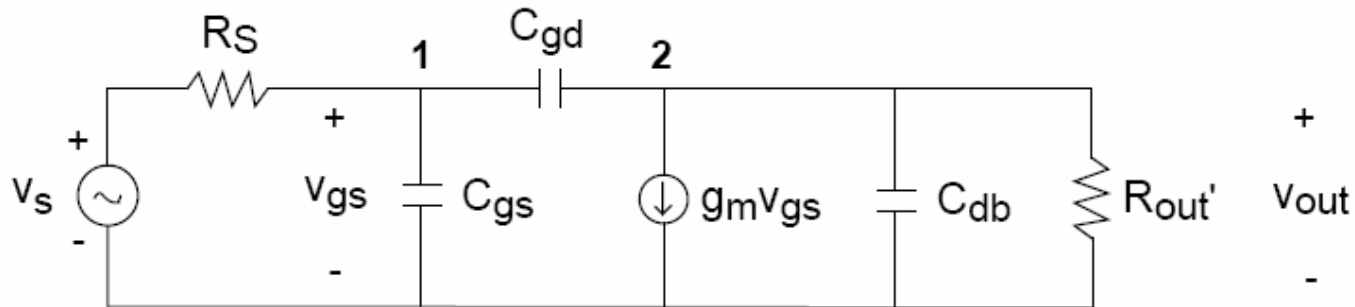

$$A_v \simeq \frac{-g_m R'_{out}}{1 + j\omega [R_S C_{gs} + R_S C_{gd} (1 + g_m R'_{out}) + R'_{out} C_{db}]}$$

$$\text{Or } A_v(\omega) = \frac{A_{v,LF}}{1 + j\frac{\omega}{\omega_H}} \quad \text{with} \quad \omega_H = \frac{1}{R_S C_{gs} + R_S C_{gd} (1 + g_m R'_{out}) + R'_{out} C_{db}}$$

Frequency response of CS limited by  $C_{gs}$ ,  $C_{gd}$  for input and  $C_{db}$  for output.

# Lect. 7: Amplifier Frequency Response

---

Compare  $f_H$  with  $f_T$

$$f_H = \frac{1}{2\pi \{ R_S [C_{gs} + C_{gd}(1 + |A_{v,LF}|)] + R'_{out} C_{db} \}}$$

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$


$$f_H \ll f_T$$

Mainly because  $f_H$  has  $A_{v,LF}$  in denominator  
making  $C_{gd}$  effectively very large

→ Miller Effect

# Lect. 7: Amplifier Frequency Response

## Miller Effect

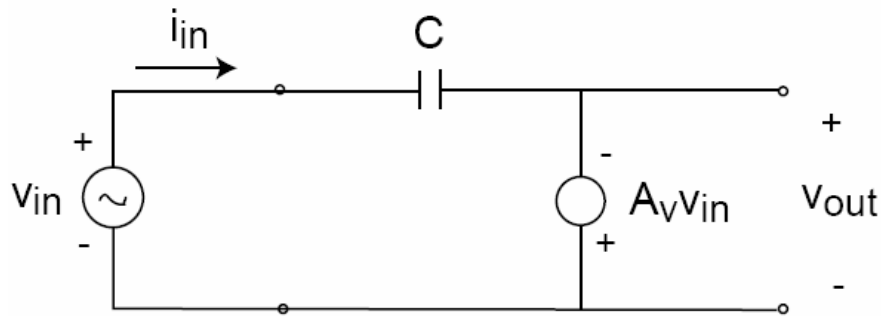

$$C_{Miller} = C(1 + A_v)$$

$$v_{in} \uparrow \Rightarrow v_{out} = -A_v v_{in} \downarrow \downarrow \Rightarrow (v_{in} - v_{out}) \uparrow \uparrow \Rightarrow i_{in} \uparrow \uparrow$$

→ Less impedance → Larger capacitance


In CS,  $C_{gd}$  causes Miller effect: Larger gain → Slower

Is it always bad? Can be used for implementing large capacitor values in IC.

# Lect. 7: Amplifier Frequency Response

---

Does CD suffer from Miller effect?

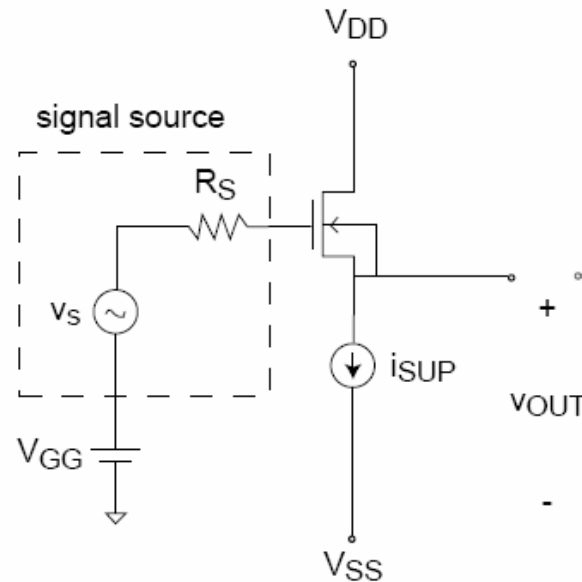


$A_v$  is almost 1!

# Lect. 7: Amplifier Frequency Response

---

Does CG suffer from Miller effect?

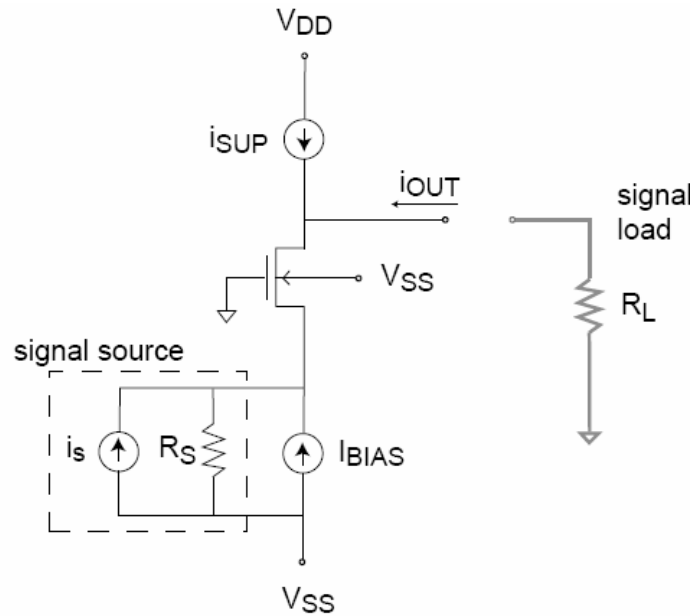


No Miller capacitor!



# Lect. 7: Amplifier Frequency Response

Design large gain, high-speed transconductance amplifier

Start with CS

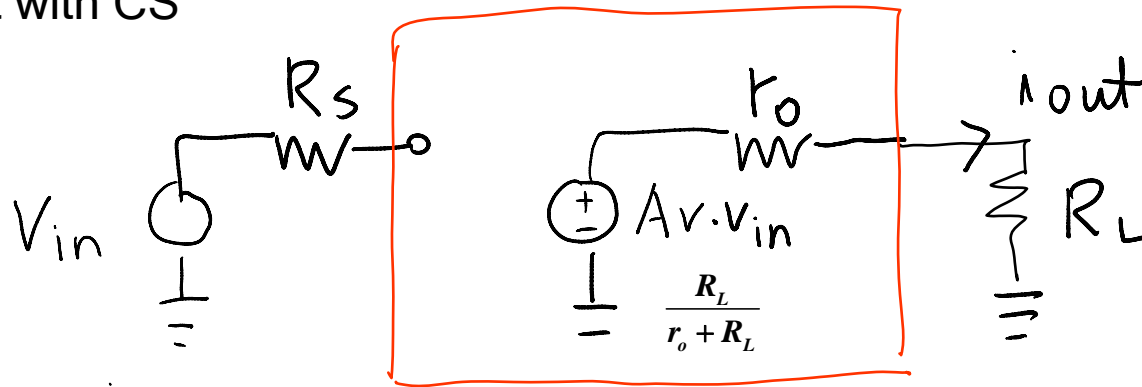

$$i_{out} = \frac{A_{vo} v_{in}}{r_o} \frac{r_o}{r_o + R_L} = \frac{-g_m r_o v_{in}}{r_o} \frac{r_o}{r_o + R_L} = -g_m v_{in} \frac{r_o}{r_o + R_L}$$

$$\frac{i_{out}}{v_{in}} = -g_m \frac{r_o}{r_o + R_L}$$


Problem if  $R_L > r_o$

→ Use current buffer

# Lect. 7: Amplifier Frequency Response

Design large gain, high-speed transconductance amplifier

Add CG Stage

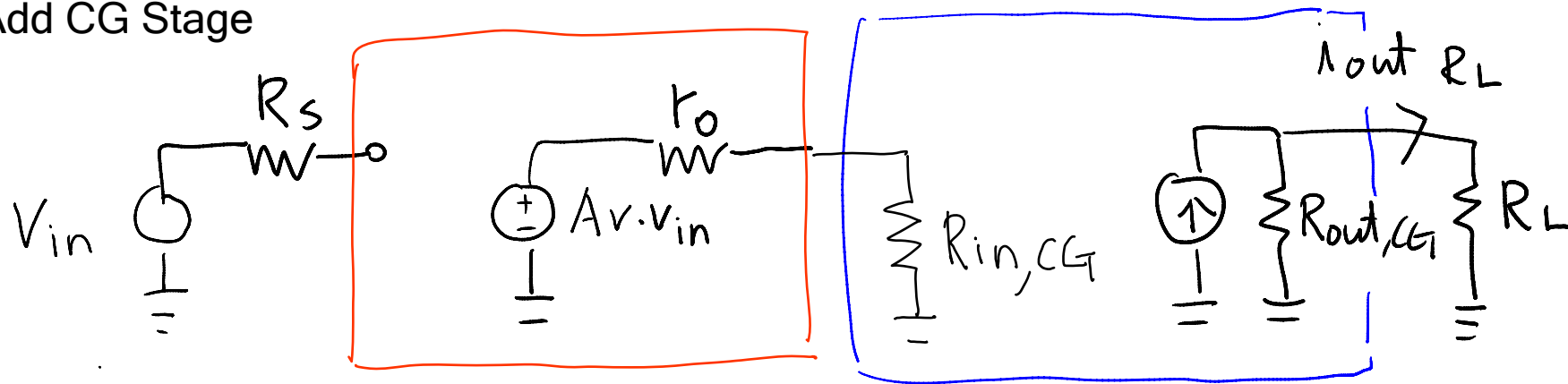

Assuming ideal current buffer,

$$\frac{i_{out}}{v_{in}} = -g_m \quad (\text{CS} + \text{CG})$$

$$\frac{i_{out}}{v_{in}} = -g_m \frac{r_o}{r_o + R_L} \quad (\text{CS only})$$

In addition, CG is fast!

For a given target gain,  
we can achieve higher speed transconductance speed amp by reducing  $g_m$ !

→ Cascode amplifier