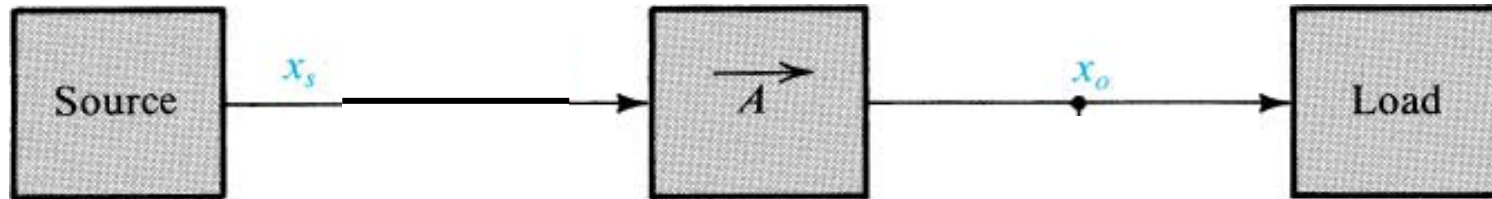


# Lect. 9: Feedback (S&S 8.1-8.2, 8-10, 8-11)

Feedback

Amplifier



$$x_o = Ax_s$$

$$x_f = \beta x_o$$

$$x_i = x_s - x_f = x_s - \beta x_o$$


$$x_o = Ax_i = A(x_s - \beta x_o)$$

$$x_o(1 + A\beta) = Ax_s$$

$$\therefore A_f = \frac{x_o}{x_s} = \frac{A}{1 + A\beta} \quad (\text{Close loop gain})$$

( $A\beta$ : loop gain)

# Lect. 9: Feedback

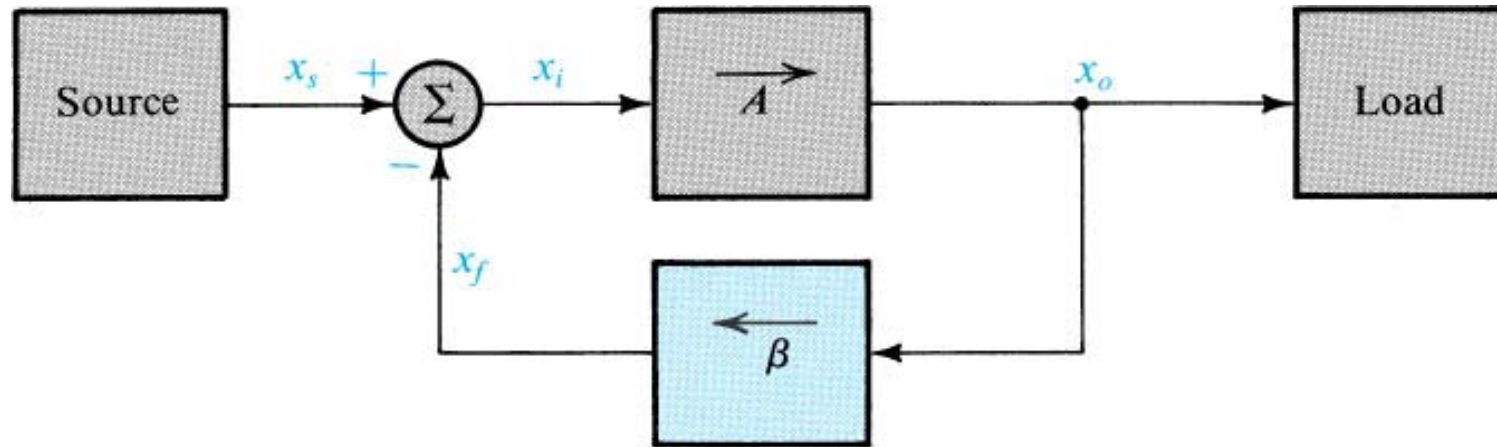


$$A_f = \frac{x_o}{x_s} = \frac{A}{1 + A\beta} \approx \frac{1}{\beta} \quad (\text{If } A\beta \gg 1)$$

What good is it?

Consider  $\frac{dA_f}{A_f} = \frac{1}{(1 + A\beta)} \frac{dA}{A} \ll \frac{dA}{A} \rightarrow A_f$  is not influenced by changes in  $A$

# Lect. 9: Feedback

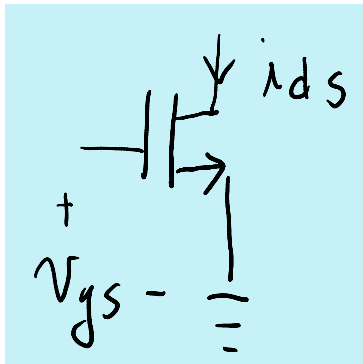
Example: Consider CS transconductance amplifier




$$G_m = i_{ds}/v_{gs} = g_m$$

Assume  $g_m$  is not very predictable

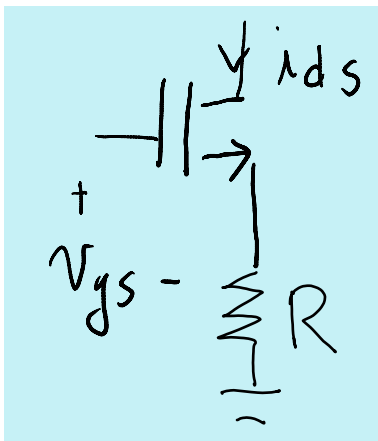→ Amplifier performance is not predictable



CS with source resistance

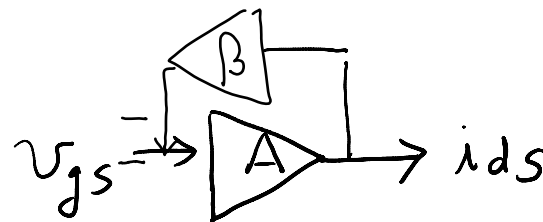

$$A = g_m \quad \beta = R$$


$$A_f = \frac{A}{1 + A\beta}$$

$$G_m = \frac{i_{ds}}{v_{gs}} = \frac{g_m}{1 + g_m R} \approx \frac{1}{R}$$

$G_m$  is controlled by  $R$ !
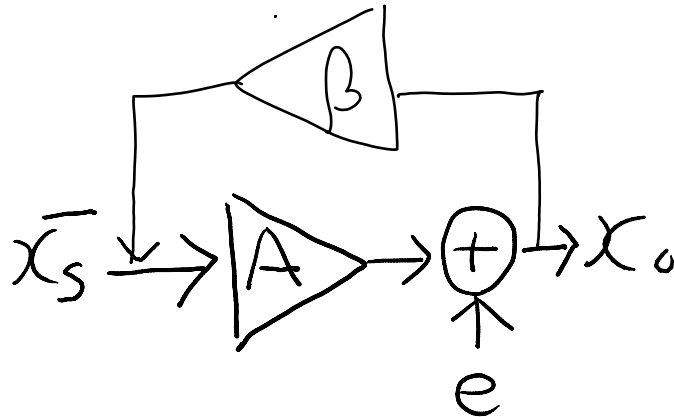
# Lect. 9: Feedback

Consider a case in which noises are added to an amplifier




Without feedback  $x_o = Ax_s + e$

With feedback  $x_o = A(x_s - \beta x_o) + e$        $x_o(1 + A\beta) = Ax_s + e$

$$\therefore x_o = \frac{A}{1 + A\beta} x_s + \frac{e}{1 + A\beta} \approx \frac{1}{\beta} x_s \quad \rightarrow \text{Output not influenced by noises}$$

# Lect. 9: Feedback

## Frequency Response of Feedback System

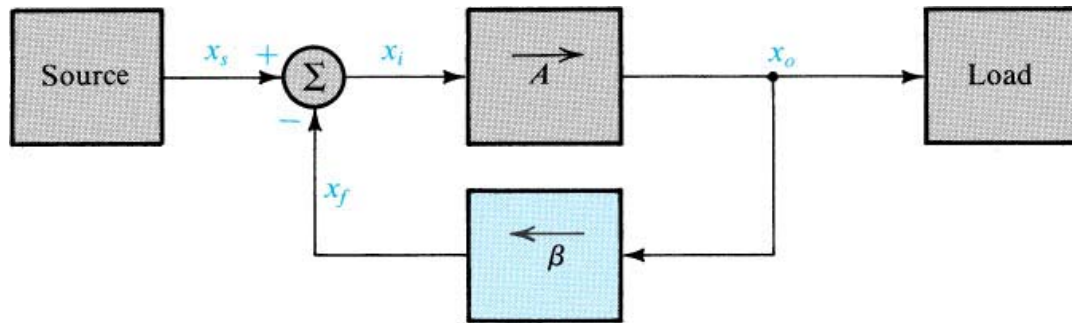

Assume  $A(s) = \frac{A_M}{1 + s/\omega_H}$

Then  $A_f(s) = \frac{A(s)}{1 + \beta A(s)}$


( $\beta$  is frequency independent)

$$A_f(s) = \frac{\frac{A_M}{1 + s/\omega_H}}{1 + \beta \frac{A_M}{1 + s/\omega_H}} = \frac{A_M}{1 + \beta A_M + s/\omega_H} = \frac{A_M / (1 + A_M \beta)}{1 + s/\omega_H (1 + A_M \beta)}$$

$\omega_{Hf} = \omega_H (1 + A_M \beta)$       Bandwidth extension!


Reduction in LF gain

# Lect. 9: Feedback

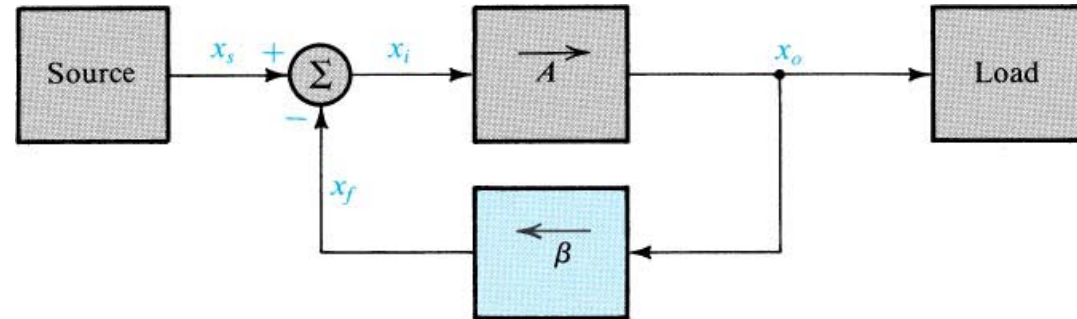

$$A(s) = \frac{A_M}{1 + s / \omega_H}$$
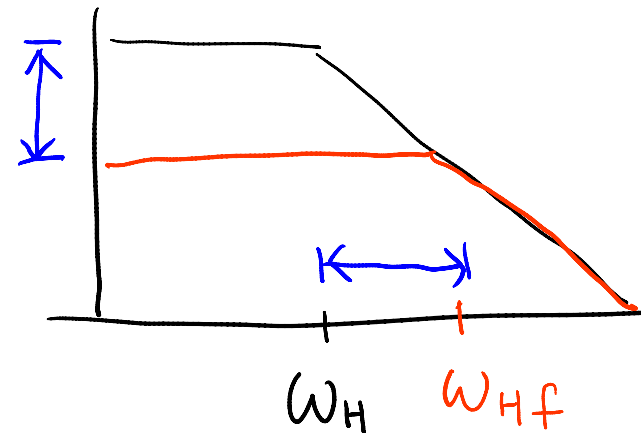
$$A_f(s) = \frac{A_M / (1 + A_M \beta)}{1 + s / \omega_H (1 + A_M \beta)}$$



# Lect. 9: Feedback

Is feedback always possible? → Stability of feedback system

$$A_f(s) = \frac{A(s)}{1 + \beta A(s)}$$


If  $\beta A(s) = -1$ , system becomes unstable !

For stable feedback system design,

Phase  $[\beta A(s)] > -180$  deg when  $|\beta A(s)| = 1$

Design  $A(s)$  with feedback application in mind


→ Provide sufficient phase margin

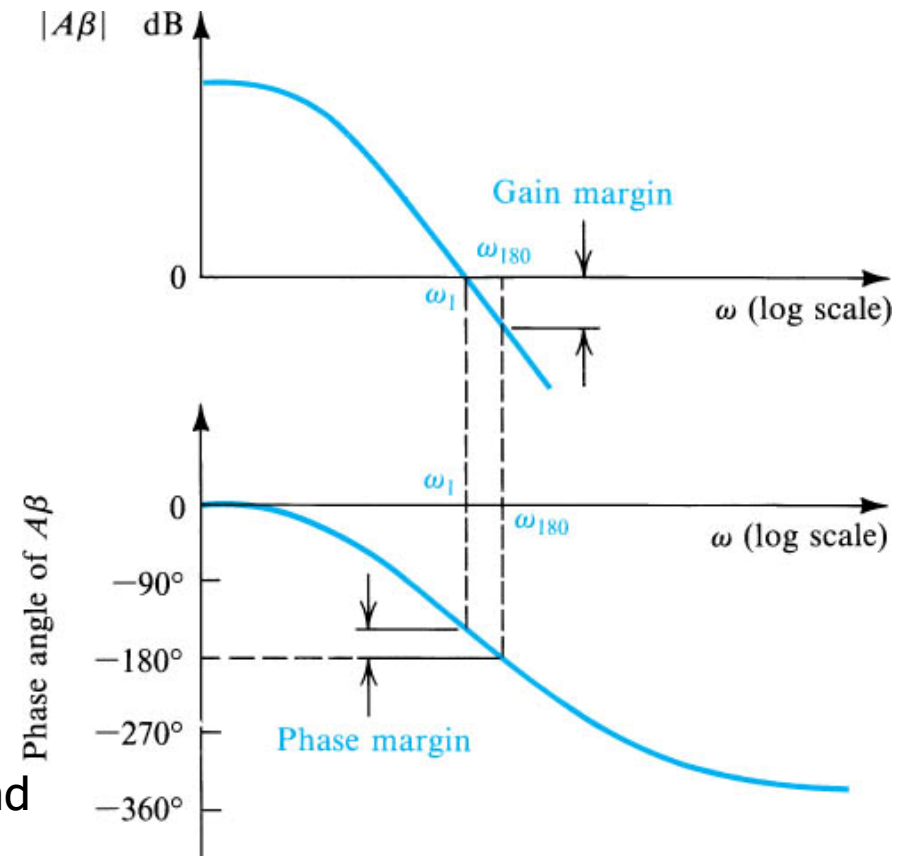
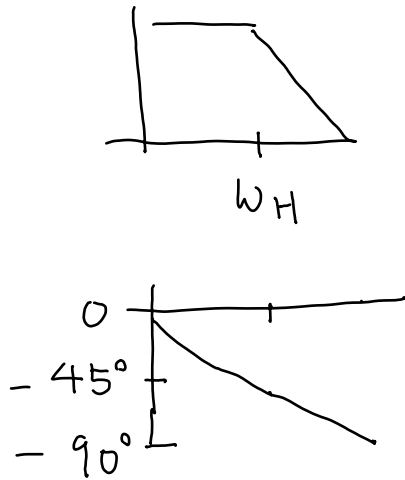
# Lect. 9: Feedback

Consider CS


$$A_v(\omega) = \frac{A_{v,LF}}{1 + j\frac{\omega}{\omega_H}}$$



$\beta A(s)$  will never reach -1

-Single-stage CS has no problem for feedback stability

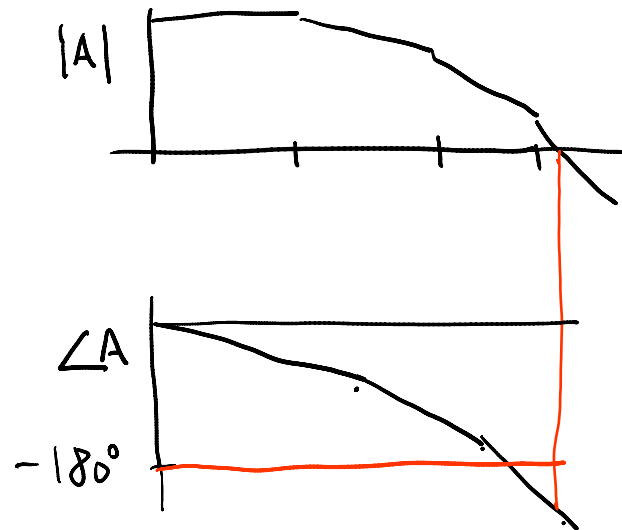- For most applications, multi-stage amplifiers are used  
→ Multi-pole system



Very careful consideration for phase margin is required!



# Lect. 9: Feedback

For a given amplifier,  
can we tell from its Bode plot  
if it is OK for a given  $\beta$ ?

Plot  $20 \log(1/\beta) = 85 \text{ dB}$

( $\beta = 5.6 \times 10^{-5}$ )


→ Difference is  $20 \log|A\beta|$

→ Determine the phase margin

What is max.  $\beta$ ?


$20 \log(1/\beta) = 60 \text{ dB}$

→ Max.  $\beta = 0.001$

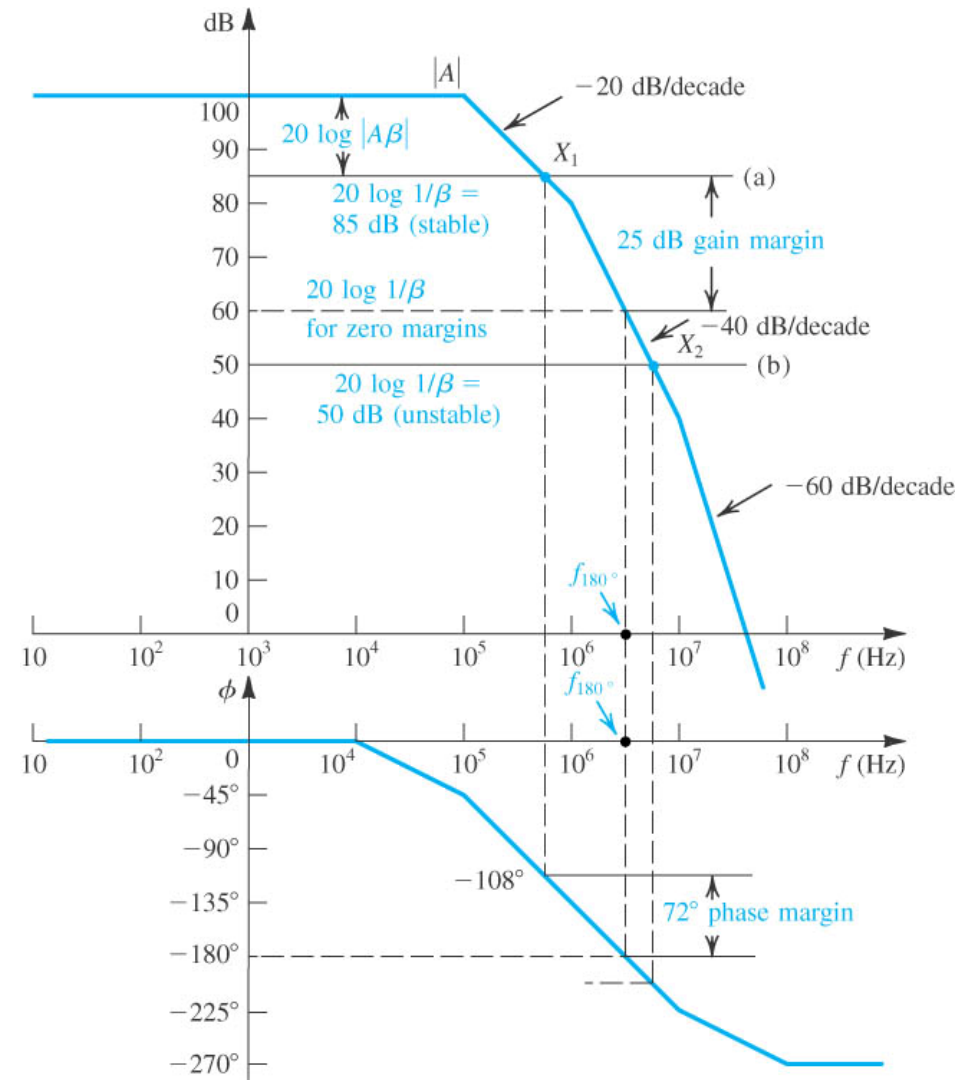

# Lect. 9: Feedback

## Bode plots for multi-pole amplifier

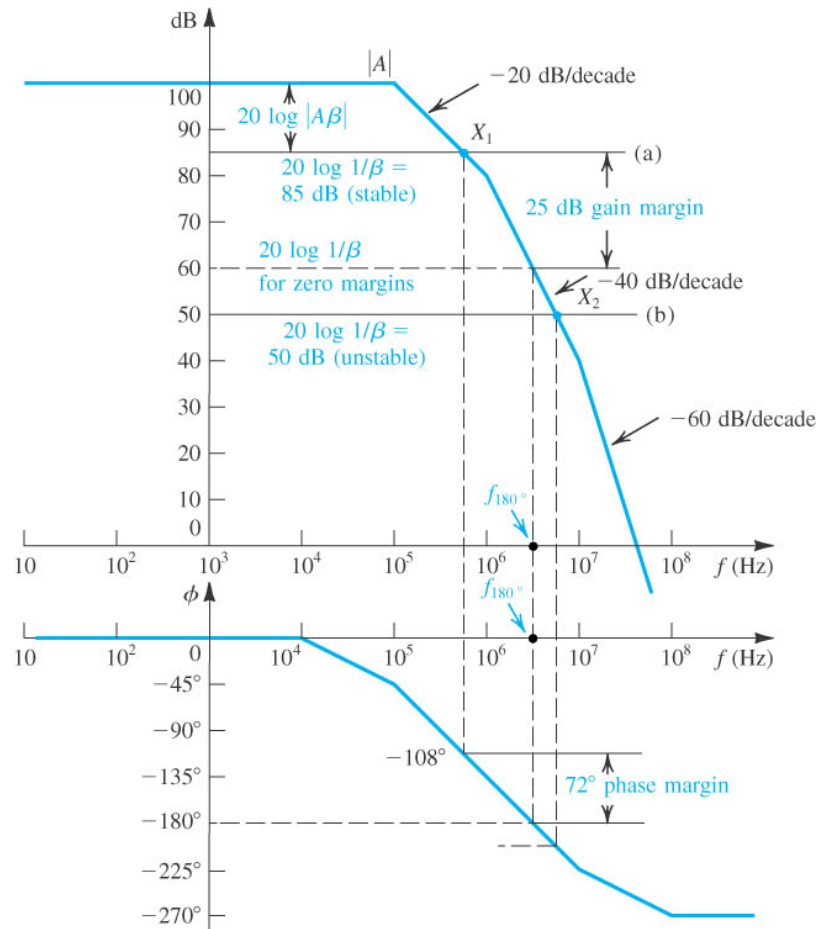

Observation:

-180 deg phase point always occurs on -40dB/decade segment of  $|A|$

If  $|A|$  intersects  $20 \log(1/\beta)$  with -20dB/decade slope,

→ Stable!