
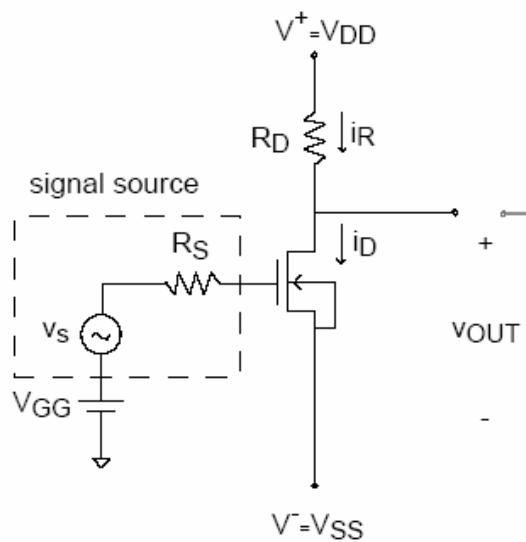


Lect. 8: Current Source and Active Load

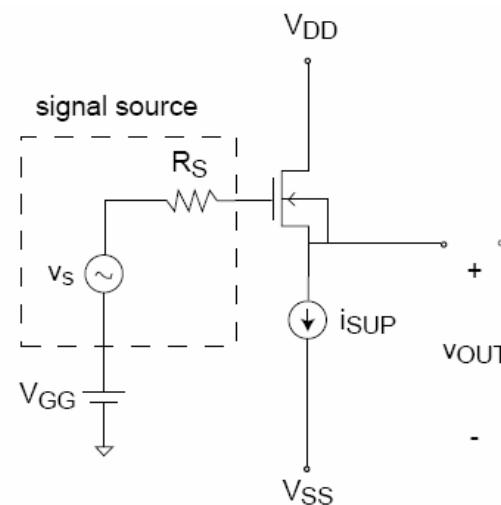
Three basic amplifier configurations: CS, CD, CG



Common Source



Common Drain
(Source Follower)

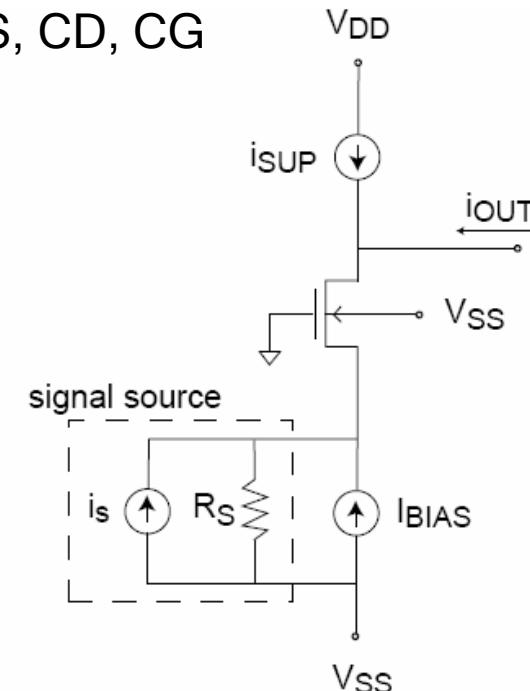


Common Gate

→ How to implement current sources and active loads?

Lect. 8: Current Source and Active Load

Constant current source:
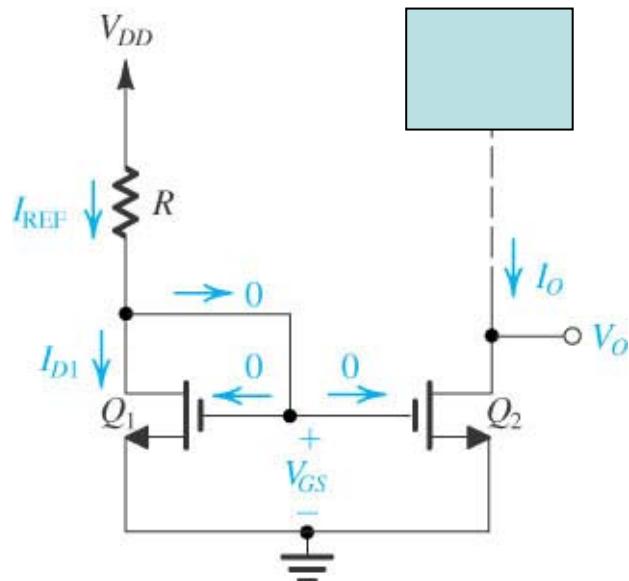
$$I_{D1} = \frac{1}{2} k_n \left(\frac{W}{L} \right)_1 (V_{GS} - V_t)^2$$



→ Current mirror

$$I_{D1} = I_{REF} = \frac{V_{DD} - V_{GS}}{R}$$

Assuming Q_1, Q_2 have same characteristics


$$I_O = I_{D2} = \frac{1}{2} k_n \left(\frac{W}{L} \right)_2 (V_{GS} - V_t)^2$$

$$\frac{I_O}{I_{REF}} = \frac{(W/L)_2}{(W/L)_1}$$

Limitation on V_O ? $V_O \geq V_{GS} - V_{tn}$

Lect. 8: Current Source and Active Load

Mismatches between I_{REF} and I_O

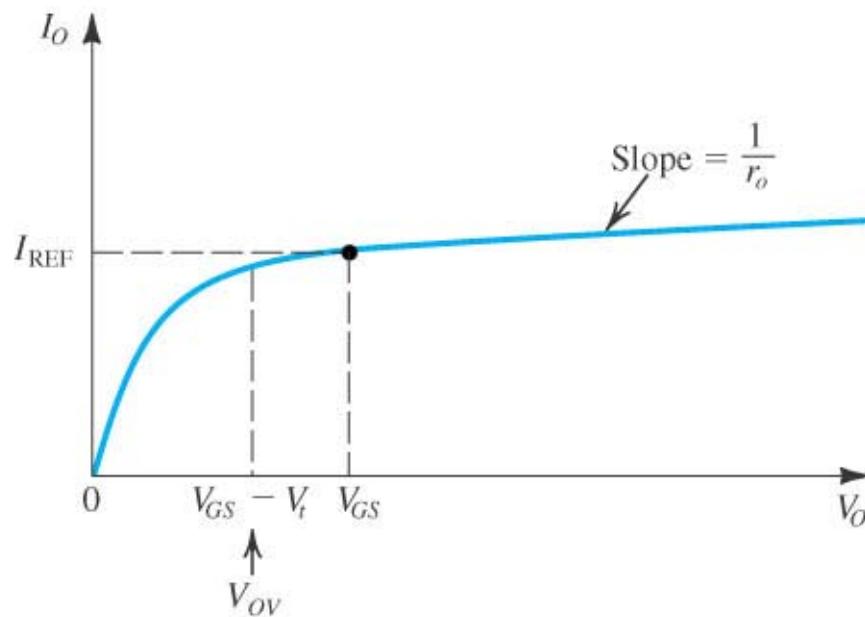


Channel-length modulation

$$I_O = I_{REF} + \frac{V_O - V_{GS}}{r_0} \approx I_{REF} + \frac{V_O}{r_0}$$

Circuit Model

Lect. 8: Current Source and Active Load

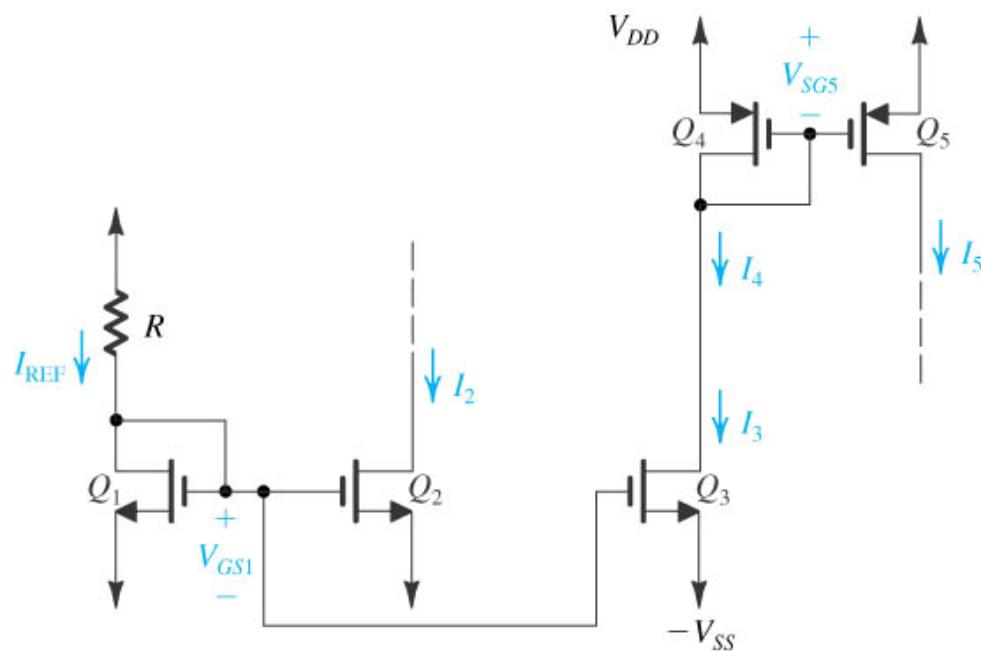


$$I_2 = I_{REF} \frac{(W/L)_2}{(W/L)_1}$$

$$I_3 = I_{REF} \frac{(W/L)_3}{(W/L)_1}$$

$$I_5 = I_4 \frac{\left(W/L\right)_5}{\left(W/L\right)_4}$$

Lect. 8: Current Source and Active Load


CS amplifier with an active load

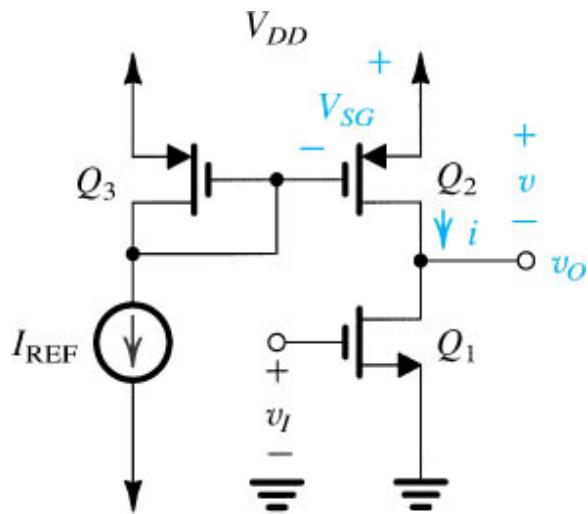

Large change in v_∞ with v_i change!

Effective Load: r_{o2}
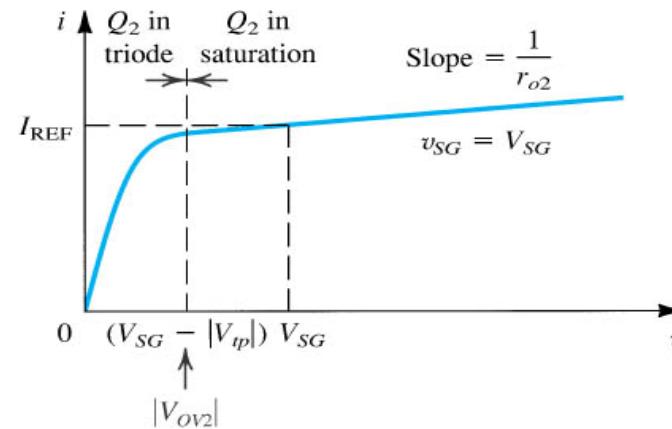
$$A_{vo} = -g_m (r_{o1} \parallel r_{o2})$$



$$V = V_{DD} - V_o$$

