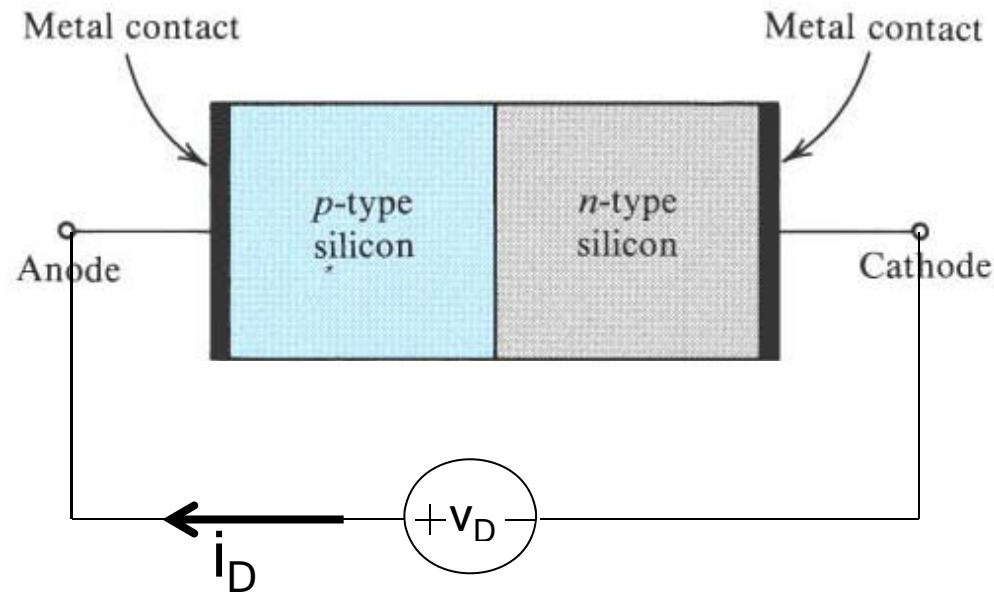


Lect. 10: Bipolar Junction Transistors

(4.1-4.4 in Razavi) —

Review of PN Junction




$v_D > 0$: $i_{\text{diffusion}} > i_{\text{drift}}$, $\rightarrow i_D > 0$, very large

$v_D < 0$: $i_{\text{diffusion}} < i_{\text{drift}}$, $\rightarrow i_D < 0$, not much

$$i_D = I_S \left[\exp\left(\frac{v_D}{V_T}\right) - 1 \right]$$

Lect. 10: Bipolar Junction Transistors

How does BJT work?

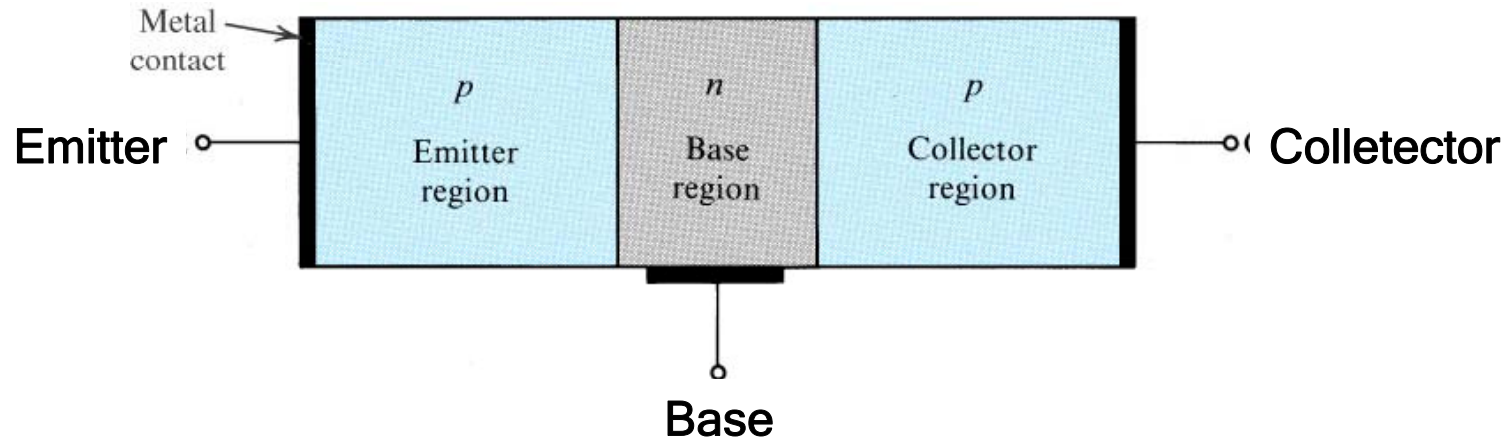

- BJT: Two PN junctions connected back-to-back
- Assume EB junction is forward-biased and CB is reverse-biased (active region).


$$i_E = I_S \left[\exp\left(\frac{V_{EB}}{V_T}\right) - 1 \right], \quad i_B, i_C = ?$$

For reverse-biased PN junction,
not much current flows because there are not many carriers (holes).


With BJT, carriers (holes) are supplied from Emitter and they flow to Collector!

$$i_C \text{ is almost equal to } i_E: i_C = \alpha i_E \quad \rightarrow \quad i_B = i_E - i_C$$

Lect. 10: Bipolar Junction Transistors

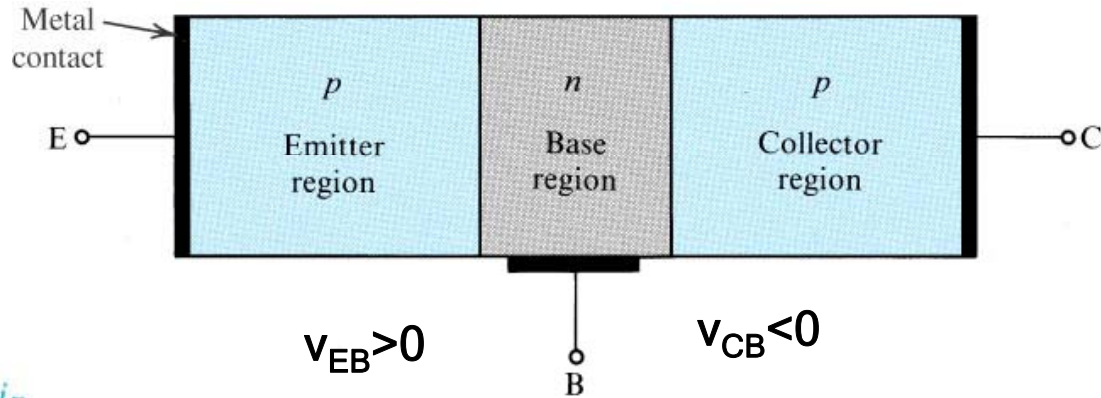

Circuit model

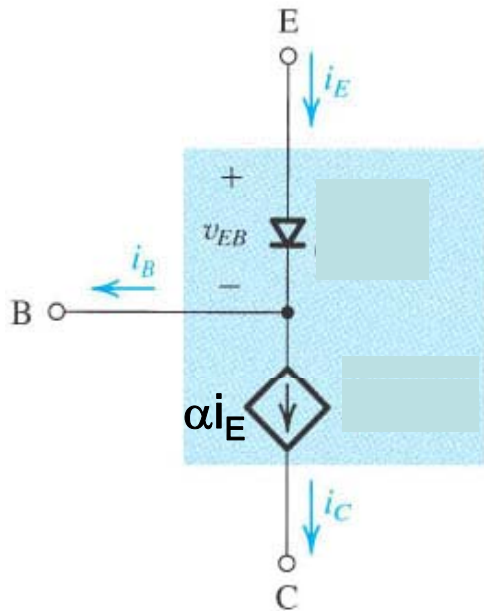

voltage-controlled current source


$$i_E = I_S [\exp(v_{EB}/V_T) - 1]$$

$$i_C = \alpha i_E$$

$$i_B = i_E - i_C = (1 - \alpha) i_E = \frac{1 - \alpha}{\alpha} i_C$$


$$= \frac{1}{\beta} i_C$$

$$\therefore i_C = \beta i_B$$


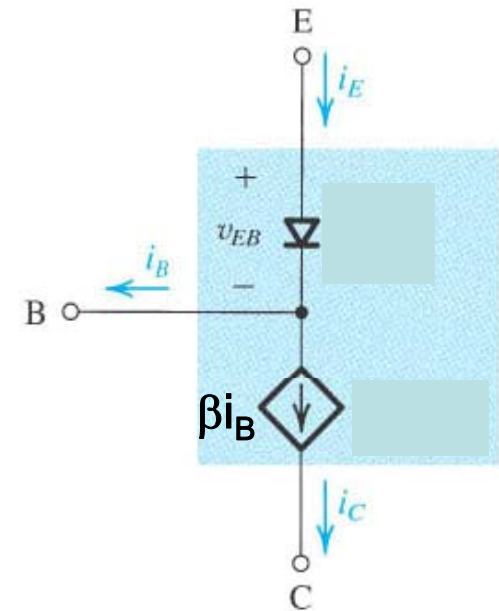


Current-controlled current source



Lect. 10: Bipolar Junction Transistors

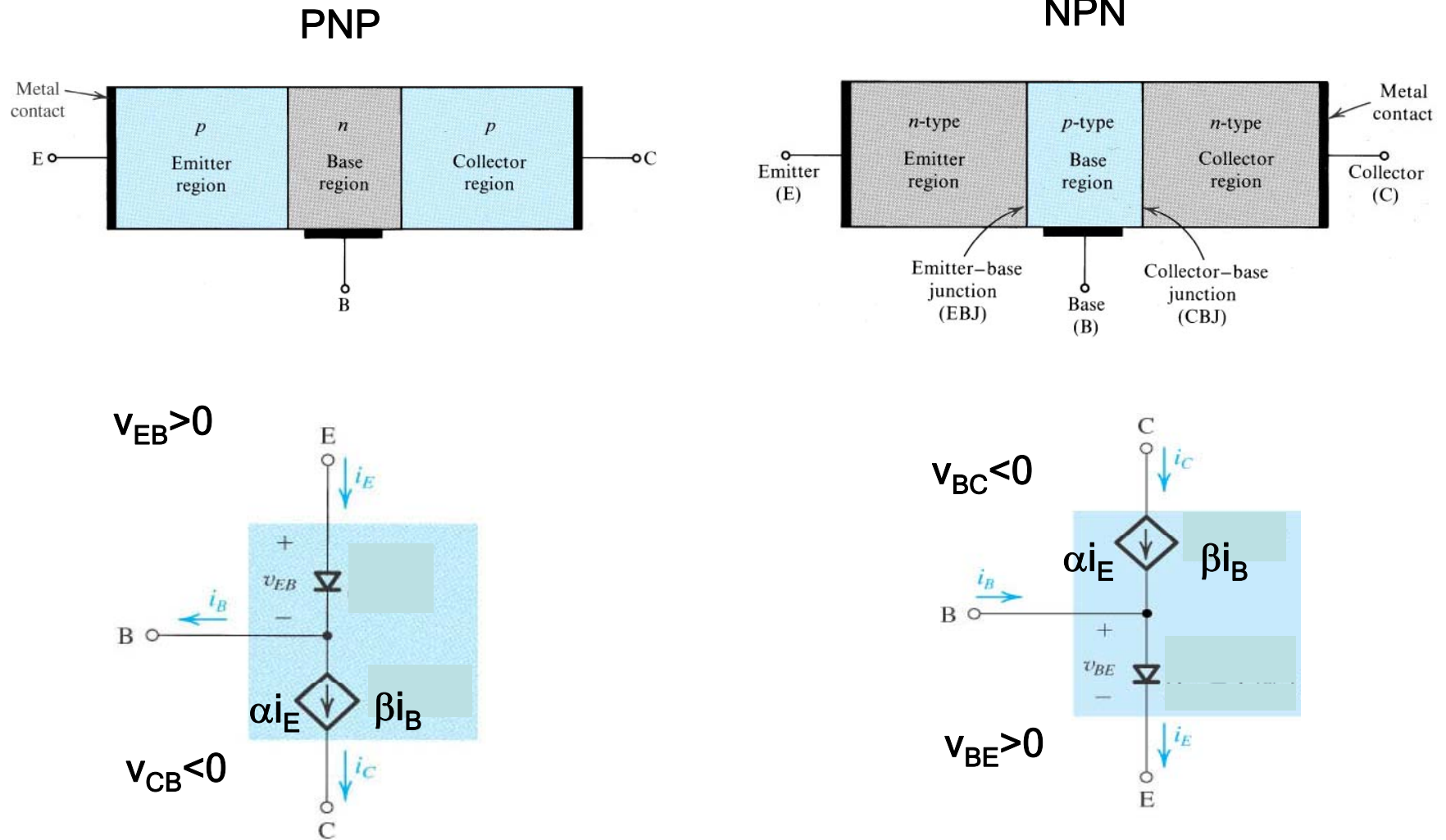

Lect. 10: Bipolar Junction Transistors

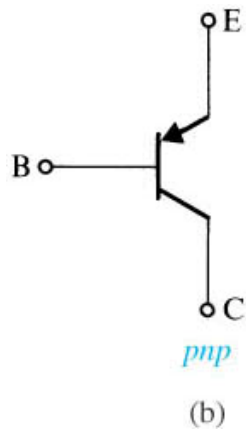
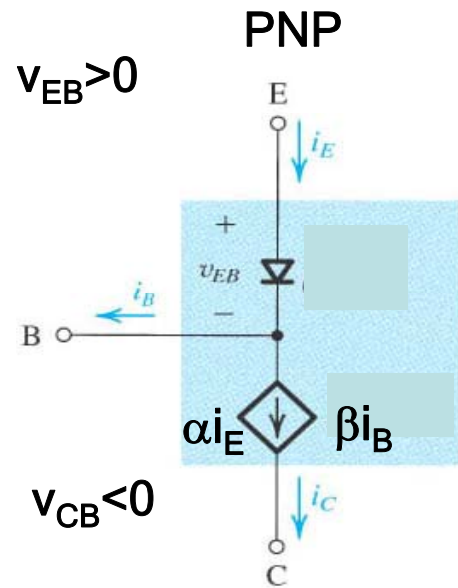


Circuit Symbols

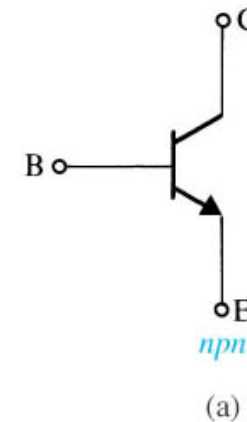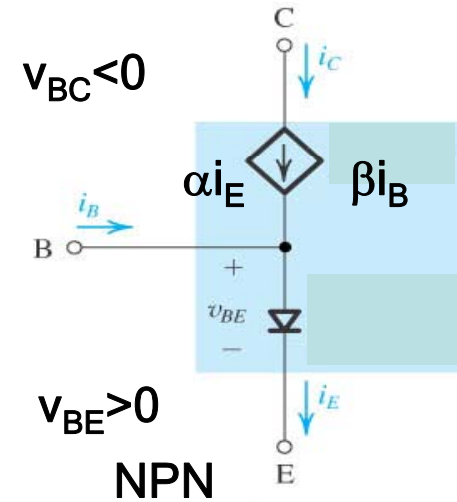

Lect. 10: Bipolar Junction Transistors




I-V Characteristics (NPN)

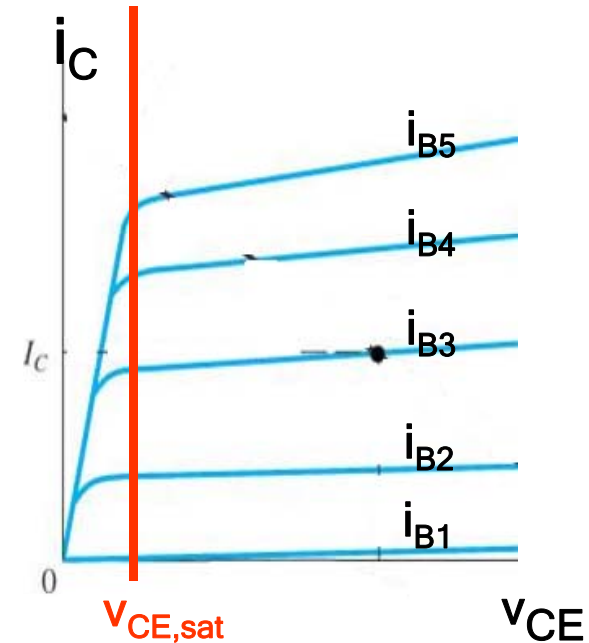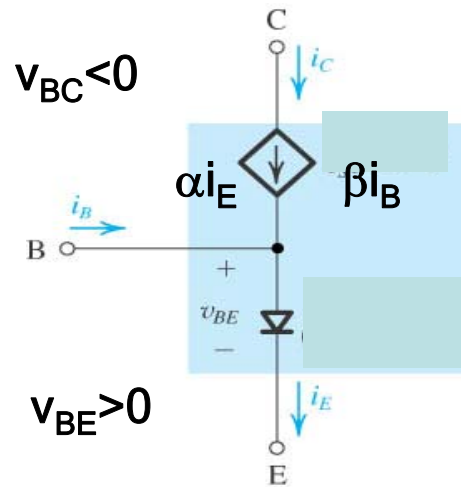

1. Model is valid only for $v_{CE} > v_{CE,sat}$ (active region)
2. Even in active region, i_C increases with v_{CE} (Early effect)
→ Not an ideal current source

Lect. 10: Bipolar Junction Transistors

Condition for active region (NPN)?

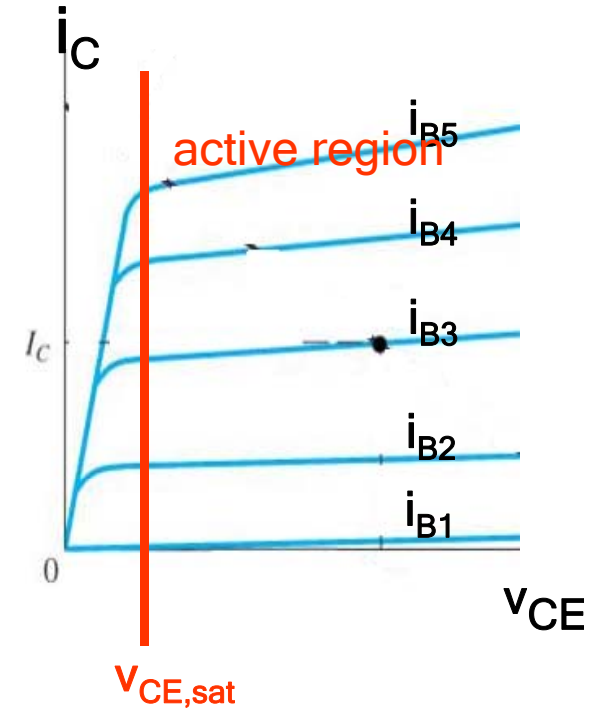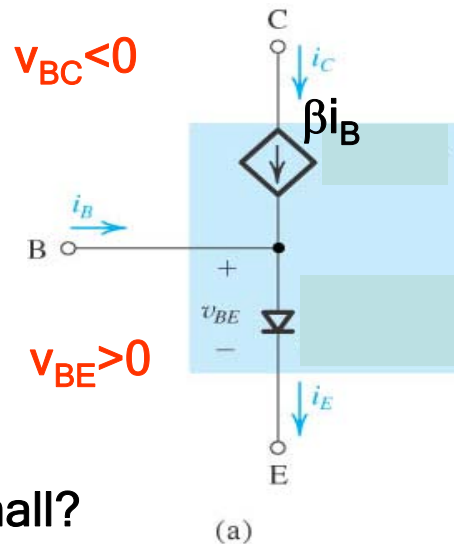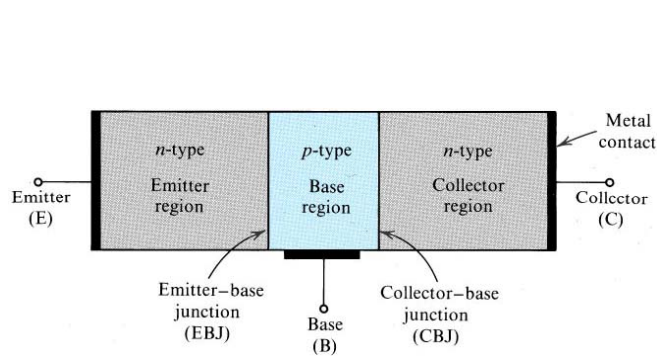

What happens when v_{CE} is small?

$$v_{BE} = v_B - v_E \quad v_{BC} = v_B - v_C \quad \rightarrow \quad v_{CE} = v_{BE} - v_{BC}$$

When BC is reverse biased $\rightarrow v_{CE} \gg 0 \rightarrow$ active region

When BC is forward biased $\rightarrow v_{CE}$ is small \rightarrow saturation

Lect. 10: Bipolar Junction Transistors

I-V Characteristics (PNP)

