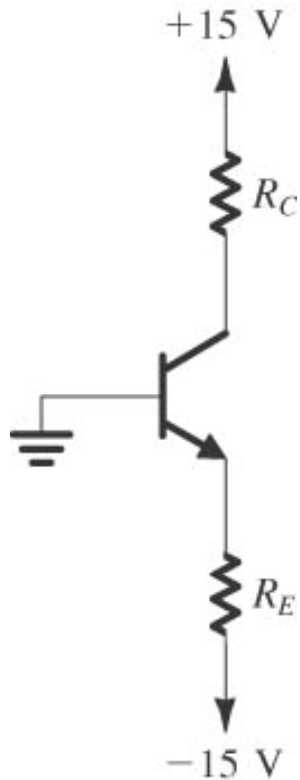


Lect. 11: BJT Circuits at DC

$\beta=100$, $v_{BE,ON}=0.7V$, $V_{CE,sat}=0.3V$.

Design the circuit so that $I_C=2mA$ and $V_C=5V$ in the active region.



(1) What is R_C ?

(2) What is I_E ?

(3) What is V_E ?

(4) What is R_E ?

(5) Is it in active region?

$$(1) R_C = \frac{10 \text{ V}}{2 \text{ mA}} = 5 \text{ k}\Omega$$

$$(2) I_E = I_B + I_C = \frac{2}{100} + 2 = 2.02 \text{ mA}$$


$$(3) V_E = -0.7V$$

$$(4) R_E = \frac{V_E - (-15)}{2.02} = 7.08 \text{ k}\Omega$$

$$(5) V_{CE} = 5 - (-0.7) = 5.7 > V_{CE,sat}$$

Lect. 11: BJT Circuits at DC

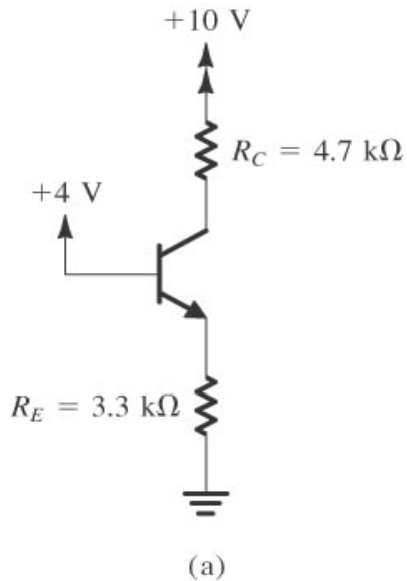Using $V_{BE,ON}=0.7V$, $\beta = 100$, $V_{CE,sat}=0.2V$



1. $V_E = ?$

2. $I_E = ?$

3. $I_C = ?$

4. $V_C = ?$

5. $I_B = ?$

$$V_E = 4 - V_{BE} = 4 - 0.7 = 3.3 \text{ V}$$

$$I_E = \frac{V_E - 0}{R_E} = \frac{3.3}{3.3} = 1 \text{ mA}$$

$$I_C = \alpha I_E$$

$$\alpha = \frac{\beta}{\beta + 1} = \frac{100}{101} \sim 0.99$$


$$I_C = 0.99 \times 1 = 0.99 \text{ mA}$$

$$V_C = 10 - I_C R_C = 10 - 0.99 \times 4.7 \sim 5.3 \text{ V}$$

$$I_B = \frac{I_E}{\beta + 1} = \frac{1}{101} \sim 0.01 \text{ mA}$$

Lect. 11: BJT Circuits at DC

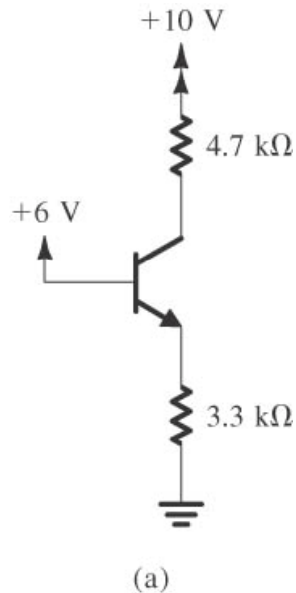Using $V_{BE,ON}=0.7V$, $\beta = 100$, $V_{CE,sat}=0.2V$



1. $V_E = ?$

2. $V_C = ?$

3. $I_B = ?$

$$V_E = +6 - V_{BE} = 6 - 0.7 = 5.3 \text{ V}$$

$$I_E = \frac{5.3}{3.3} = 1.6 \text{ mA}$$

$$V_C = 10 - 4.7 \times I_C = 10 - 7.52 = 2.48 \text{ V}$$


$$V_{CE} = 2.48 - 5.3 = -2.82 \text{ (not possible)}$$

$$V_C \sim V_E + V_{CEsat} = 5.3 + 0.2 = +5.5 \text{ V}$$

$$I_C = \frac{+10 - 5.5}{4.7} = 0.96 \text{ mA}$$

$$I_B = I_E - I_C = 1.6 - 0.96 = 0.64 \text{ mA}$$


Lect. 11: BJT Circuits at DC

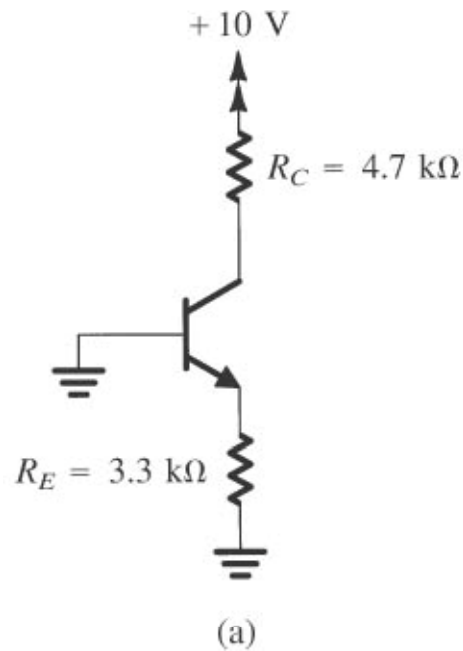

1. $V_E = ?$
2. $V_C = ?$
3. $I_B, I_C, I_E = ?$

Transistor is cut-off!

Lect. 11: BJT Circuits at DC

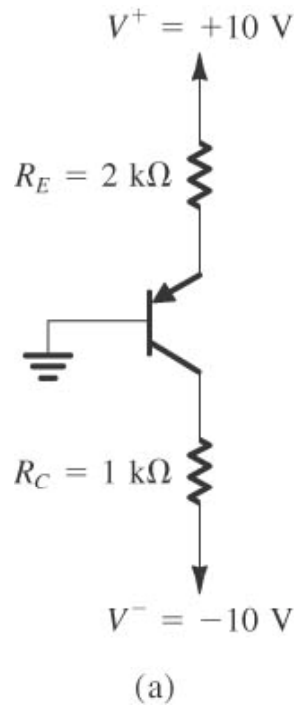

$$\beta = 100$$

1. $V_E = ?$

2. $I_C = ?$

3. $V_C = ?$

4. $I_B = ?$

$$V_E = V_{EB} = 0.7 \text{ V}$$

$$I_E = \frac{V^+ - V_E}{R_E} = \frac{10 - 0.7}{2} = 4.65 \text{ mA}$$


$$I_C = \alpha I_E = 0.99 \times 4.65 = 4.6 \text{ mA}$$

$$V_C = V^- + I_C R_C \\ = -10 + 4.6 \times 1 = -5.4 \text{ V}$$

$$I_B = \frac{I_E}{\beta + 1} = \frac{4.65}{101} = 0.05 \text{ mA}$$

$$V_{EC} = 0.7 - (-5.4) > V_{EC,sat}$$

Lect. 11: BJT Circuits at DC

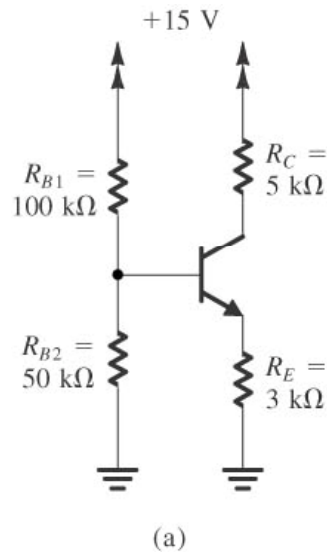

$$\beta = 100$$

1. $I_E = ?$
2. $V_C = ?$

$$V_{BB} = +15 \frac{R_{B2}}{R_{B1} + R_{B2}} = 15 \frac{50}{100 + 50} = +5 \text{ V}$$

$$R_{BB} = (R_{B1} // R_{B2}) = (100 // 50) = 33.3 \text{ k}\Omega$$

$$V_{BB} = I_B R_{BB} + V_{BE} + I_E R_E$$

$$I_B = \frac{I_E}{\beta + 1}$$

$$I_E = \frac{V_{BB} - V_{BE}}{R_E + [R_{BB} / (\beta + 1)]}$$

$$I_E = \frac{5 - 0.7}{3 + (33.3 / 101)} = 1.29 \text{ mA}$$

$$I_C = \alpha I_E = 1.28 \text{ mA}$$

$$V_C = +15 - I_C R_C = 15 - 1.28 \times 5 = 8.6 \text{ V}$$

$$I_B = \frac{1.29}{101} = 0.0128 \text{ mA}$$


$$V_B = V_{BE} + I_E R_E$$

$$= 0.7 + 1.29 \times 3 = 4.57 \text{ V}$$

$$V_E = V_B - V_{BE}$$

$$= 4.57 - 0.7 = 3.87 \text{ V}$$

Lect. 11: BJT Circuits at DC

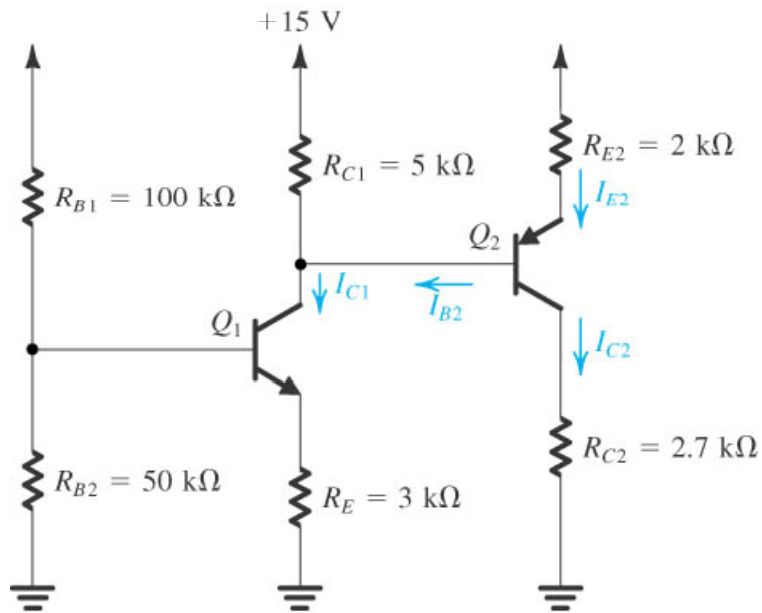

(a)

$\beta = 100$

1. $V_{C,1} = ?$
2. $I_{B2} = ?$

Ignoring I_{B2}


$$V_{C1} = +15 - I_{C1}R_{C1} \\ = 15 - 1.28 \times 5 = +8.6 \text{ V}$$

$$V_{E2} = V_{C1} + V_{EB}|_{Q2} = 8.6 + 0.7 = +9.3 \text{ V}$$

$$I_{E2} = \frac{+15 - V_{E2}}{R_{E2}} = \frac{15 - 9.3}{2} = 2.85 \text{ mA}$$

$$I_{B2} = \frac{I_{E2}}{\beta_2 + 1} = \frac{2.85}{101} = 0.028 \text{ mA}$$

Lect. 11: BJT Circuits at DC

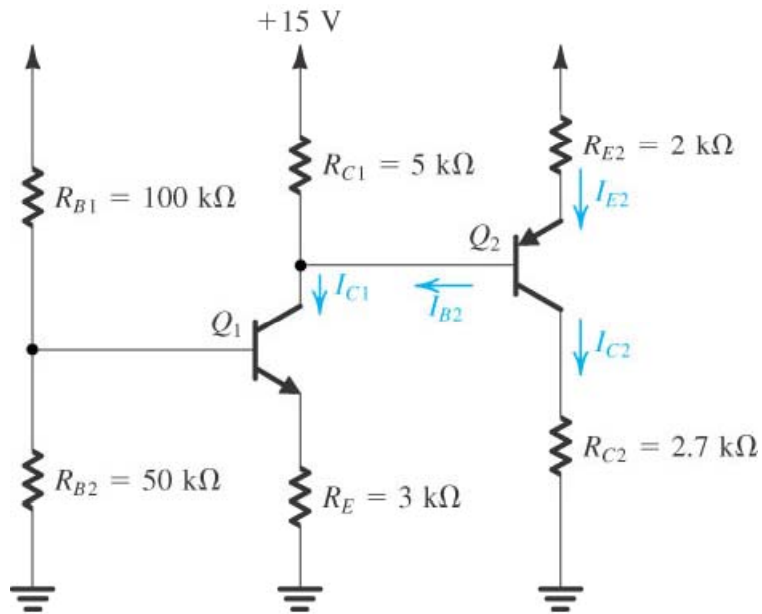

$$\beta = 100$$

1. $V_{C,1} = ?$
2. $I_{B2} = ?$

Considering I_{B2} ,

Does V_{C1} go up or down?

$$\text{Current in } R_{C1} = I_{C1} - I_{B2} = 1.28 - 0.028 = 1.252 \text{ mA}$$

$$V_{C1} = 15 - 5 \times 1.252 = 8.74 \text{ V} \quad (\text{Before, } 8.6 \text{ V})$$

$$V_{E2} = 8.74 + 0.7 = 9.44 \text{ V}$$

$$I_{E2} = \frac{15 - 9.44}{2} = 2.78 \text{ mA}$$

$$I_{B2, \text{new}} = \frac{2.78}{101} = 0.0275 \text{ mA} \quad (\text{Before, } 0.028 \text{ mA})$$