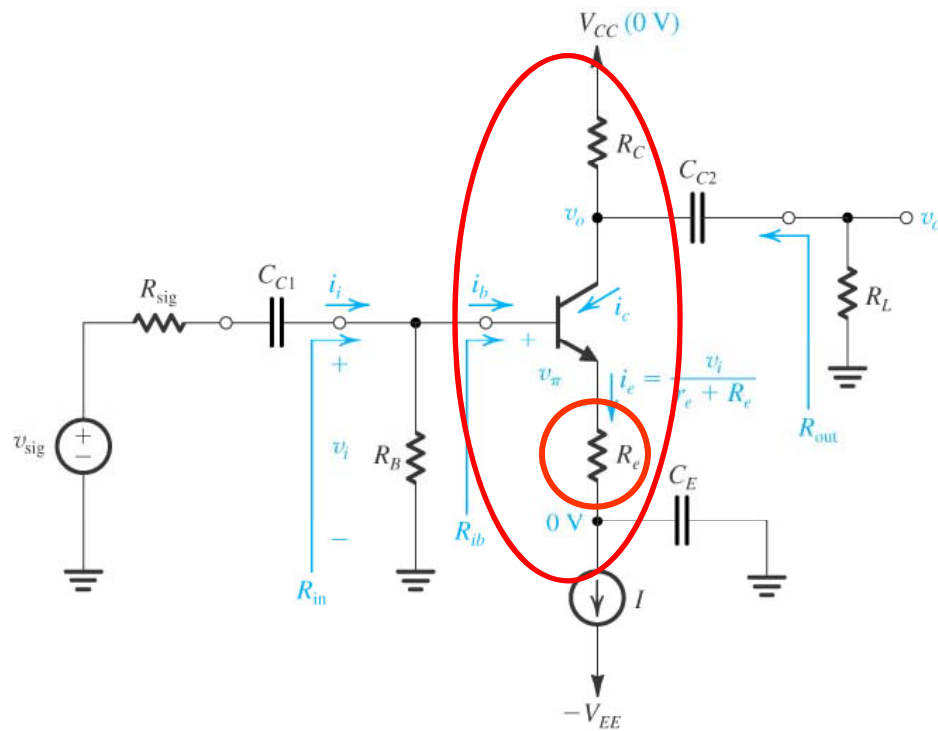



# Lect. 14: BJT CE Amplifier with Emitter Resistance

Common-Emitter with emitter resistance (degeneration)



(a)


Voltage Gain,  $R_{in}$ ,  $R_{out}$

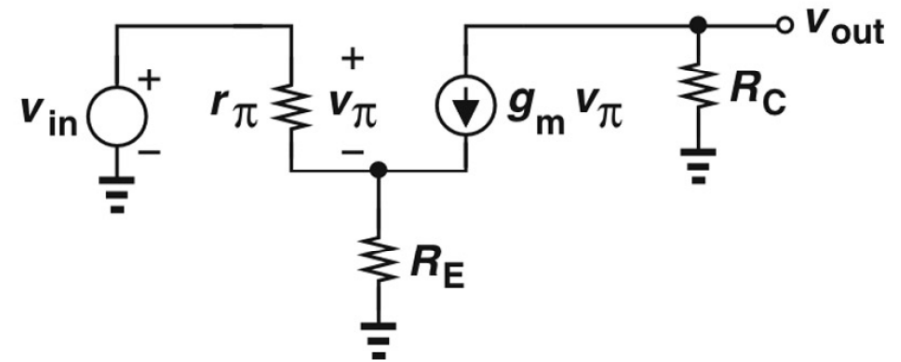

(Ignore  $r_o$  for simplicity)

# Lect. 14: BJT CE Amplifier with Emitter Resistance


Common-Emitter with emitter resistance

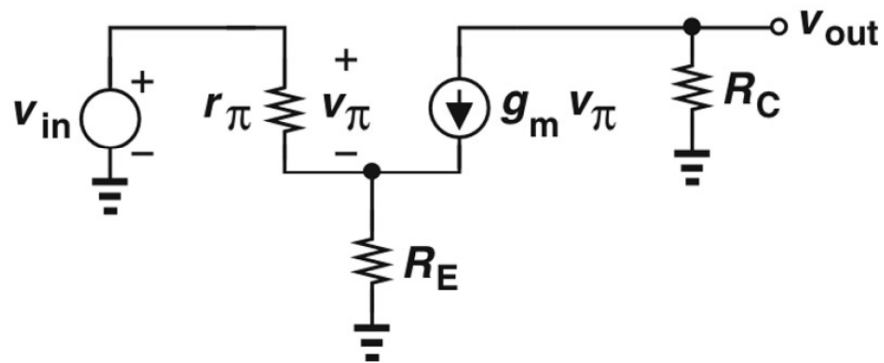

Voltage Gain = ?

$$A_v = -\frac{g_m R_C}{1 + \left(\frac{1}{r_{\pi}} + g_m\right) R_E}$$
$$\sim -\frac{g_m R_C}{1 + g_m R_E}$$
$$= -\frac{R_C}{\frac{1}{g_m} + R_E}$$
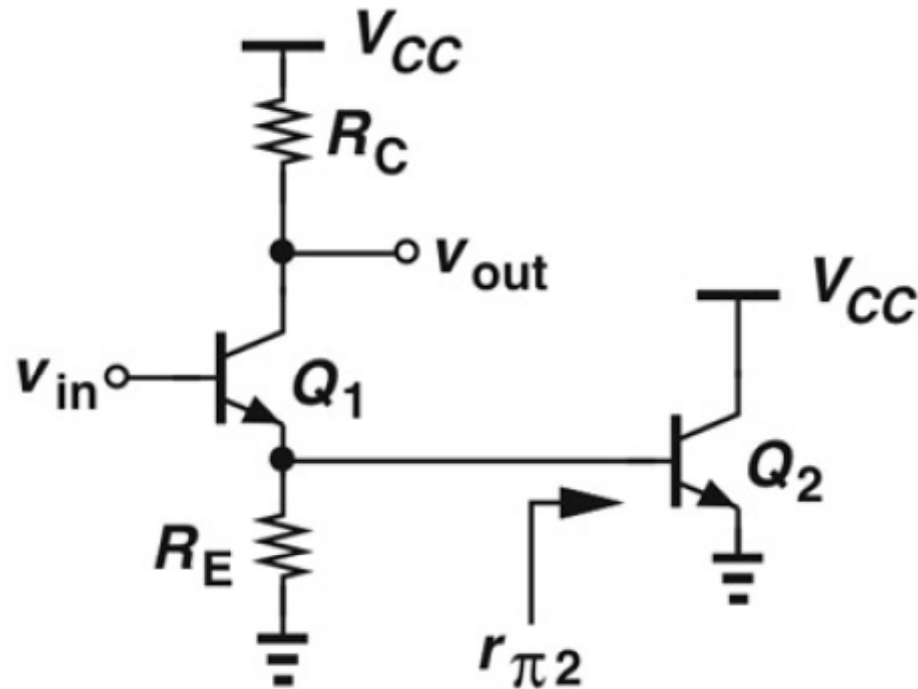
# Lect. 14: BJT CE Amplifier with Emitter Resistance



Voltage Gain = ?


From CE with ER

$$A_v \sim -\frac{R_C}{\frac{1}{g_m} + R_E}$$

$$A_v \sim -\frac{R_C}{\frac{1}{g_m} + R_E \parallel r_{\pi 2}}$$

# Lect. 14: BJT CE Amplifier with Emitter Resistance


Common-Emitter with emitter resistance

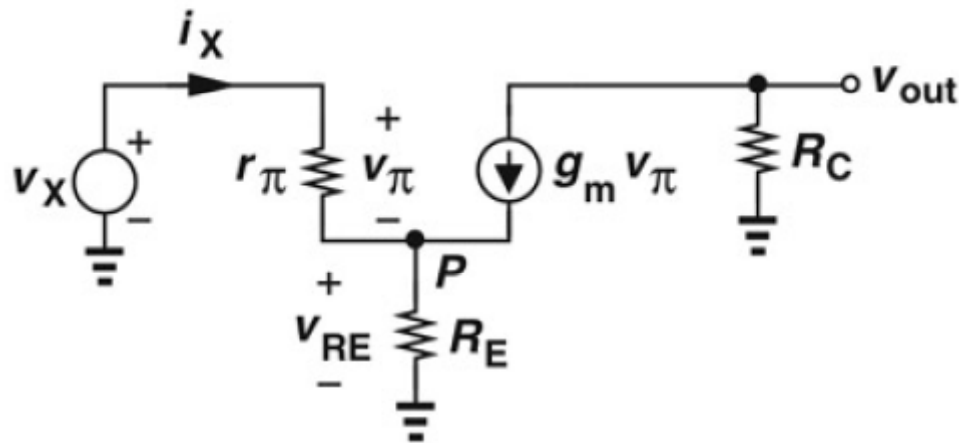

$R_{in} = ?$


$$v_X = r_\pi i_X + R_E (1 + \beta) i_X$$
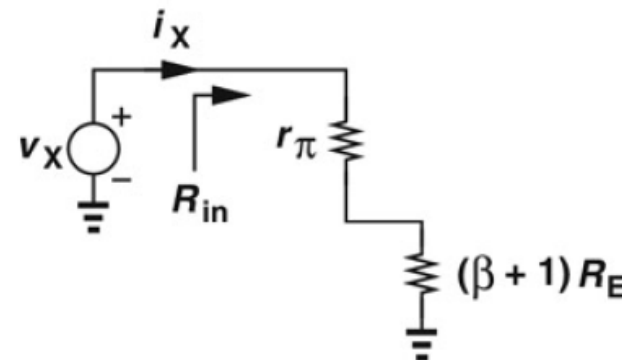
$$R_{in} = \frac{v_X}{i_X} = r_\pi + (\beta + 1) R_E$$



# Lect. 14: BJT CE Amplifier with Emitter Resistance

Common-Emitter with emitter resistance

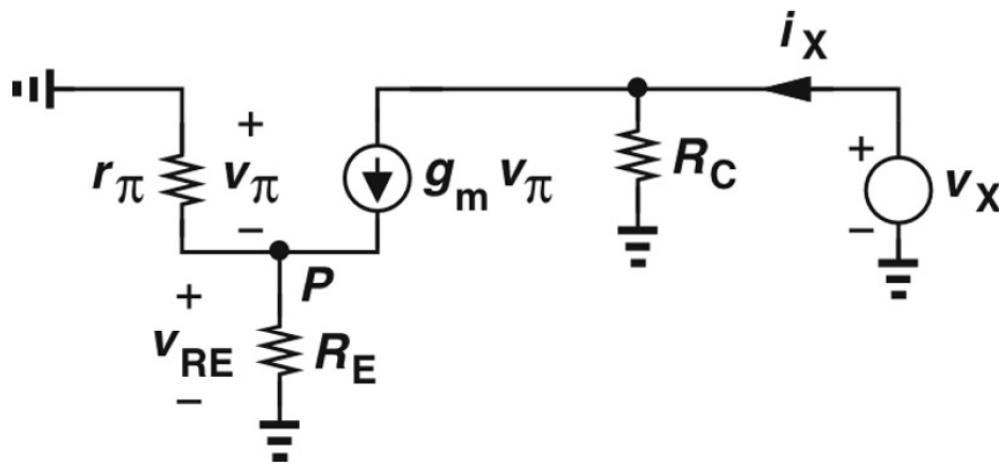

$$v_{\pi} + \left( \frac{v_{\pi}}{r_{\pi}} + g_m v_{\pi} \right) R_E = 0$$

$$v_{\pi} = 0$$

$$R_{out} = R_C$$

$$R_{out} = ?$$