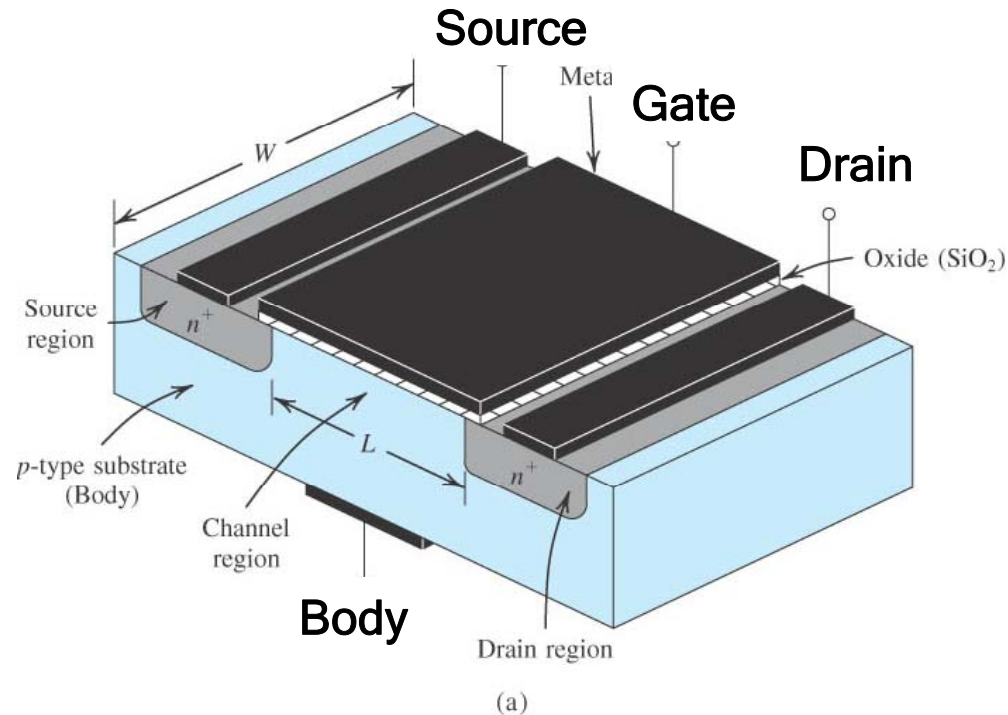


# Lect. 19: MOSFET

(Razavi 6.2,6.3)


MOSFET: Metal Oxide Semiconductor Field Effect Transistor



Control current flow between S and D with voltage applied at G  
NMOS, PMOS

# Lect. 19: MOSFET

## NMOS: n-channel MOSFET


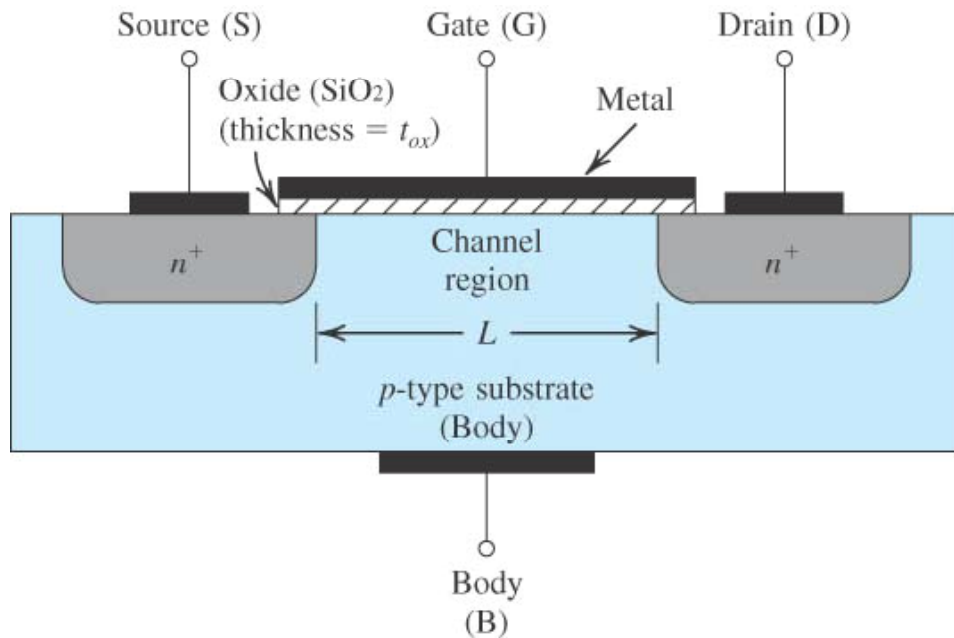


Can currents flow between S and D?

→ Need carriers (electrons)

→ Apply gate voltage ( $v_{GS} > V_T > 0$ )  
( $V_T$ : Threshold voltage)

# Lect. 19: MOSFET

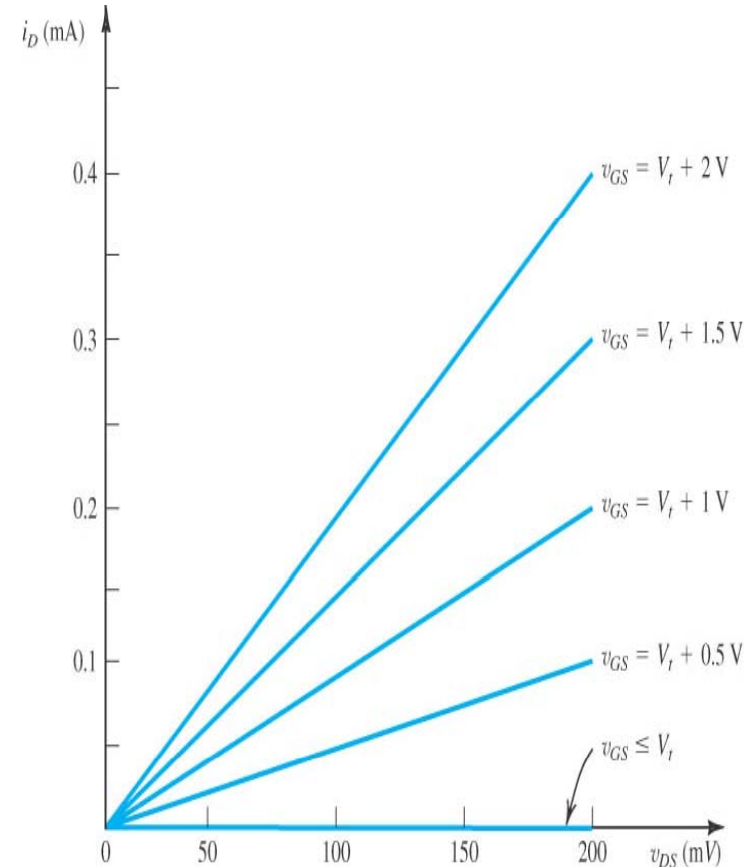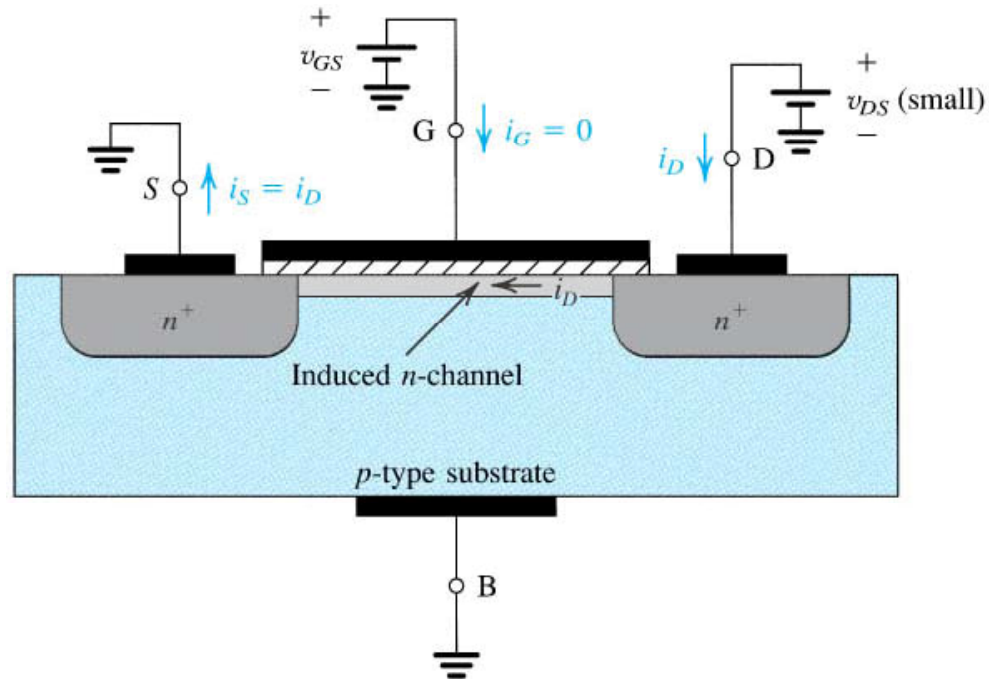


With  $v_{GS} > v_T$  (threshold voltage), channel is formed.

(Gate and p-substrate is acting as a capacitor)

More carriers with higher  $v_{GS}$

How does  $i_D$  change with  $v_{DS}$ ?

# Lect. 19: MOSFET

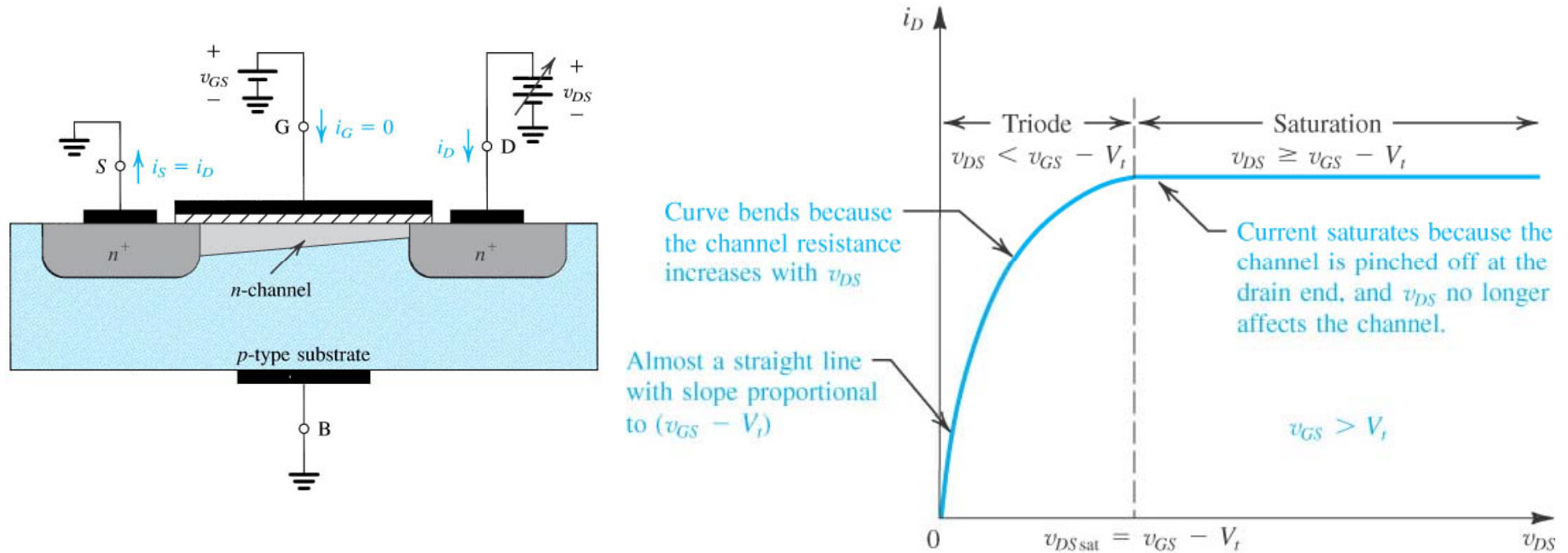

- With  $v_{DS}$  increase,  $i_D$  begins to saturate



→ Less carriers in Drain side ( $v_{GD} = v_{GS} + v_{SD} = v_{GS} - v_{DS}$ )

When  $v_{DS} = v_{GS} - v_T$ , ( $v_{GD} = v_T$ ), channel is pinched off

→ No further increase in  $i_D$


# Lect. 19: MOSFET

## MOSFET (NMOS) I-V Characteristics

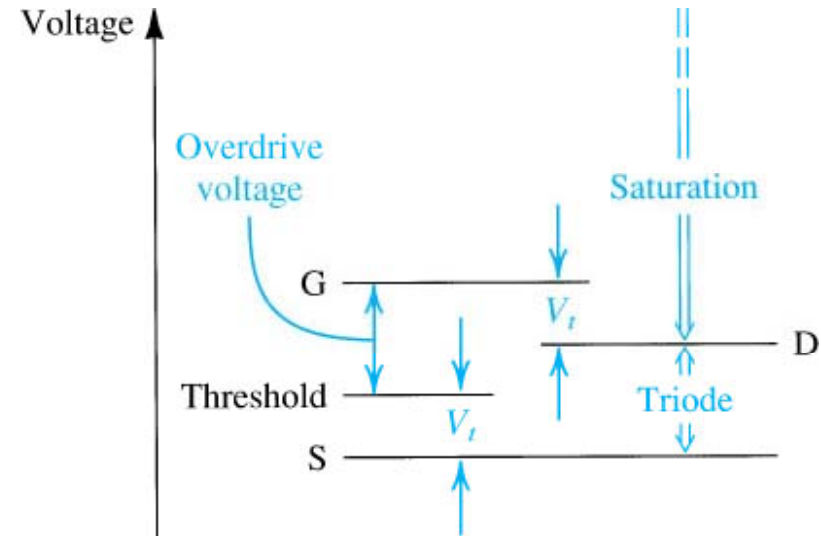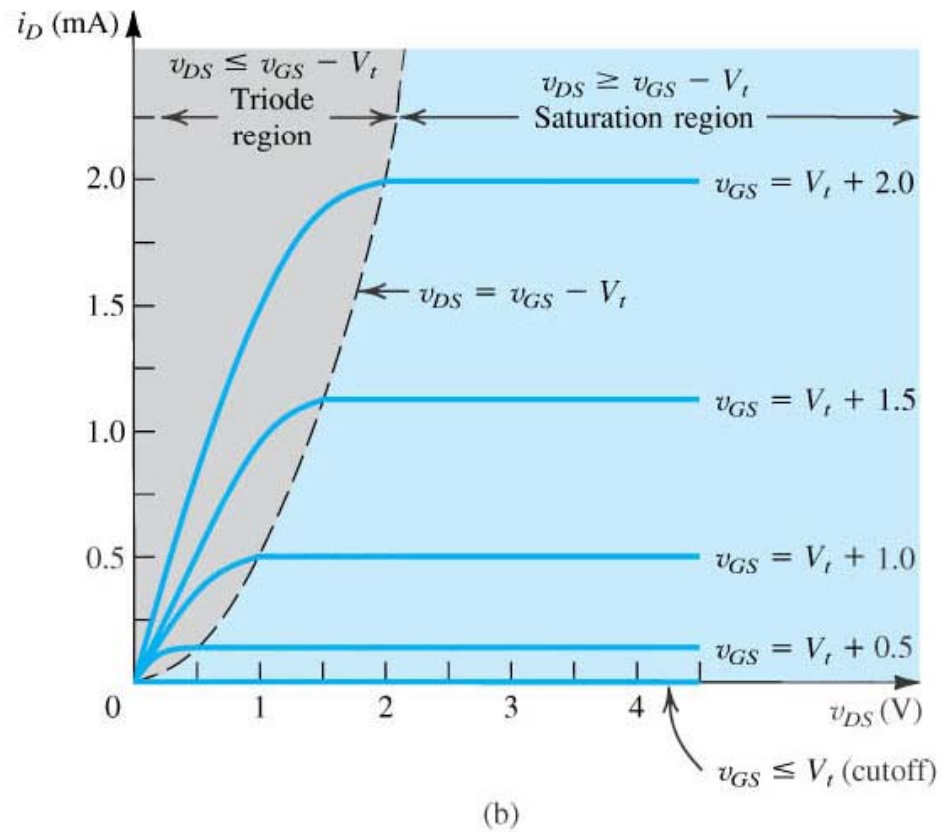


# Lect. 19: MOSFET


## NMOS: n-channel MOSFET

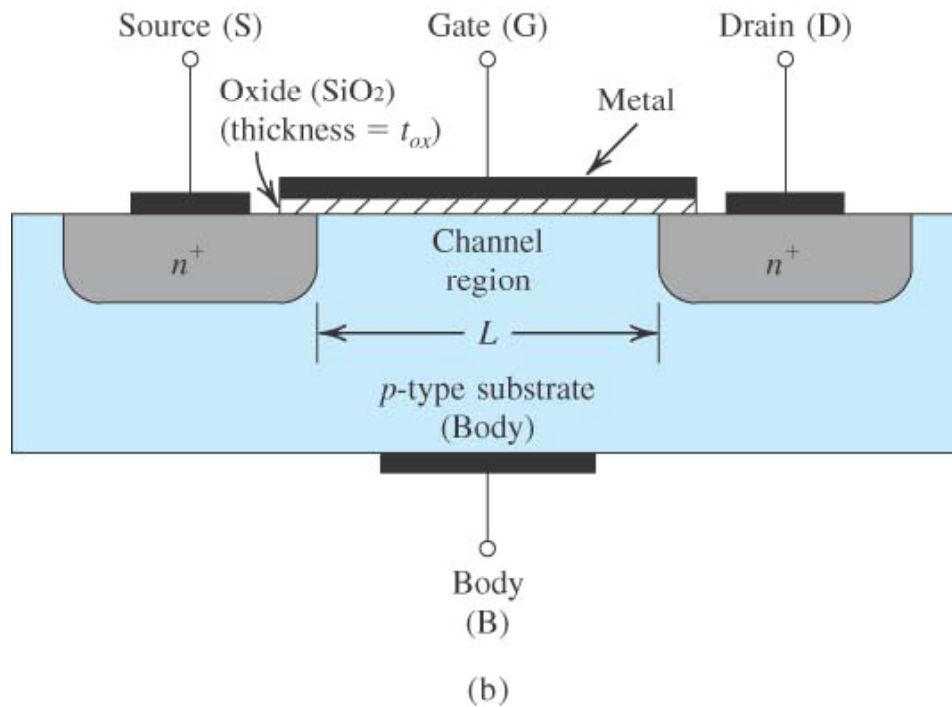

## Circuit Symbols

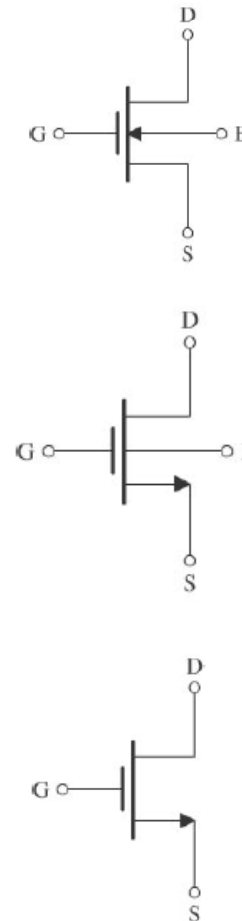

# Lect. 19: MOSFET

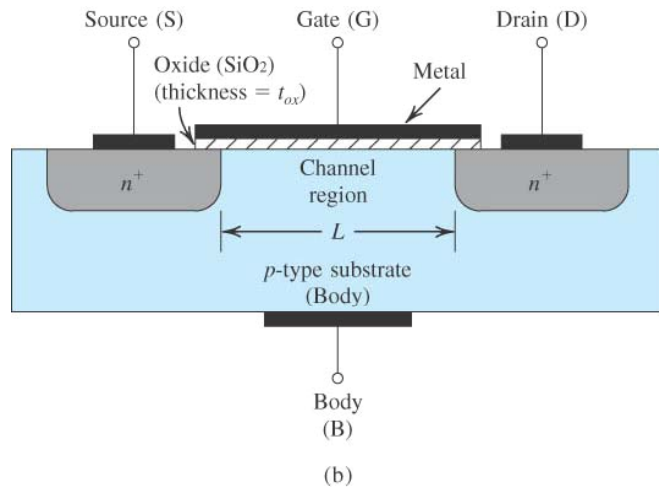


With more detailed analyses (but still approximate),

$$\text{In triode, } i_D = \mu_n C_{ox} \frac{W}{L} \left[ (v_{GS} - V_t) \cdot v_{DS} - \frac{1}{2} v_{DS}^2 \right]$$

$$(v_{GS} > V_t \text{ and } v_{DS} \leq v_{GS} - v_T)$$

$$\text{In saturation, } i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{GS} - V_t)^2$$
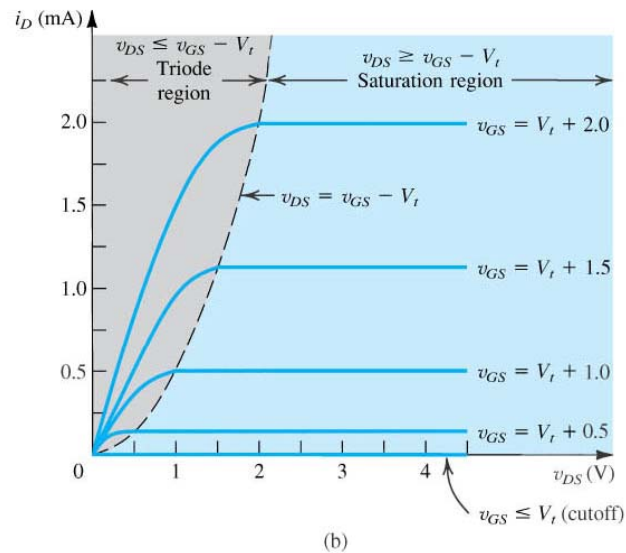
$$(v_{GS} > V_t \text{ and } v_{DS} \geq v_{GS} - v_T)$$



$\mu_n$  : electron mobility

$C_{ox}$  : oxide capacitance


$V_t$  : threshold voltage

$$k' = \mu_n C_{ox}$$
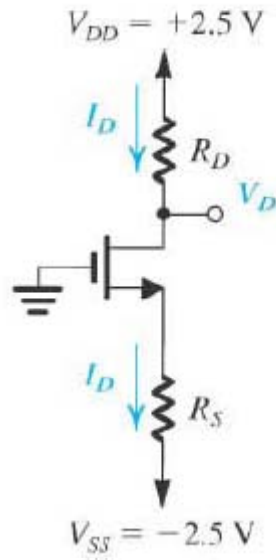
# Lect. 19: MOSFET

Determine  $R_D$  and  $R_S$  so that  $I_D=0.4 \text{ mA}$  and  $V_D=0.5\text{V}$ .

$V_t= 0.7\text{V}$ ,  $\mu_n C_{ox} (k') = 100 \mu\text{A/V}^2$ ,  $L= 1\mu\text{m}$ ,  $W= 32\mu\text{m}$



1. What region is the MOSFET in?
2. What is  $V_S$ ?
3.  $R_D$  and  $R_S$ ?




# Lect. 19: MOSFET

---
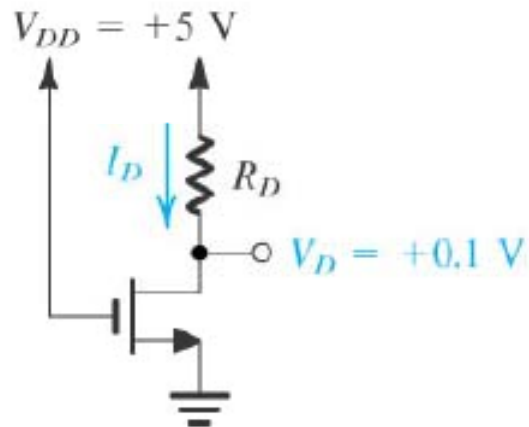
## Example 4.4

Determine  $R_D$  so that  $V_D = 0.1\text{V}$ .

$$V_t = 1\text{V}, \mu_n C_{ox} W/L = 1\text{mA/V}^2$$



1. What region is the MOSFET in?
2. What is  $I_D$ ?
3. What is  $R_D$ ?