
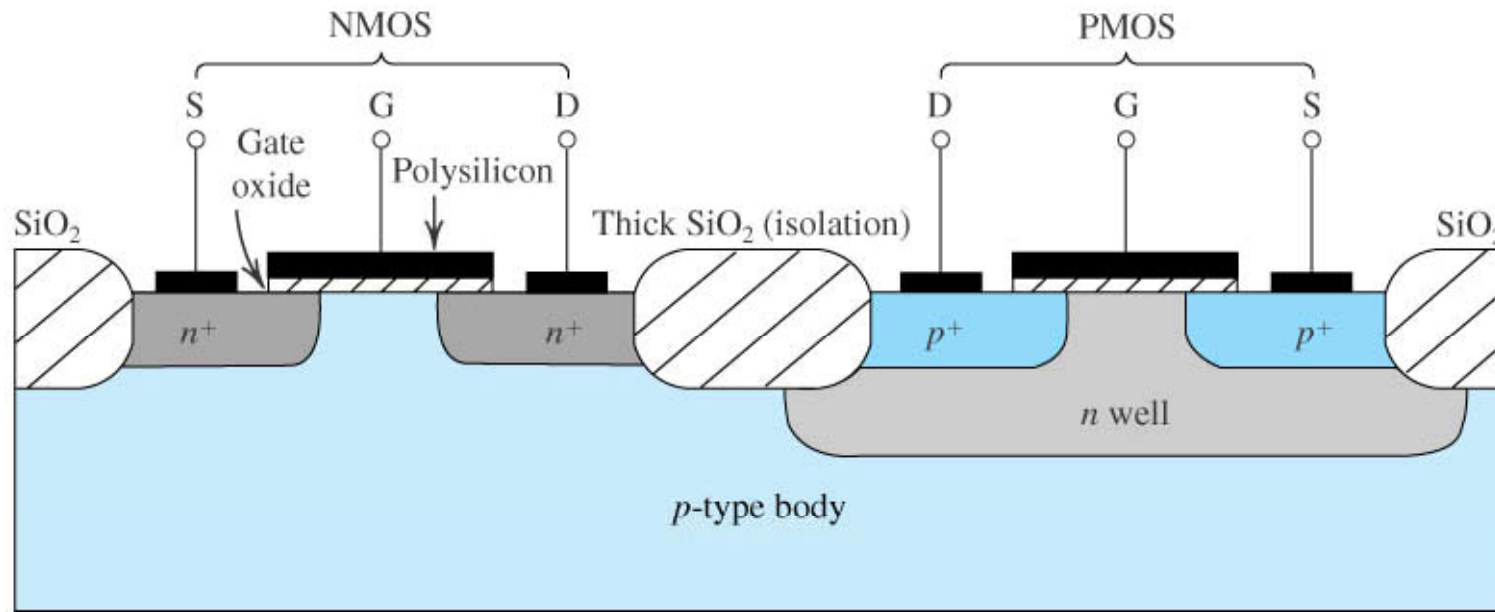


Lect. 20: PMOS


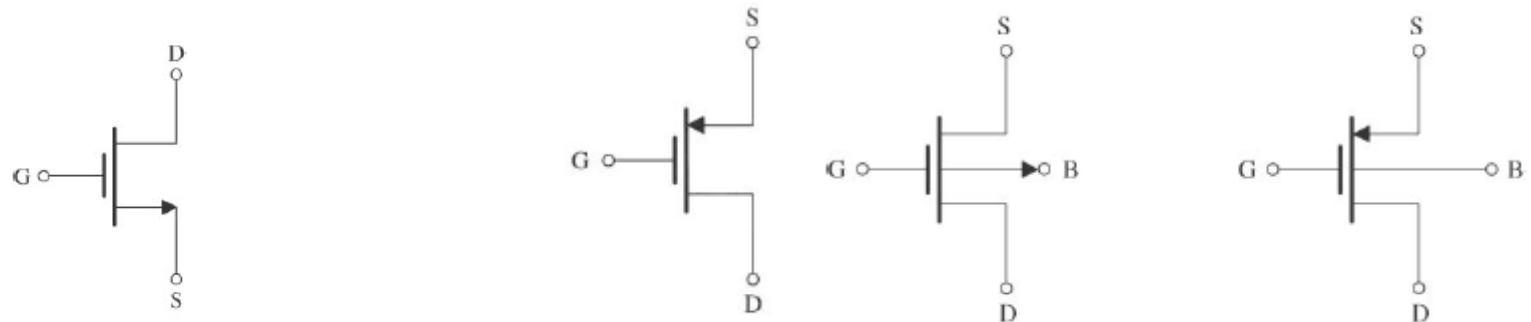


NMOS: electrons flow from Source to Drain

PMOS: holes flow from Source to Drain





Lect. 20: PMOS

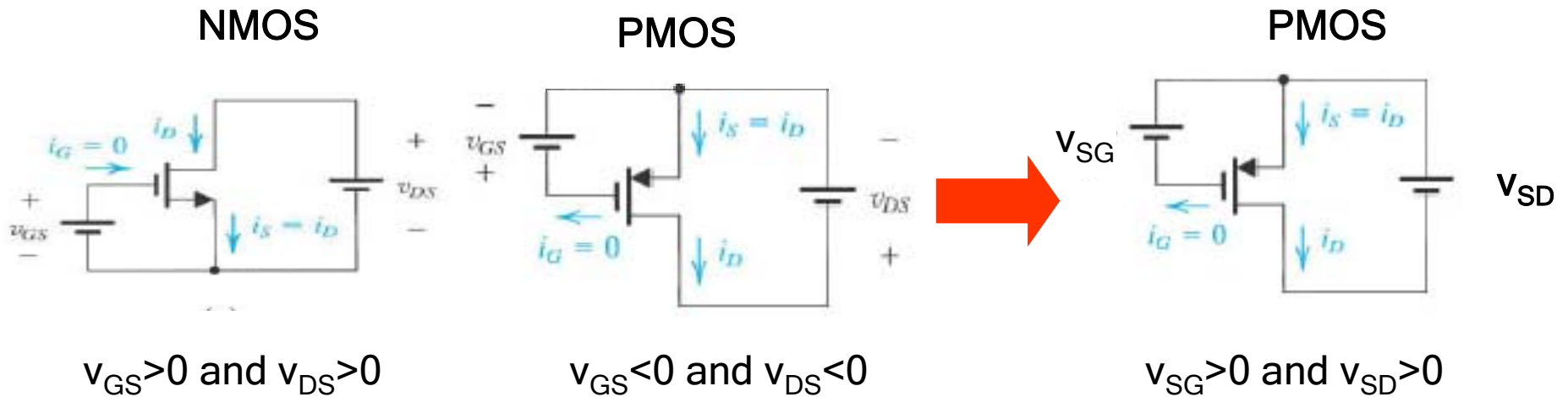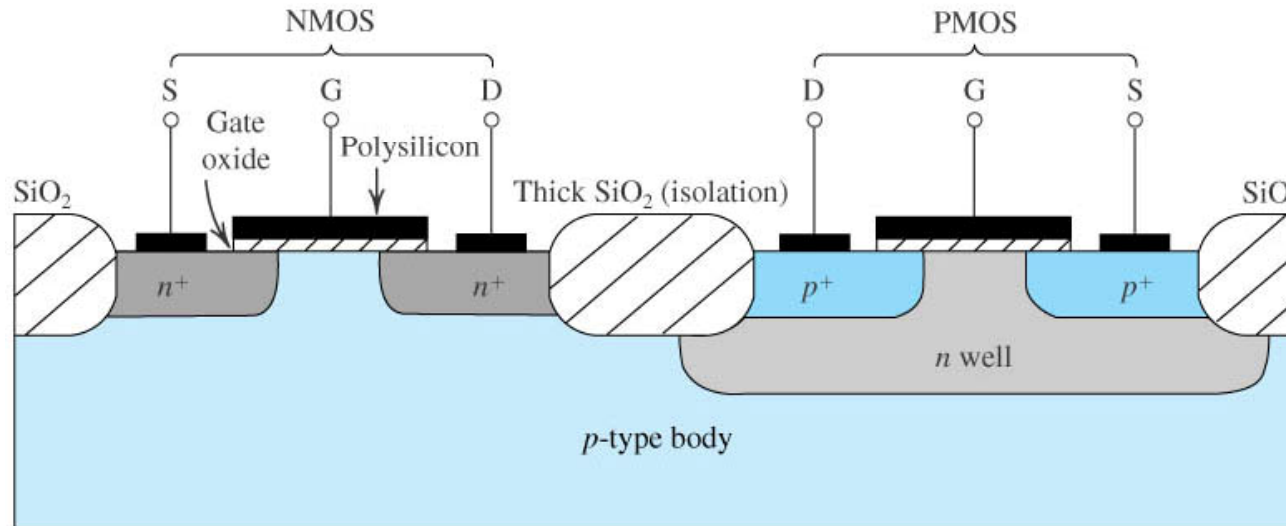

Lect. 20: PMOS

PMOS

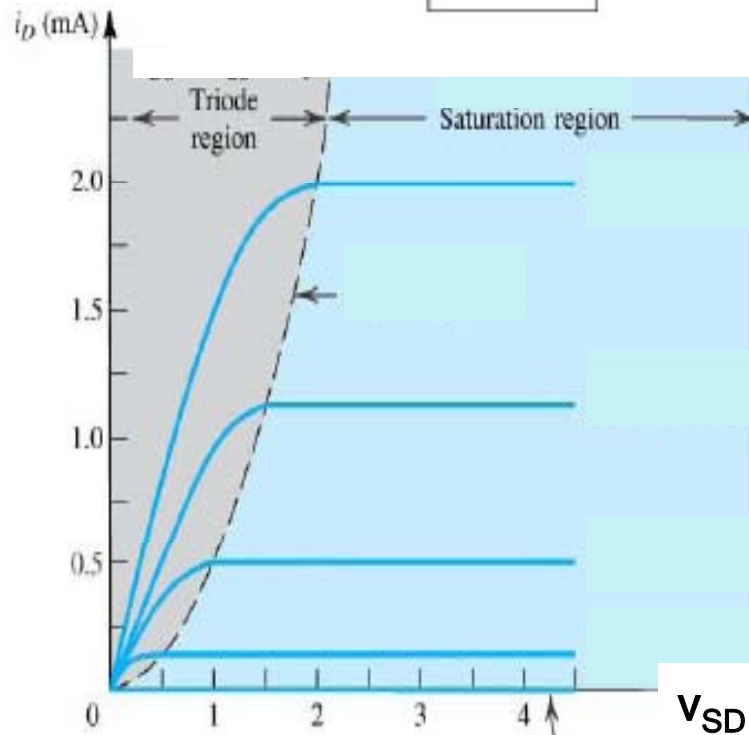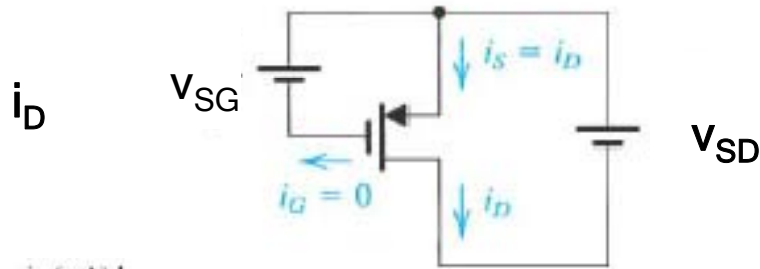

$$v_{SG} < |V_t| : i_D = 0$$

$$v_{SG} > |V_t| \text{ and } v_{SD} < v_{SG} - |V_t| \text{ (triode):}$$


$$i_D = \mu_p C_{ox} \frac{W}{L} \left[(v_{SG} - |V_t|) \cdot v_{SD} - \frac{1}{2} v_{SD}^2 \right]$$

$$v_{SG} > |V_t| \text{ and } v_{SD} > v_{SG} - |V_t| \text{ (saturation):}$$

$$i_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (v_{SG} - |V_t|)^2$$

Lect. 20: PMOS

NMOS

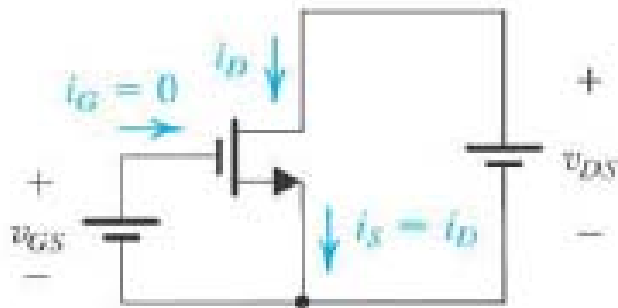

$$v_{GS} < V_t : i_D = 0$$


$$v_{GS} > V_t \text{ and } v_{DS} < v_{GS} - V_t \text{ (triode) :}$$

$$i_D = \mu_n C_{ox} \frac{W}{L} \left[(v_{GS} - V_t) \cdot v_{DS} - \frac{1}{2} v_{DS}^2 \right]$$

$$v_{GS} > V_t \text{ and } v_{DS} > v_{GS} - V_t \text{ (saturation):}$$

$$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{GS} - V_t)^2$$

PMOS

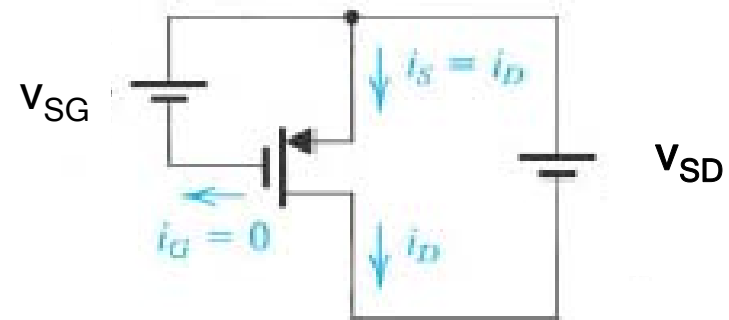

$$v_{SG} < |V_t| : i_D = 0$$

$$v_{SG} > |V_t| \text{ and } v_{SD} < v_{SG} - |V_t| \text{ (triode) :}$$


$$i_D = \mu_p C_{ox} \frac{W}{L} \left[(v_{SG} - |V_t|) \cdot v_{SD} - \frac{1}{2} v_{SD}^2 \right]$$

$$v_{SG} > |V_t| \text{ and } v_{SD} > v_{SG} - |V_t| \text{ (saturation):}$$

$$i_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (v_{SG} - |V_t|)^2$$

Lect. 20: PMOS

Example 4.6

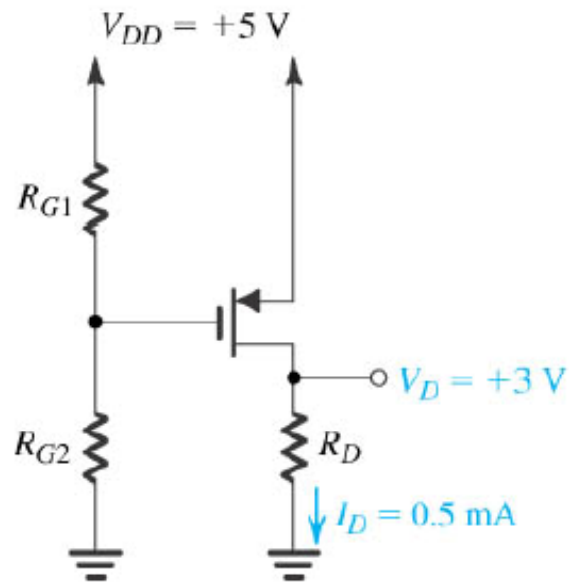

Design the circuit so that PMOS is in saturation and $I_D = 0.5 mA$, $v_D = 3V$. What is the max. R_D possible?

$$V_T = -1V, k'(W/L) = 1 mA/V^2$$

1. What is v_G ?
2. What is R_{G2}/R_{G1} ?
3. What is R_D ?
4. What happens when R_D increases?

Lect. 20: PMOS

Determine i_{Dn} , i_{Dp} , v_O for $v_I = 0, 2.5, -2.5V$.

$v_{Tn}=1V$, $v_{Tp}= -1V$, both transistors have $k'(W/L)=1mA/V^2$.

With $v_I=0V$,


- Top and bottom symmetric
- $v_O=0V$
- Both transistors in saturation
- $i_{Dn}, i_{Dp}=1.125mA$

With $v_I=2.5V$,

- Q_P is off and Q_N is in triode
- $i_{Dp}=0$, $i_{Dn}= 0.244mA$

With $v_I=-2.5V$,

- Q_N is off and Q_P is in triode
- $i_{Dn}=0$, $i_{Dp}=0.244mA$

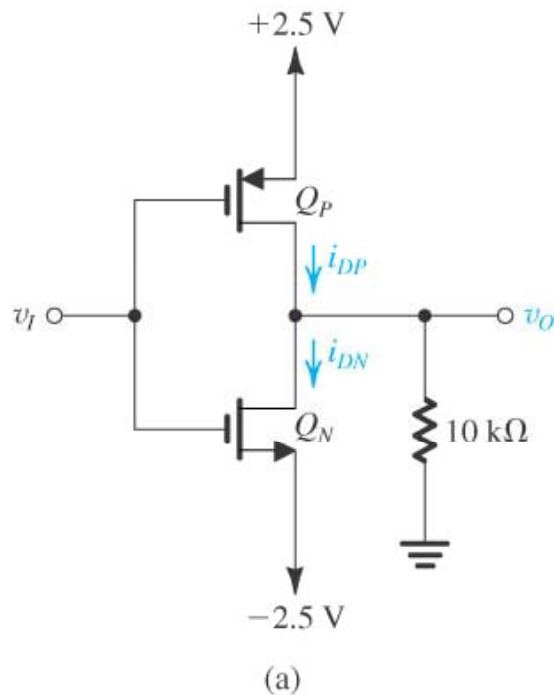

Lect. 20: PMOS

Homeworks:

For the following MOS circuits, determine $V_1 \dots V_7$. Use $|V_t| = 2\text{V}$, $k' W/L = 1\text{mA/V}^2$.

