
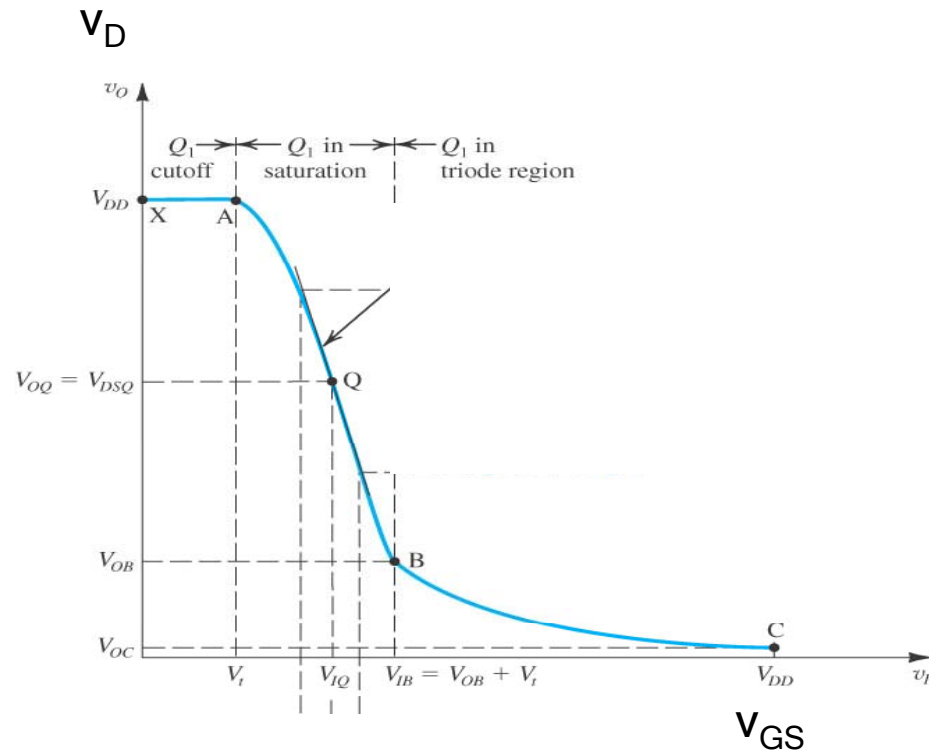


# Lect. 21: MOSFET Small-signal Model

(Razavi 6.3.1) =

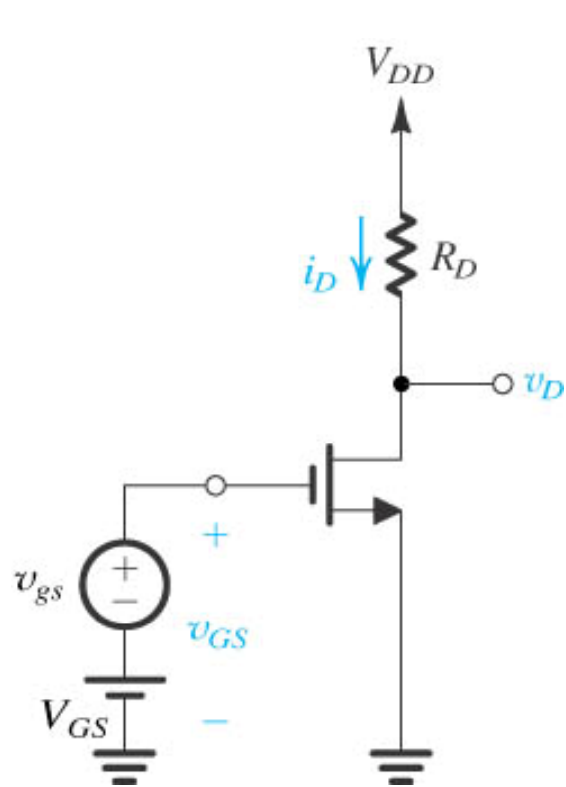


(c)
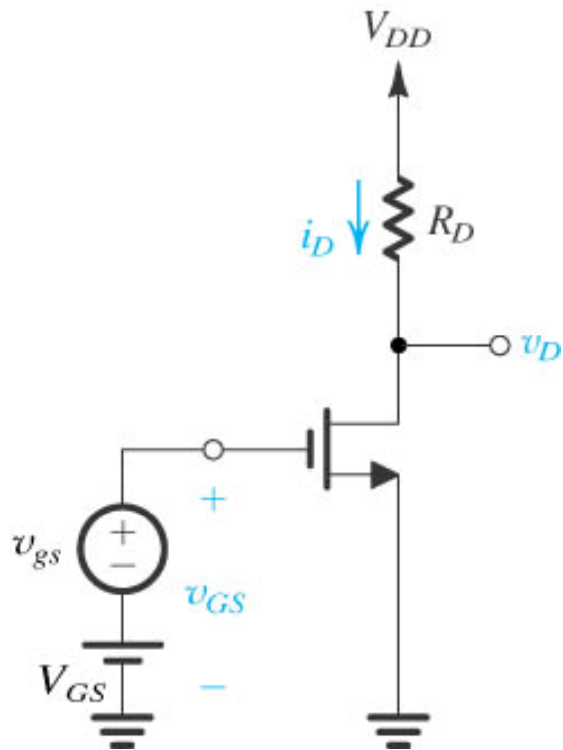
# Lect. 21: MOSFET Small-signal Model

(Razavi 6.3.1) =

Decompose all signals into Large Signals and Small Signals



$$V_{GS} = V_{GS} + v_{gs}$$


$$i_D = I_D + i_d$$

$$V_D = V_D + v_d$$

Large signals provide biases.

Small signals are amplified.  
( $v_d = A_v v_{gs}$ ).

What is  $A_v = v_d / v_{gs}$ ?

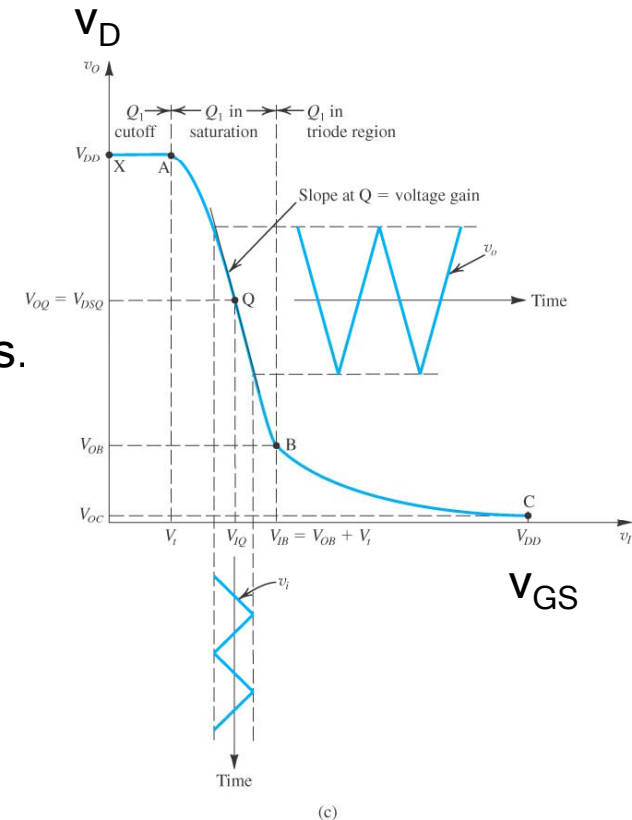

# Lect. 21: MOSFET Small-signal Model

Small signal model for NMOS in saturation

$$v_{GS} = V_{GS} + v_{gs}, \quad v_{DS} = V_{DS} + v_{ds}$$


$$i_G = I_G + i_g, \quad i_D = I_D + i_d$$

→  $i_g, i_d$  as functions of  $v_{gs}, v_{ds}$


$$i_g = 0$$

$$\text{From } i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{GS} - V_T)^2 \text{ with } v_{GS} = V_{GS} + v_{gs}$$

$$\begin{aligned} i_d - \left. \frac{di_D}{dv_{GS}} \right|_{V_{GS}} \cdot v_{gs} &= \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T) \cdot v_{gs} \\ &= g_m \cdot v_{gs} \end{aligned}$$

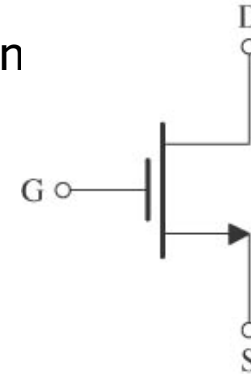


(c)

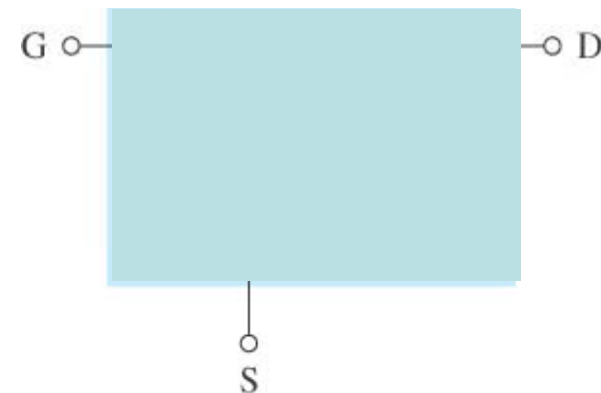

(a)

# Lect. 21: MOSFET Small-signal Model

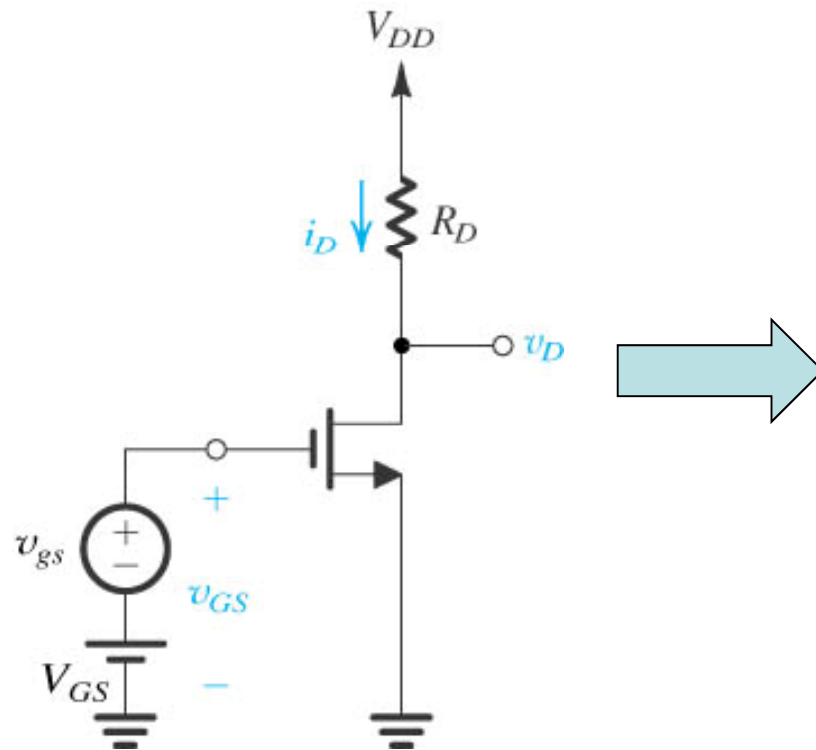


Small signal circuit

$$v_d = -g_m v_{gs} R_D$$


# Lect. 21: MOSFET Small-signal Model

Various expressions for  $g_m$

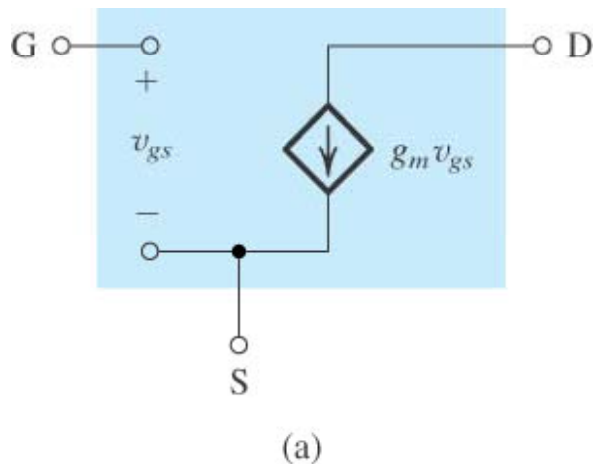

$$\begin{aligned} \text{From } i_D &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{GS} - V_T)^2 \\ g_m &= \left. \frac{di_D}{dv_{GS}} \right|_{V_{GS}} = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T) \\ &= \frac{2I_D}{V_{GS} - V_T} \\ &= \sqrt{2\mu_n C_{ox} \cdot \frac{W}{L} \cdot I_D} \end{aligned}$$

# Lect. 21: MOSFET Small-signal Model

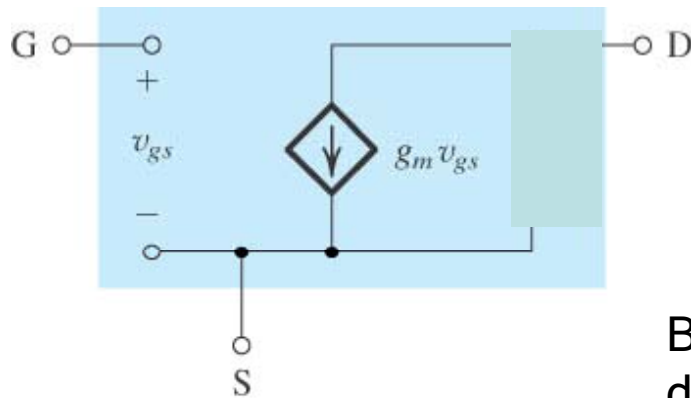

(b)

→ No change in  $i_d$  with  $v_{ds}$

$$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{GS} - V_T)^2$$

But in real MOSFET devices  $i_D$  increases due to channel length modulation

$$i_D = \frac{1}{2} k' \frac{W}{L} (1 + \lambda \cdot v_{DS}) (v_{GS} - V_t)^2$$

$$\Delta i_D = \frac{\partial i_D}{\partial v_{GS}} \cdot \Delta v_{GS} + \frac{\partial i_D}{\partial v_{DS}} \cdot \Delta v_{DS} \quad \frac{\partial i_D}{\partial v_{GS}} = k' \frac{W}{L} (1 + \lambda \cdot v_{DS}) (v_{GS} - V_t) = \frac{2i_D}{v_{GS} - V_t} = g_m$$


$$\frac{\partial i_D}{\partial v_{DS}} = \frac{1}{2} k' \frac{W}{L} \lambda (v_{GS} - V_t)^2 = \frac{1}{r_0}$$

$$i_d = g_m \cdot v_{gs} + \frac{v_{ds}}{r_0}$$
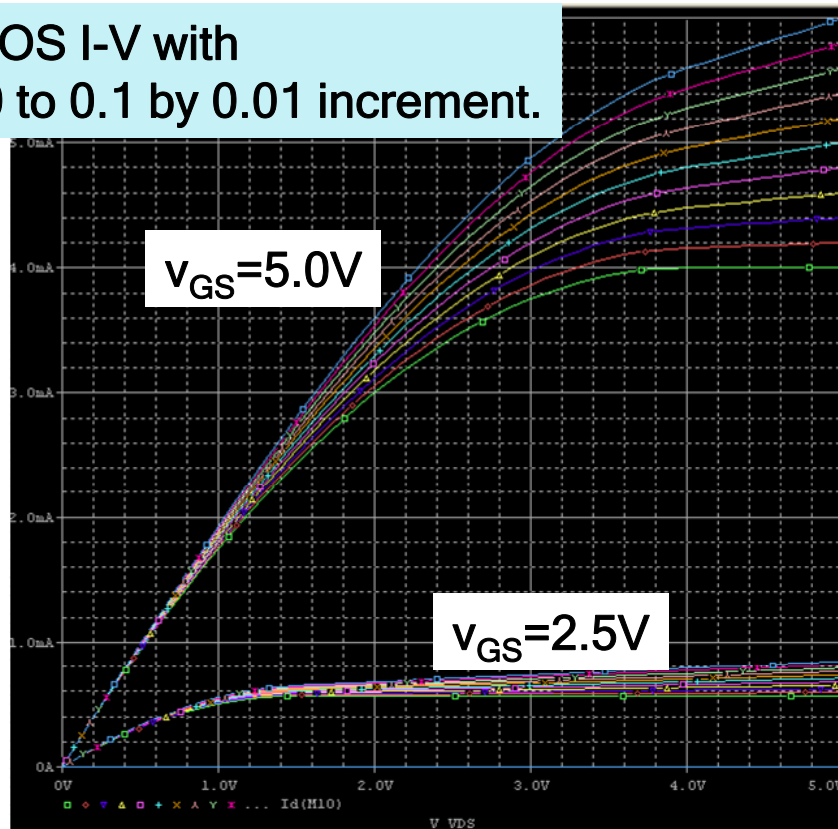
# Lect. 21: MOSFET Small-signal Model


Small signal model for NMOS with channel-length modulation

NMOS I-V with  
 $\lambda=0$  to  $0.1$  by  $0.01$  increment.



$$i_D = \frac{1}{2} k' \frac{W}{L} (1 + \lambda \cdot v_{DS}) (v_{GS} - V_t)^2$$

# Lect. 21: MOSFET Small-signal Model

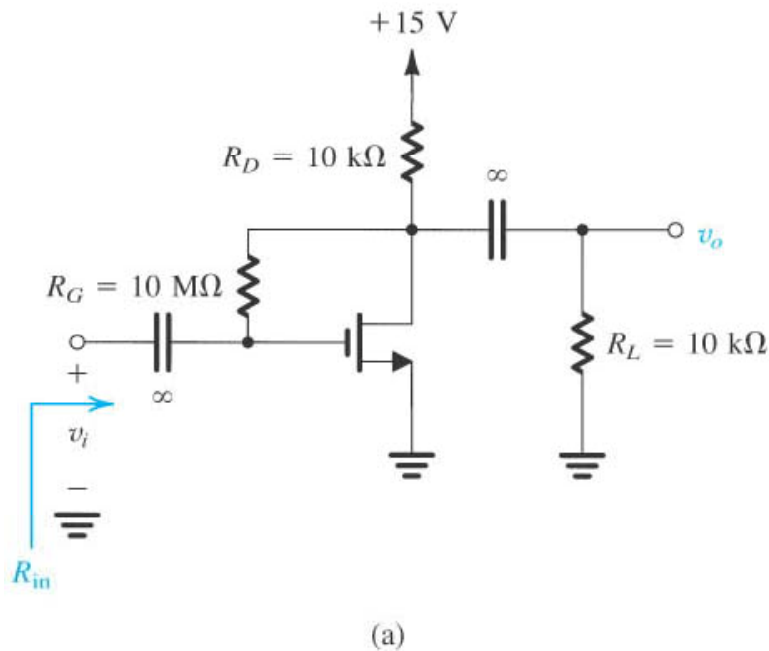

## Ex. 4.10


$V_t = 1.5\text{V}$ ,  $k' (W/L) = 0.25\text{mA/V}^2$

1. Determine bias conditions.
2. Derive small signal circuit model.
3. Voltage gain?
4. Input resistance?
5. Max.  $v_i$ ?



# Lect. 21: MOSFET Small-signal Model

1. Determine bias conditions.

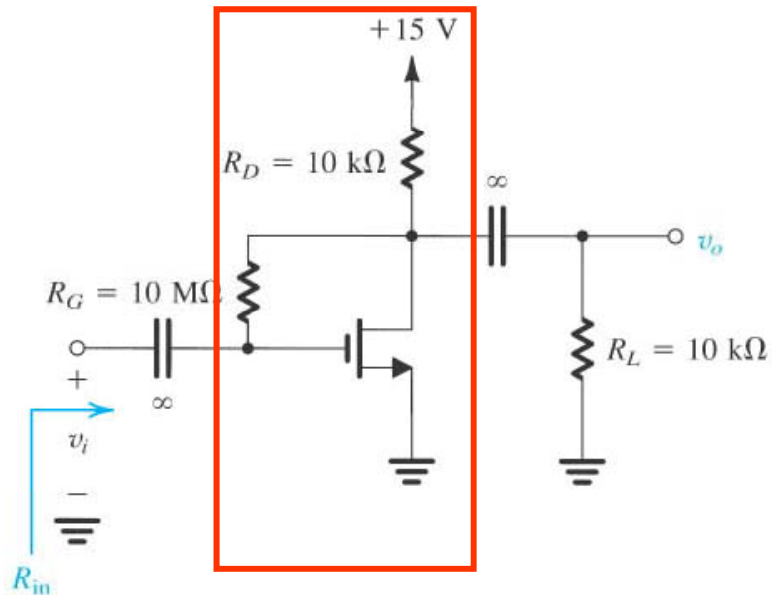

$$V_t = 1.5\text{V}, k' (W/L) = 0.25\text{mA/V}^2$$

$$I_D = 0.5 \times 0.25 (V_D - 1.5)^2$$

$$V_D = 15 - R_D I_D$$

$$I_D = 1.06\text{mA}, V_D = 4.4\text{V}$$


In saturation?

$$g_m = k' (W/L) (V_{GS} - V_t) = 0.725\text{mA/V}$$

# Lect. 21: MOSFET Small-signal Model

## Voltage Gain

### Small-Signal model

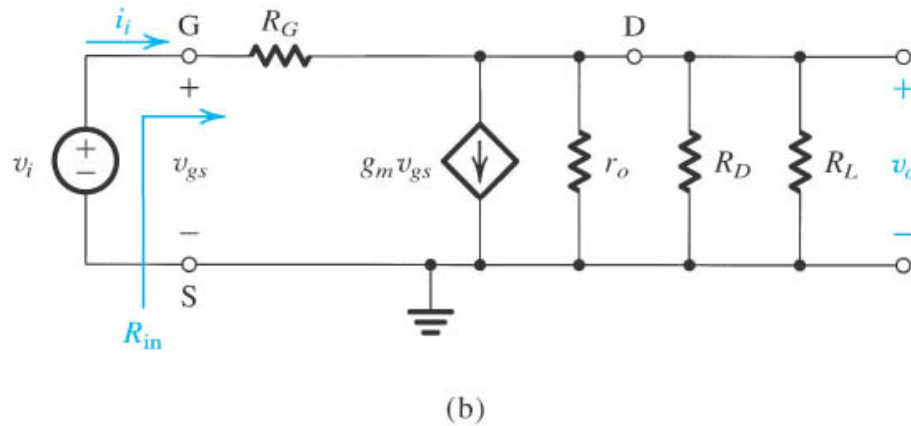

$$R_D = 10\text{k}\Omega, R_L = 10\text{k}\Omega, R_G = 10\text{M}\Omega, r_o = 47\text{k}\Omega$$


$$v_o = -g_m \cdot v_i \cdot (R_D \parallel R_L \parallel r_o)$$

$$A_v = \frac{v_o}{v_i} = -g_m \cdot (R_D \parallel R_L \parallel r_o) = -3.3$$

# Lect. 21: MOSFET Small-signal Model

$$R_D = 10\text{K}\Omega, R_L = 10\text{K}\Omega, R_G = 10\text{M}\Omega$$

Input Resistance

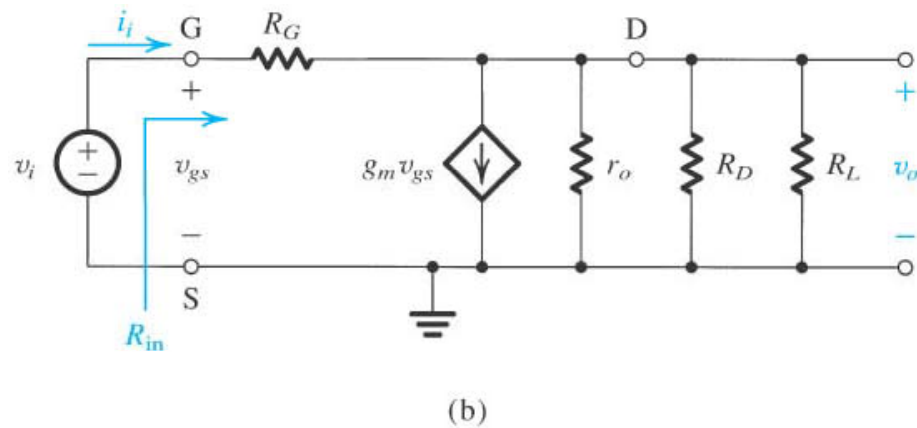


$$R_{in} = \frac{v_i}{i_i}$$

$$i_i = \frac{v_i - v_o}{R_G} = \frac{v_i}{R_G} \left(1 - \frac{v_o}{v_i}\right)$$

$$\therefore R_{in} = \frac{v_i}{i_i} = \frac{R_G}{1 - A_v} = 2.33 \text{ M}\Omega$$

# Lect. 21: MOSFET Small-signal Model

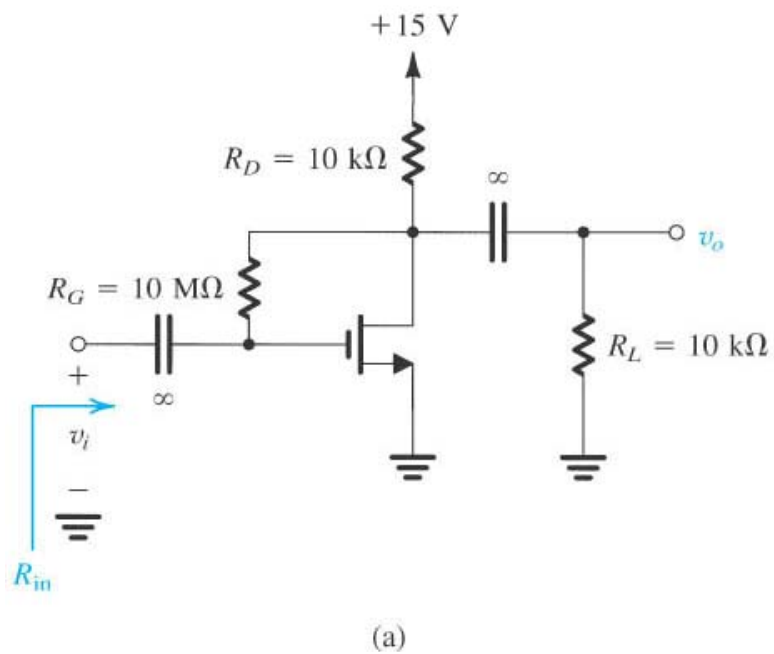

For Max.  $v_i$ ,  $v_{DS} > v_{GS} - V_t$  (saturation)

$$V_{DS} - |A_V| v_{i,\max} = V_{GS} + v_{i,\max} - V_t$$
$$v_{i,\max} = 0.34\text{V}$$

# Lect. 21: MOSFET Small-signal Model

---

Small signal model for PMOS ?

Identical to NMOS small signal model!

Homework: Due before Tutorial on 11/9

Determine small-signal resistance  $R_x$  and  $R_y$  in the following circuits.

Assuming  $M_1$  and  $M_2$  are in saturation.

Consider the channel length modulation but not body effect.

