
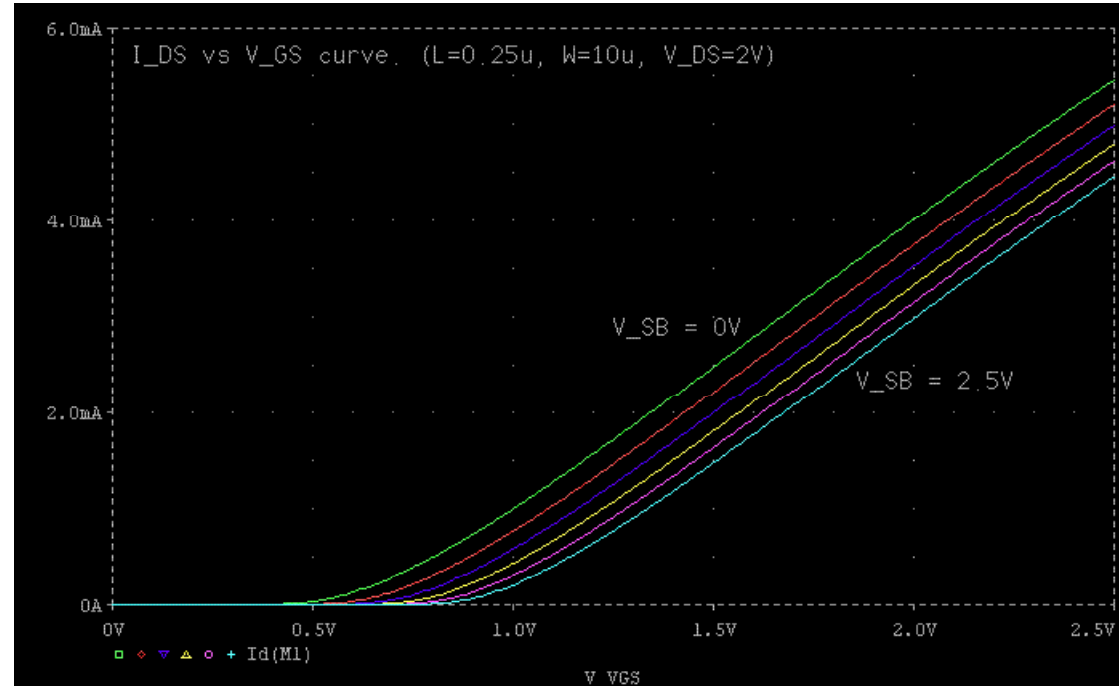

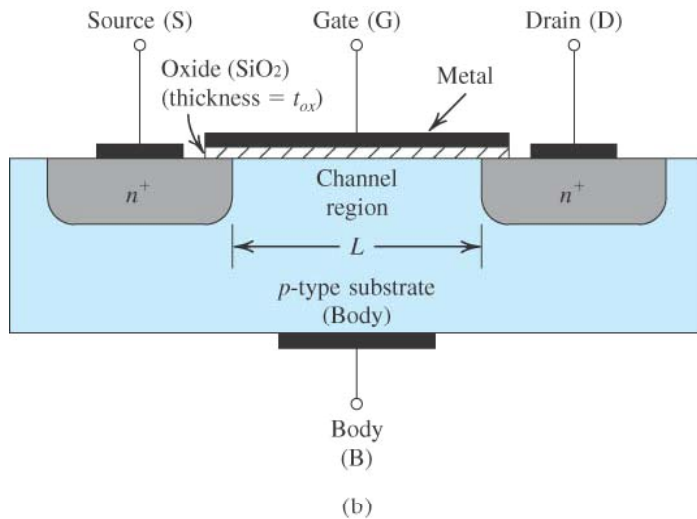
# Lect. 22: MOSFET Small-Signal Model (2)

Body effect: Voltage applied to B causes a change in threshold voltage





→  $V_t$  increases as  $V_{SB}$  increases

Decreased  $V_B$  requires higher  $V_G$  for threshold
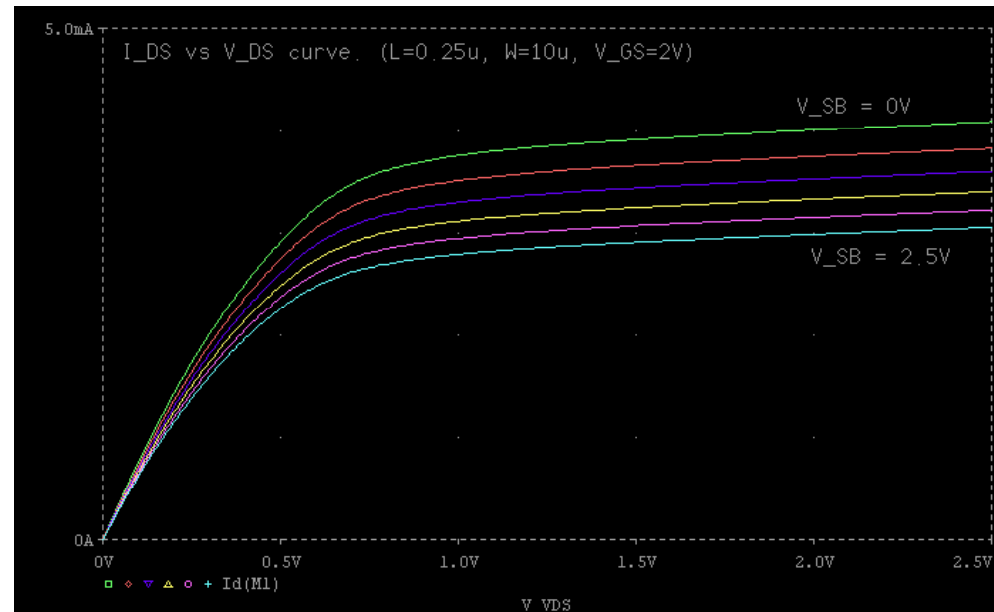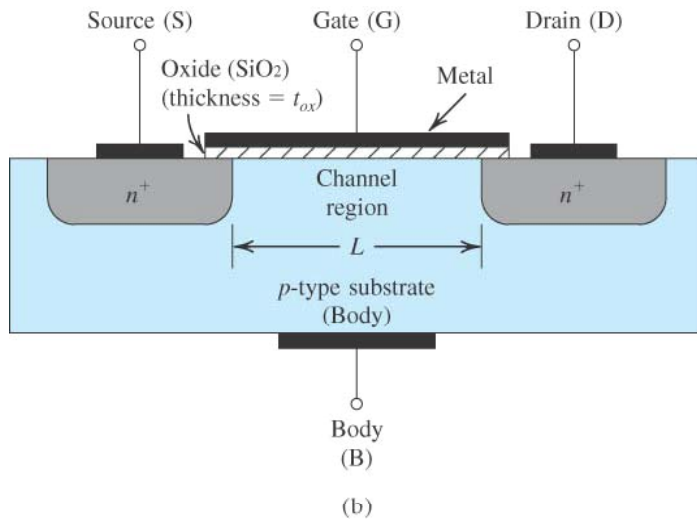
# Lect. 22: MOSFET Small-Signal Model (2)


Body effect: Voltage applied to B causes a change in threshold voltage



→ Smaller  $I_D$  with higher  $V_{SB}$

→ Larger  $I_D$  with higher  $V_{BS}$
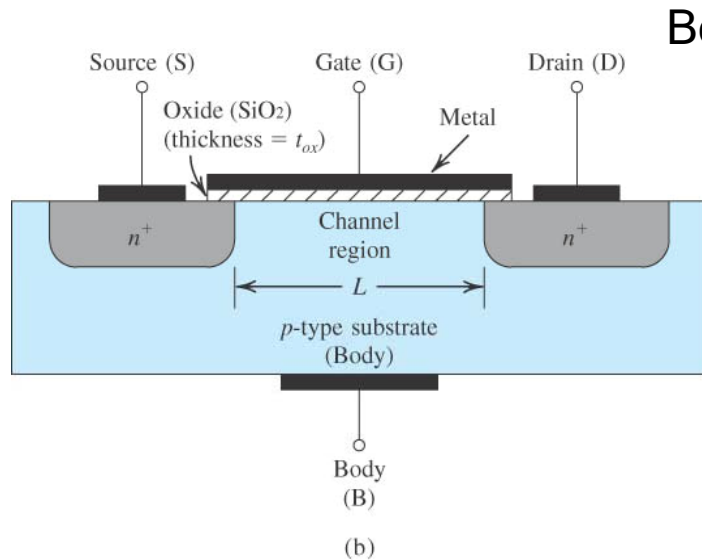
# Lect. 22: MOSFET Small-Signal Model (2)



Body effect:

$$V_t = V_{t0} + \gamma [\sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f}]$$

$$V_t = V_{t0} \text{ when } V_{SB} = 0$$

$\phi_f$  and  $\gamma$  process-dependent parameters



If S and B can be tied, no body effect.

In ICs, B is connected to

- the most negative supply voltage (NMOS)
- the most positive supply voltage (PMOS)

# Lect. 22: MOSFET Small-Signal Model (2)

Small-signal model including Body effect

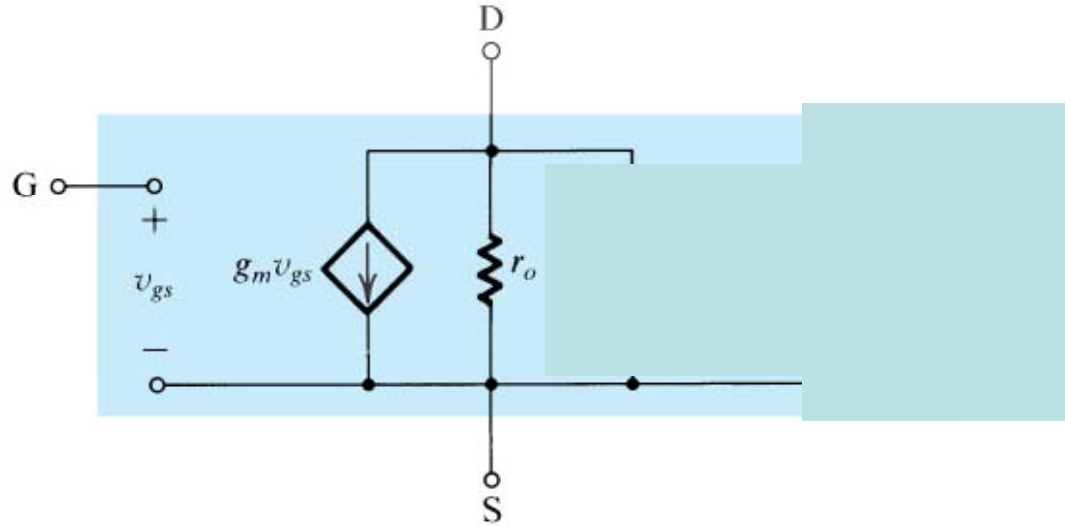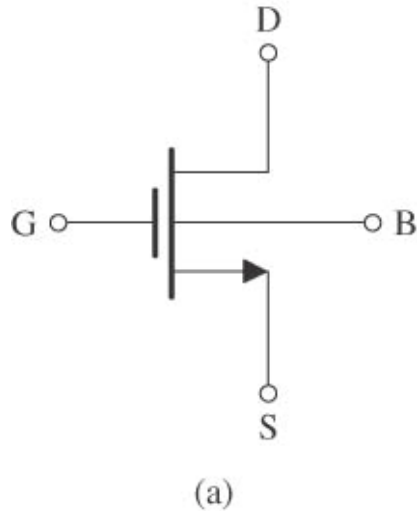

Practically, Body Effect  
Is not easy to model analytically.


→ Simulation

$$g_{mb} \equiv \left. \frac{\partial i_D}{\partial v_{BS}} \right|_{\substack{v_{GS} = \text{constant} \\ v_{DS} = \text{constant}}}$$

$$g_{mb} \equiv \chi g_m \quad (\chi : 0.1 - 0.3)$$

# Lect. 22: MOSFET Small-Signal Model (2)

## High-Frequency Model for MOSFET

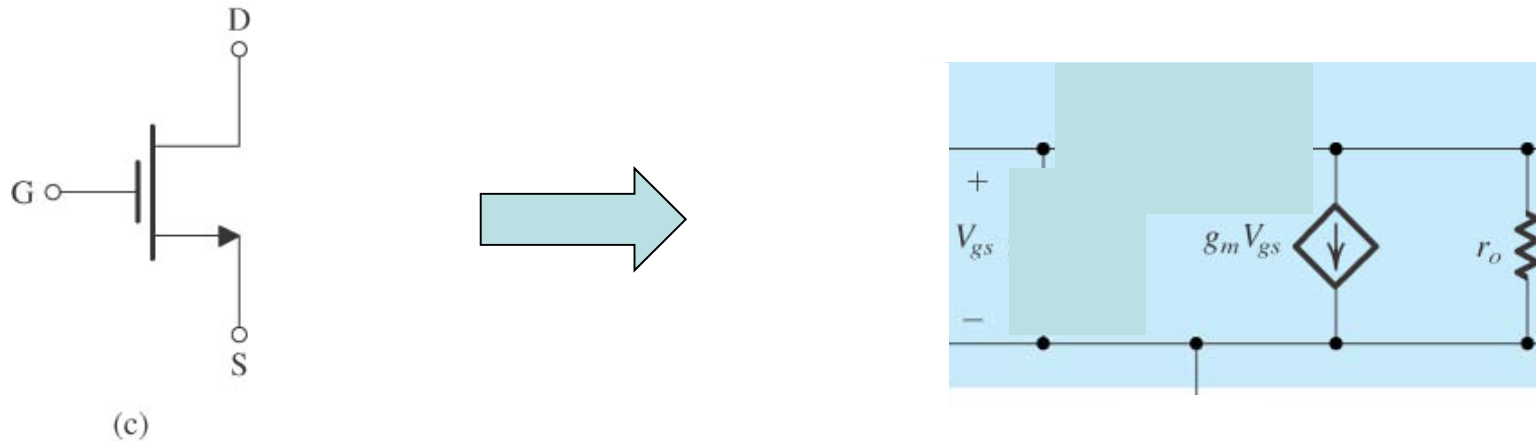


Unit-Gain Frequency ( $f_t$ ):

Frequency at which magnitude of the short-circuit current gain of CS configuration becomes 1

$$\text{Or } \text{Mag}(I_o(\omega)/I_i(\omega)) = 1$$
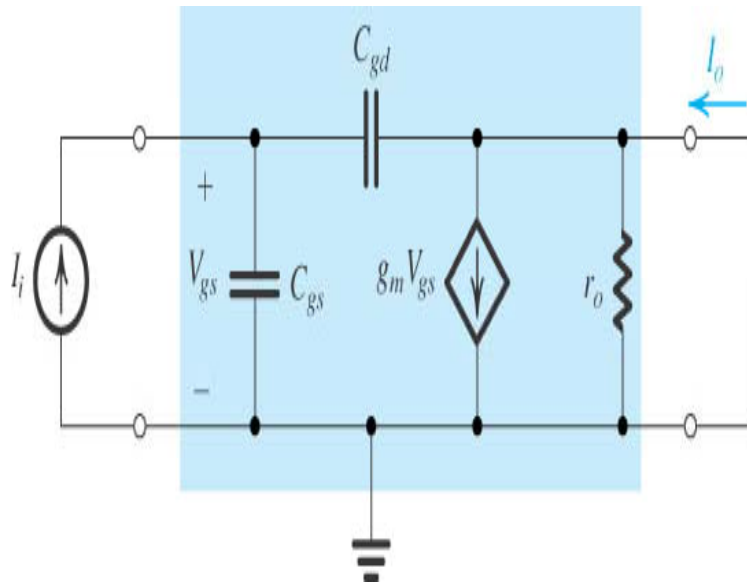
# Lect. 22: MOSFET Small-Signal Model (2)

How fast can a MOSFET transistor operate?  $f_t$



$$I_0 = g_m V_{gs} - \frac{V_{gs}}{1/j\omega C_{gd}} = g_m V_{gs} - j\omega C_{gd} V_{gs} = g_m V_{gs} \quad (\because g_m \gg \omega C_{gd})$$

$$V_{gs} = I_i \cdot \left( \frac{1}{j\omega C_{gd}} \parallel \frac{1}{j\omega C_{gs}} \right) = I_i \cdot \frac{1}{j\omega(C_{gd} + C_{gs})}$$

$$\therefore \frac{I_0}{I_i} = \frac{g_m}{j\omega(C_{gd} + C_{gs})}$$

$$\text{For } \left| \frac{I_0}{I_i} \right| = 1, \quad \omega = \frac{g_m}{C_{gd} + C_{gs}}$$

$$\text{Or } f_T = \frac{g_m}{2\pi(C_{gd} + C_{gs})} \quad (\text{Unit-gain Frequency})$$

How to make MOSFET faster?

Which is faster NMOS or PMOS?

Current state-of-the-art NMOS has  $f_T$  approaching 100 GHz.

# Lect. 22: MOSFET Small-Signal Model (2)

- Modern transistors are very complicated in their structure.
- Many parameters are needed to model their characteristics accurately in SPICE
- SPICE parameters for 0.25 $\mu$ m NMOS are shown
- For detailed explanations, See *MOSFET Users' Manual* at [www-device.eecs.berkeley.edu/~bsim3/get.html](http://www-device.eecs.berkeley.edu/~bsim3/get.html)

```
MODEL orbit2L2N NMOS ( LEVEL = 7
+TNOM = 27 TOX = 5.6E-9
+XJ = 1E-7 NCH = 2.3549E17 VTH0 = 0.3654765
+K1 = 0.4732214 K2 = 7.994532E-4 K3 = 1E-3
+K3B = 3.0713494 W0 = 1E-7 NLX = 1.617898E-7
+DVT0W = 0 DVT1W = 0 DVT2W = 0
+DVT0 = 0.455178 DVT1 = 0.6258687 DVT2 = -0.5
+U0 = 280.4589023 UA = -1.607126E-9 UB = 2.806549E-18
+UC = 3.290051E-11 VSAT = 1.07496E5 A0 = 1.8770435
+AGS = 0.3310181 B0 = -3.173524E-8 B1 = -1E-7
+KETA = -8.69841E-3 A1 = 8.317145E-5 A2 = 0.6592347
+RDSW = 200 PRWG = 0.4477477 PRWB = 0.0208175
+WR = 1 WINT = 0 LINT = 1.392558E-10
+DWG = -2.28419E-8
+DWB = -6.95781E-10 VOFF = -0.0910963 NFACTOR = 1.202941
+CIT = 0 CDSC = 2.4E-4 CDSCD = 0
+CDSCB = 0 ETA0 = 5.0732E-3 ETAB = 6.262008E-5
+DSUB = 0.0310034 PCLM = 1.5101091 PDIBLC1 = 0.897659
+PDIBLC2 = 2.924029E-3 PDIBLCB = 0.0651312 DROUT = 1
+PSCBE1 = 7.017738E8 PSCBE2 = 2.271109E-4 PVAG = 8.531511E-3
+DELTA = 0.01 RSH = 4.6 MOBMOD = 1
+PRT = 0 UTE = -1.5 KT1 = -0.11
+KT1L = 0 KT2 = 0.022 UA1 = 4.31E-9
+UB1 = -7.61E-18 UC1 = -5.6E-11 AT = 3.3E4
+WL = 0 WLN = 1 WW = 0
+WWN = 1 WWL = 0 LL = 0
+LLN = 1 LW = 0 LWN = 1
+LWL = 0 CAPMOD = 2 XPART = 0.5
+CGDO = 4.59E-10 CGSO = 4.59E-10 CGBO = 5E-10
+CJ = 1.78338E-3 PB = 0.99 MJ = 0.4661295
+CJSW = 4.154041E-10 PBSW = 0.9563049 MJSW = 0.3162462
+CF = 0 PVTH0 = -9.648921E-3 PRDSW = -10
+PK2 = 3.534961E-3 WKETA = 0.0120981 LKETA = -3.31688E-3 )
```

# Lect. 22: MOSFET Small-Signal Model (2)

---

How to do PSPICE simulation?

→ Instructions will be given during next tutorial (11/9)

Bring your own notebook computer if you can