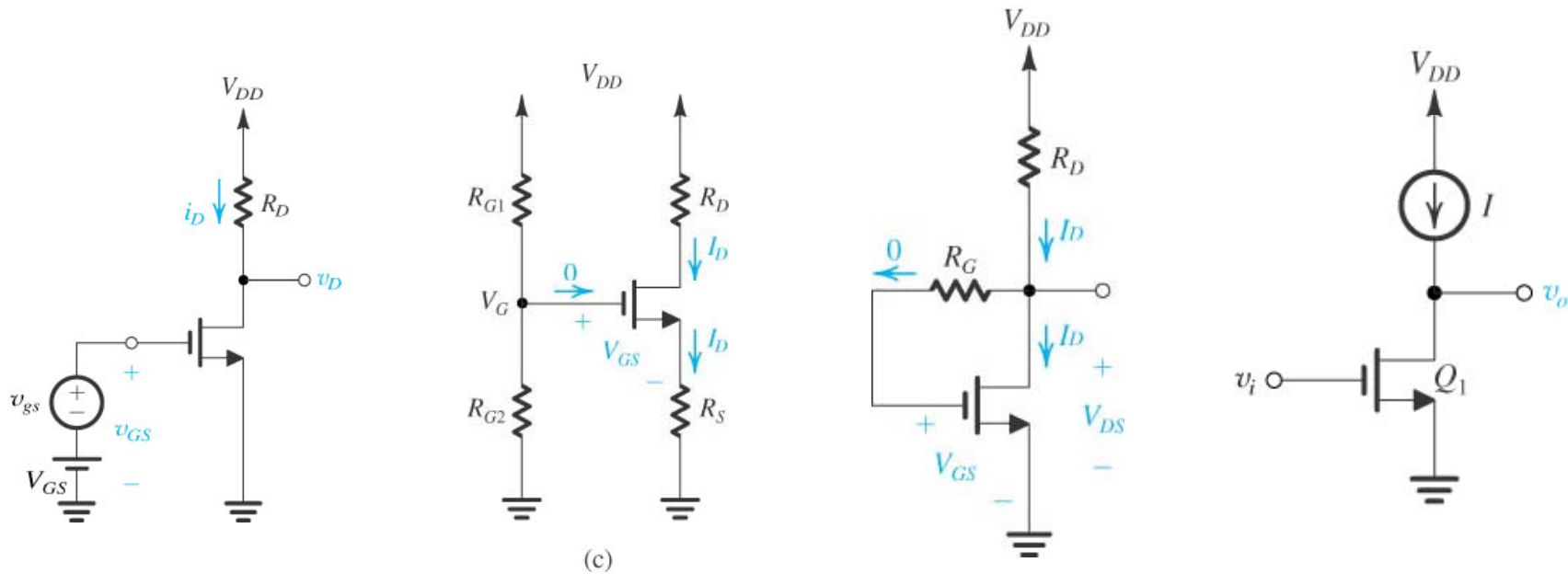


Lect. 23: MOSFET Current Mirror and Active Load

Various bias techniques for MOSFET circuits




How do we make a constant current source with MOSFETs?

Lect. 23: MOSFET Current Mirror and Active Load

Constant current source:

$$I_{D1} = \frac{1}{2} k'_n \left(\frac{W}{L} \right)_1 (V_{GS} - V_t)^2$$
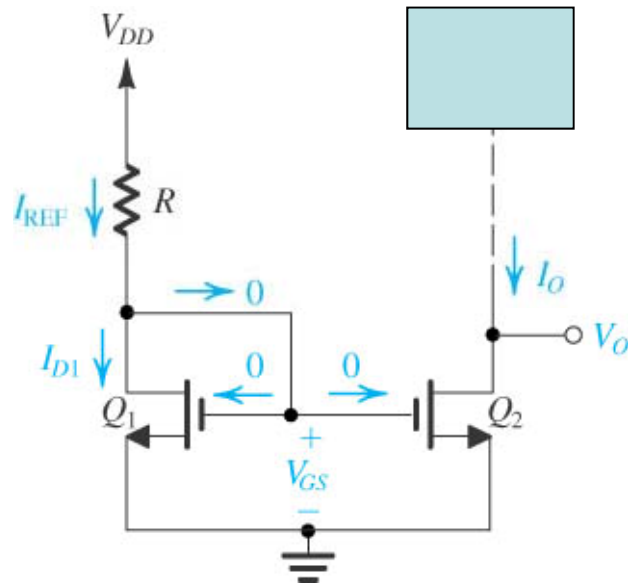
$$I_{D1} = I_{REF} = \frac{V_{DD} - V_{GS}}{R}$$



→ Current mirror

Assuming Q_1, Q_2 have same properties (k'_n),

$$I_O = I_{D2} = \frac{1}{2} k'_n \left(\frac{W}{L} \right)_2 (V_{GS} - V_{tn})^2$$



$$\frac{I_O}{I_{REF}} = \frac{(W/L)_2}{(W/L)_1}$$

Limitation on V_o ? $V_o \geq V_{GS} - V_t$

Lect. 23: MOSFET Current Mirror and Active Load

Mismatches between I_{REF} and I_O

Due to channel-length modulation

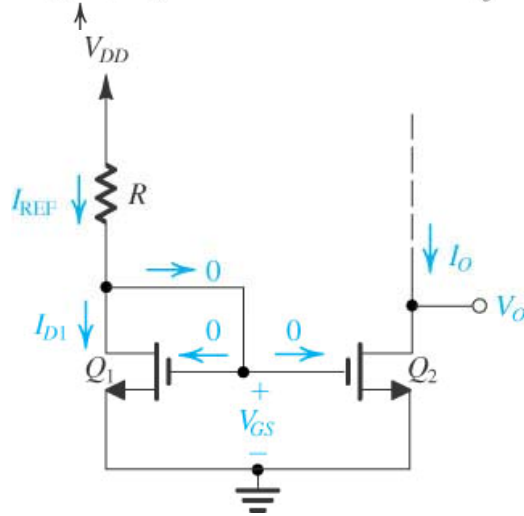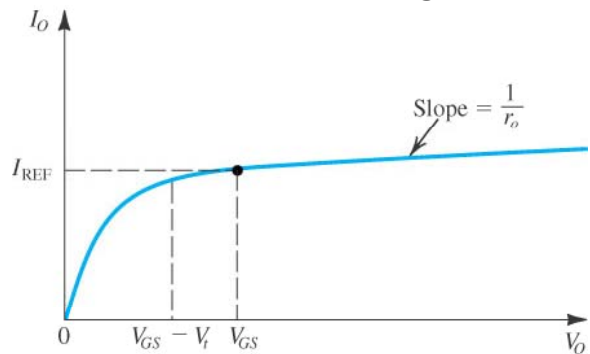

For two Q_1 and Q_2

$$I_O = I_{REF} \text{ only if } V_{DS1} = V_{DS2} \rightarrow V_O = V_{GS}$$

As V_O increased, I_O increases from I_{REF}


$$I_O = I_{REF} + \frac{V_O - V_{GS}}{r_o}$$

Comparison with BJT current mirror?


Lect. 23: MOSFET Current Mirror and Active Load

$V_{DD}=3V$, Q_1 and Q_2 are identical with
 $L=1\mu\text{m}$, $W=100\mu\text{m}$, $V_t=0.7V$, $k_n'=200\mu\text{A/V}^2$,
 $r_o=200\text{k}\Omega$

1. Determine R for $I_O=100\mu\text{A}$.
2. What is the lowest value for V_O ?
3. How much I_O changes when V_O changes 1V?

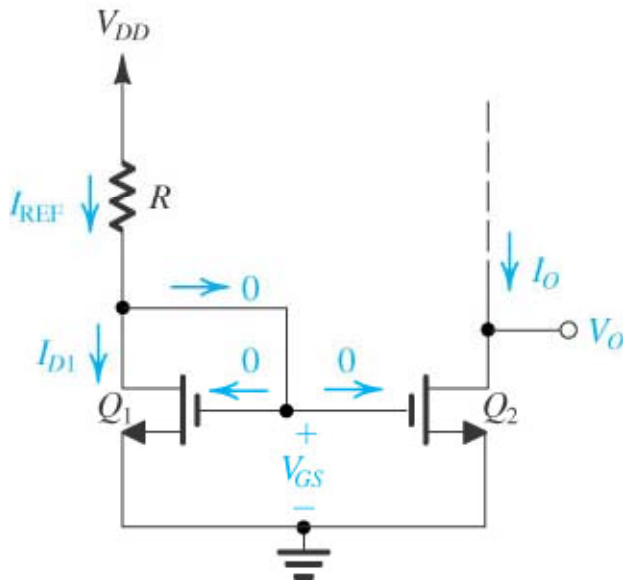

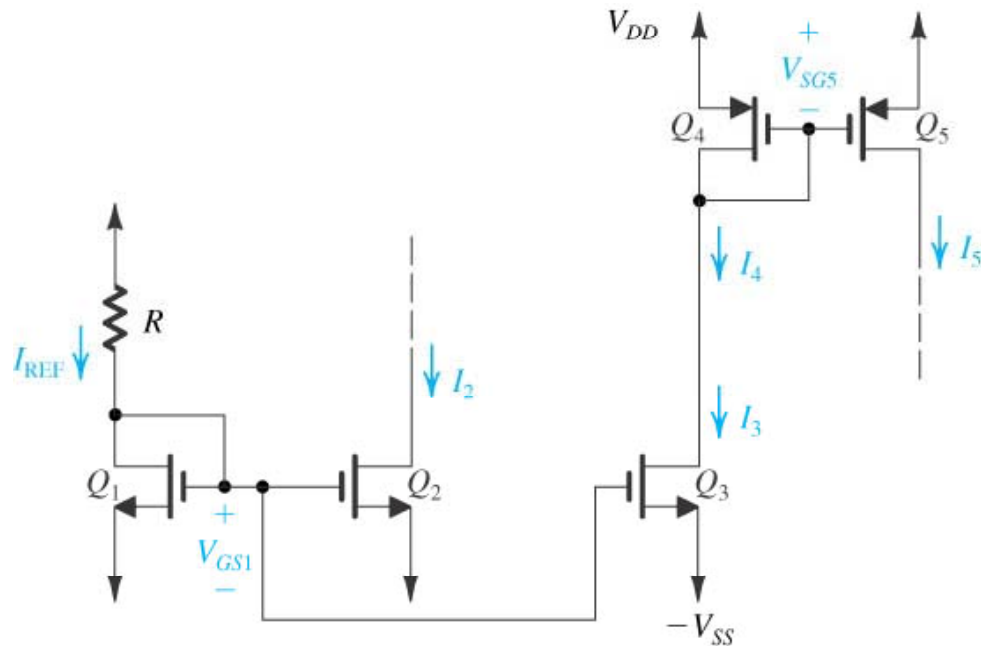Lect. 23: MOSFET Current Mirror and Active Load



$$I_2 = I_{REF} \frac{(W/L)_2}{(W/L)_1}$$


$$I_3 = I_{REF} \frac{(W/L)_3}{(W/L)_1}$$

$$I_3 = I_4$$

$$I_5 = I_4 \frac{(W/L)_5}{(W/L)_4}$$

Current-steering circuits: current source (Q₅), current sink (Q₂)

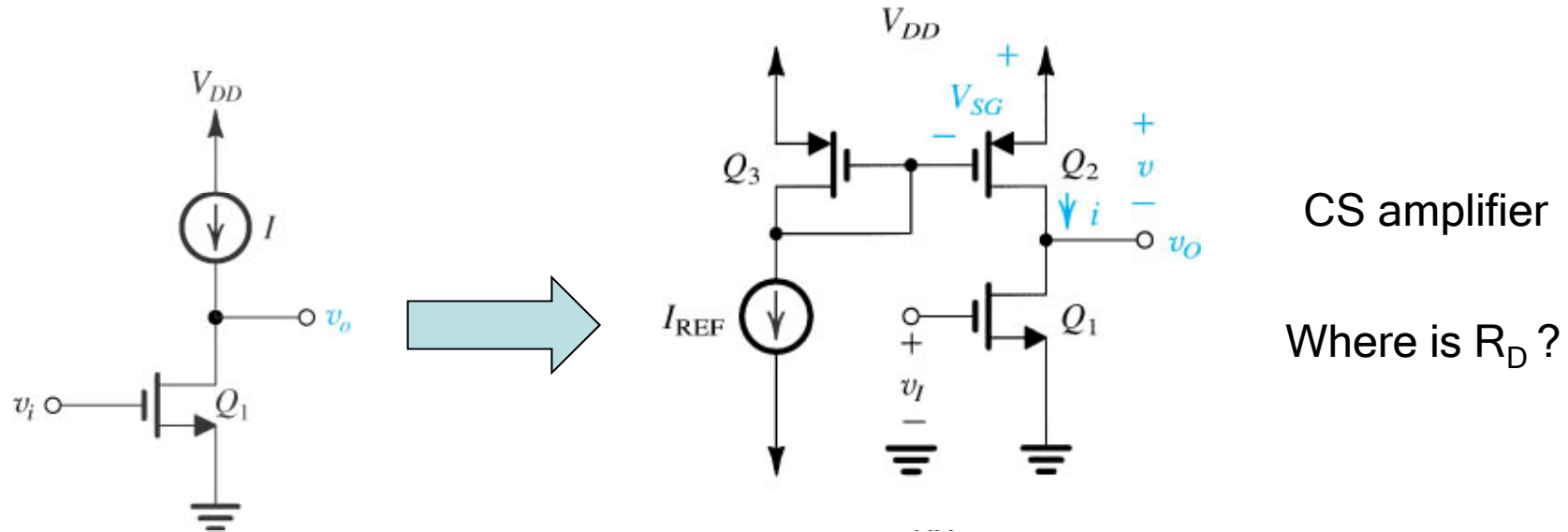Lect. 23: MOSFET Current Mirror and Active Load



CS amplifier

Where is R_D ?




Current source as a resistor → Active load

(Remember Q_2 has r_o)


Lect. 23: MOSFET Current Mirror and Active Load

Large change in v_o with v_i change!
 → Large amplifier gain

Load-line analysis

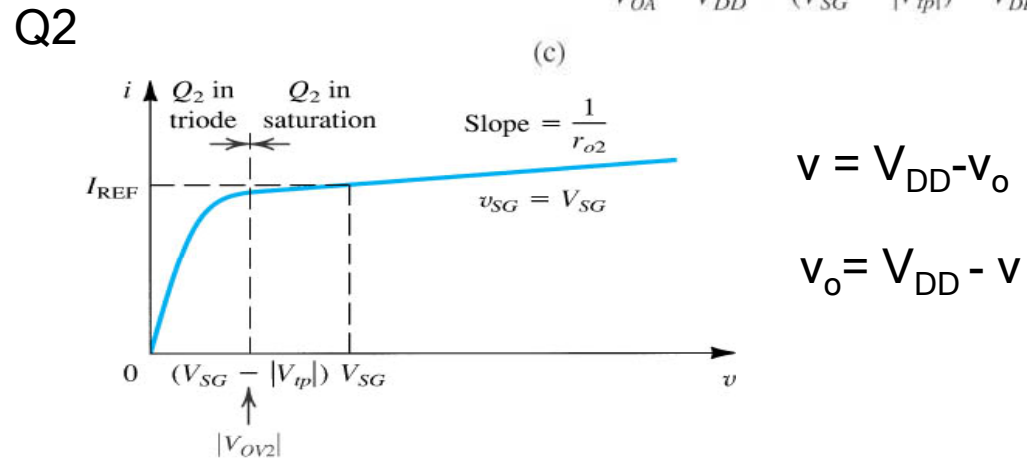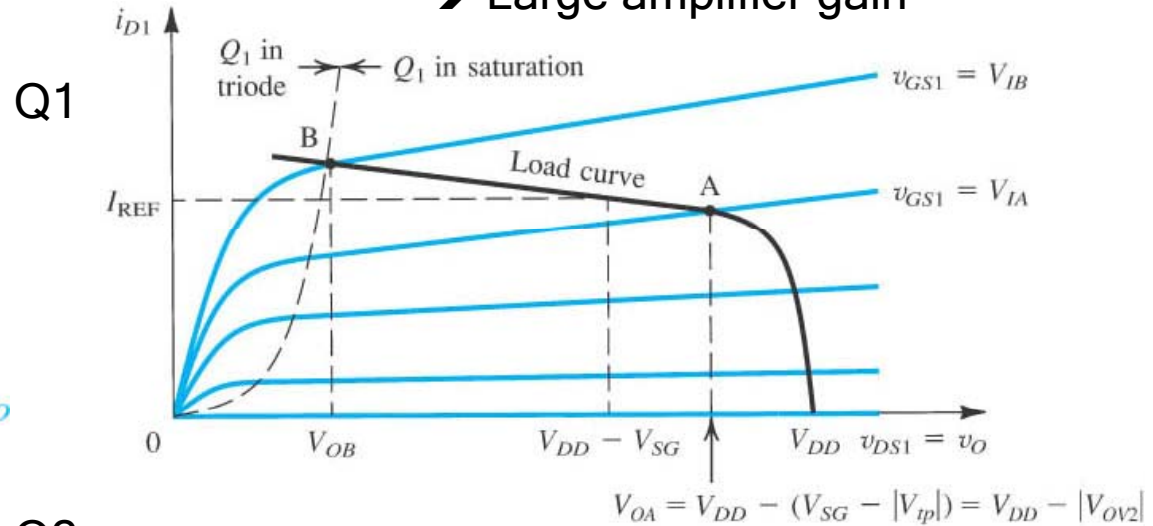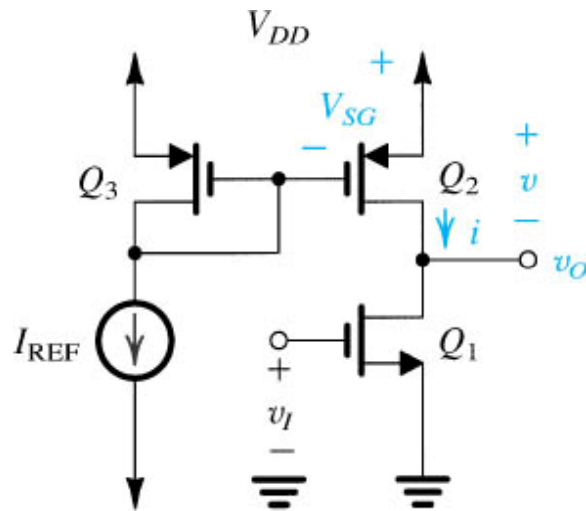

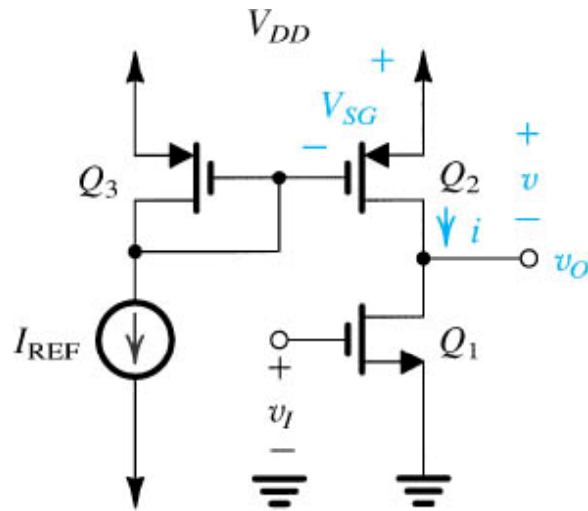Lect. 23: MOSFET Current Mirror and Active Load



Gain for CS amplifier with PMOS current mirror

$$-g_m (r_{O1} \parallel r_{O2})$$


PMOS current mirror provides large “Drain” resistance (Active Load) as well as bias current!

→ Good for IC!

Lect. 23: MOSFET Current Mirror and Active Load

$V_{DD}=3V$, $V_{tn}=|V_{tp}|=0.6V$, $k_n'=200\mu A/V^2$, $k_p'=65\mu A/V^2$,
 $L=0.4\mu m$, $W=4\mu m$, $r_{o1}=200k\Omega$, $r_{o2,3} = 100k\Omega$,
 $I_{REF}=100\mu A$.

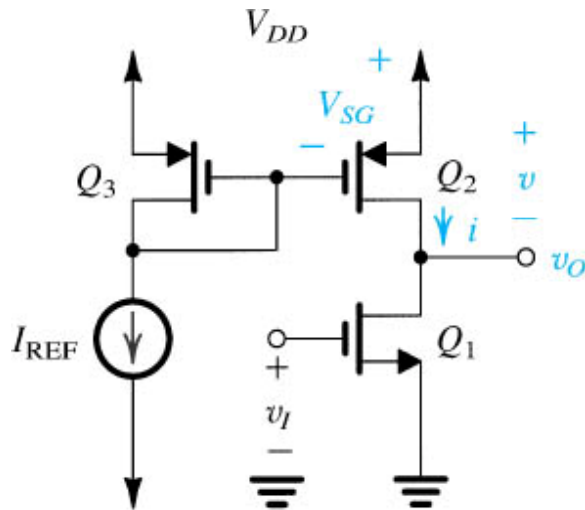1. What is the small-signal voltage gain, v_o/v_i ?
2. What is the maximum v_o for which the above is valid?



$$1. A_v = -g_{m1}(r_{o1} \parallel r_{o2})$$

$$g_{m1} = \sqrt{2k_n' \left(\frac{W}{L}\right)_1 I_{REF}} = \sqrt{2 \times 200 \times \frac{4}{0.4} \times 100} = 0.63 \text{ mA/V}$$

$$\therefore A_v = -0.63(\text{mA/V}) \cdot (200 \parallel 100)(\text{k}\Omega) = -42$$

$$2. \text{ For } Q_3, I_{REF} = \frac{1}{2} k_p' \left(\frac{W}{L}\right)_3 (V_{SG,3} - |V_{tp}|)^2 + \frac{V_{SD,3}}{r_o}$$

$$100 = \frac{1}{2} \times 65 \left(\frac{4}{0.4}\right) (V_{SG} - 0.6)^2 + \frac{V_{SG,3}}{100K}$$

$$\therefore V_{SG} \sim 1.12V$$

$$\text{For } v_{O,\max}, V_{SD2,\min} = V_{SG} - |V_{tp}| = 1.12 - 0.6 = 0.52V$$

$$\therefore v_{O,\max} = V_{DD} - V_{SD2,\min} = 2.48V$$