
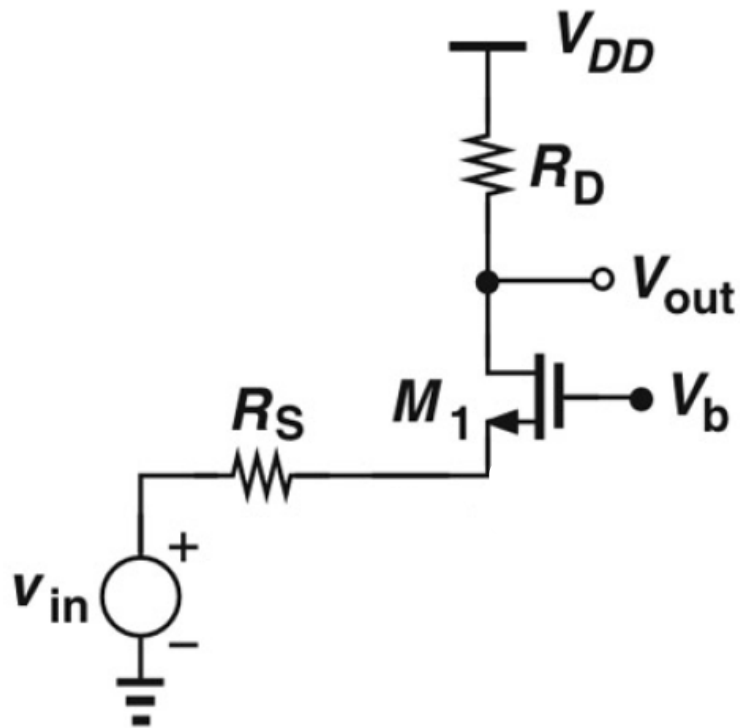


Lect. 25: CG Amplifier

Common-Gate Amplifier

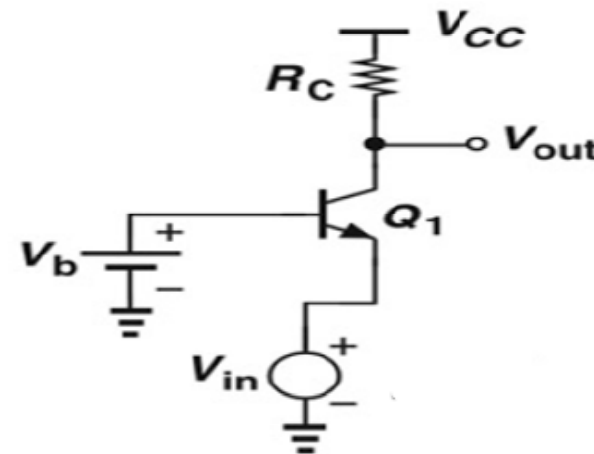

Remember BJT CB in Test #1 Prob. 3




Small R_{in} ($r_{\pi}/(\beta+1)$), Large R_{out} (R_C)
Unit short-ckt current gain ($\beta/(\beta+1)$)

→ Current buffer

Lect. 25: CG Amplifier

Common-Gate Amplifier

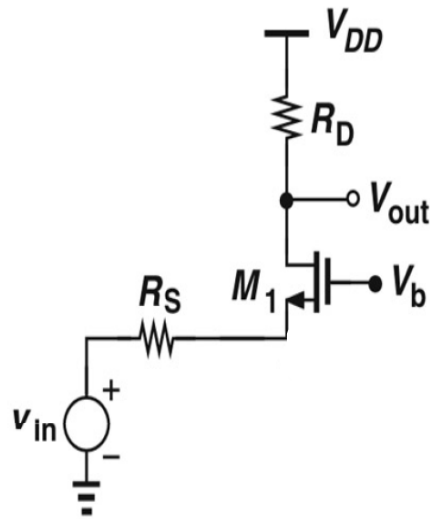

(Ignore r_o , Body effect)

$$R_{in} = 1/g_m$$

$$R_{out} = R_D$$


$$\text{Short-ckt current gain} = 1$$

$$\text{Voltage gain (without } R_S) = g_m R_D$$


$$\text{Voltage gain (with } R_S) = g_m R_D / (1 + g_m R_S)$$

Lect. 25: CG Amplifier

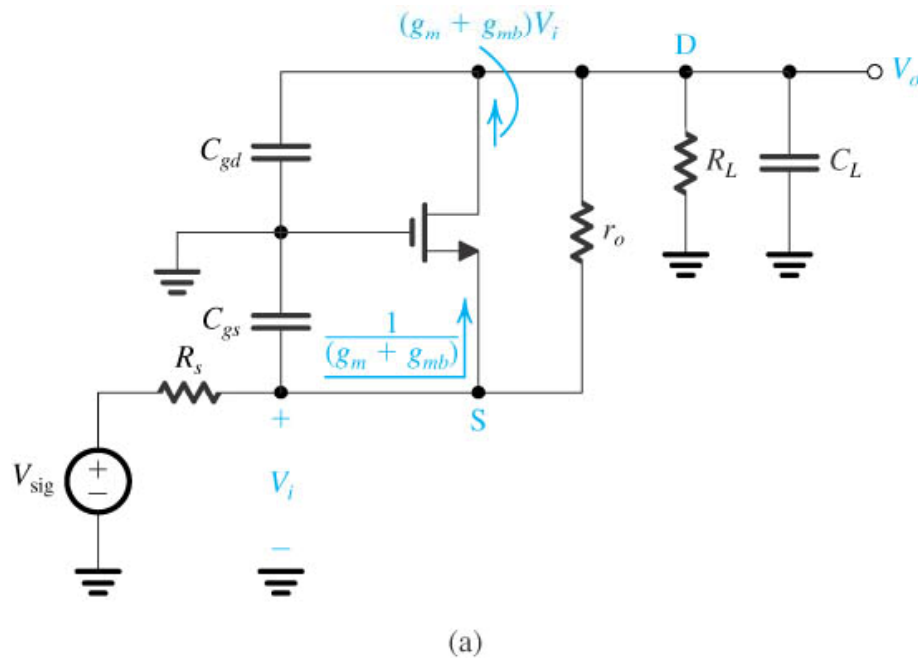Frequency Response: Use open-circuit time constant method.




For C_{gs}

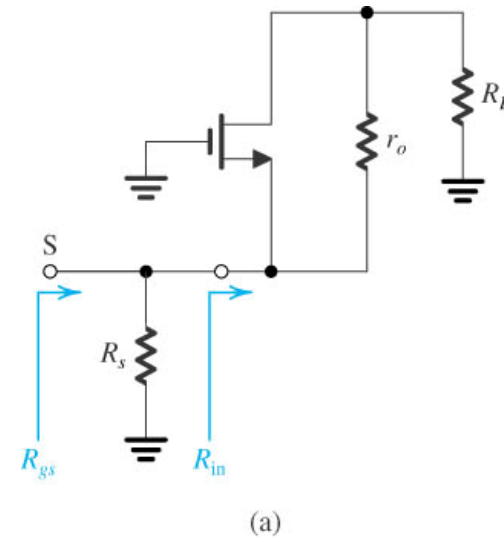

$$R_{gs} = R_s || R_{in}$$


Lect. 25: CG Amplifier

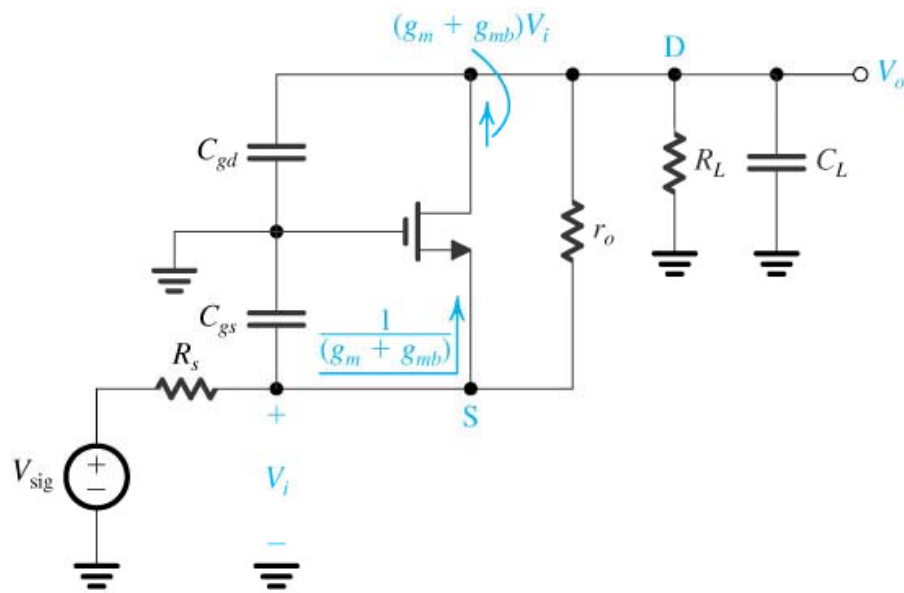Frequency Response: Use open-circuit time constant method.



(a)

For $C_{gd} \parallel C_L$

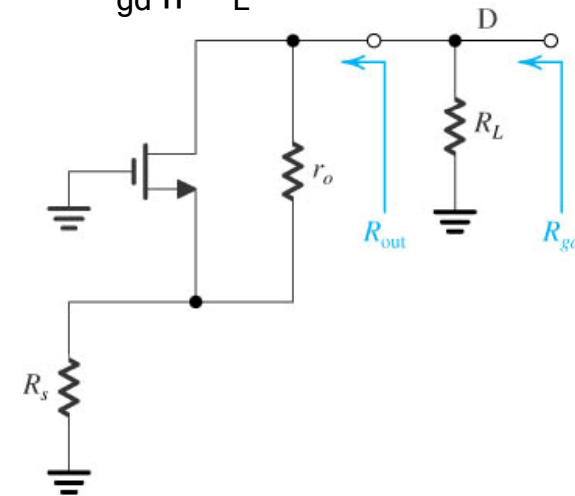


$$R_{gd} = R_L \parallel R_{out}$$

$$f_H = \frac{1}{2\pi \left[C_{gs} (R_s \parallel R_{in}) + (C_{gd} + C_L) (R_L \parallel R_{out}) \right]}$$


Lect. 25: CG Amplifier

Comparison of CG with CS

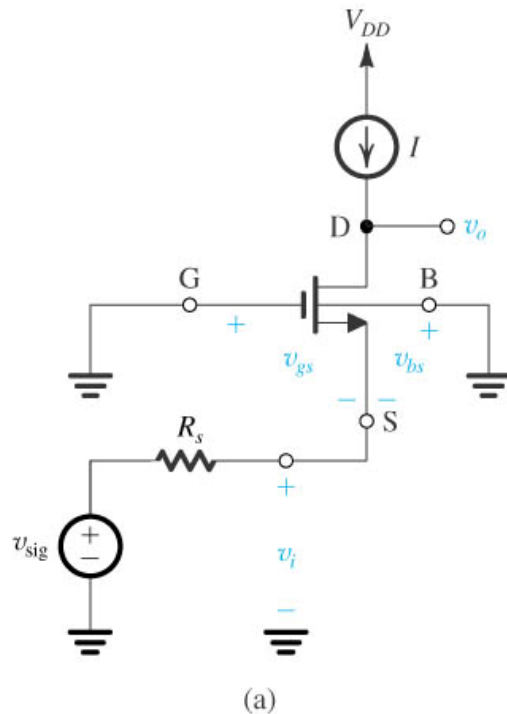

$$f_H = \frac{1}{2\pi [C_{gs}(R_s \parallel R_{in}) + (C_{gd} + C_L)(R_L \parallel R_{out})]}$$

Which is larger? Why?

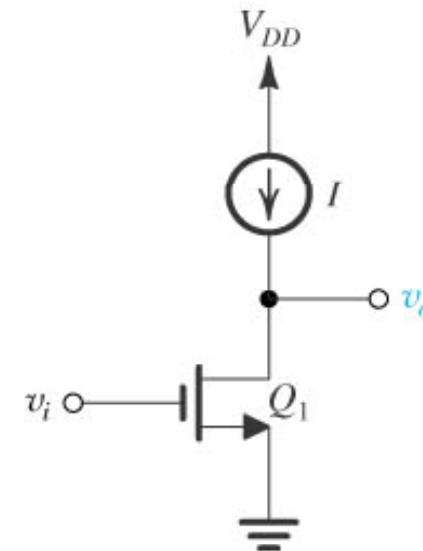

$$f_H = \frac{1}{2\pi [C_{gs}R_{sig} + C_{gd}[R_{sig}(1 + g_m R_L') + R_L'] + C_L R_L']}$$

CG does not suffer from Miller effect