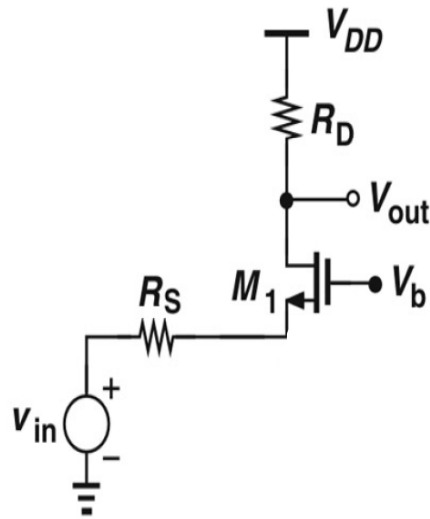


# Lect. 26: Cascode Amplifier (Razavi 9.1)


## Common-Gate Amplifier



$$R_{out} = R_D$$

( $r_o$ ,  $R_S$  ignored)

## Influence of $r_o$ and $R_S$ ?

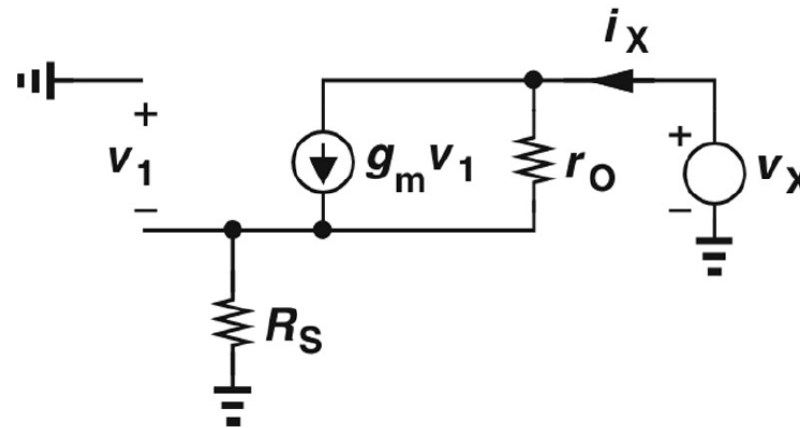


$$v_x/i_x = r_o(1 + g_m R_S) + R_S$$

$$\rightarrow g_m r_o R_S$$

# Lect. 26: Cascode Amplifier

---

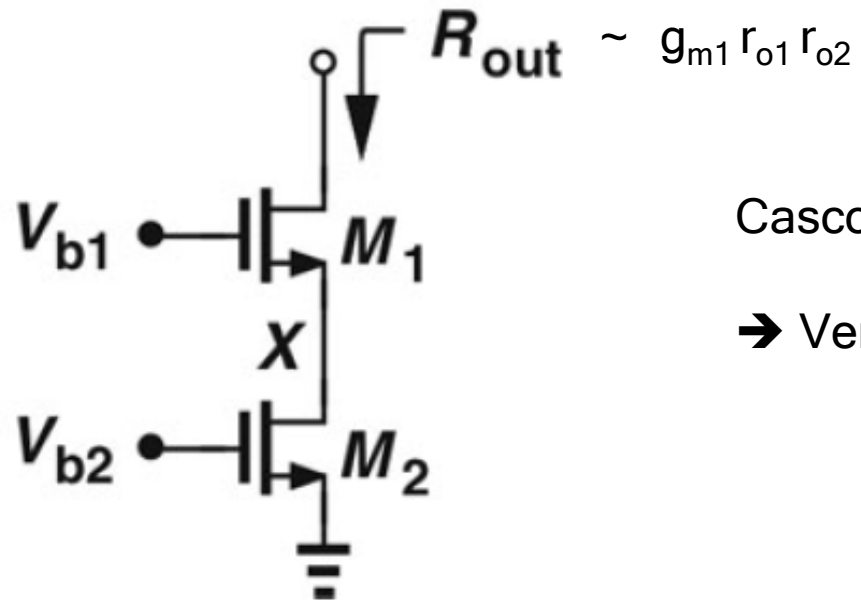


Cascode configuration

→ Very high output resistance

# Lect. 26: Cascode Amplifier


Cascode amplifier

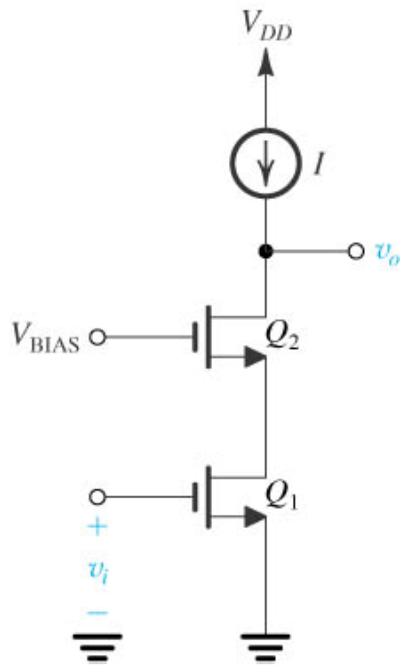

$R_{in}$ :

$R_{out} : g_{m2} r_{o2} r_{o1}$

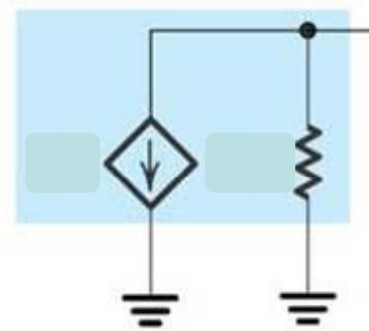$G_m$ , Transconductance Gain  $\rightarrow g_{m1}$




Voltage Gain:  $-G_m \times R_{out}$

$$\therefore A_{vo} \sim -g_{m1} r_{o1} g_{m2} r_{o2}$$

If  $Q_1$  and  $Q_2$  are identical,  $A_{vo} \sim -(g_m r_o)^2$

# Lect. 26: Cascode Amplifier

## Cascode Amplifier

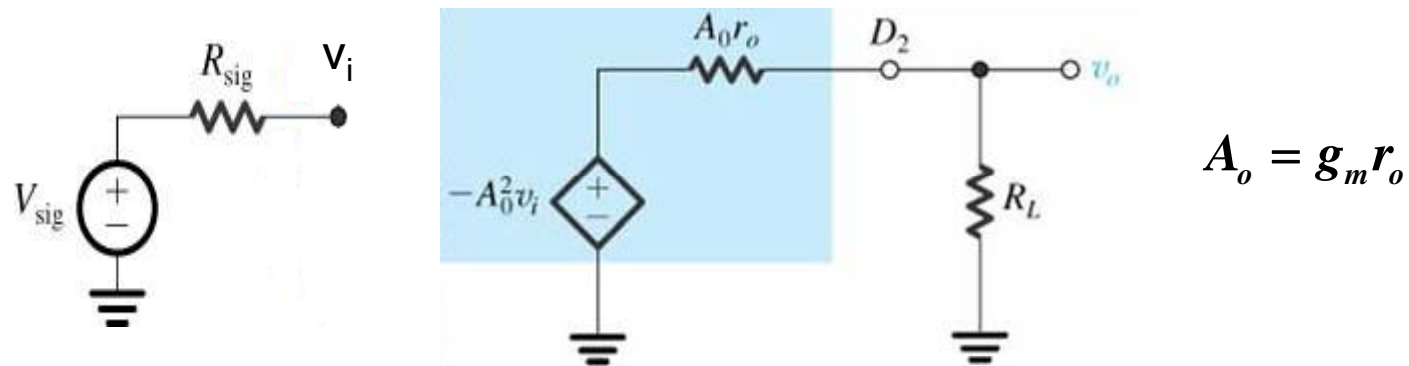



Compared with CS,

$$R_{\text{out}}: r_o \rightarrow A_o r_o$$

$$A_{v_o}: -g_m r_o \rightarrow -(g_m r_o)^2$$

# Lect. 26: Cascode Amplifier

Miller Effect?

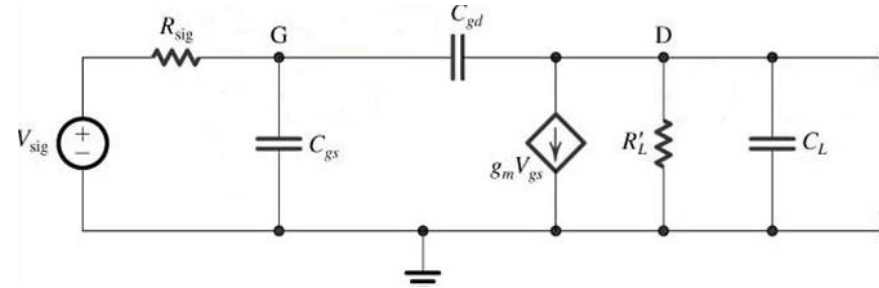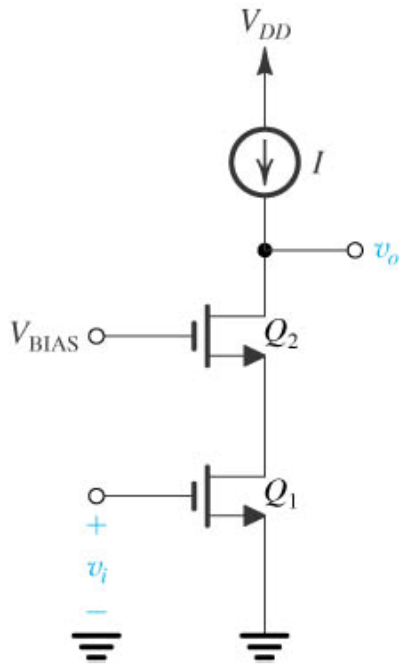

Remember Miller effect is due to  $C_{gd}$


$$R_{d1} = ?$$

$$R_{d1} = r_{o1} \parallel \frac{1}{g_{m2}}$$

Reduction of Miller effect with small  $R_{d1}$

# Lect. 26: Cascode Amplifier

## Double Cascode

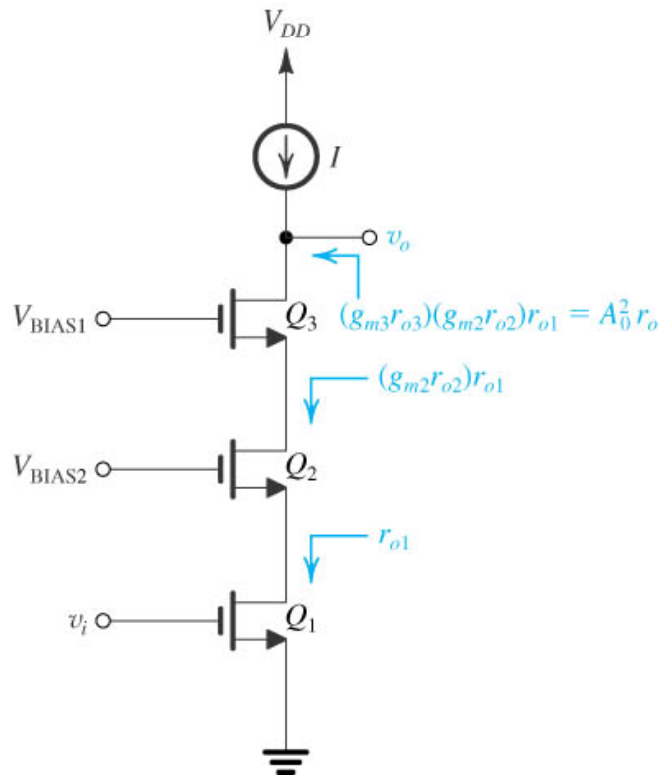

Higher output resistance

But limited range for output swing

## Folded Cascode

