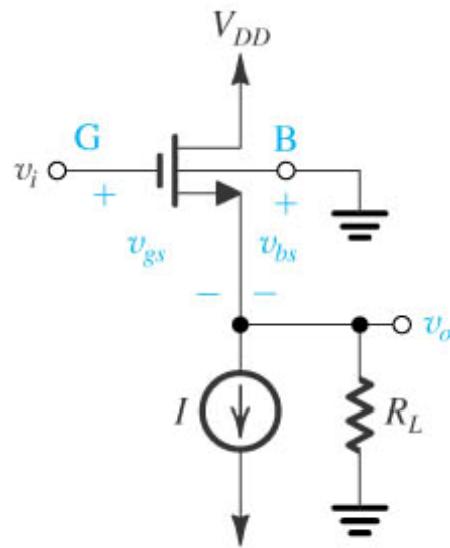



# Lect. 27: Source Follower (Razavi 7.4)

---

Ignoring body effect



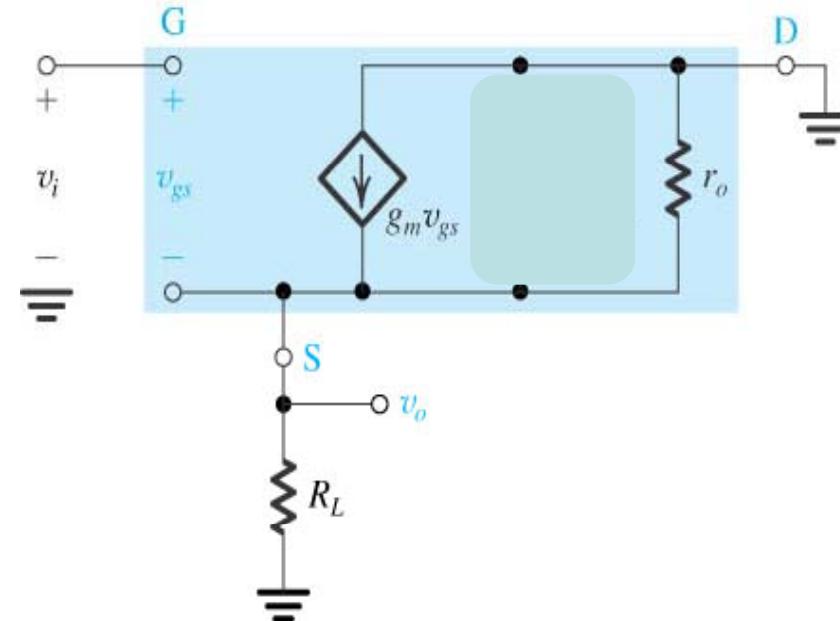Source Follower  
(Common-Drain Amplifier)




$$R_{in} =$$

$$R_{out} = 1/g_m \parallel r_o$$

# Lect. 27: Source Follower

---

## Voltage Gain

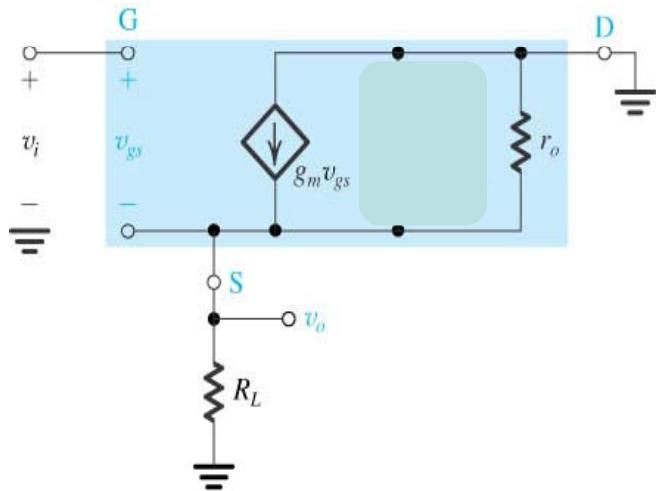

$$v_o = g_m v_{gs} (r_o \parallel R_L)$$

$$v_{gs} = v_i - v_o$$


$$v_o = g_m (v_i - v_o) (r_o \parallel R_L)$$

$$v_o (1 + g_m \cdot r_o \parallel R_L) = v_i g_m \cdot r_o \parallel R_L$$

$$\therefore \frac{v_o}{v_i} = \frac{g_m \cdot r_o \parallel R_L}{1 + g_m \cdot r_o \parallel R_L}$$

$$= \frac{r_o \parallel R_L}{\frac{1}{g_m} + r_o \parallel R_L}$$



# Lect. 27: Source Follower

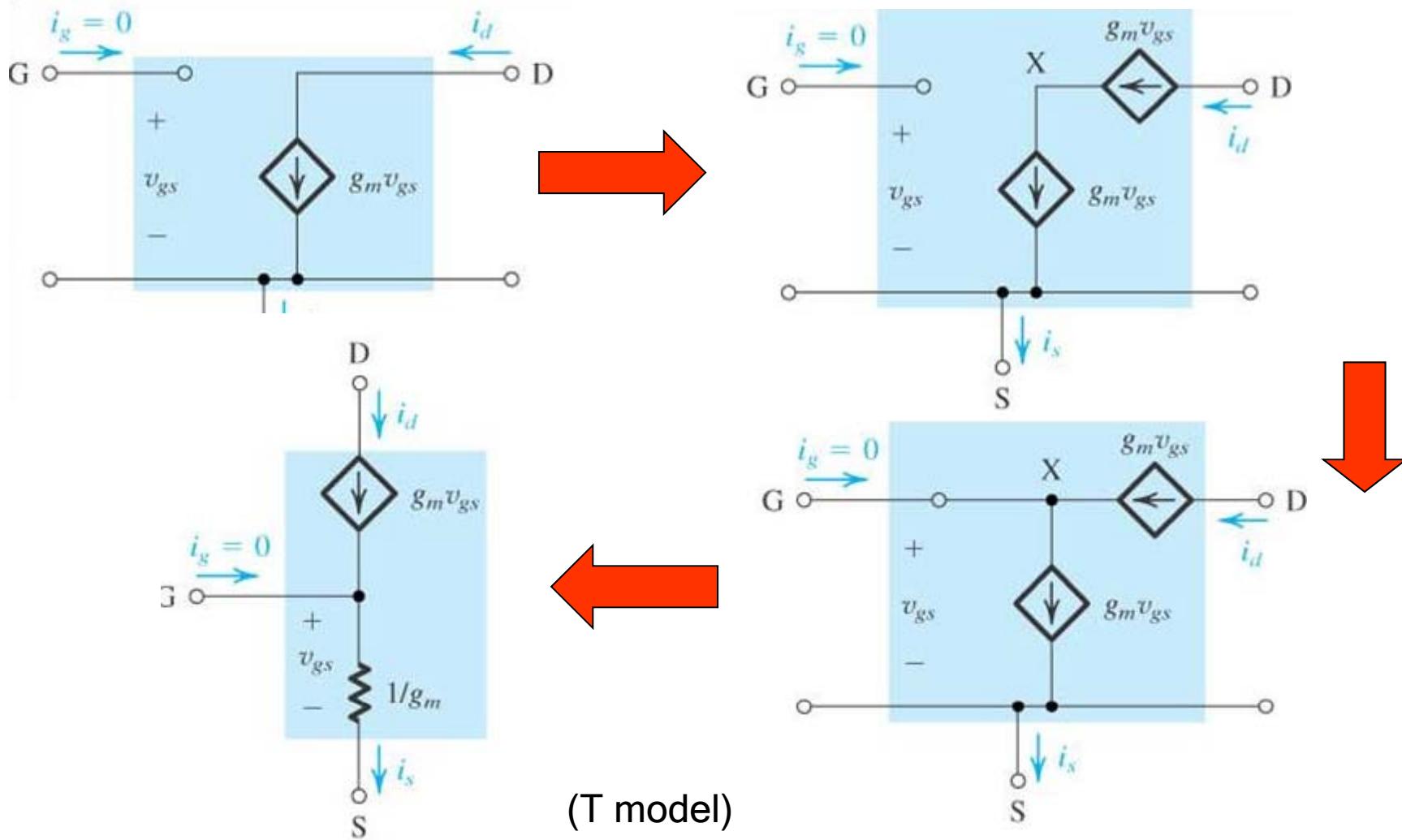

# Lect. 27: Source Follower

---


Voltage Gain using the T-model?

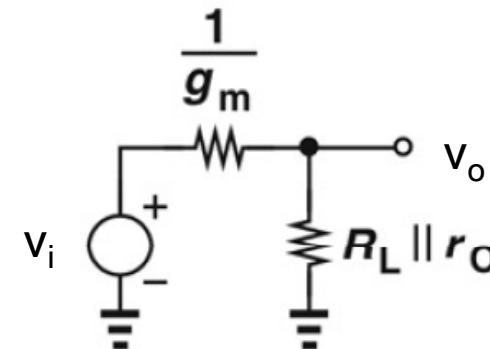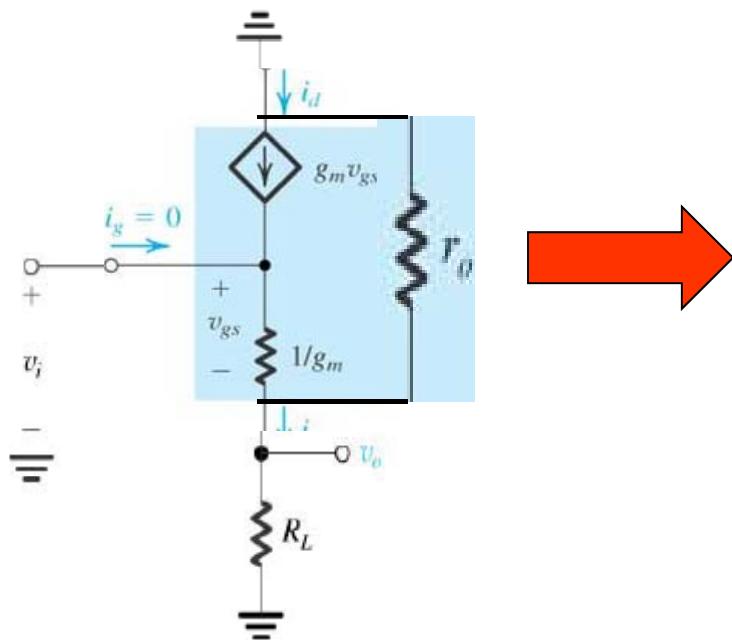

$$\therefore \frac{v_o}{v_i} = \frac{r_o \parallel R_L}{\frac{1}{g_m} + r_o \parallel R_L}$$

# Lect. 27: Source Follower

---

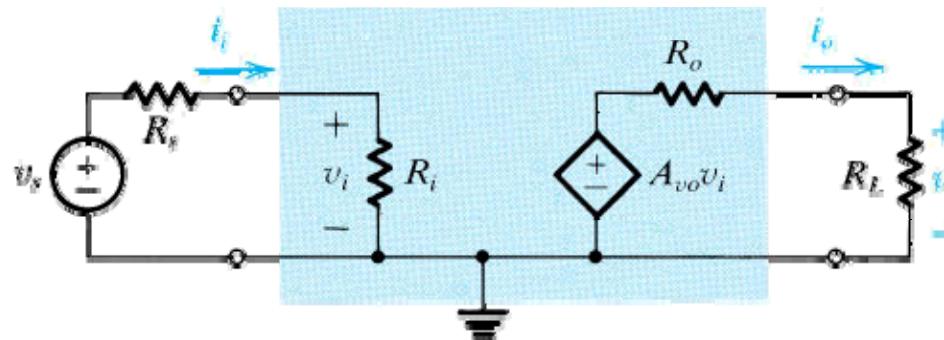


$$v_o = \frac{R_L}{R_L + R_o} A_{vo} v_i = \frac{R_L}{R_L + R_o} A_{vo} \frac{R_i}{R_i + R_s} v_s \sim v_s$$

Source Follower: Large  $R_i$ , Small  $R_o$ ,  $A_{vo}$  close to one

→ Voltage buffer

# Lect. 27: Source Follower

---

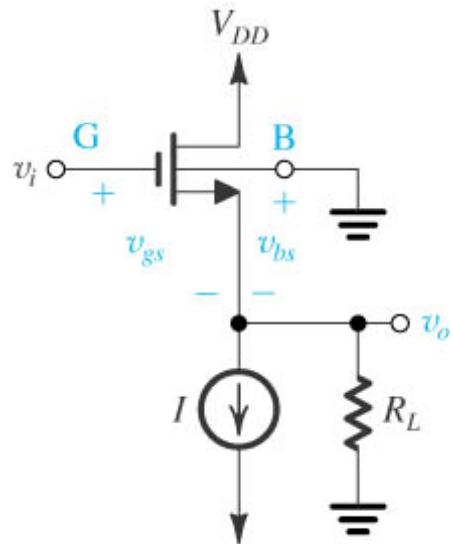

For  $v_I = V_I + v_i$

$$v_O = V_O + v_o = V_O + v_i$$


$v_O$  shifts  $v_I$  by the amount of  $(V_I - V_O = V_{GS})$

→ Level shifter

# Lect. 27: Source Follower

---

## Frequency Response

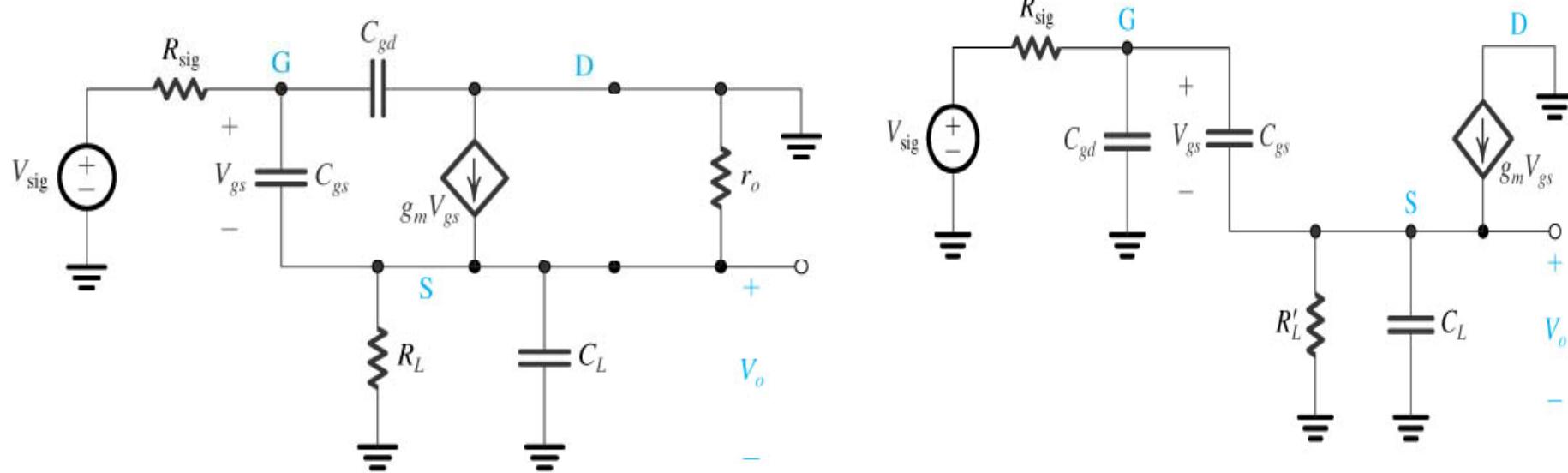

Miller Effect?

Source Follower is fast!