
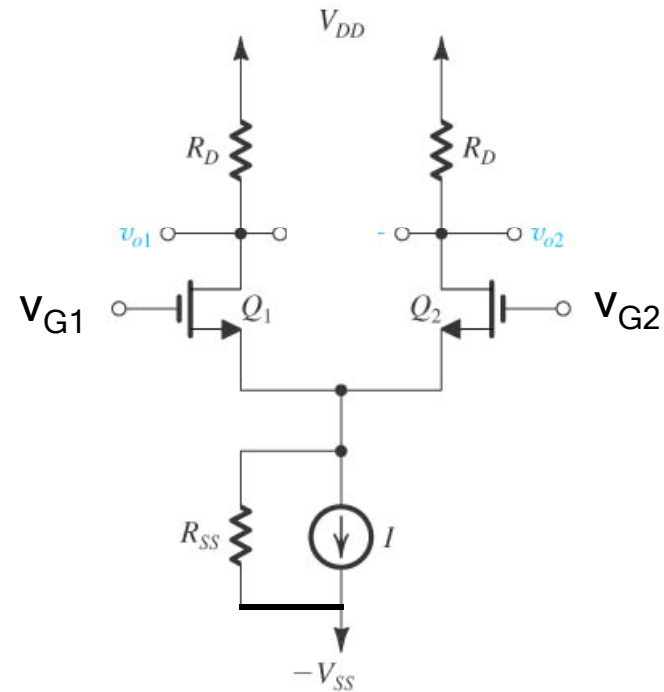


Lect. 29: MOS Differential Amplifiers(2)



Non-Ideal effects

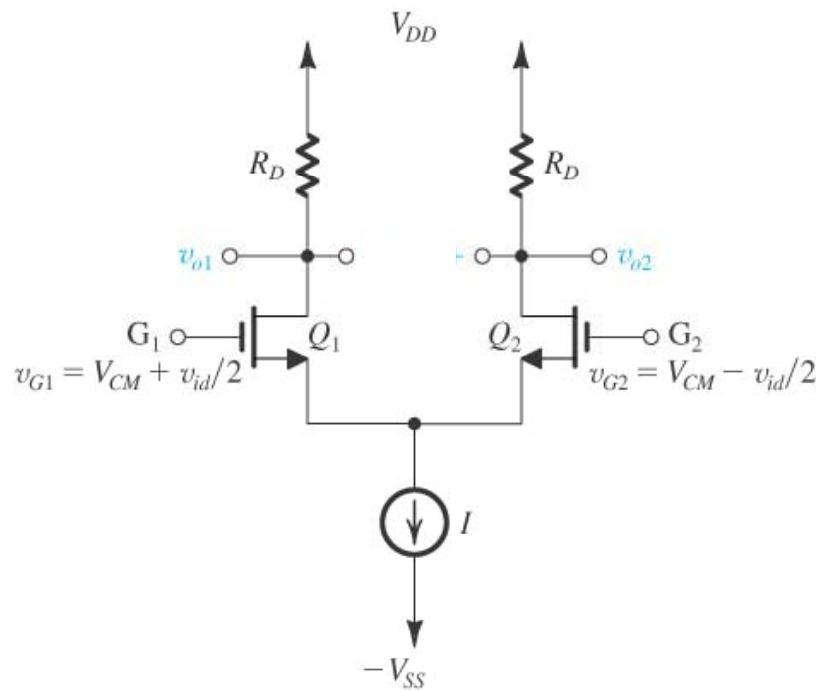

What if the current source is NOT ideal?

Lect. 29: MOS Differential Amplifiers(2)

Make it left-right symmetric

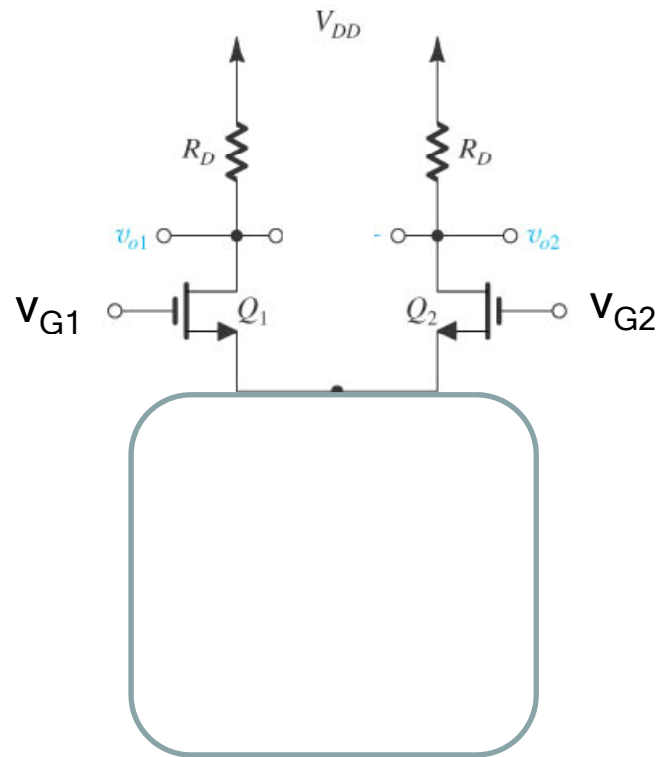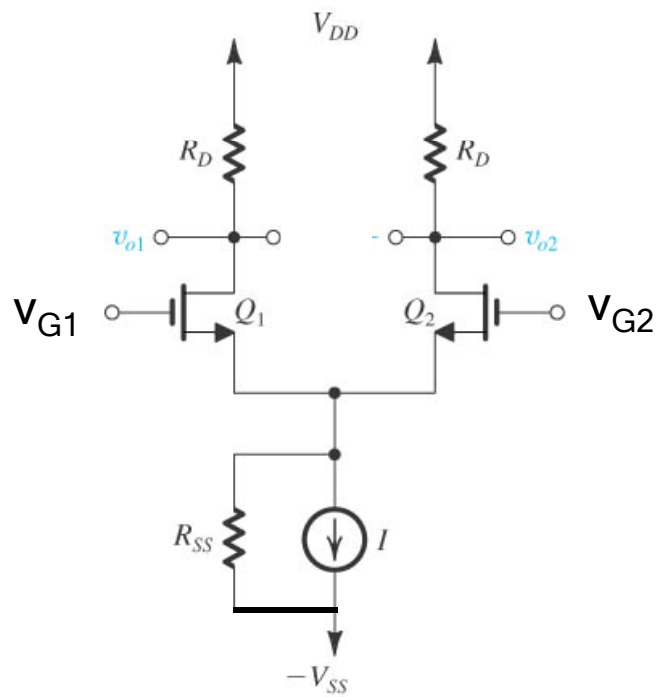

CM response?


DM response?

Lect. 29: MOS Differential Amplifiers(2)

Any difference?

Without R_{SS} , v_{G1} does affect v_{o1} in CM

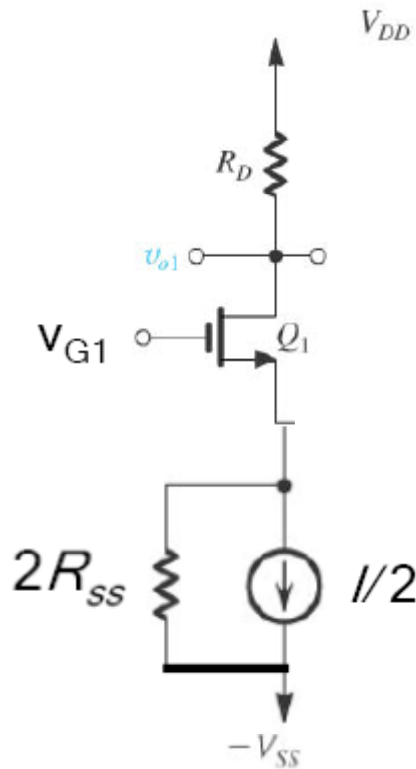With R_{SS} → Common-Source with source resistance



$$\frac{v_{o1}}{v_{G1}} = ?$$

(Ignoring r_o)

$$v_{o1} = -g_m v_{gs} R_D$$

$$v_{gs} = v_{G1} - g_m v_{gs} (2R_{SS})$$


$$v_{gs} = \frac{v_{G1}}{1 + 2g_m R_{SS}}$$

$$\frac{v_{o1}}{v_{G1}} = -\frac{g_m R_D}{1 + 2g_m R_{SS}} \sim -\frac{R_D}{2R_{SS}}$$

With non-ideal current source, v_{G1} does affect v_{o1} in CM → But $v_{o1} - v_{o2} = 0$

Lect. 29: MOS Differential Amplifiers(2)

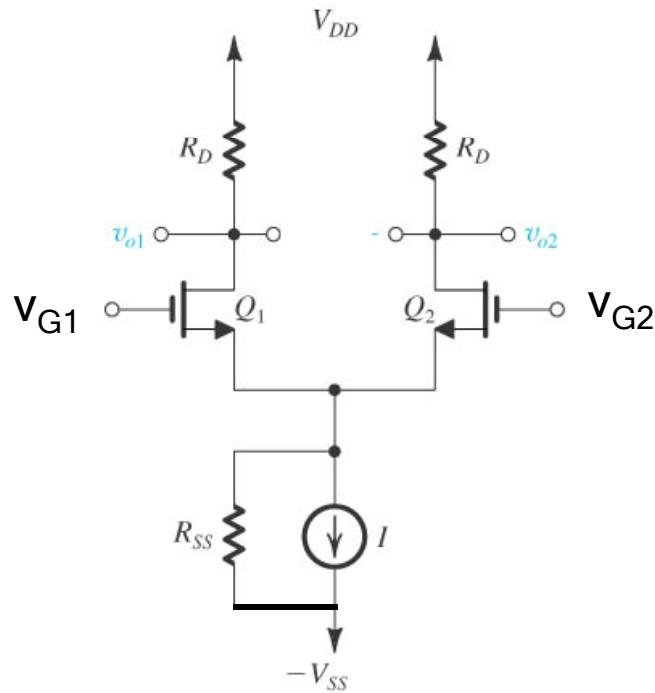But if we take output as $v_{o1}-v_{o2}$
 R_{SS} doesn't affect the output



$$\text{CMRR (Common-Mode Rejection Ratio)} = \left| \frac{A_d}{A_{cm}} \right|$$


$$A_d = \frac{v_{od}}{v_{id}} = -g_m R_D \text{ (Ignoring } r_o \text{)}$$

$$A_{cm} = \frac{v_{od}}{v_{icm}} = \frac{v_{o1} - v_{o2}}{v_{icm}} = 0$$

$$\text{CMRR} = \infty$$

Lect. 29: MOS Differential Amplifiers(2)

What if R_D 's are NOT matched?

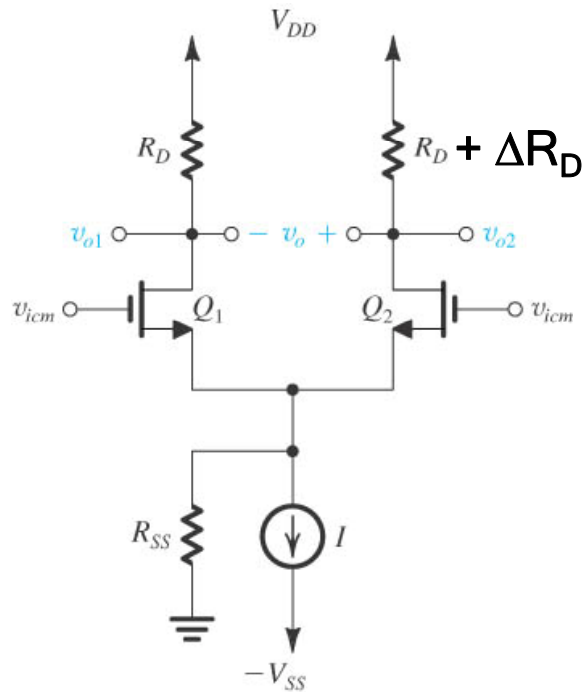

Assuming $\Delta R_D \ll R_D$

→ Use results obtained for symmetric CM and DM.

CM (small signal)

$$v_{o1} \sim -\frac{R_D}{2R_{SS}} \cdot v_{icm}, \quad v_{o2} \sim -\frac{R_D + \Delta R_D}{2R_{SS}} \cdot v_{icm}$$

$$v_{o1} - v_{o2} \sim \frac{\Delta R_D}{2R_{SS}} \cdot v_{icm} \quad \therefore A_{cm} = \frac{v_{o1} - v_{o2}}{v_{icm}} \sim \frac{\Delta R_D}{2R_{SS}}$$


→ CM gain

Assuming DM gain does not get affected

$$A_d \sim -g_m R_D$$

Lect. 29: MOS Differential Amplifiers(2)

What if R_D 's are NOT matched?

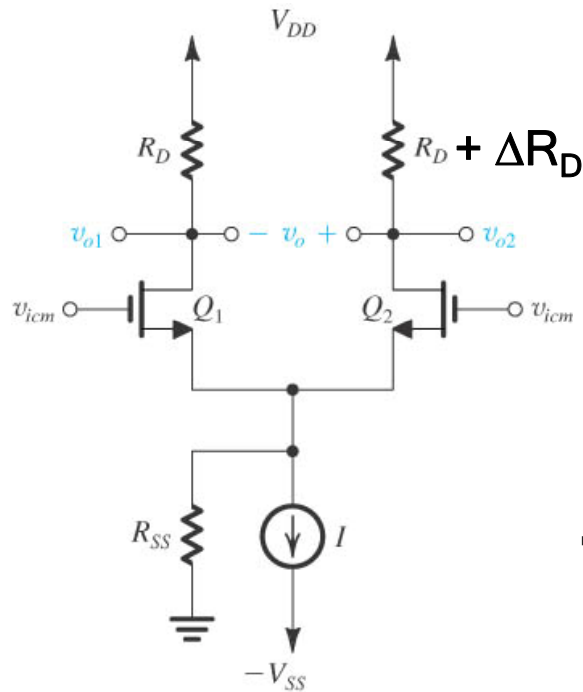

$$\text{CMRR (Common-mode rejection ratio)} = \left| \frac{A_d}{A_{cm}} \right| \sim \frac{g_m R_D}{\frac{\Delta R_D}{2R_{SS}}}$$

Any mismatches in differential pair causes finite CMRR

→ Common-mode input affects output difference

Lect. 29: MOS Differential Amplifiers(2)

What if we want to have single-ended output?

For DM,


$$\frac{v_o}{-v_{id}/2} = -g_m R_D$$

$$\therefore A_d = \frac{v_o}{v_{id}} = \frac{g_m R_D}{2} \quad (\text{ignoring } r_o)$$

For CM,

$$\frac{v_o}{v_{cm}} \sim -\frac{R_D}{2R_{ss}}$$


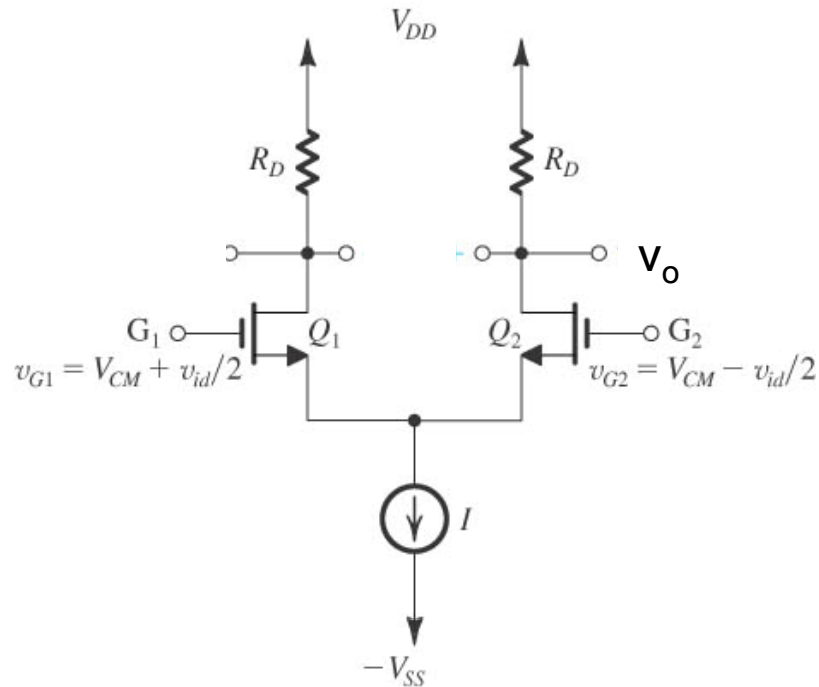
$$\text{CMRR} \sim \frac{\frac{g_m R_D}{2}}{\frac{R_D}{2R_{ss}}} = g_m R_{ss}$$



Finite CMRR for single-ended output

Lect. 29: MOS Differential Amplifiers(2)


Can we do better?

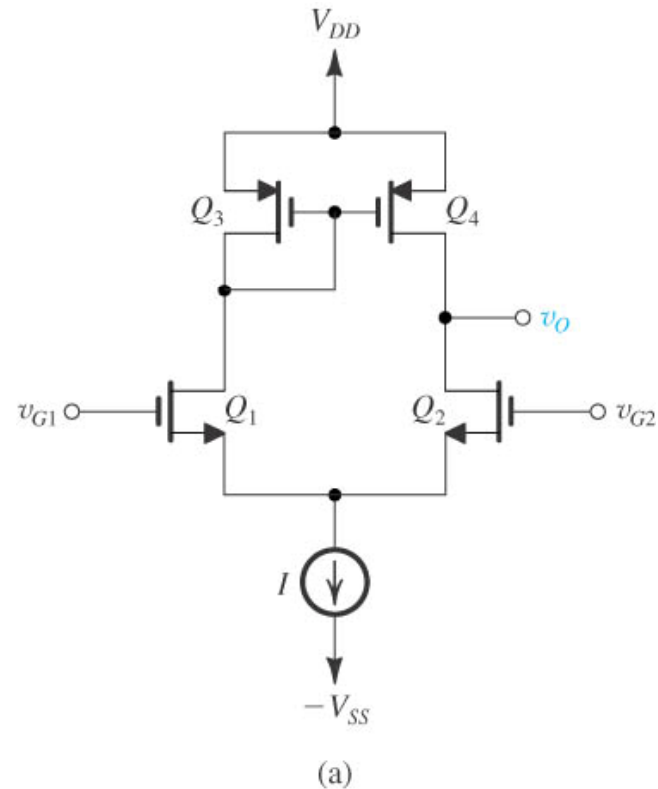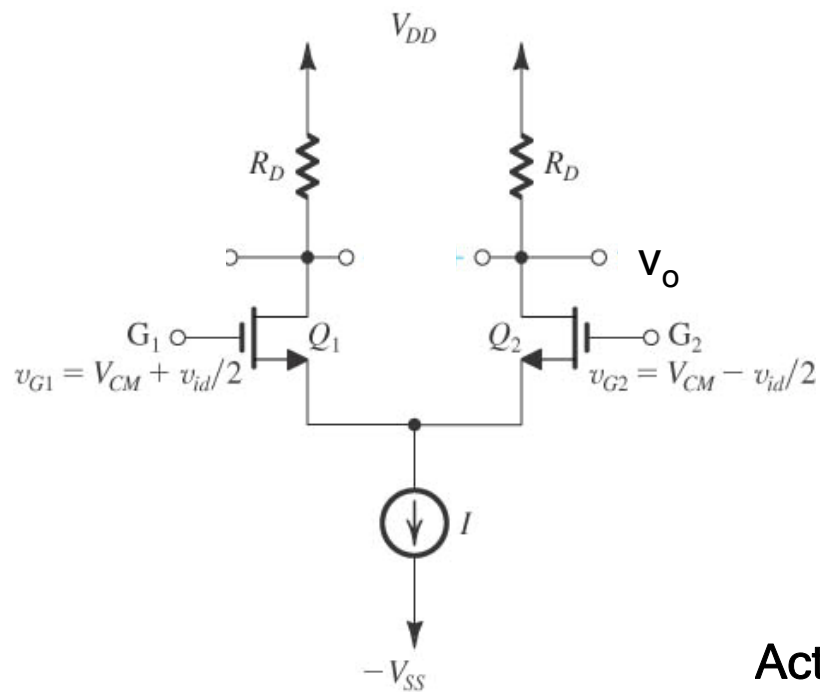

Active-loaded (current mirror) MOS differential pair

No resistors → small size, better matching

Lect. 29: MOS Differential Amplifiers(2)

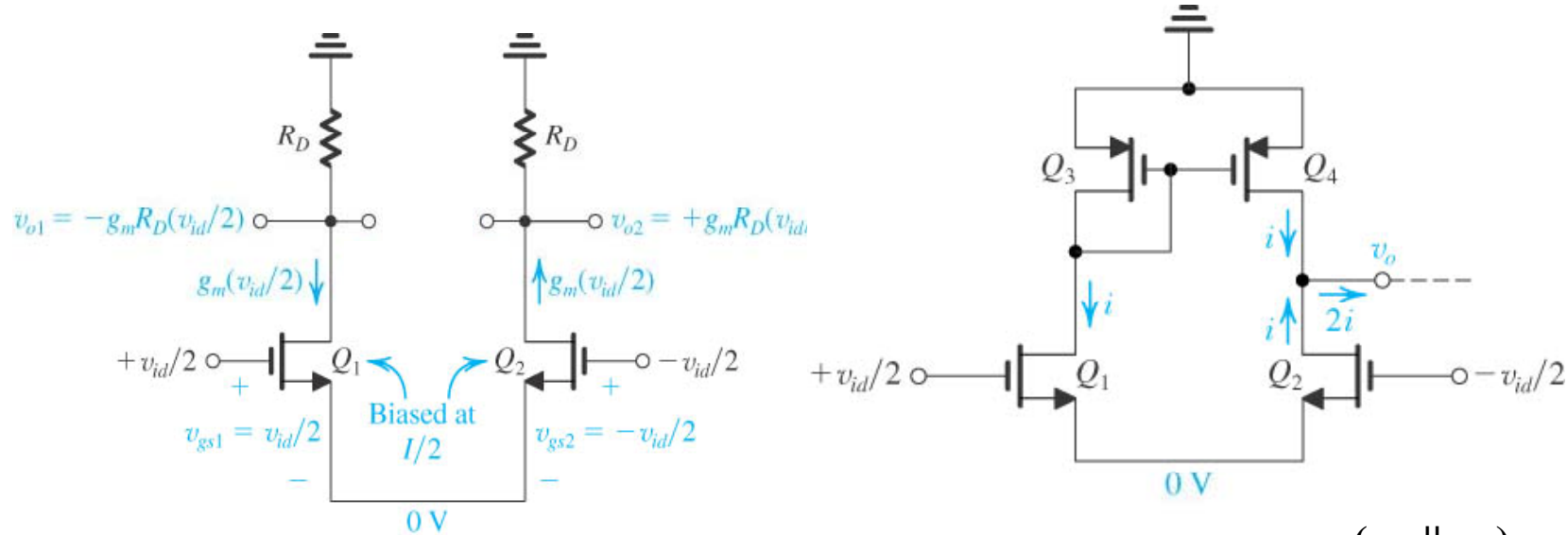

$$\frac{v_{o2}}{v_{id}} = \frac{g_m (R_D \parallel r_o)}{2}$$

Assuming symmetry $\frac{v_o}{v_{id}} = \frac{g_m (r_{on} \parallel r_{op})}{2}$

But detailed analysis (Razavi 10.6.2) can show

$$\frac{v_o}{v_{id}} = g_m (r_{on} \parallel r_{op})$$

Factor of 2 improvement due to current mirror!