
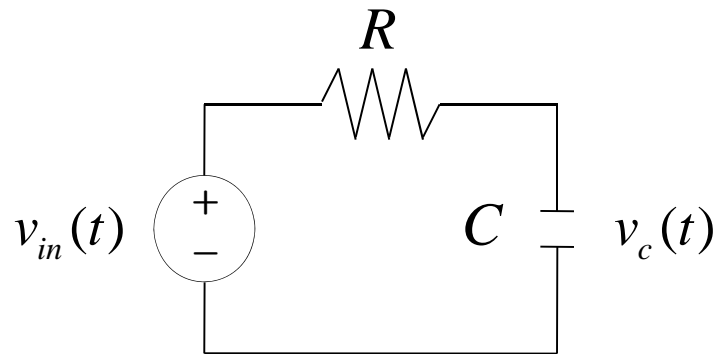


Lect. 3: Review of Basic Circuits (2)

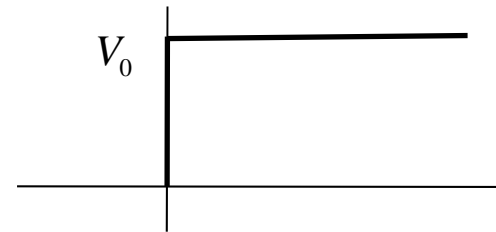

When $v_{in}(t)$



$v_c(t) = ?$


- Initially, capacitor has no charges, $v_c(t) = 0$ ($Q = CV$)
- Current flows from v_{in} to C through R
- Charges build up and $v_c(t) \uparrow$ $\left(i = C \frac{dv}{dt} \right)$
- Current flow gets smaller
- Eventually no current flows, $v_c(t) = V_0$

Lect. 3: Review of Basic Circuits (2)

$$v_{in}(t) - i(t)R = v_c(t)$$

$$i(t) = C \frac{dv_c(t)}{dt}$$
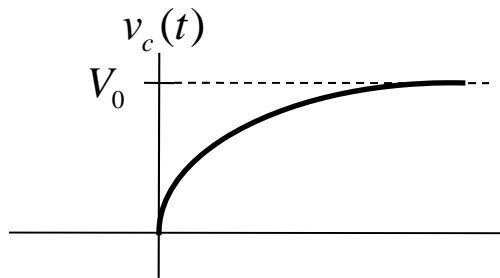
$$v_{in}(t) - RC \frac{dv_c(t)}{dt} = v_c(t) \quad \therefore \frac{dv_c(t)}{dt} + \frac{v_c(t)}{RC} = \frac{v_{in}(t)}{RC} \quad ; 1^{\text{st}}\text{-order differential eq.}$$



$$v_c(t) = V_0(1 - e^{-t/\tau})$$

$$t = 0 \quad v_c(t) = 0$$

$$t = \infty \quad v_c(t) = V_0$$

Lect. 3: Review of Basic Circuits (2)

Special case: sinusoidal steady-state

Assume $v_{in}(t) = V_{in} e^{j\omega t}$

In linear circuit, frequency does not change.

Only magnitude and phase change.

$$\therefore v_c(t) = V_c e^{j\omega t} \quad (V_{in}, V_c: \text{phasors})$$

Substituting above into the governing eq.

$$j\omega V_c e^{j\omega t} + \frac{V_c e^{j\omega t}}{RC} = \frac{V_{in} e^{j\omega t}}{RC} \quad V_c (j\omega + \frac{1}{RC}) = \frac{V_{in}}{RC}$$

Lect. 3: Review of Basic Circuits (2)

$$V_c = V_{in} \cdot \frac{1}{RC} \cdot \frac{1}{j\omega + \frac{1}{RC}} = V_{in} \cdot \frac{1}{j\omega RC + 1}$$


$$\therefore v_c(t) = V_{in} \cdot \frac{1}{j\omega RC + 1} \cdot e^{j\omega t} = \frac{1}{j\omega RC + 1} \cdot v_{in}(t)$$

→ $v_c(t)$ experiences magnitude and phase change from $v_{in}(t)$

$$\text{Our interest: } \left| \frac{1}{j\omega RC + 1} \right|, \angle \frac{1}{j\omega RC + 1}$$

Lect. 3: Review of Basic Circuits (2)

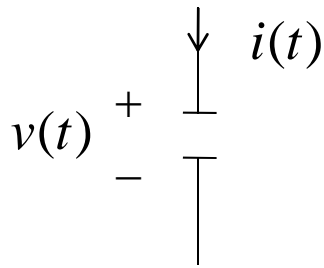
In sinusoidal steady-state,
we can define impedance, $V(\omega) / I(\omega)$, for any circuit element



$$v(t) = Ve^{j\omega t}$$

$$i(t) = Ie^{j\omega t} = C \frac{dv(t)}{dt} = Cj\omega Ve^{j\omega t}$$

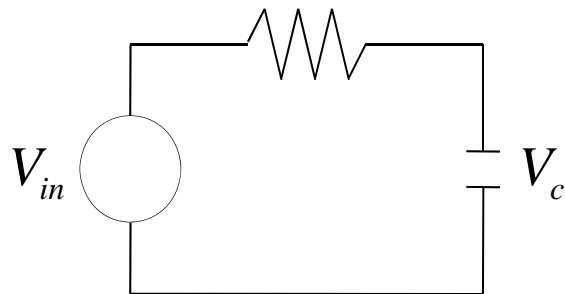
$$\therefore \frac{V}{I} = Z(\omega) = \frac{1}{j\omega C}$$



Using voltage divider,


$$\frac{V_c}{V_{in}} = \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} = \frac{1}{1 + j\omega RC}$$

Lect. 3: Review of Basic Circuits (2)

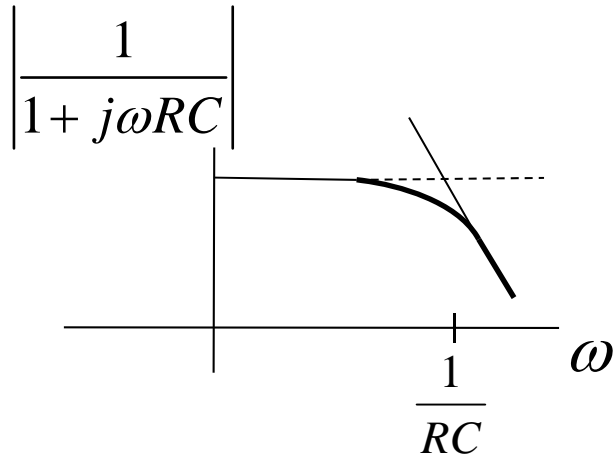

$$\omega \ll 1 \quad || \sim 1$$

$$\omega \gg 1 \quad || \sim \frac{1}{\omega RC}$$

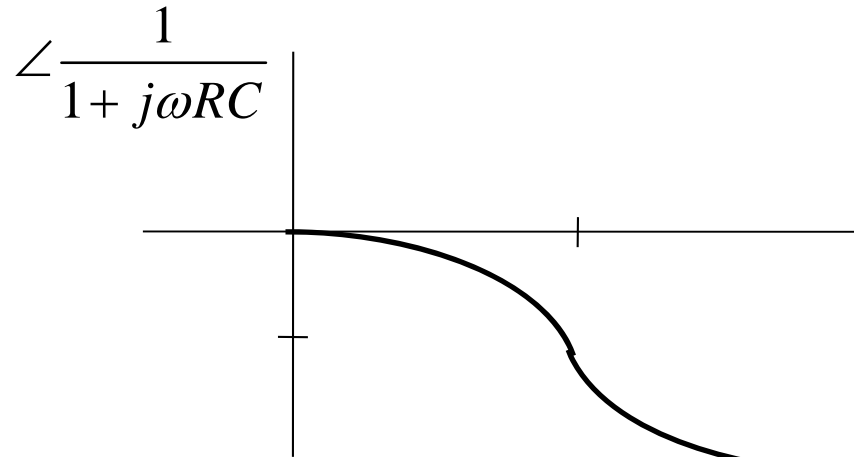

$$\omega \ll 1 \quad \angle \sim 0$$

$$\omega = \frac{1}{RC} \quad \frac{V_c}{V_{in}} = \frac{1}{j+1} \quad \angle = -45^\circ$$

$$\omega \gg 1 \quad \frac{V_c}{V_{in}} \sim \frac{1}{j\omega} \quad \angle \sim -90^\circ$$

Lect. 3: Review of Basic Circuits (2)

Homework: (1) Determine $v_L(t)$ in the RL circuit below. $v_{in}(t)$ is shown below.

(2) Plot $\left| \frac{V_L(\omega)}{V_{in}(\omega)} \right|$ and $\angle \frac{V_L(\omega)}{V_{in}(\omega)}$.

