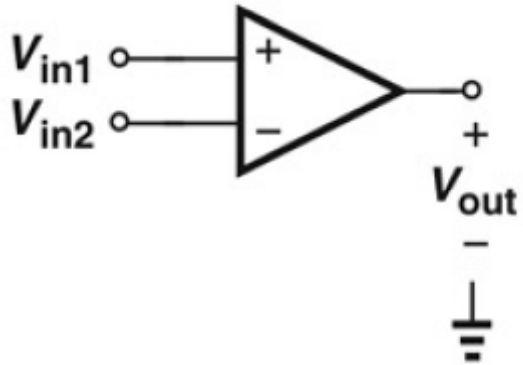



Lect. 4: Ideal Operational Amplifiers (Razavi 8.1-8.3)



Operational amplifier (Op Amp)

- One of the most widely used electronic circuit
- Characteristics
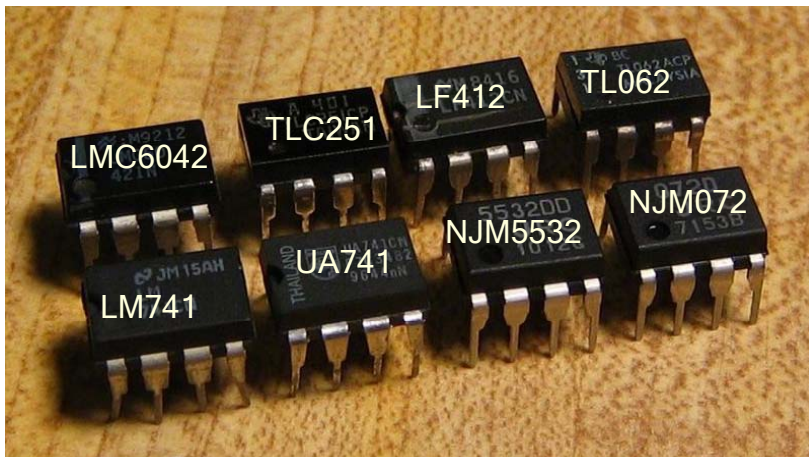
$$V_{out} = A_v(V_{in1} - V_{in2}) \text{ with very large } A_v$$




Input resistance R_{in1} and R_{in2} very large

→ Assumed infinite

→ No currents into +, - input

Lect. 4: Ideal Operational Amplifiers

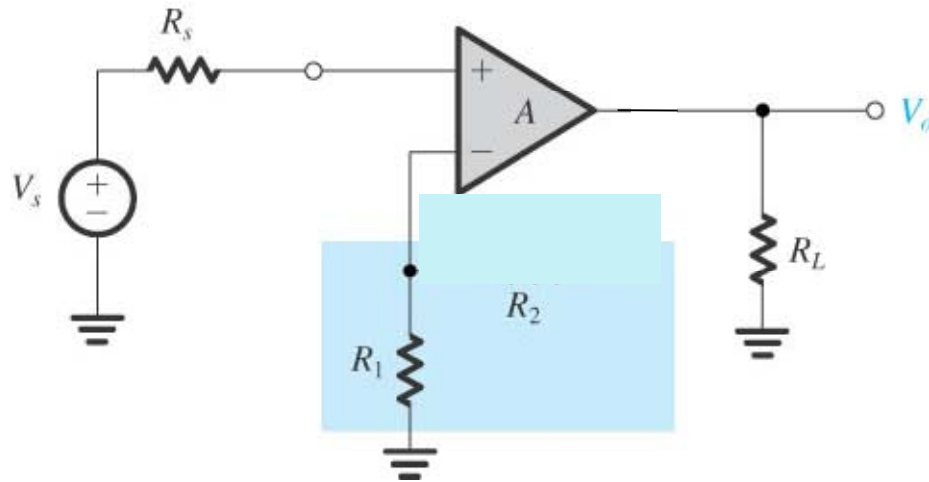

$$V_o = A_v(V_s - 0)$$

With feedback

$$V_o = A_v \left(V_s - V_o \cdot \frac{R_1}{R_1 + R_2} \right)$$


$$V_o \left(1 + \frac{A_v R_1}{R_1 + R_2} \right) = A_v V_s$$

$$\therefore \frac{V_o}{V_s} = \frac{A_v}{1 + \frac{A_v R_1}{R_1 + R_2}} \sim \frac{R_1 + R_2}{R_1}$$

No dependence on A_v , R_L

(Closed-loop gain)

Lect. 4: Ideal Operational Amplifiers

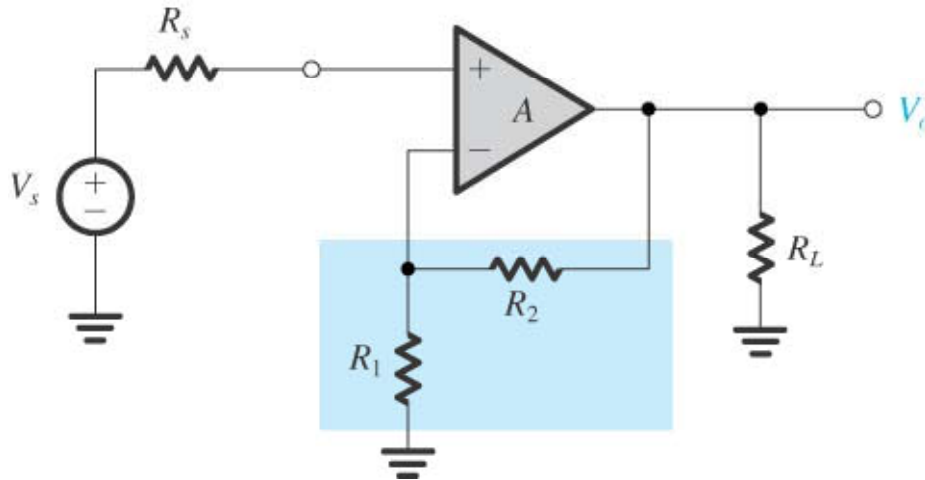

$$\frac{V_o}{V_s} = \frac{R_1 + R_2}{R_1}$$

The same result can be obtained by assuming $V^+ = V^-$ (Virtual Short)

$$V_s = V_o \frac{R_1}{R_1 + R_2}$$

→ Feedback tries to maintain $V^+ = V^-$


$$\therefore \frac{V_o}{V_s} = \frac{R_1 + R_2}{R_1}$$

Use virtual short condition for Op-Amp analysis!

→ Ideal Op-Amp analysis

Lect. 4: Ideal Operational Amplifiers


What good is it?

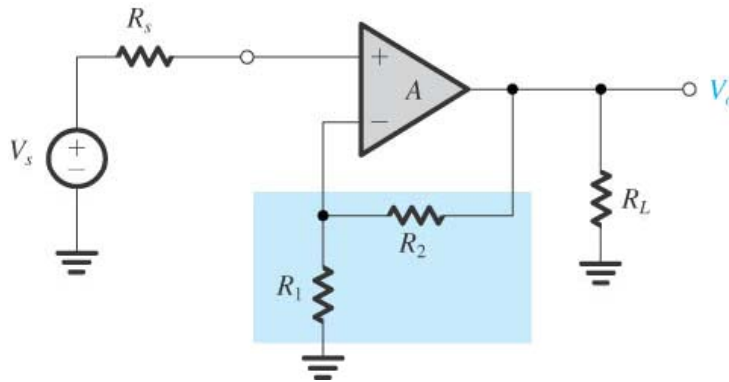

$$\frac{V_o}{V_s} = \frac{R_1 + R_2}{R_1} \quad \text{Voltage amplifier}$$

- Same gain regardless of R_L
- Gain is stable and can be easily changed


Voltage amplifier with negative gain?

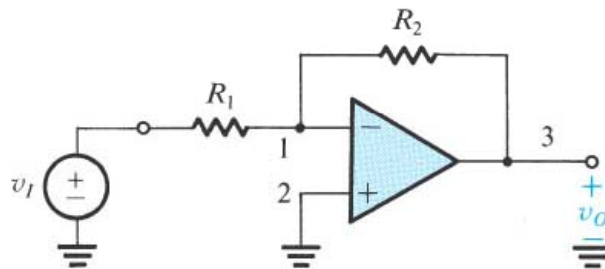

$$V_o = -\frac{R_2}{R_1} V_I$$


Lect. 4: Ideal Operational Amplifiers

Current amplifier

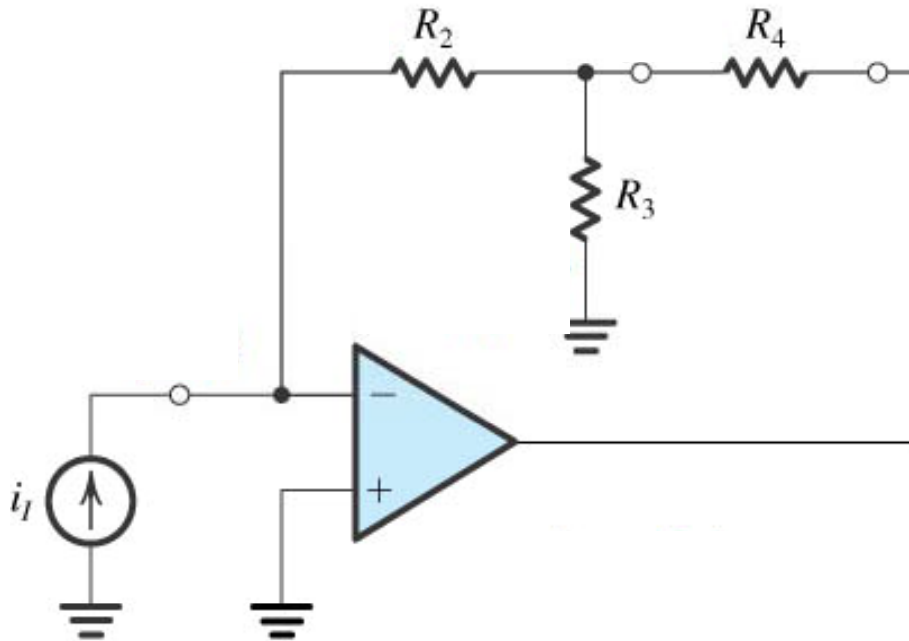


$$A_i = \frac{i_4}{i_i} = \left(1 + \frac{R_2}{R_3}\right)$$

Lect. 4: Ideal Operational Amplifiers

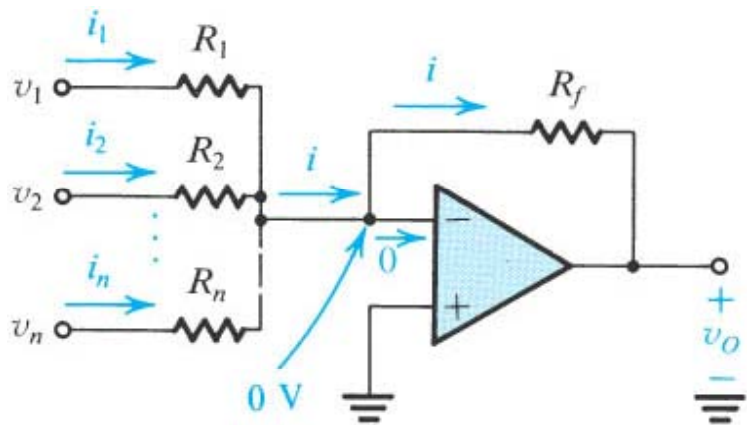


weighted summer (adder)

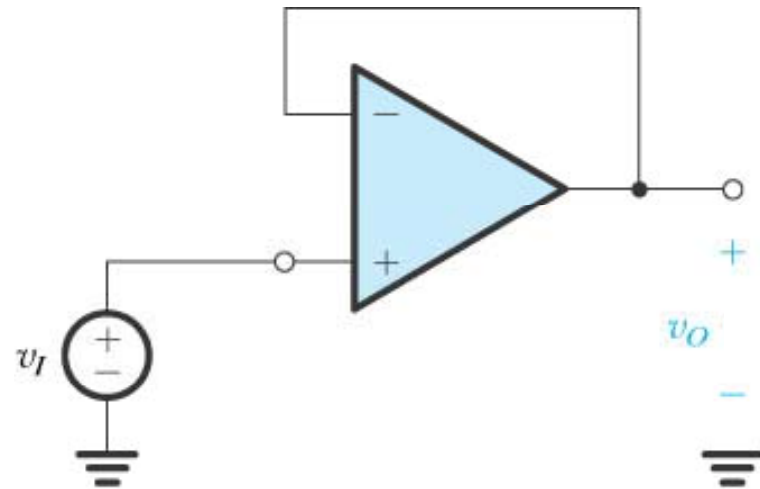

(a)

voltage buffer

Lect. 4: Ideal Operational Amplifiers

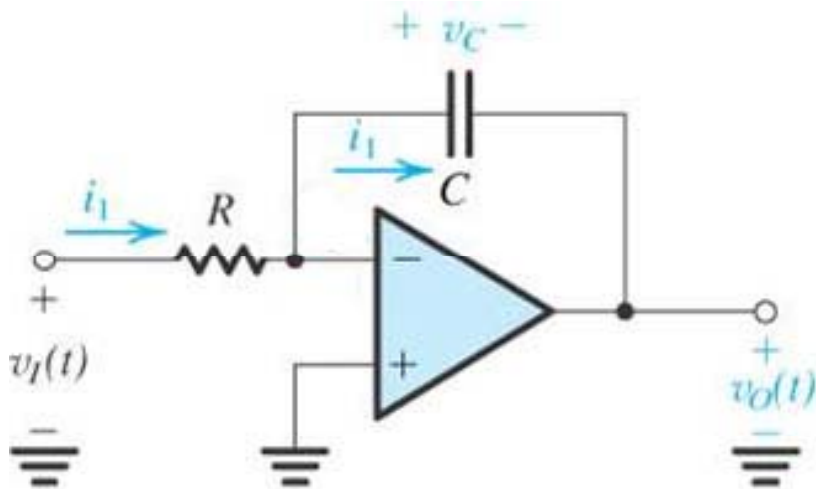

$$C \frac{dv_o(t)}{dt} = -\frac{v_i(t)}{R}$$

$$v_o(t) - v_o(t=0) = -\frac{1}{RC} \int_0^t v_i(t) dt$$

Integrator

Differentiator?

Op amps are used for many analog signal processing applications!

What is inside op amp? Transistor circuits!

What are transistors?

Lect. 4: Ideal Operational Amplifiers

Homework:

- Prob. 8.11 and 8.28 in Razavi
- Due on 9/14 Before Tutorial