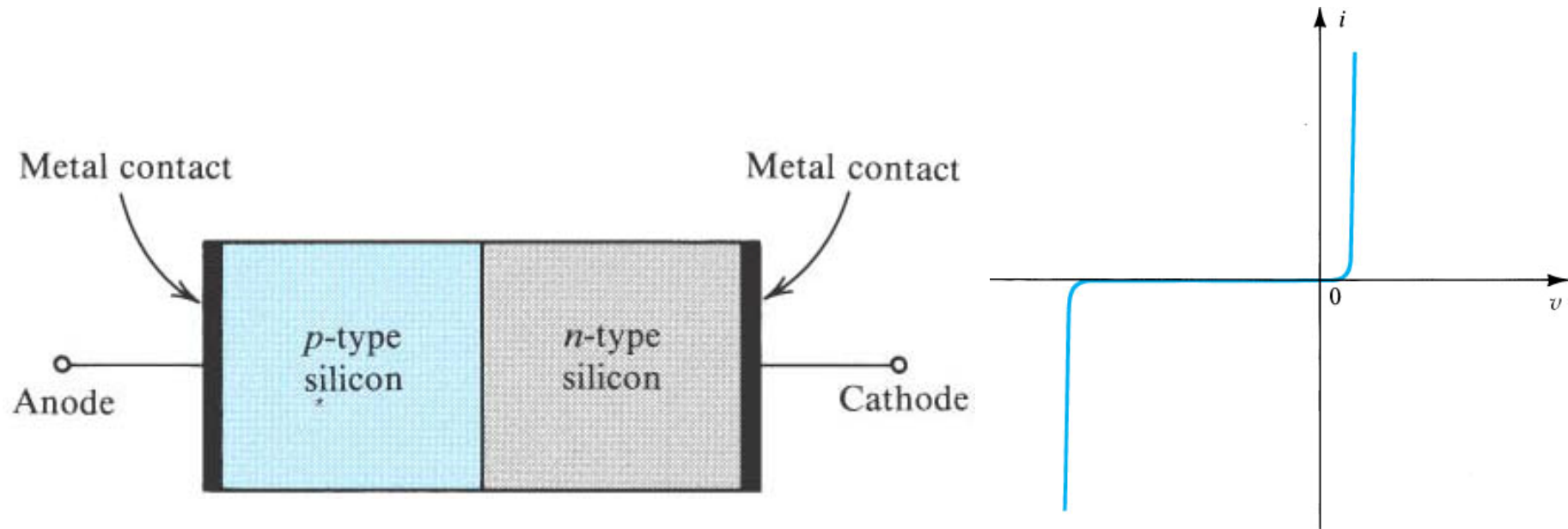


Lect. 5: PN Junction Diode (Razavi 2.2, 3.1)

What is a PN junction diode?




Questions:

Why the I-V characteristics?
What circuit applications?

I-V characteristics

Lect. 5: PN Junction Diode

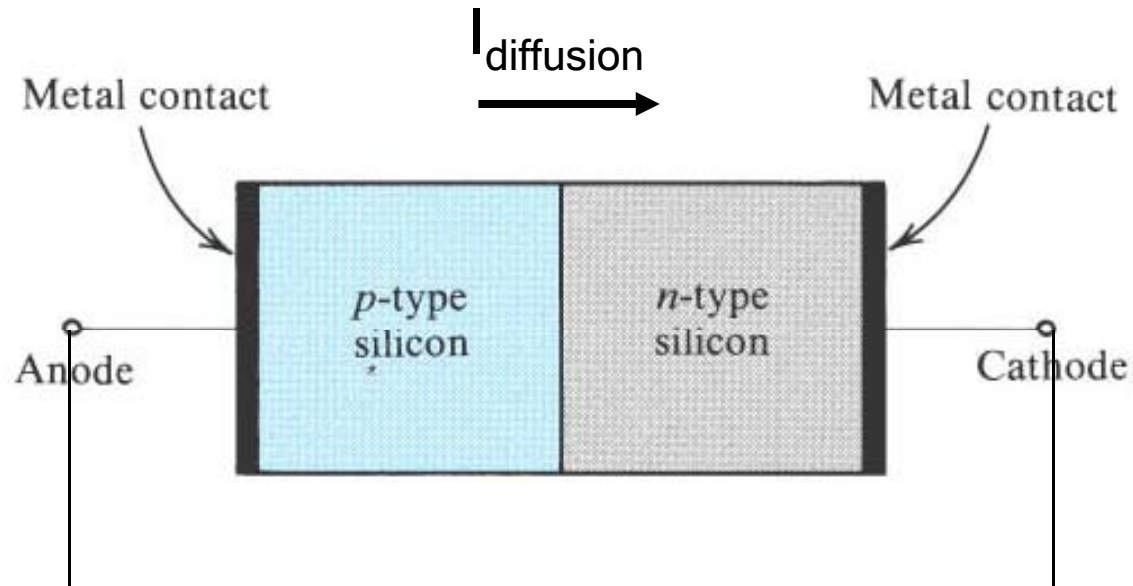
Do currents flow when two terminals are shorted?



Diffusion of holes (P to N) and electrons (N to P)

→ Diffusion currents (due to diffusion) to the right

Lect. 5: PN Junction Diode

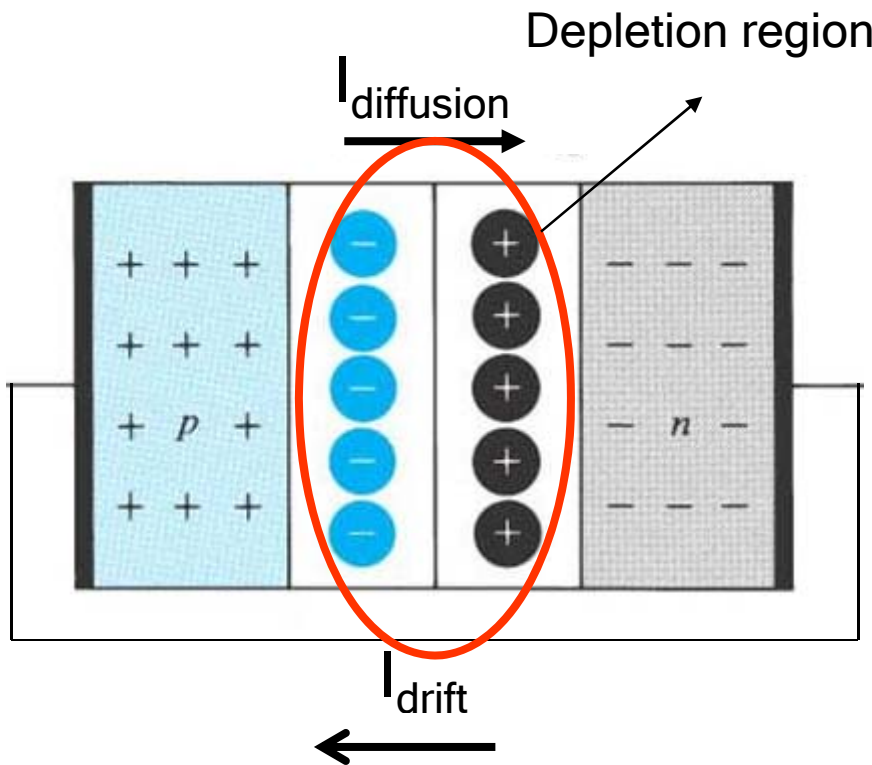

Diffusion causes depletion of carriers
→ depletion region

Depletion layer provides built-in E-field

Built-in E-field produces drift current

$$I_{\text{total}} = I_{\text{diffusion}} + I_{\text{drift}} = 0$$

No currents due to balance between diffusion and drift currents

Lect. 5: PN Junction Diode

With bias voltage,

Balance between diffusion and drift currents is broken.

$V > 0$: Forward Bias


$$I_{\text{diffusion}} \gg I_{\text{drift}}$$

→ $I_D > 0$, very large currents if V is sufficiently large

$V < 0$: Reverse Bias


$$I_{\text{diffusion}} < I_{\text{drift}}$$

→ $I_D < 0$, but very little currents until breakdown

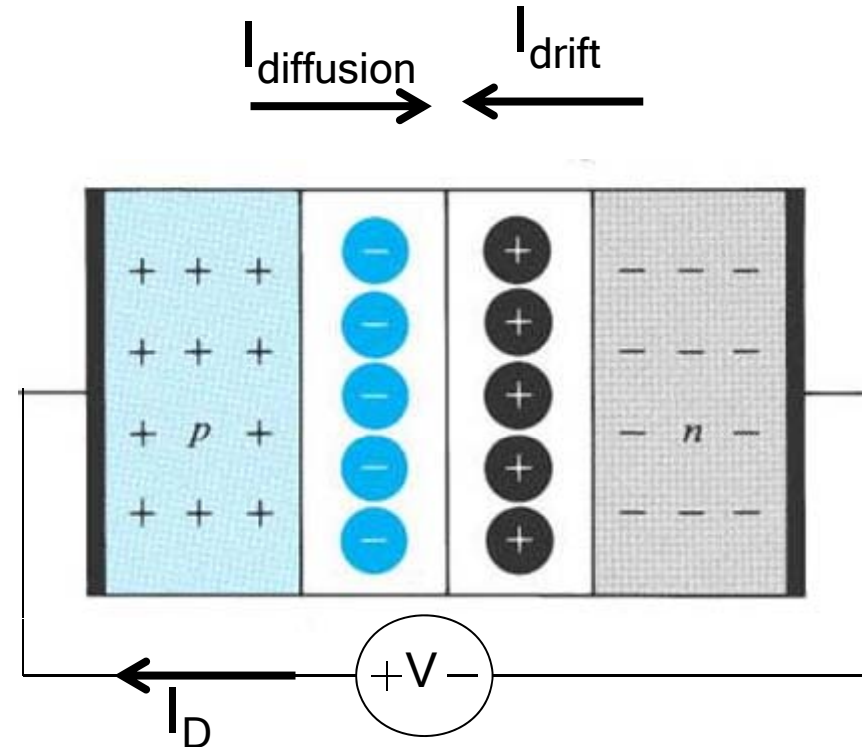


Lect. 5: PN Junction Diode

With more detailed analyses

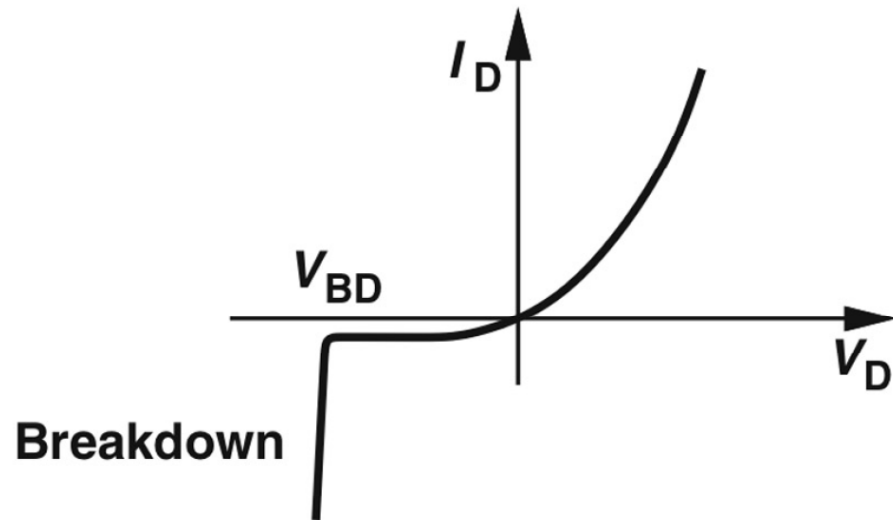

Breakdown

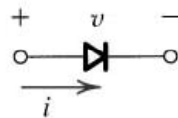

$$i = I_S [\exp(v/V_T) - 1]$$

($v > -V_{BD}$)

I_S : saturation current
usually very small


V_T : thermal voltage

$$\left(= \frac{kT}{q} \sim 25\text{mV at Room Temp.} \right)$$

V_{BD} : Breakdown voltage

Lect. 5: PN Junction Diode

Diode circuit analysis

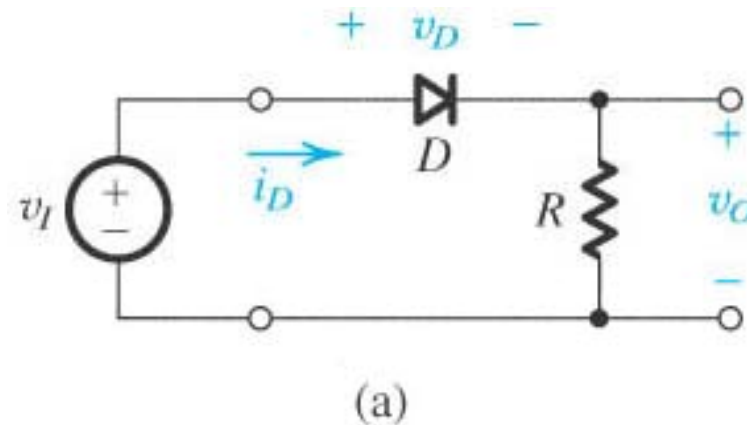

What are v_D , i_D , v_O as function of v_I ?

Lect. 5: PN Junction Diode


Node analysis: 3 unknowns

$$v_I - v_D - v_O = 0$$

$$v_O = i_D \cdot R$$

$$i_D = I_S [\exp(v_D / V_T) - 1]$$

(Assume V_{BD} is very large)

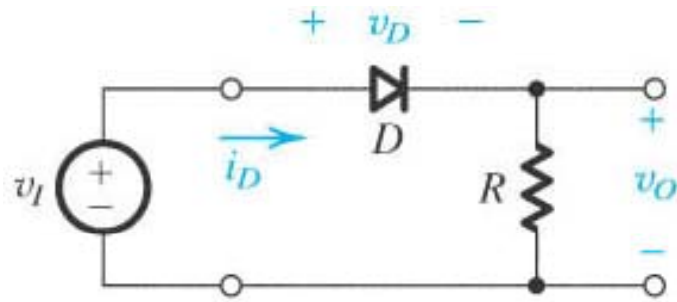


(a)

Can we solve it?

Computers can → SPICE

Lect. 5: PN Junction Diode



Graphical analysis (load line analysis)

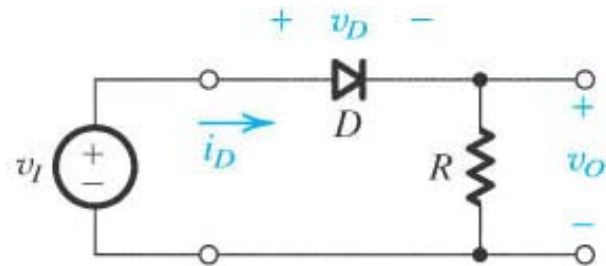

(a)


$$i_D = \frac{v_O}{R} = \frac{v_I - v_D}{R}$$

$$i_D = I_S [\exp(v_D/V_T) - 1]$$

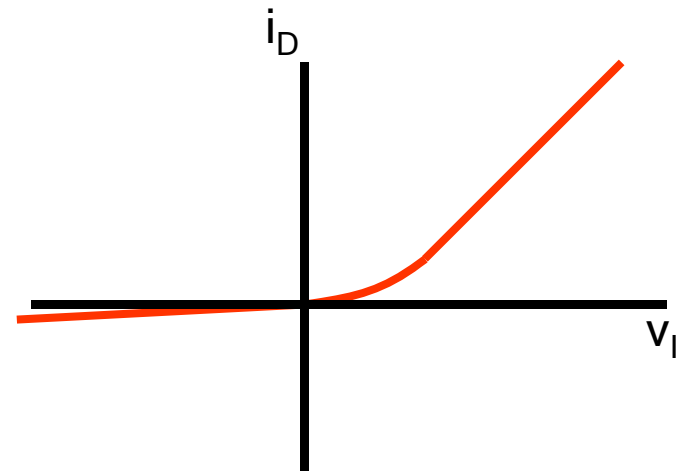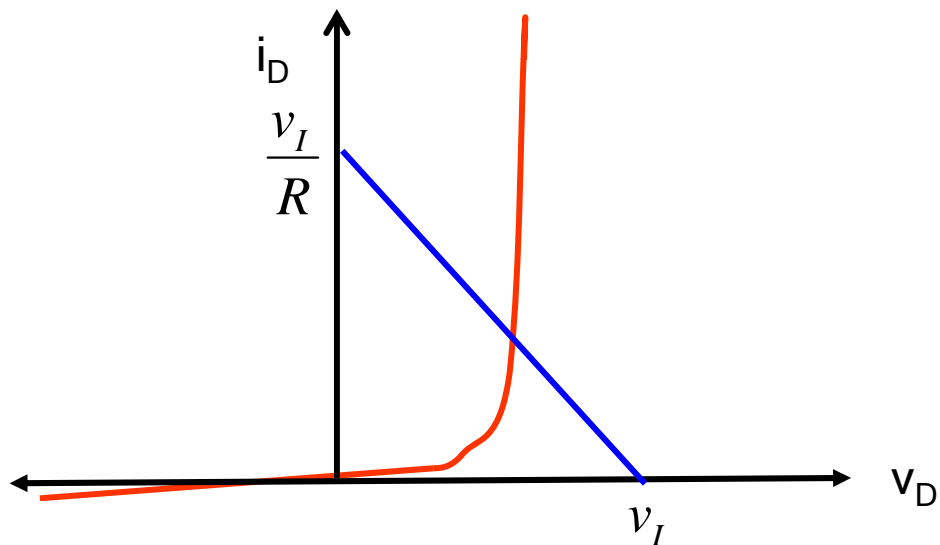

Graph for every circuit problem?

Lect. 5: PN Junction Diode

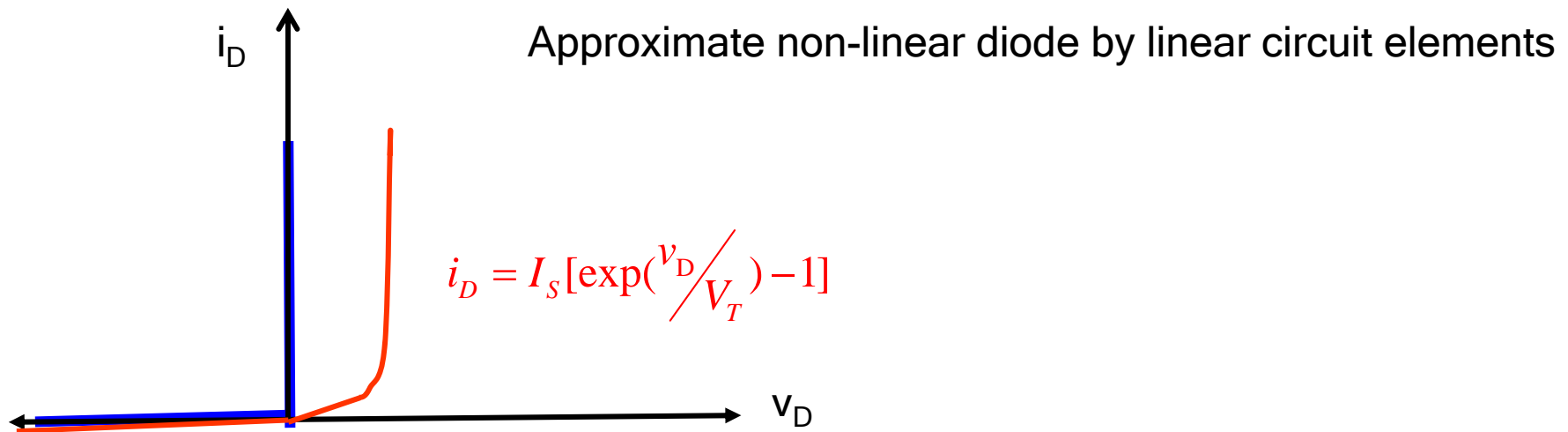


Diode is either On (Short) or Off (Open)

If $i_D > 0$ (Diode On), $v_D = 0$ (short)

If $v_D < 0$ (Diode Off), $i_D = 0$ (open)

→ Ideal diode model

Lect. 5: PN Junction Diode

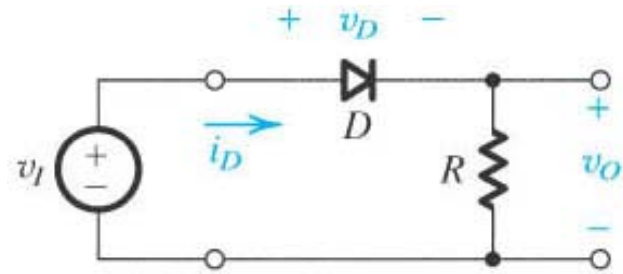

(a)

If $i_D > 0$ (Diode On), $v_D = 0$ (short)



If $v_D < 0$ (Diode Off), $i_D = 0$ (open)

Assume diode on, $v_D = 0$, $v_O = v_I$

$$i_D = \frac{v_I}{R} > 0 \quad \therefore v_I > 0$$

Assume diode off, $i_D = 0$ (open) and $v_D < 0$

$$v_D = v_I - v_O < 0 \quad \therefore v_I < 0$$

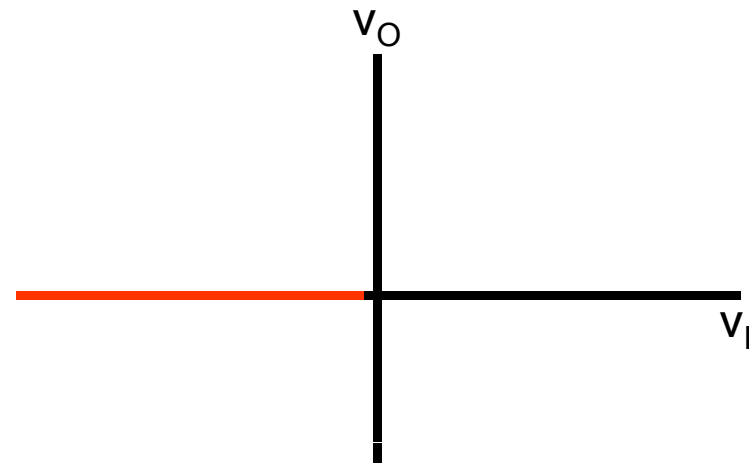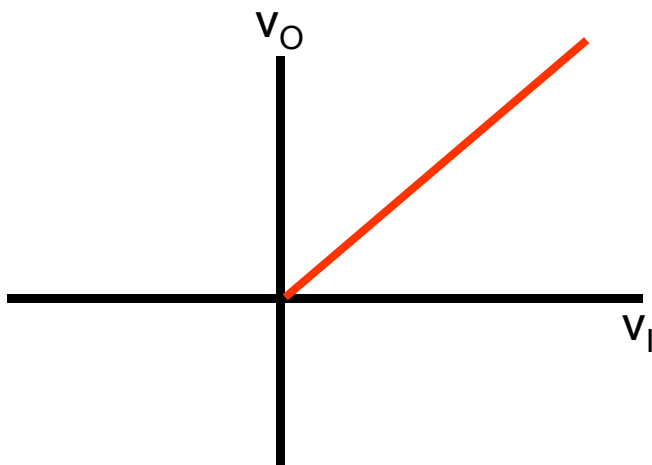


Lect. 5: PN Junction Diode

If $i_D > 0$ (Diode On), $v_D = 0$ (short)

If $v_D < 0$ (Diode Off), $i_D = 0$ (open)


Determine I, V using the ideal diode model

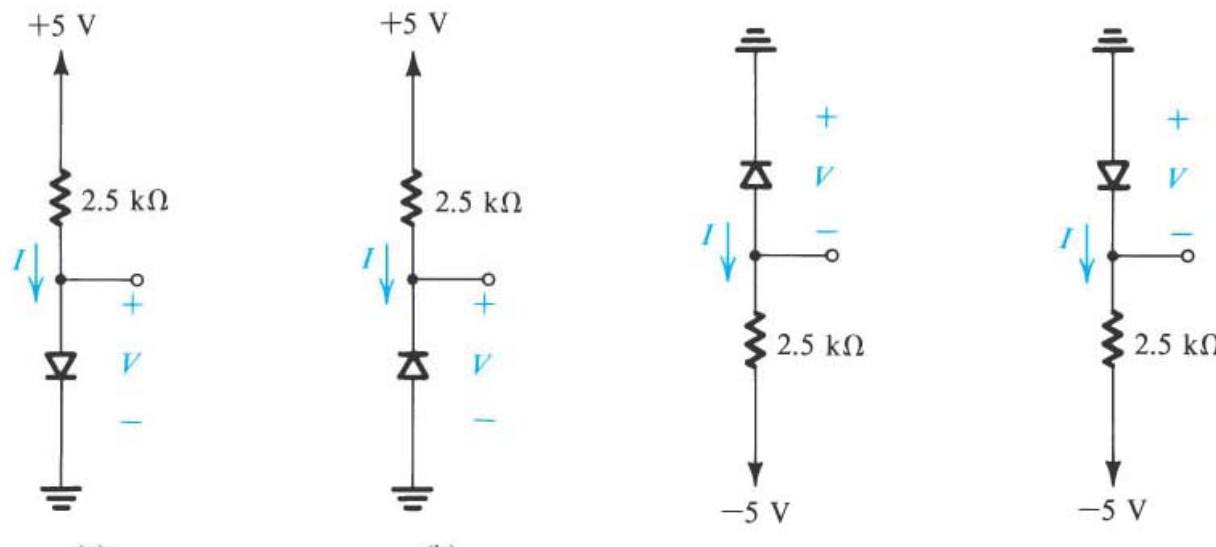

Lect. 5: PN Junction Diode

If $i_D > 0$ (Diode On), $v_D = 0$ (short)

If $v_D < 0$ (Diode Off), $i_D = 0$ (open)

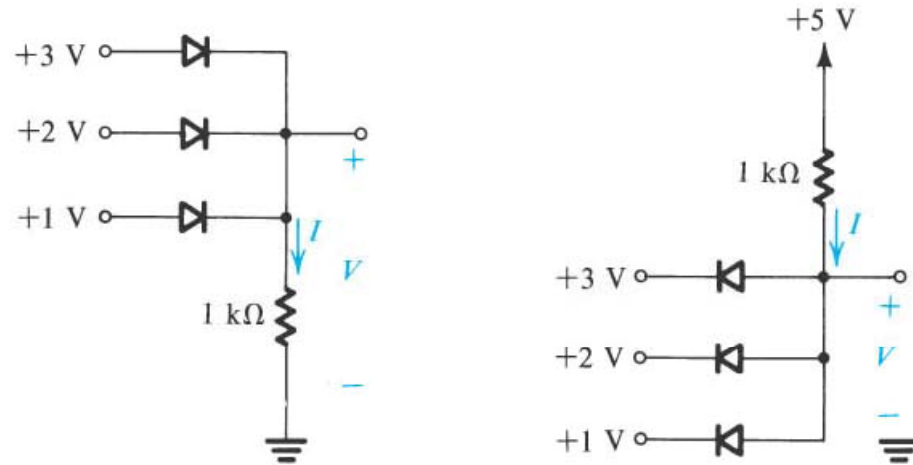

Lect. 5: PN Junction Diode

Homework (Due on 9/14 before tutorial):

- Prob. 3.9 in Razabi