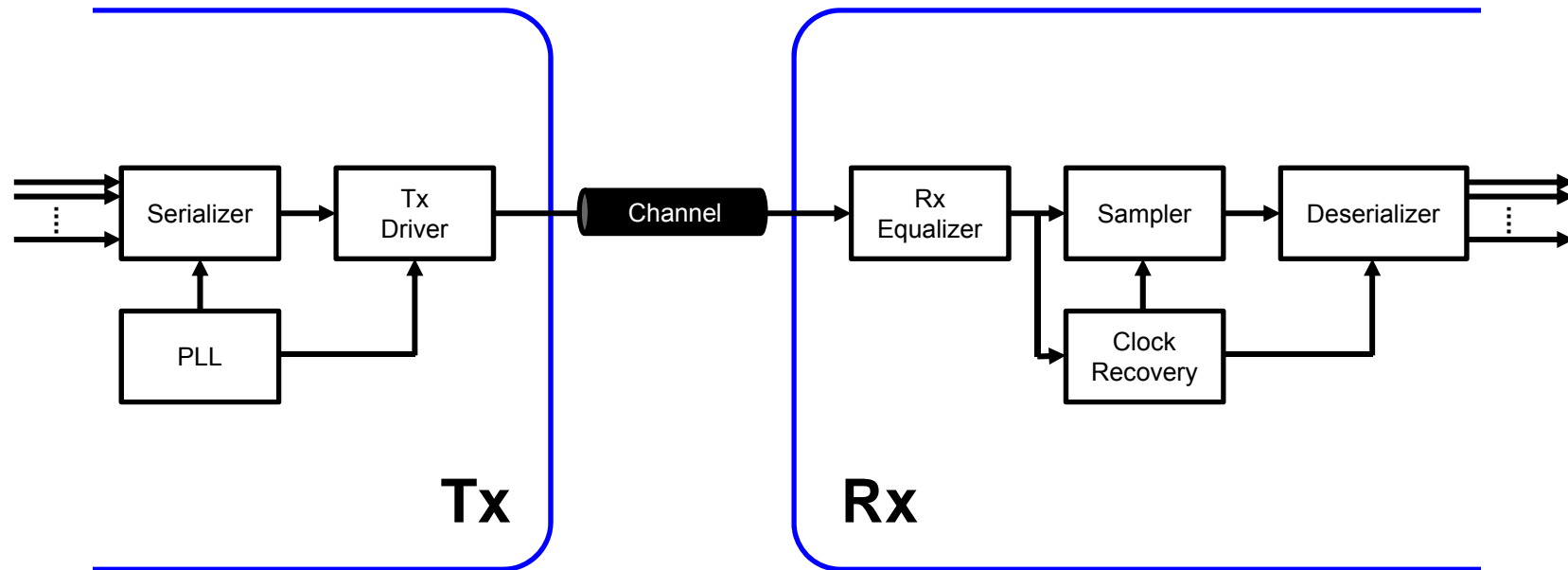


High-speed Serial Interface

Lect. 14 – Clock and Data Recovery (Continuous-mode CDR)



Block diagram

- Where are we today?



Why CDR?

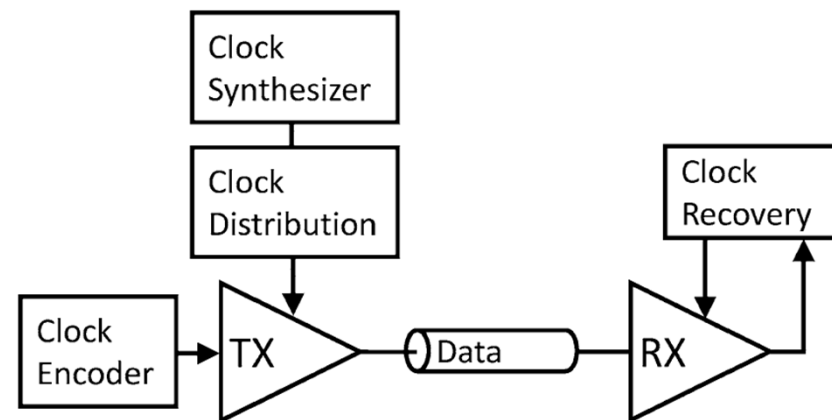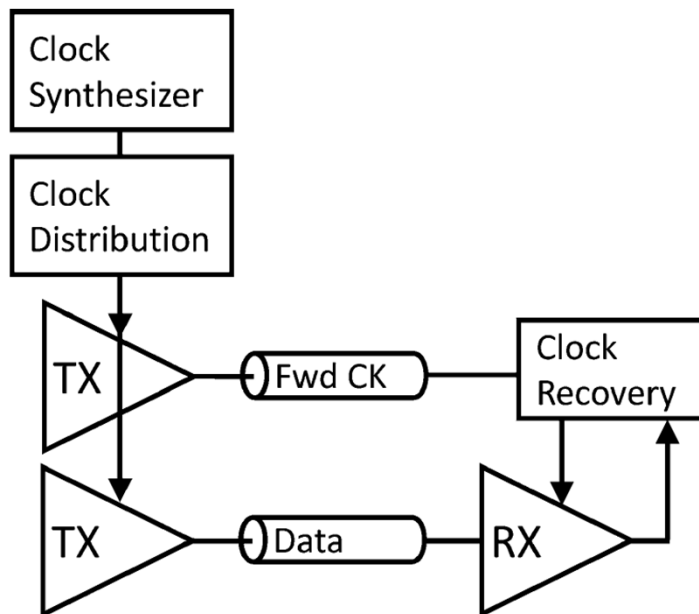
- Clocking architecture for interfaces
 - Forwarded clocking vs. embedded clocking



Bryan Casper - "Clocking Analysis, Implementation and Measurement Techniques for High-Speed Data Links—A Tutorial", 2009 TCAS1



Why CDR?

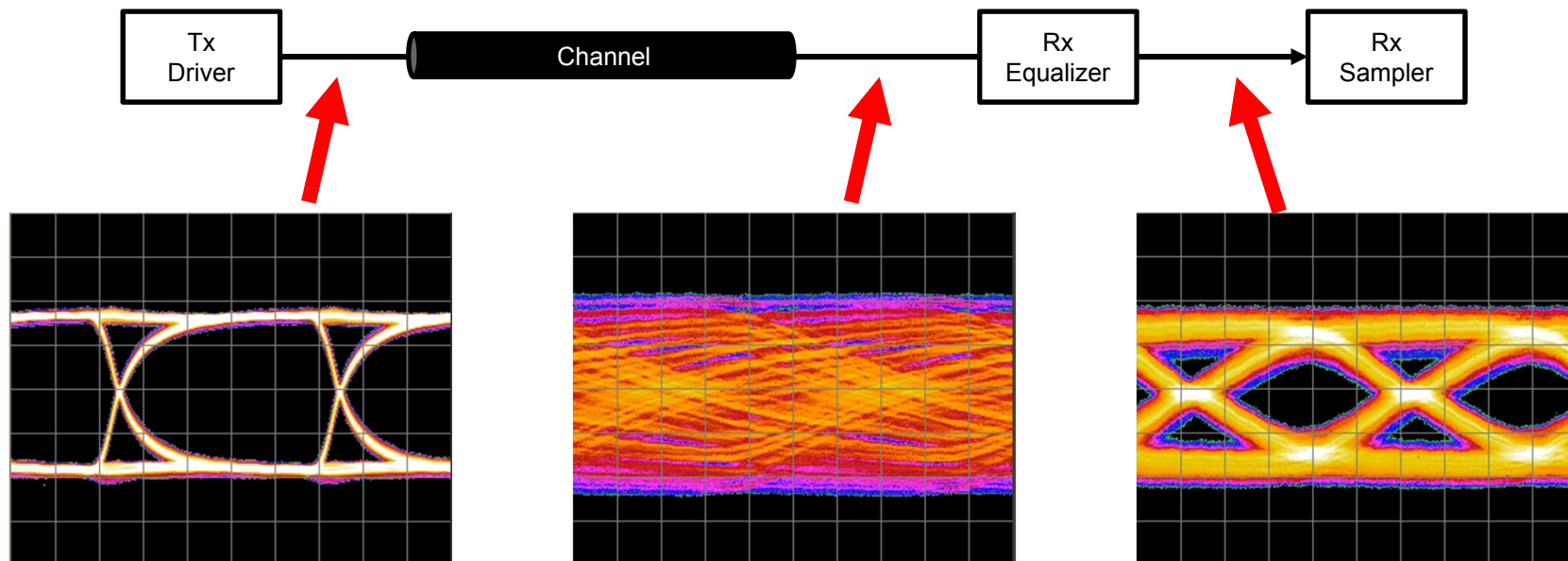- High-frequency loss in channel causes ISI \rightarrow closed eye
- Equalizer cannot fully open the eye
- Noises during transmission




Why CDR?

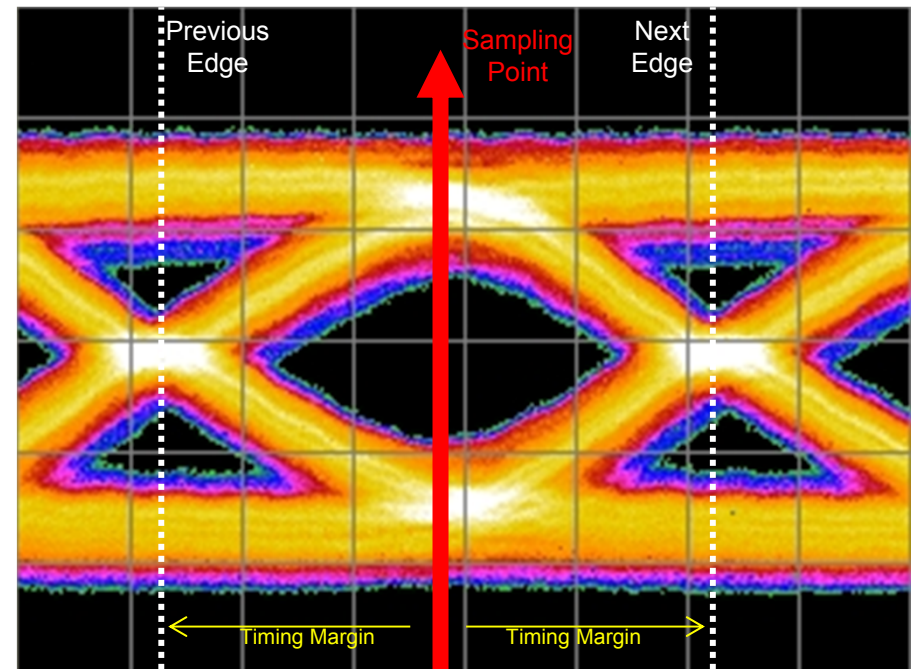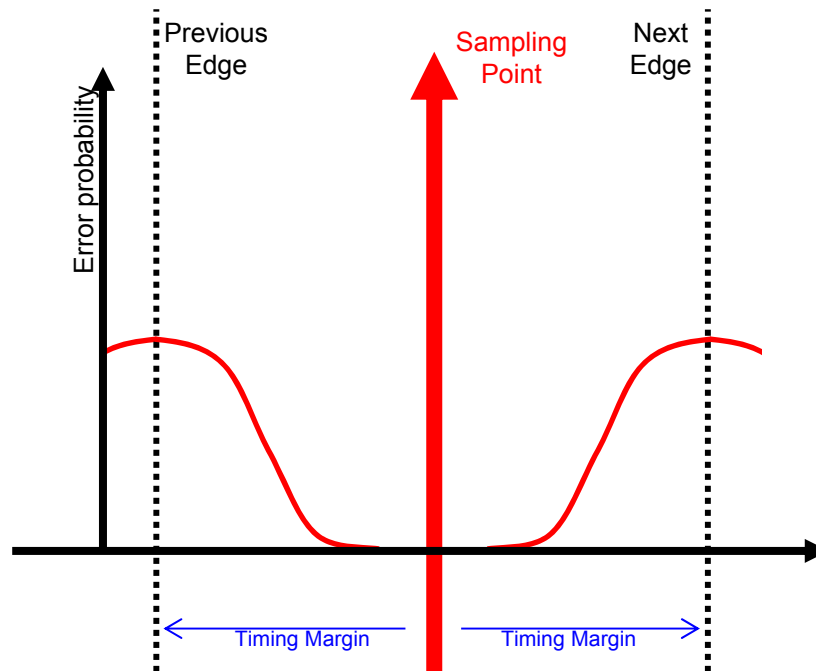- To find the best sampling point
 - Best sampling point for lowest error probability
 - Depends on noise (jitter) profile




Edge-tracking

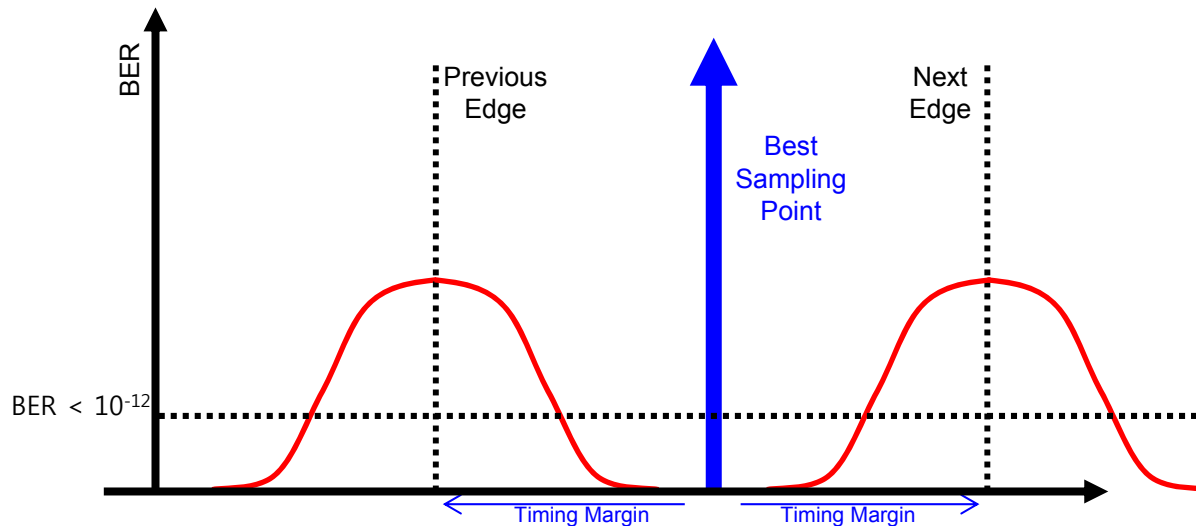- Difficult to find the best sampling point
 - Target BER for HIS: (often) $< 10^{-12}$
 - BER $< 10^{-12}$ takes long measurement time
 - For 1Gb/s, 1000s > 15 min




Edge-tracking

 - Tracking edges is easier
 - Phase information from transition edges
 - Best sampling point is determined from the edges → middle of two adjacent edges
 - Continuous identical data (CID) sequence affects CDR performance
 - For many applications, balanced coding scheme is employed to guarantee minimum transition
 - For 8b10b coded signaling, probability of transition ~ 50%.



PLL-based CDR

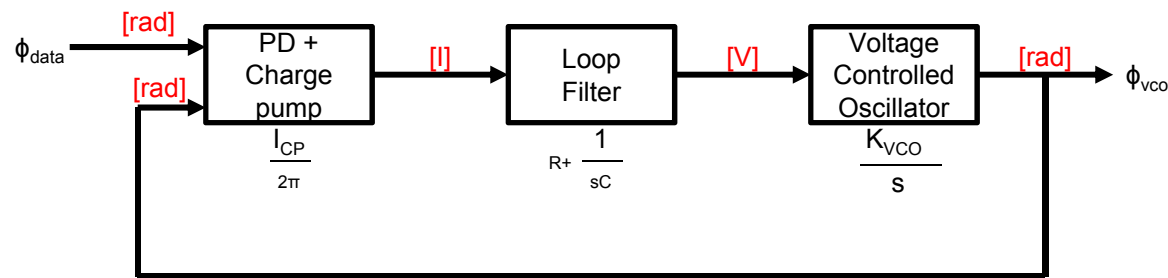- PLL-based edge-tracking CDR
 - Based on PLL with no divider



- Difference in PD
 - PLL: Reference clock
 - CDR: Data
- PD should detect data transition and phase difference between data and clock


Phase detector

- Linear vs. bang-bang
 - Linear phase detector produces output proportional to phase difference → PLL-like behavior
 - Bang-bang phase detector produces only UP or DN signal corresponding to the sign of phase error.

Phase detector

- XOR PD

 
- Retimed data (B) compared with input data
- Phase comparison results produced only when there is data transition
- Duration of Y: Phase error
- However, output (Y) shows only positive value
- Average value of Y depends on transition density
- Reference pulse with fixed duration when data transition?




Razavi-"Challenges in the Design of High-Speed Clock and Data Recovery Circuits" IEEE Communication magazine 2002

Phase detector

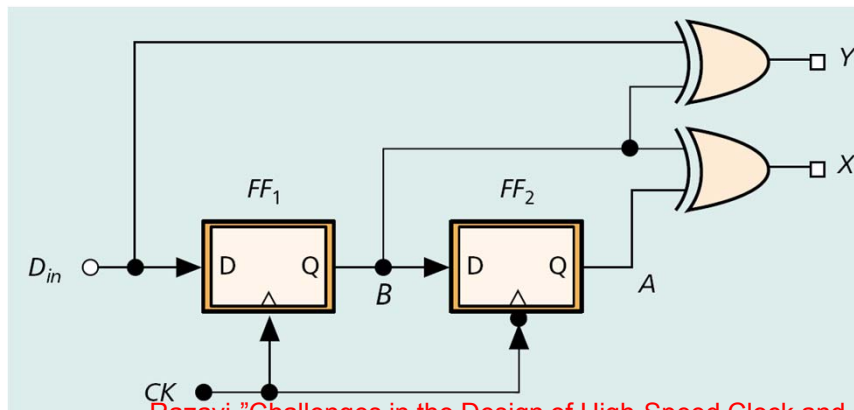- Hogge PD
 - Y: Identical to XOR PD output
 - X: Reference signal
 - Duration of half the period when there is data transition
 - Y used as Up and X as Dn for charge pump
 - CK slows down until X and Y have the same duration
 - A, B: Recovered data



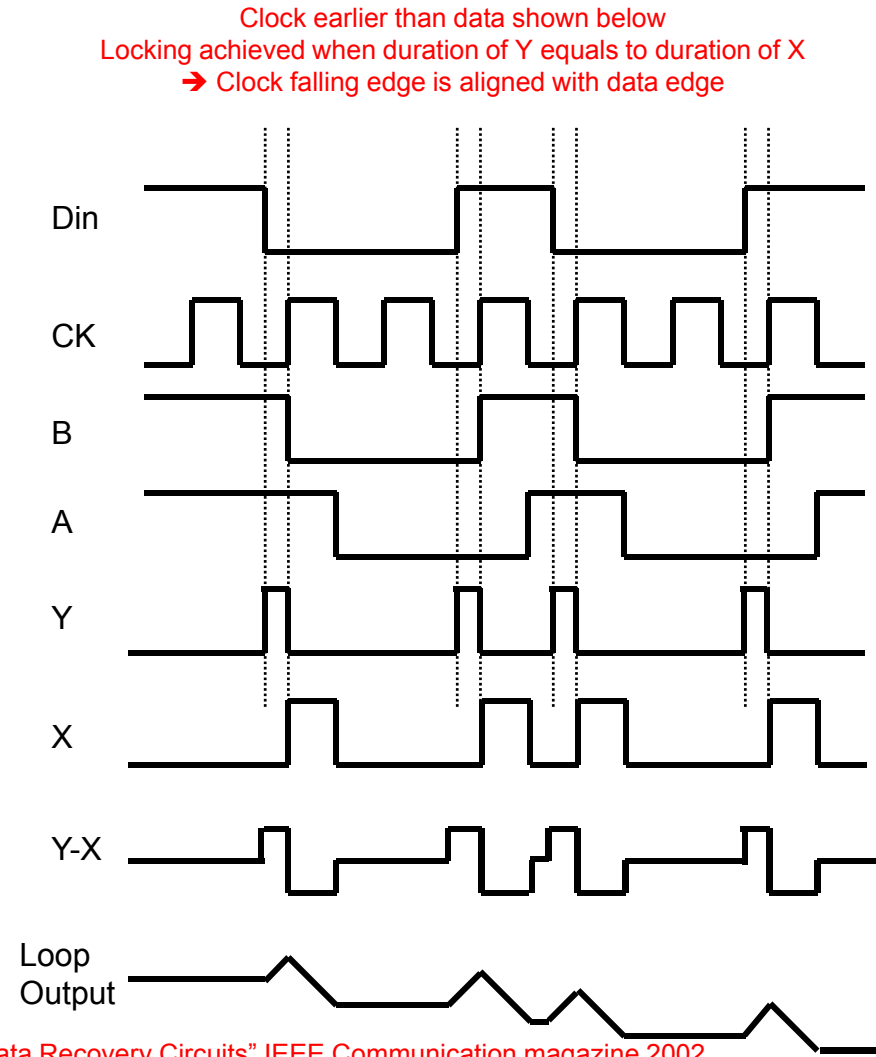Razavi-"Challenges in the Design of High-Speed Clock and Data Recovery Circuits" IEEE Communication magazine 2002




Phase detector

- Limit of linear phase detector
 - Static phase offset
 - Steady-state error in feedback system if open-loop gain is not sufficient
 - Clk-to-Q delay (ΔT) of FF1 results in hardware limited phase offset
 - Y wider by ΔT
 - When locked, charge pump output voltage becomes triangular wave
 - Short pulse generation
 - Pulse width is proportional to phase error.
 - Reference pulse (X) is short (1/2 of data period)
 - With larger phase error, phase error pulse (Y) becomes shorter
 - Distorted pulse shapes in high speed operation

Phase detector

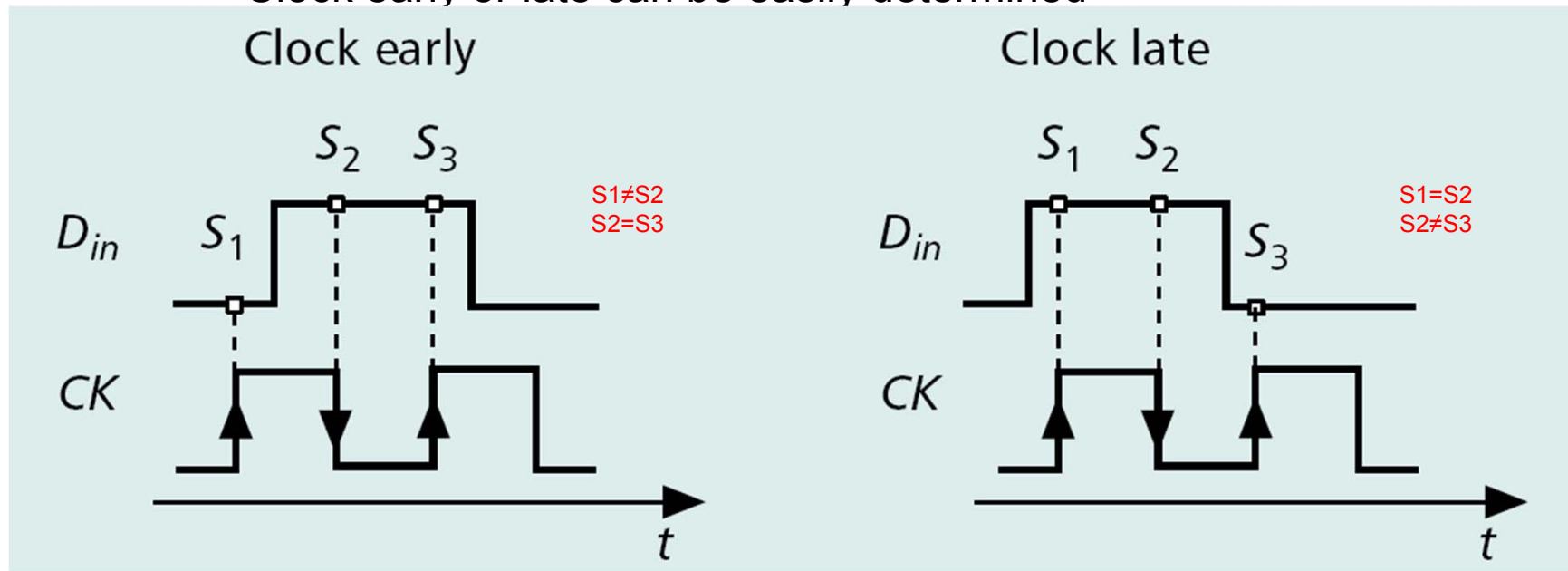
- Bang-bang phase detector
 - Possible to find sign of phase error by 2x-oversampling
 - If two adjacent sampling produces different values, then transition
 - Clock early or late can be easily determined



Razavi-"Challenges in the Design of High-Speed Clock and Data Recovery Circuits" IEEE Communication magazine 2002

Phase detector

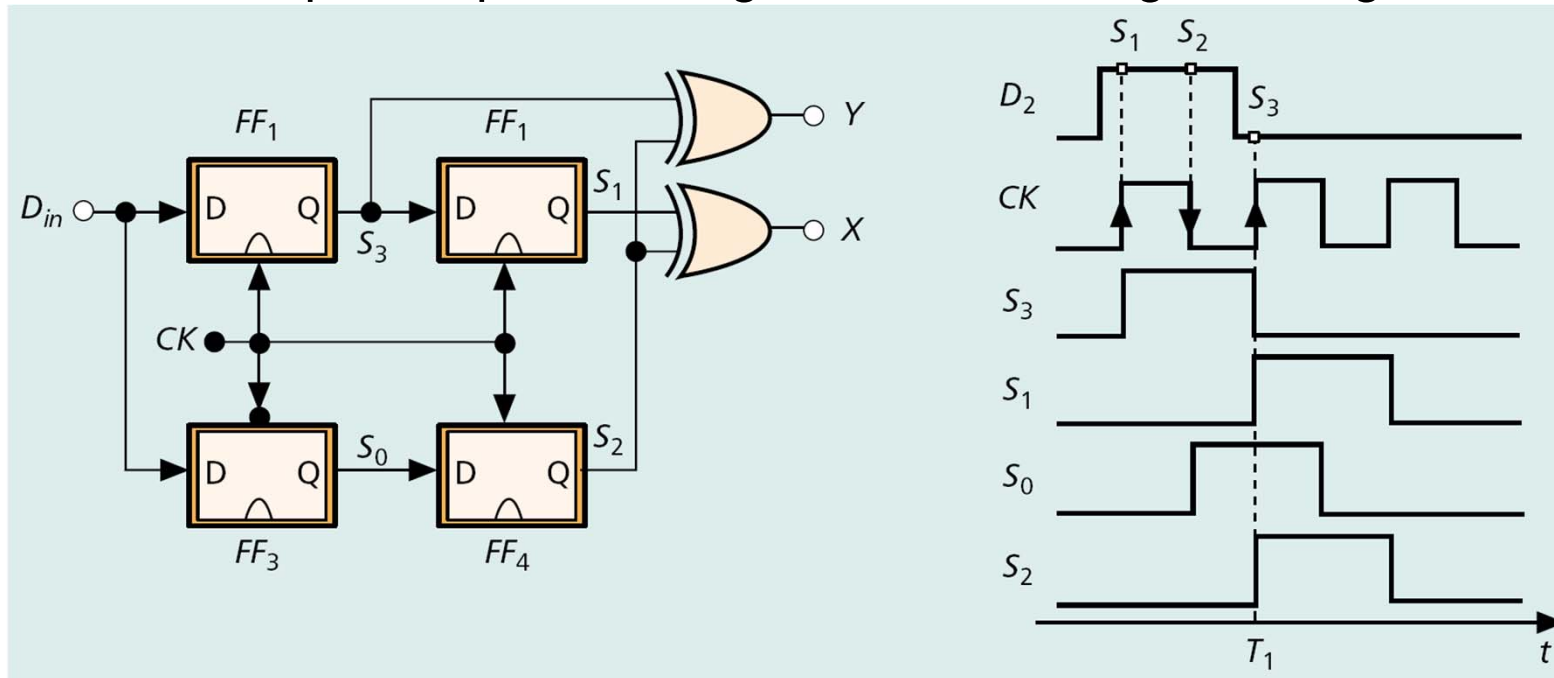- Alexander phase detector
 - FF1 samples at positive edge and FF3 at negative edge




Clock later than data shown above
 At T_1 , $Y = S_2 \text{ XOR } S_3 \rightarrow 1$
 $X = S_1 \text{ XOR } S_2 \rightarrow 0$
 \rightarrow Clock later than data
 Y: UP, X: DN

Phase detector


- Advantage of bang-bang phase detector
 - Up or Down pulse width fixed (only when there is data transition)
 - Duration: Two periods
 - PD gain is ideally infinite around $\Delta\phi = 0$
 - no static phase offset in feedback analysis
- Disadvantage
 - Simple loop analysis not possible with infinite PD gain
 - In reality, input jitter affects PD gain (SP paper)

Reduced sampling rate

 - Reducing sampling rate
 - Half-rate sampling




- Quad-rate sampling

 

Reduced sampling rate


- Quad-rate bang-bang phase detector

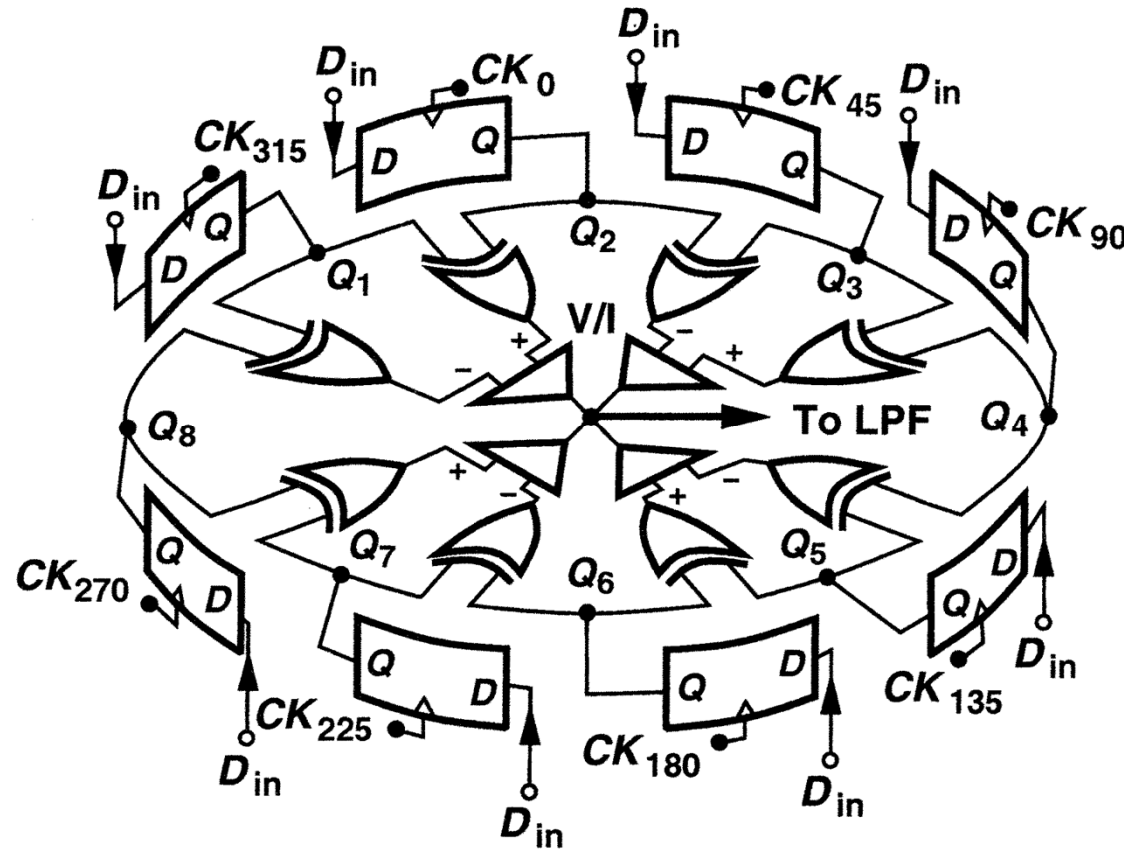

Jri Lee - "A 40-Gb/s Clock and Data Recovery Circuit in 0.18- μ m CMOS Technology" JSSC 2003 (SP)

PI (Phase Interpolator)-Based CDR

- CDR using PI-based phase controller

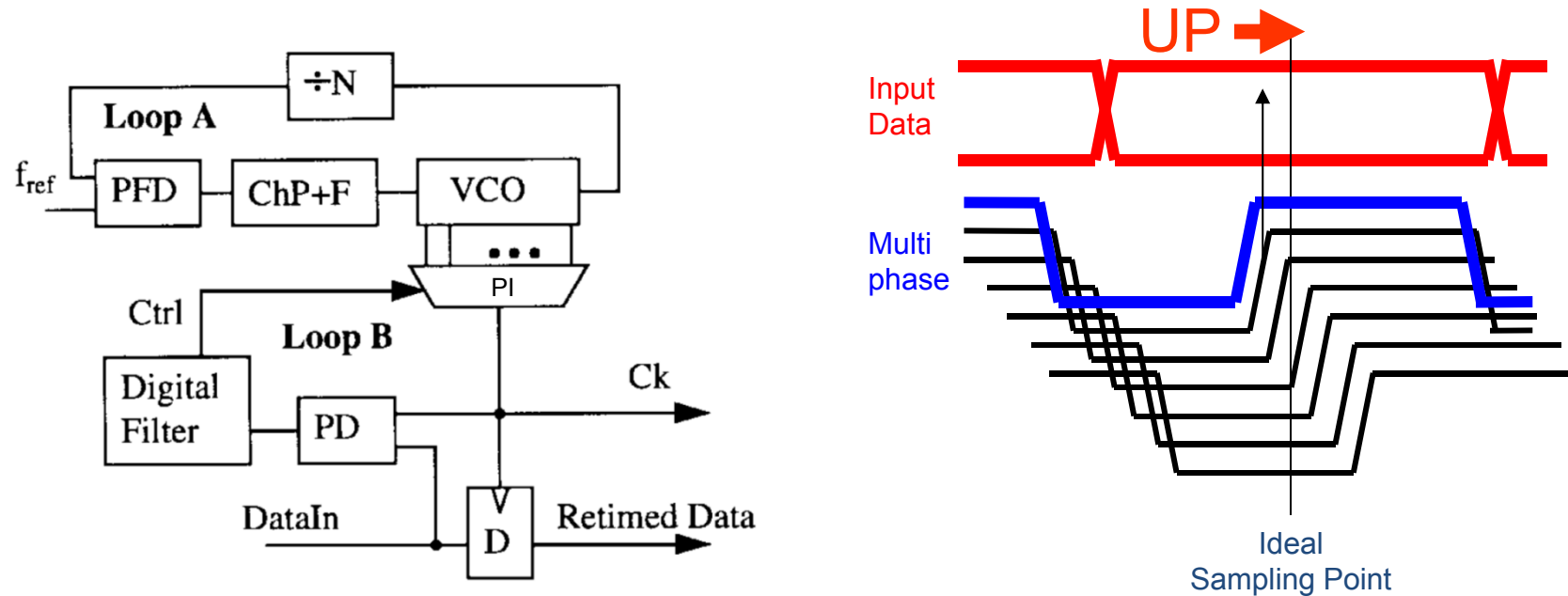

-- Generate the correct phase clock signal with several available from VCO

- Large Bandwidth for Loop A \rightarrow suppress VCO jitter
- Small Bandwidth for Loop B \rightarrow suppress input jitter

Patrik Larsson-" A 2-1600-MHz CMOS Clock Recovery PLL with Low-Vdd Capability", JSSC 1999

Phase controller



- PI-based phase controller

- Phase interpolator produces mid-phase between I/Q input clocks
- Implemented as current-mode summation
- Possible phase range: 90 degs

$$f(t) = \alpha \cdot \cos \omega t + \beta \cdot \sin \omega t$$


$$= \sqrt{\alpha^2 + \beta^2} \cos(\omega t + \phi)$$
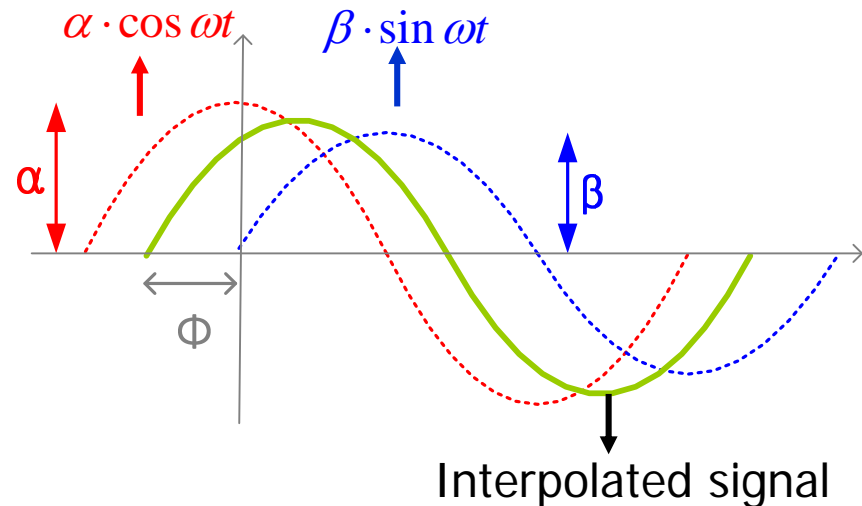 
$$\phi = \tan^{-1}\left(\frac{\beta}{\alpha}\right), \quad \frac{\beta}{\alpha} = \tan \phi$$



Phase controller

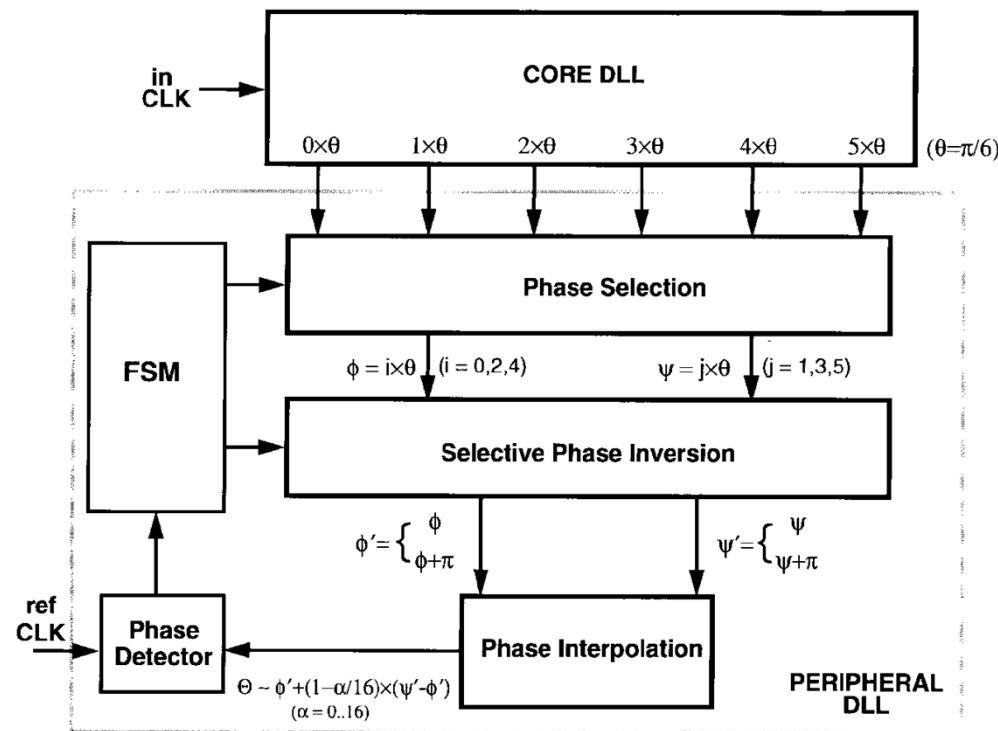
- PI-based phase controller (DLL)
 - Rotating two input clocks, it is possible to generate 360° phase.



Stefanos Sidiropoulos-"A Semidigital Dual Delay-Locked Loop" JSSC 1997
High-Speed Circuits and Systems Lab., Yonsei University

Phase controller


- PI-based phase controller

 


Patrik Larsson-" A 2-1600-MHz CMOS Clock Recovery PLL with Low-V_{dd} Capability", JSSC 1999
High-Speed Circuits and Systems Lab., Yonsei University

Phase controller

 
- PI-based phase controller
 - Linearization of PI output phase




< Schematic of Linear DAC >

 

< Schematic of Non-linear DAC >

 

< Transfer char. of Linear DAC >

 

< Transfer char. of Non-linear DAC >

Patrik Larsson-" A 2-1600-MHz CMOS Clock Recovery PLL with Low-Vdd Capability", JSSC 1999