



Project 1

Design Guide

High-Speed Circuits & Systems Lab.
Dept. of Electrical and Electronic Engineering
Yonsei University


Introduction

The Project is composed of 3-parts

1. Current Mirror Design
2. Single-Stage Differential OTA Design
3. Mirrored OTA with Compensation RC Design

Deadline : Submit hardcopy
until 11:59 PM on Apr. 26, 2015 @ B629


Current Mirror

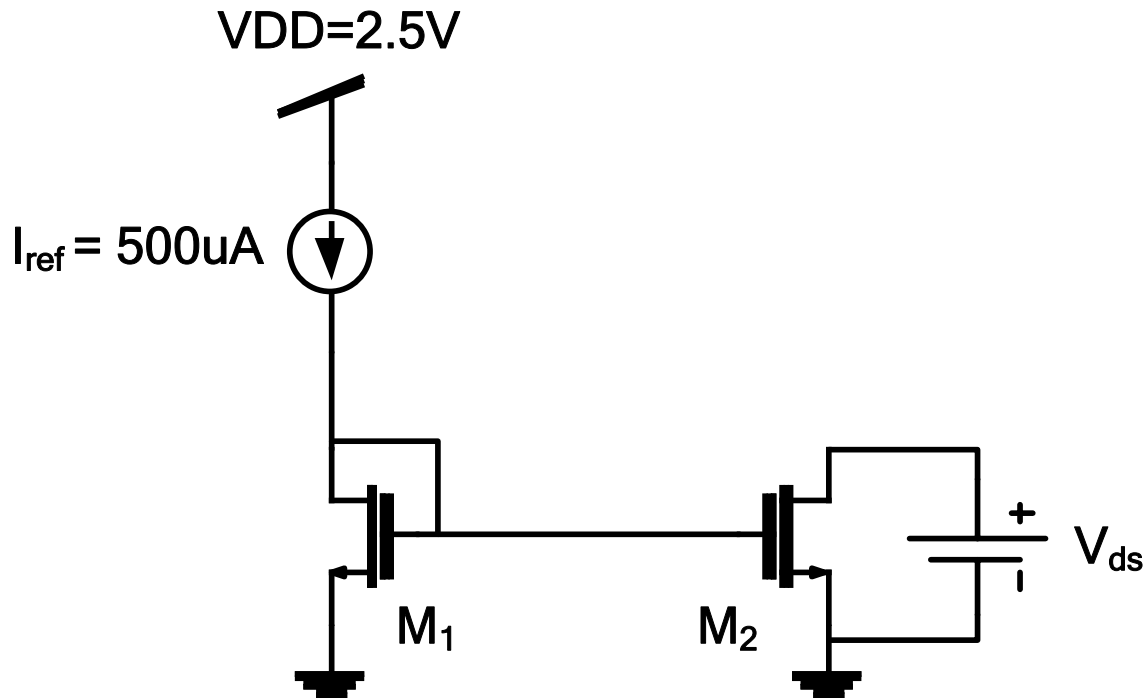

Design Specification

Parameter	Value
V _{ds}	< 0.7V
Output Resistance	>63KOhm
Current Copy	>99%


Simulation Guide

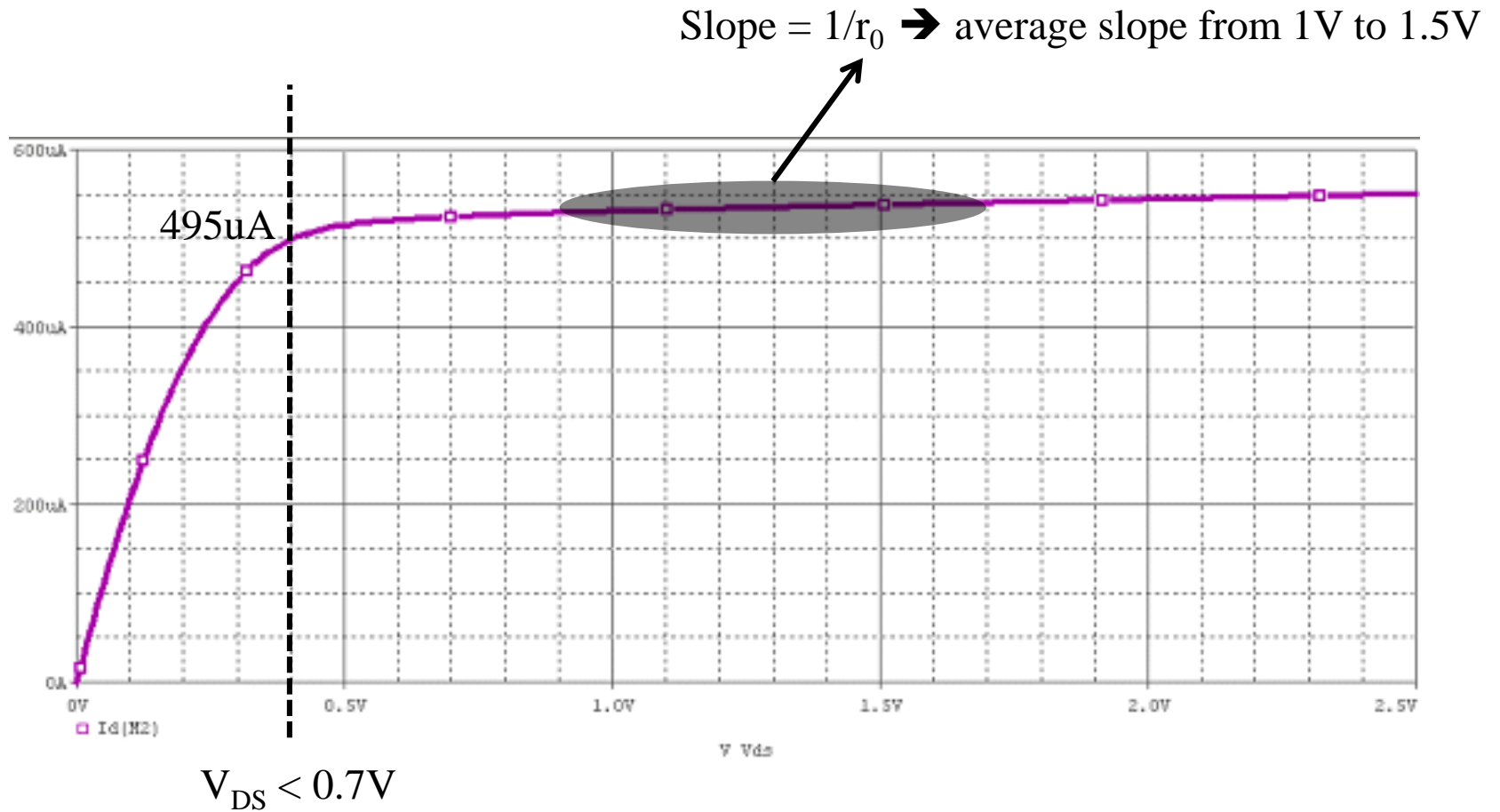


Simulation Tips

Differential input pair

Part Name : 'e'

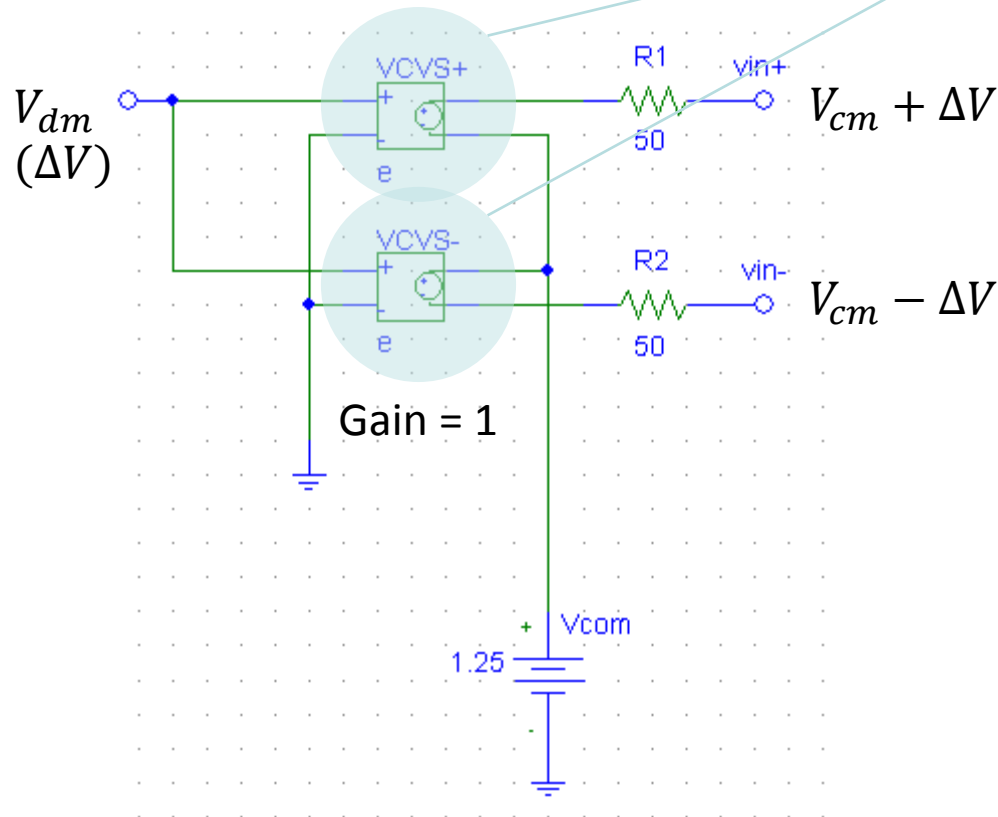


Single-Stage Differential OTA

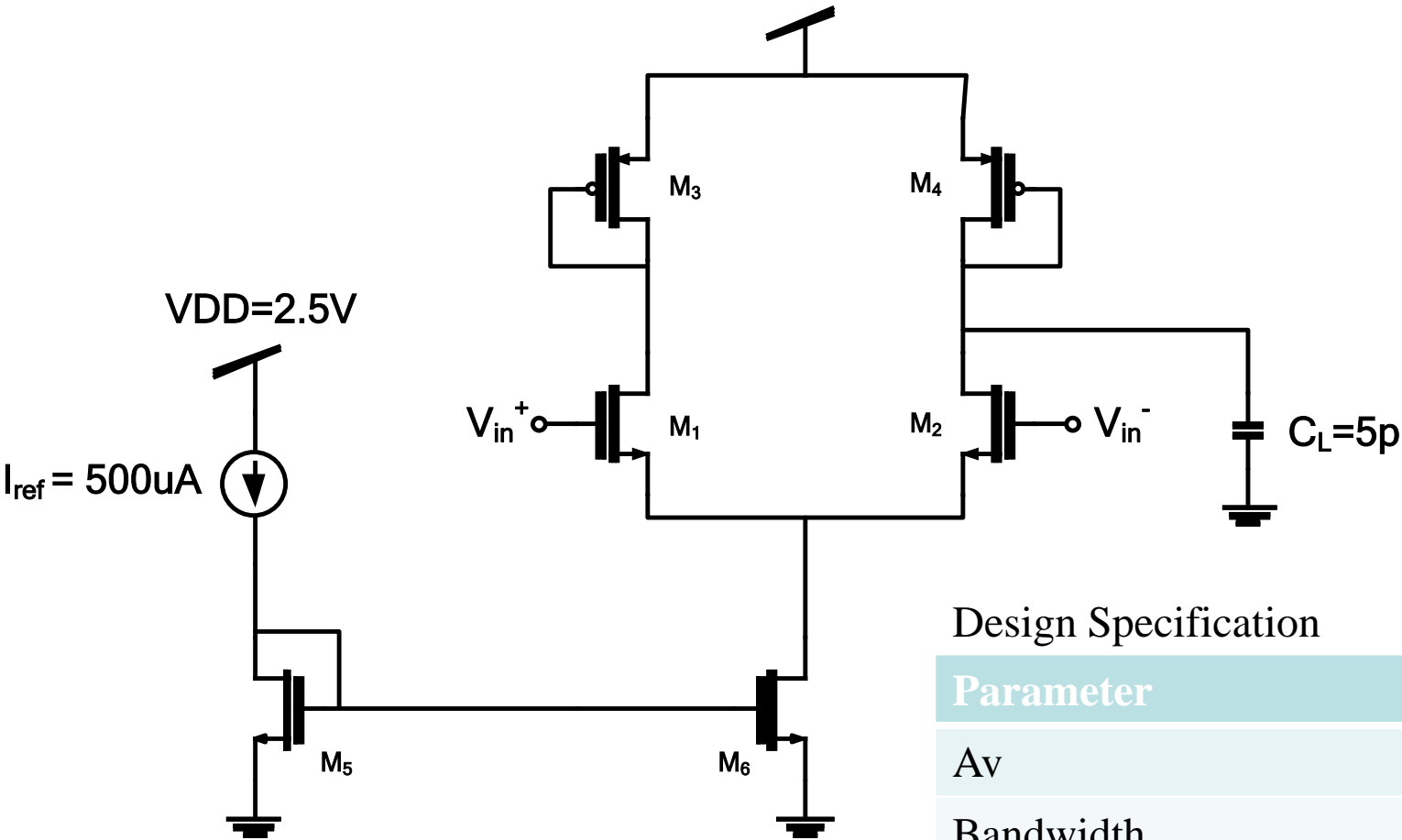


Design Specification

Parameter	Value
A_v	$>16\text{dB}$
Bandwidth	$>20\text{MHz}$
ICMR	$>1.1\text{V}$
Power Consumption	$<1.5\text{mW}$

Simulation Guide

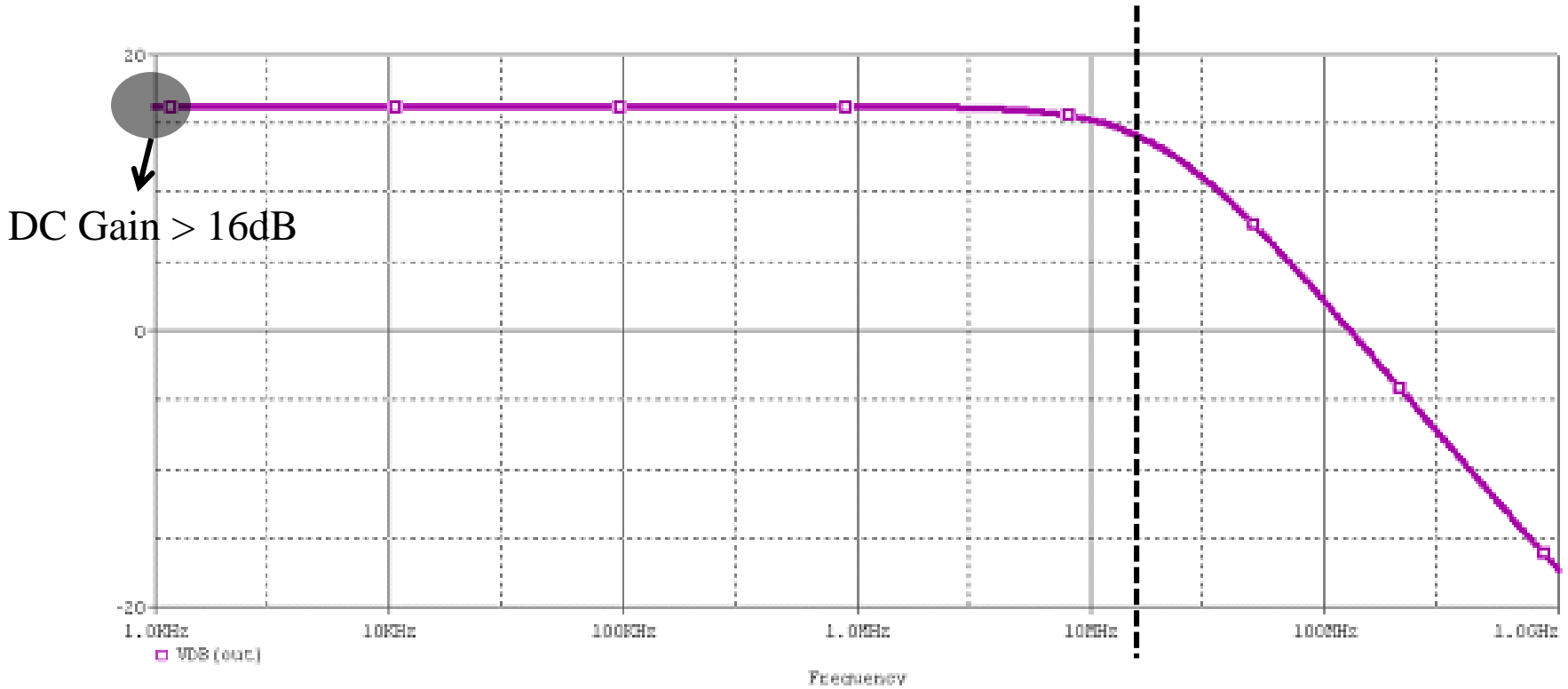


Simulation Guide

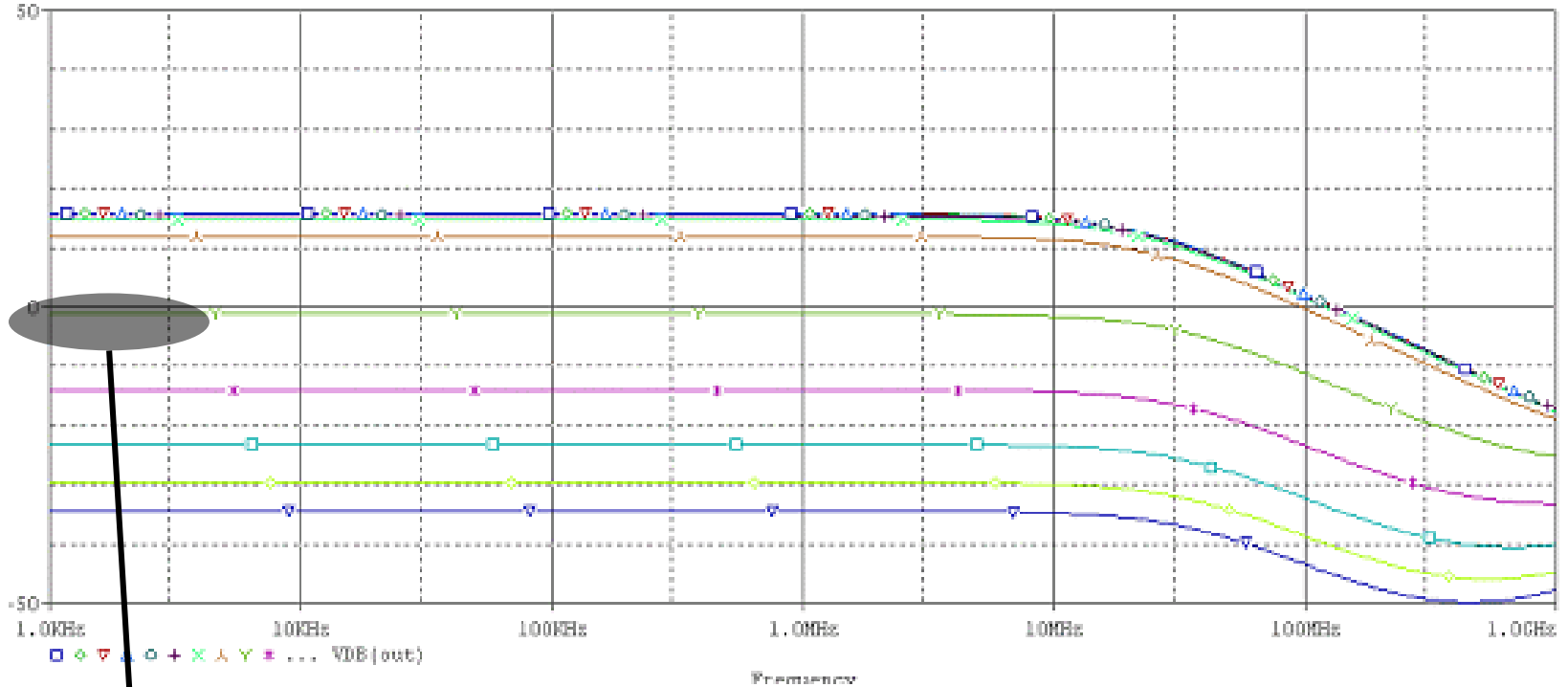

V_{max}

$$ICMR = V_{max} - V_{min} > 1.1V$$


Simulation Guide

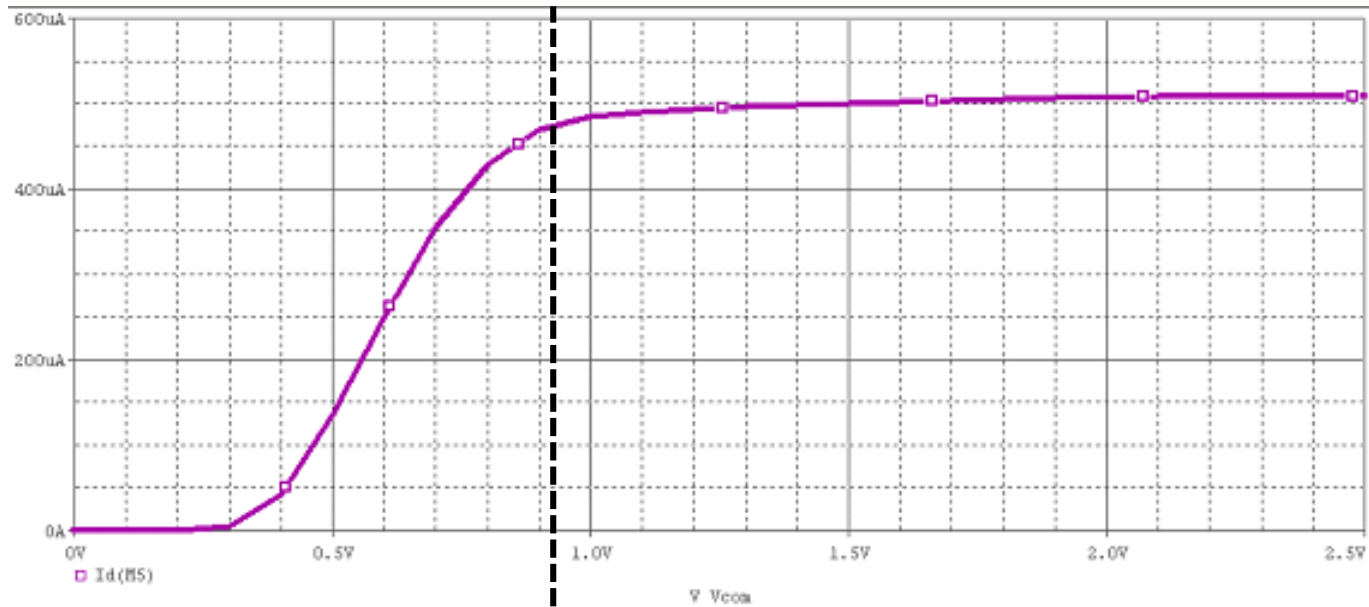


V_{min}
:Current copied 90% @ M6

Simulation Guide
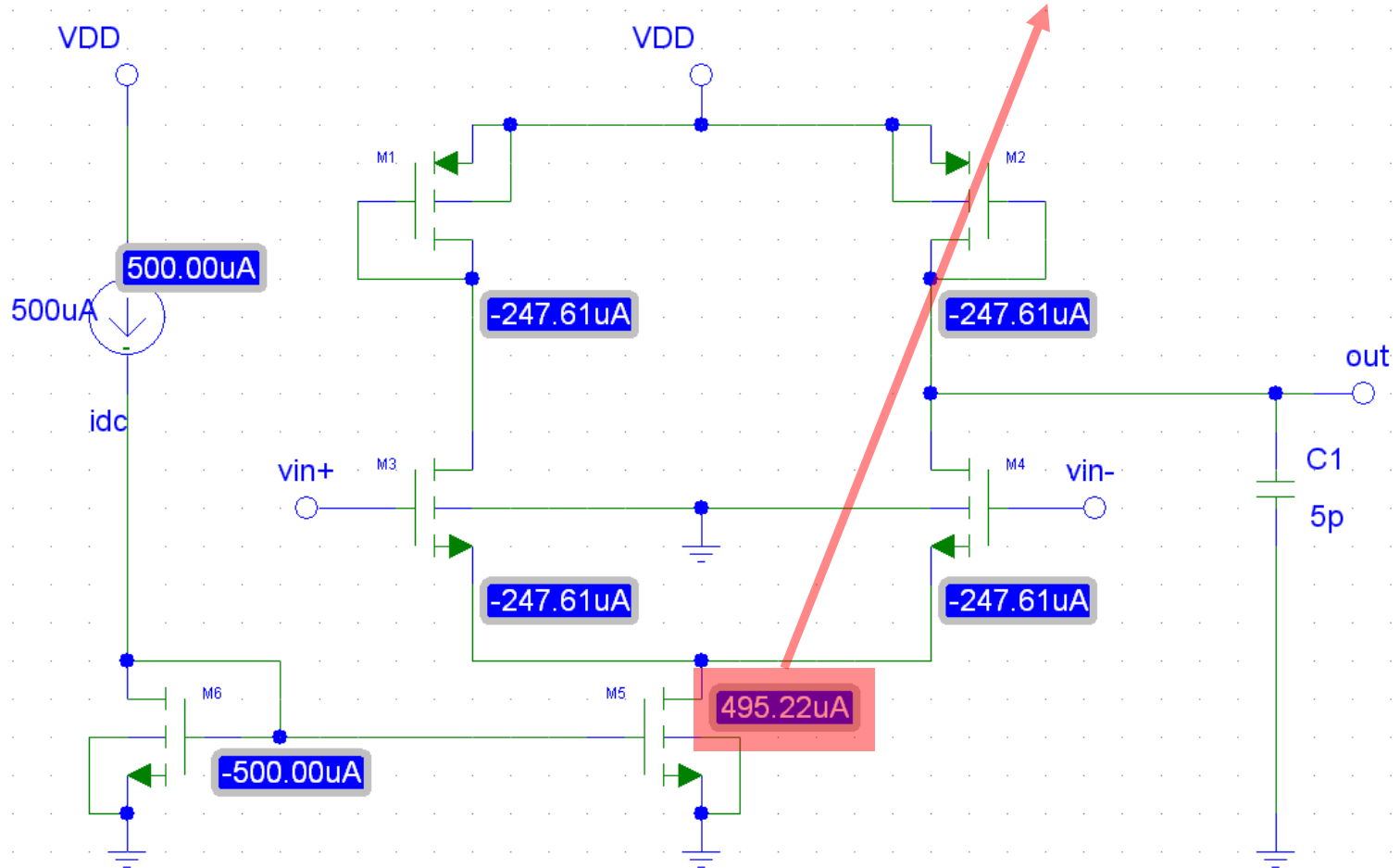
$$\text{Power} = \text{Total Current} * \text{VDD} < 1.5\text{mW}$$




Mirrored OTA

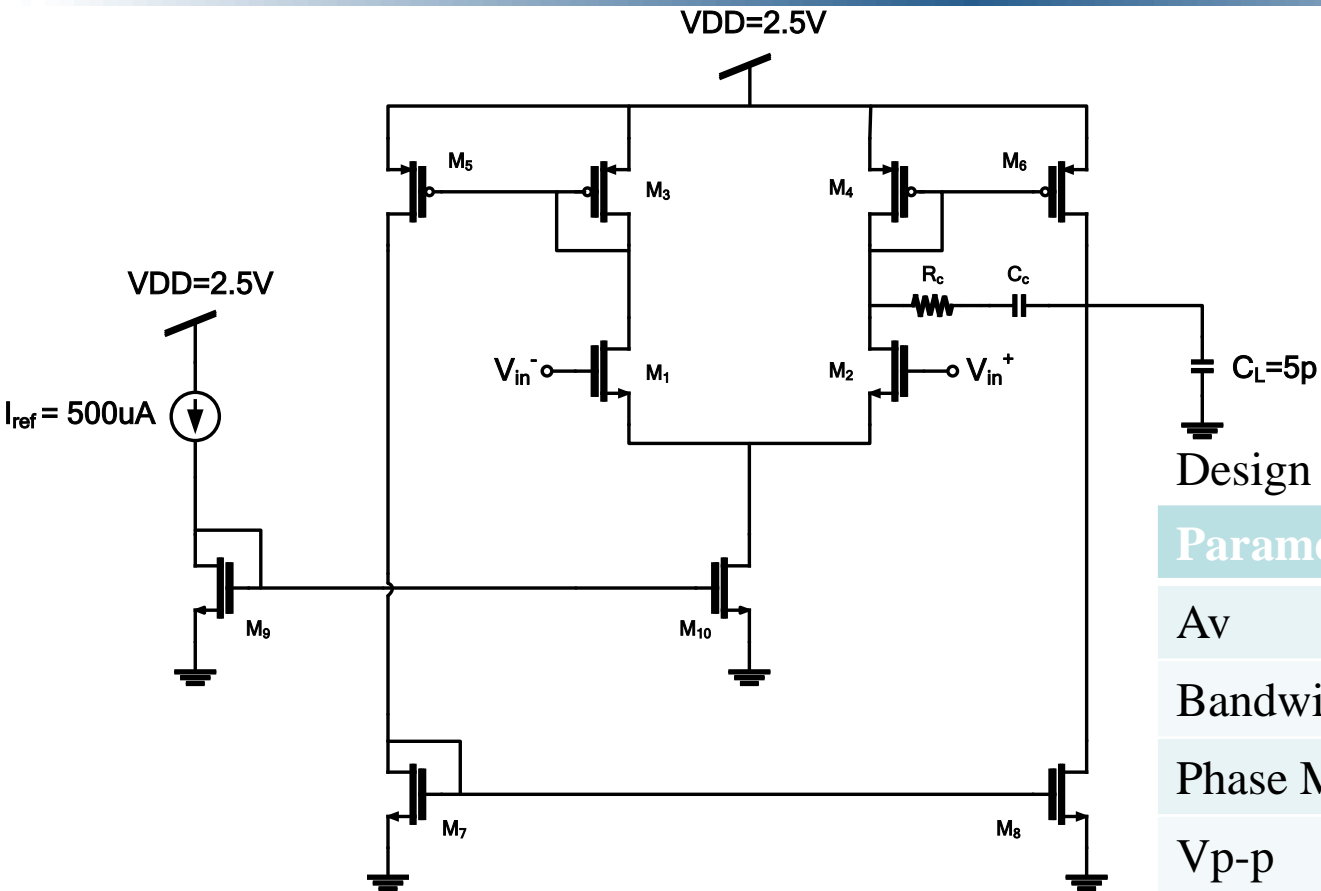


Design Specification

Parameter	Value
A_v	>56dB
Bandwidth	>60kHz
Phase Margin	>65
V_{p-p}	>1.5V
Slew Rate	>13V/us
CMRR	>85dB
Power Consumption	<2.5mW


Simulation Guide

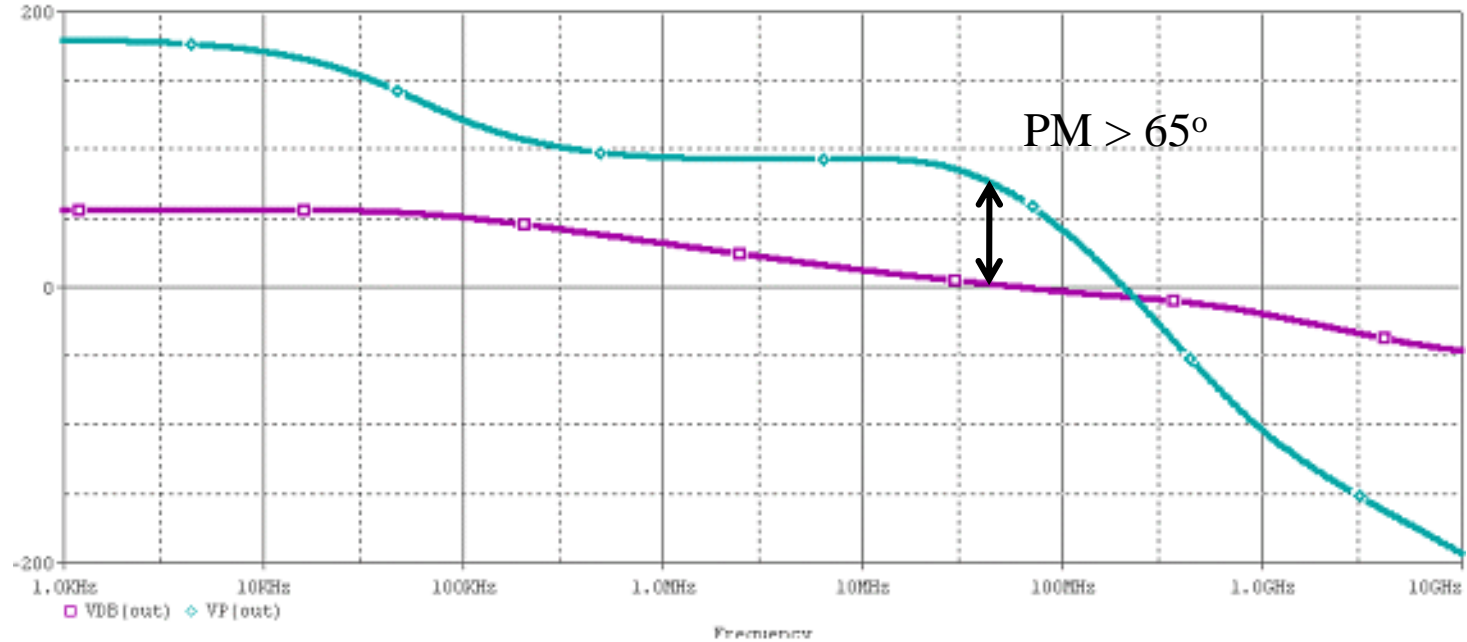


Simulation Guide

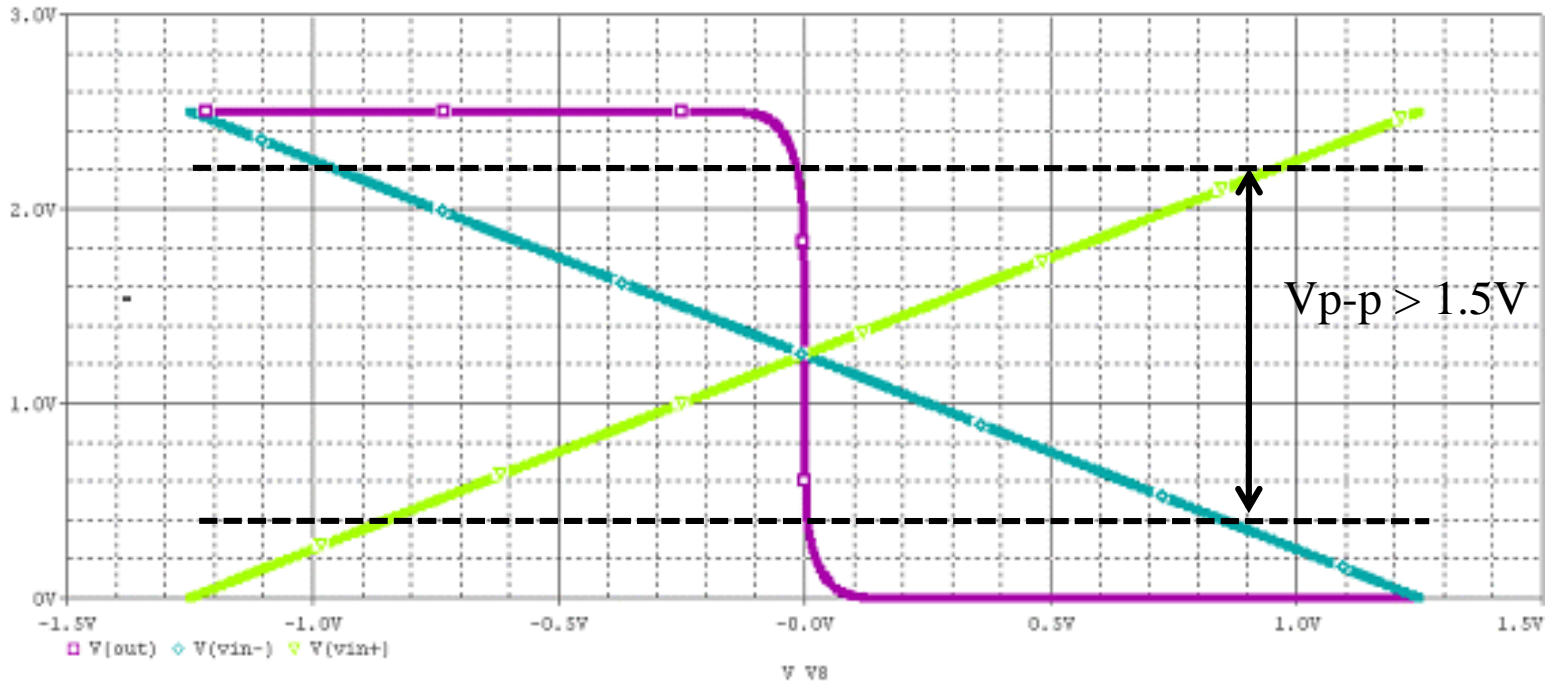


Simulation Guide

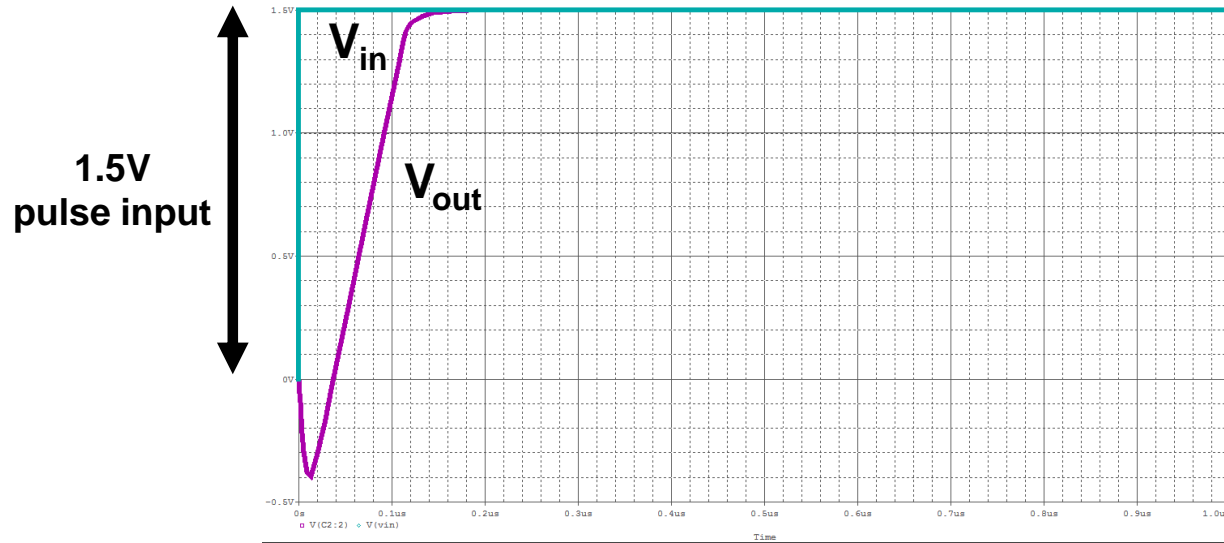

Derivative

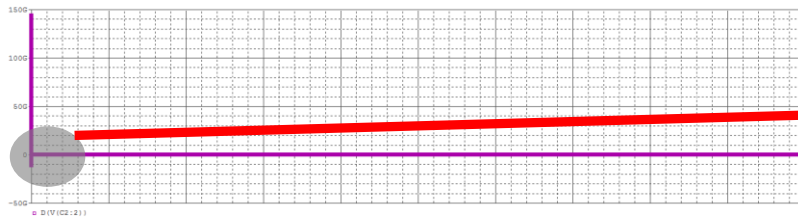


Slew rate > 13M V/s

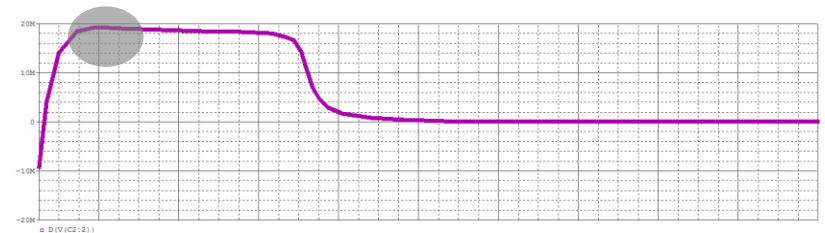


Simulation Guide
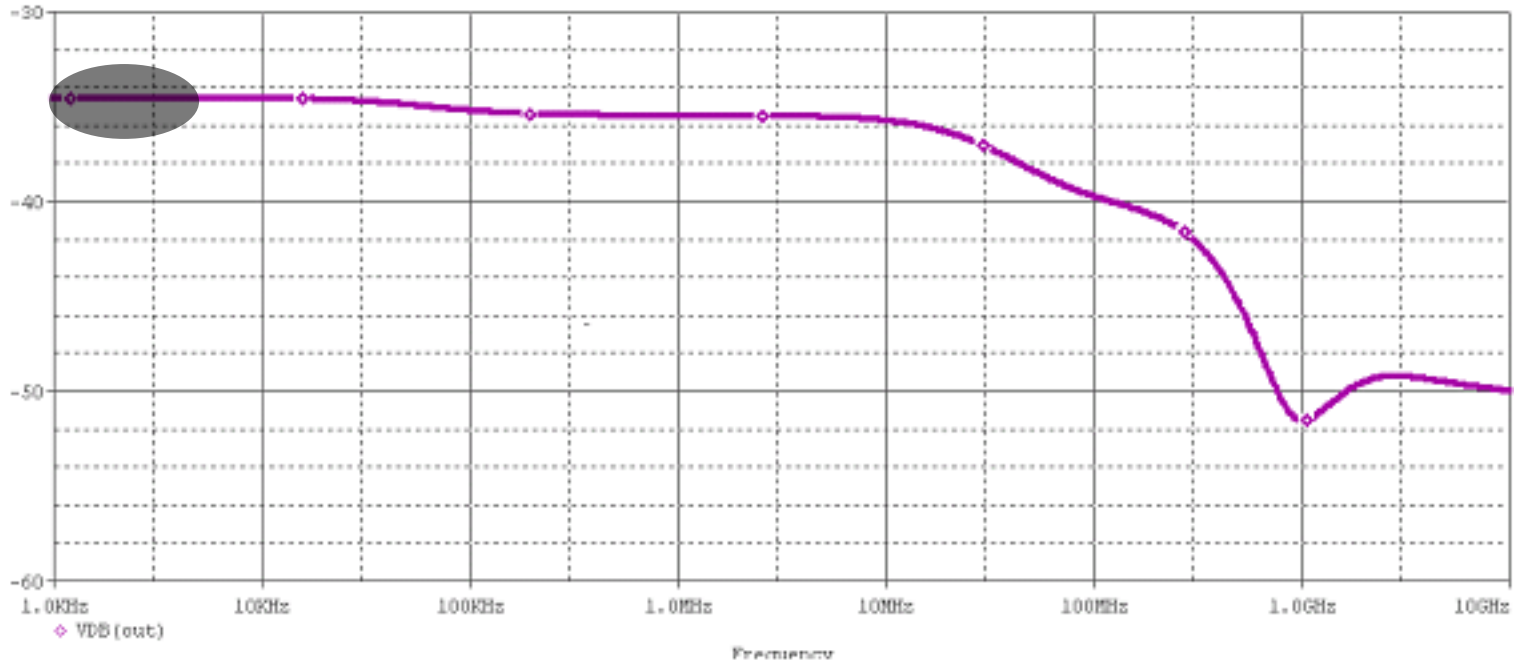
$$\text{CMRR} = A_{dv} / A_{cv} > 85\text{dB}$$



Simulation Tips

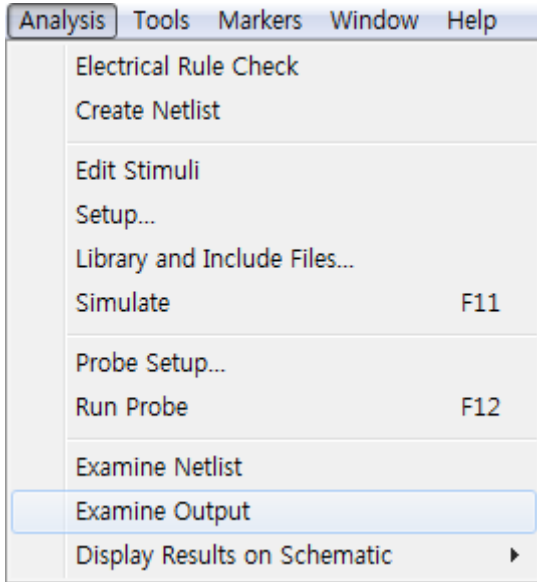

```
**** MOSFETS
```

```
NAME      M_M3      M_M4      M_M2      M_M5      M_M1
MODEL     orbit2L2N orbit2L2N orbit2L2P orbit2L2N orbit2L2P
```

I_D , V_{DS} , V_{GS} , V_{TH} , etc...

Grading Policy

- Current mirror[5], Single stage OTA[25], Mirrored OTA[50], Report[20]
- 10 extra points will be given for up to five designs that satisfy all the specifications and produce highest gain-bandwidth products for Part III in the class
- Three best designs will be selected and their designers will be given opportunities to present their results in class in English for extra 5 points.
- GB product = Gain * BW = $10^{\frac{Gain[dB]}{20}}$ * BW[Hz]