




# **Project 2**

# **Design Guide**

**High-Speed Circuits & Systems Lab.**  
**Dept. of Electrical and Electronic Engineering**  
**Yonsei University**

# Goal

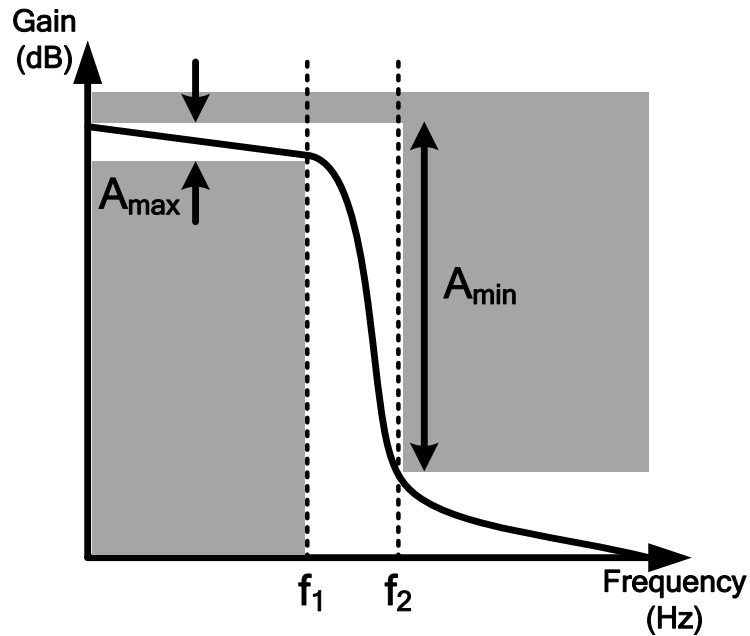

## Specification



- Butterworth LPF
- Filter DC gain = 0dB
- $A_{max} < 0.25\text{dB}$ ,  $A_{min} > 20.3\text{dB}$
- $f_1 = 7\text{kHz}$ ,  $f_2 = 18\text{kHz}$

- I. Filter Design with MATLAB[10]
- II. Design an active RC Butterworth LPF[30]
- III. Design a switched-capacitor LPF[40]
- IV. Report[20]

# MATLAB

- Hand Calculation → determine the filter transfer function
- Confirm with MATLAB
- Functions to use in MATLAB
  - **poly(A)** : returns a row vector whose elements are the coefficients of the characteristic polynomial
  - **tf(num,den)** : creates a continuous-time transfer function with numerator(s) and denominator(s) specified by num and den.
  - **[z,p,k] = buttap(n)** : returns the poles and gain of an order n Butterworth analog lowpass filter prototype
  - **Bodemag(sys)** : plots the magnitude of the frequency response of the LTI model SYS
  - More detailed function properties : Help → Product help
  - Please attach code in report with annotations


# Result Example

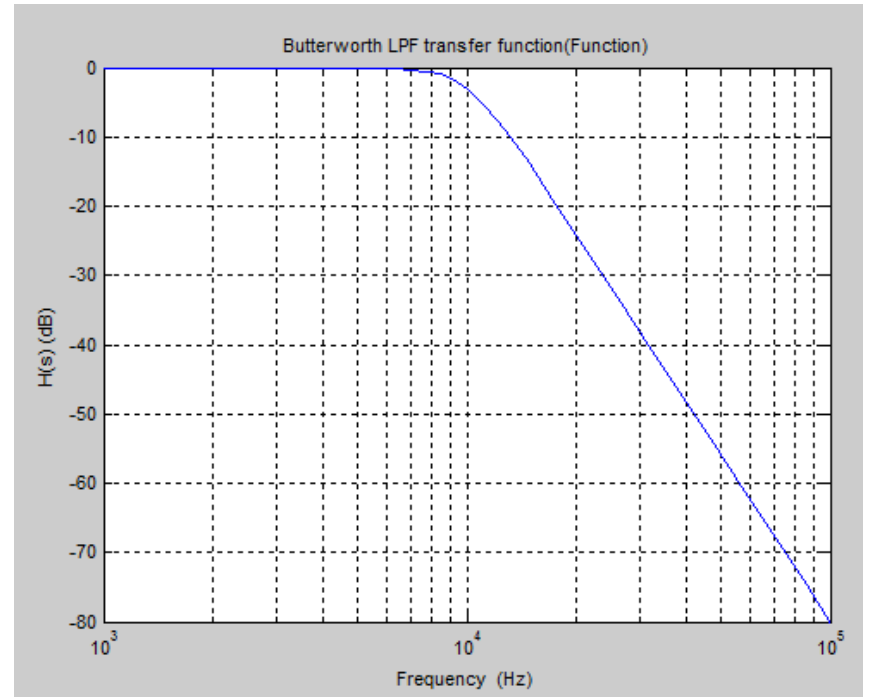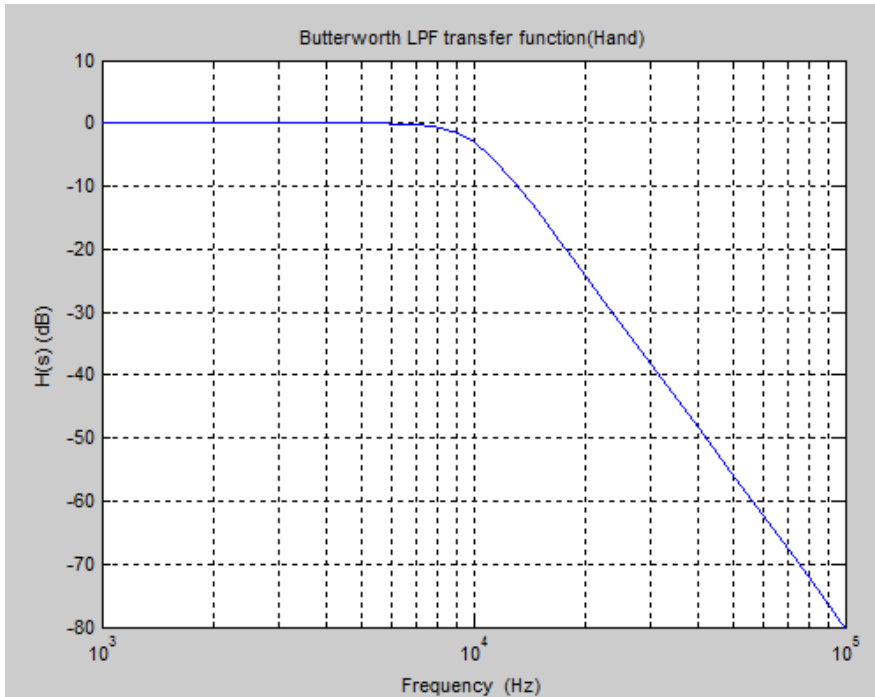


# Active RC LPF
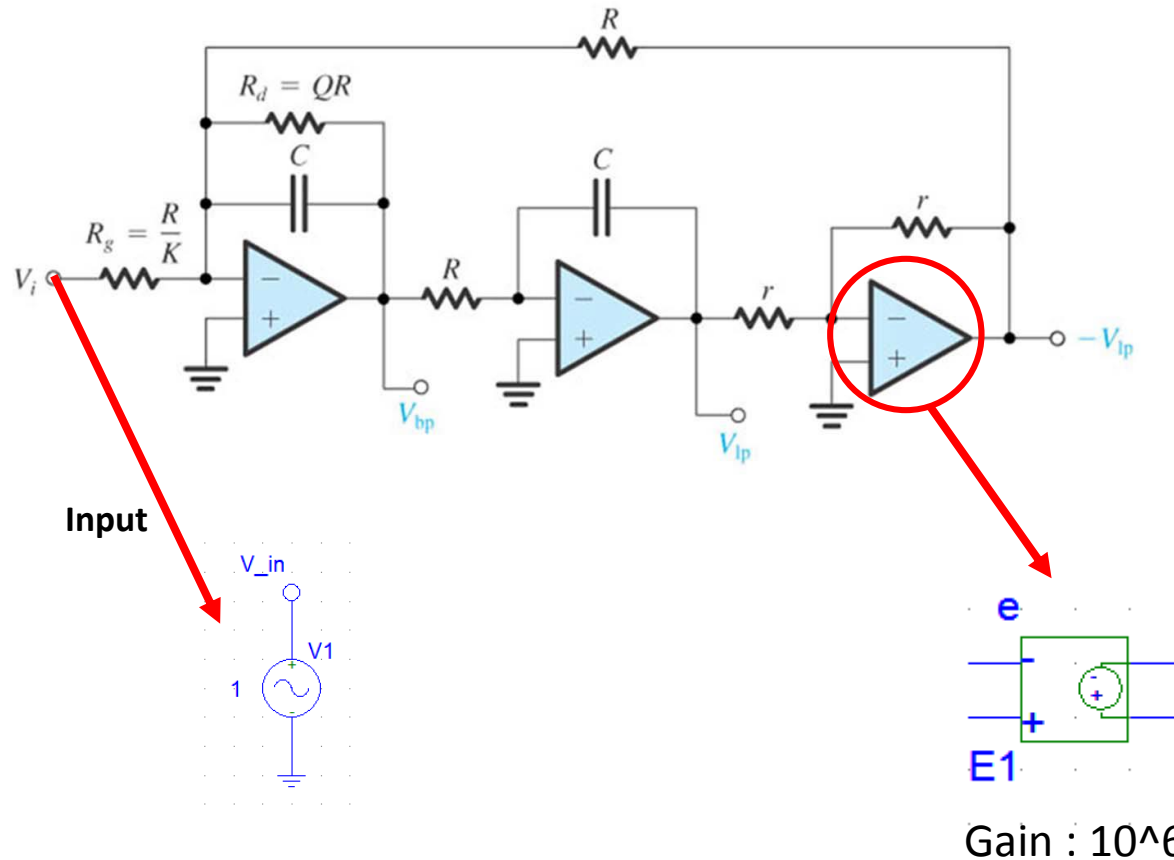
## Tow-Thomas Filter



- $R \leq 2M\Omega$
- $10pF \leq C \leq 100pF$



# Result Example

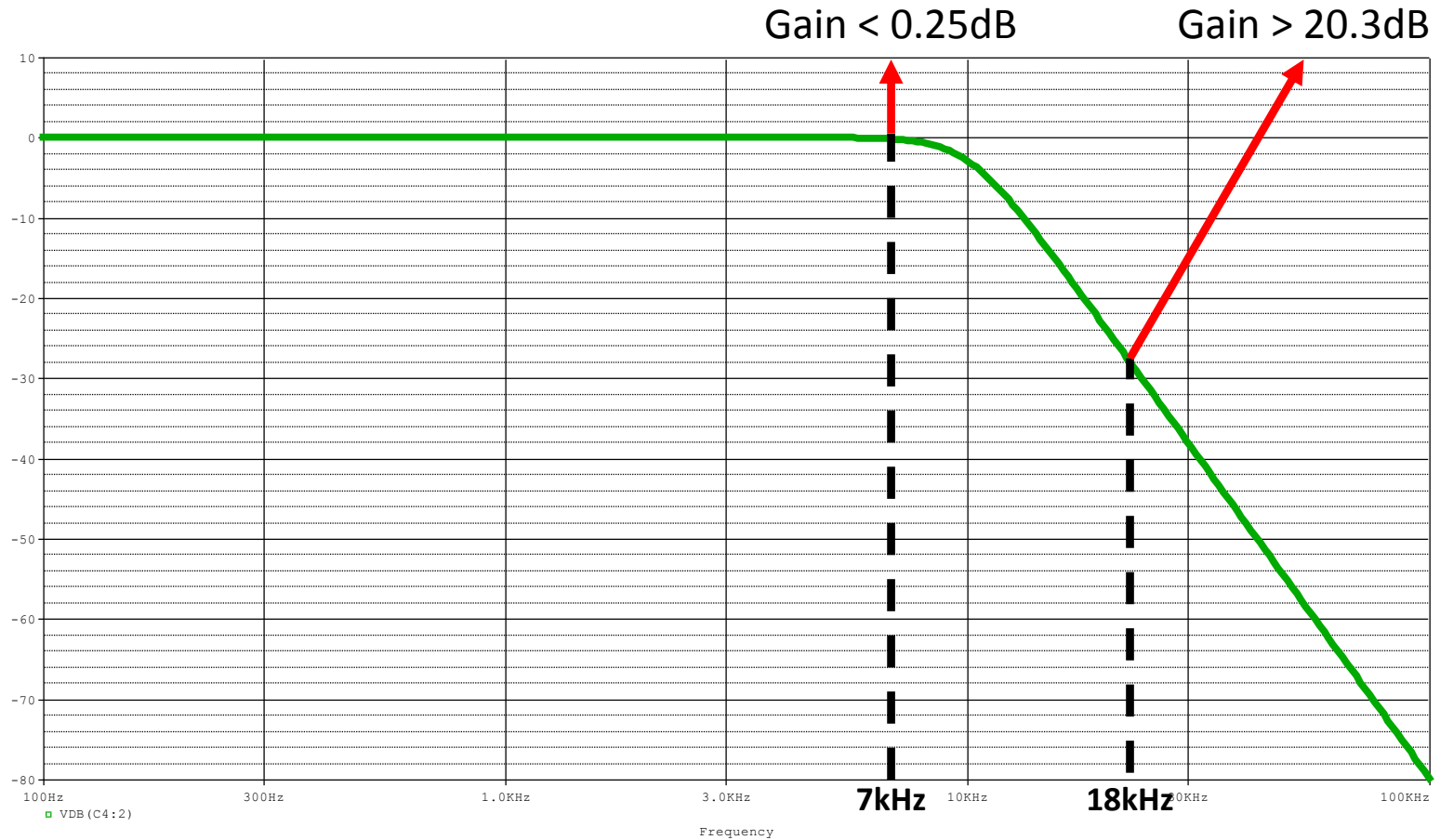


# Switched-Capacitor LPF

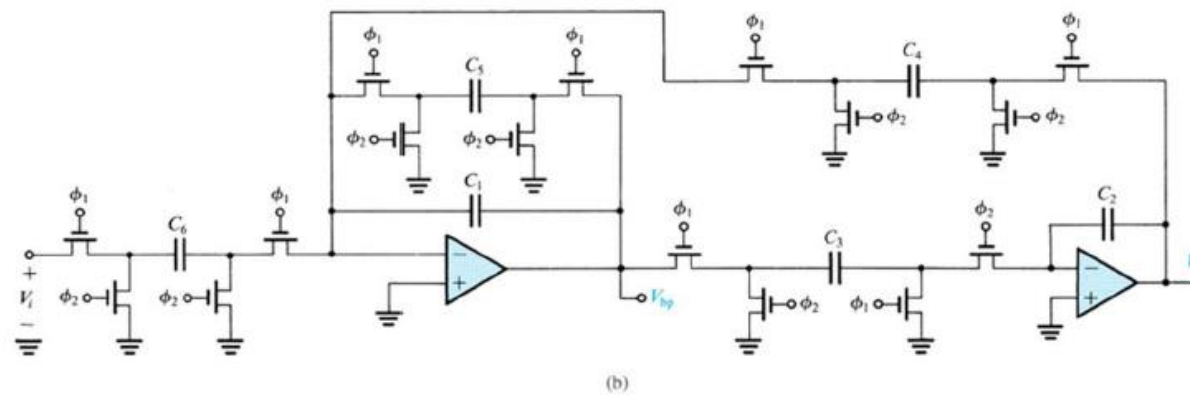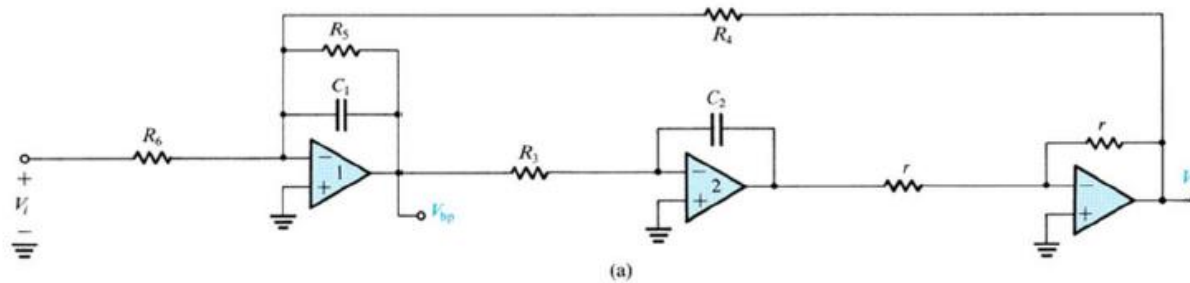


Replace resistors with switched capacitors such as (a)  $\rightarrow$  (b)

# Pspice elements

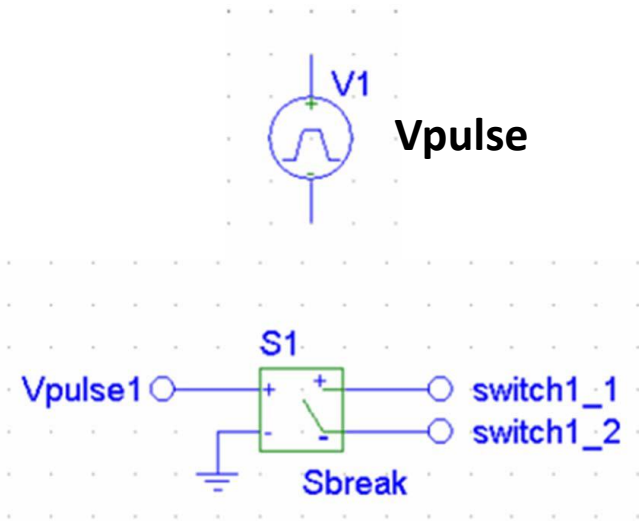


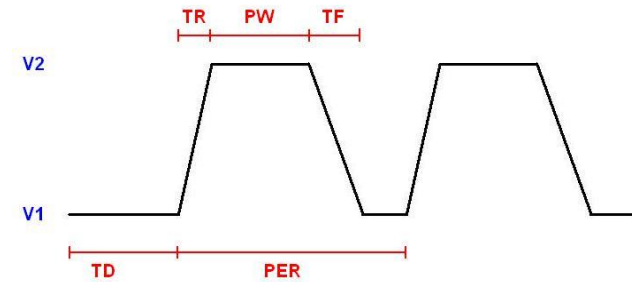
- Vpulse
  - td : time delay
  - tr : rising time
  - tf : falling time
  - PW : pulse width
  - PER : period
- Sbreak
  - Ideal switch




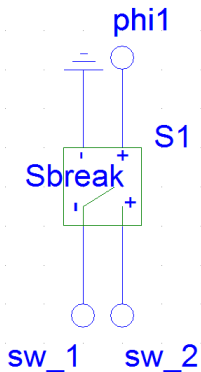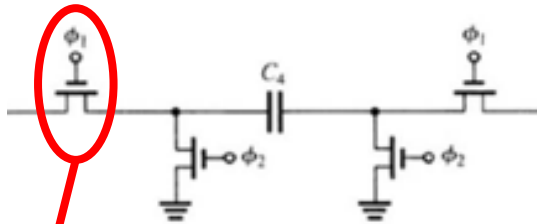
# Pspice Schematic


- $10pF \leq C \leq 100pF$
- Sampling frequency = 500kHz
- Need transient simulation!
- Input : impulse





V1=0, V2=1, td=1u, tr=tf=1p, PW=1u, Period=2u

V1=1, V2=0, td=1u, tr=tf=1p, PW=1u, Period=2u

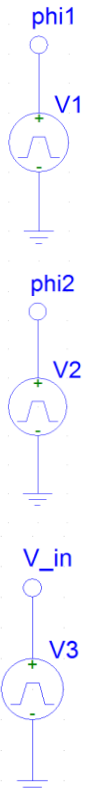V1=0, V2=1, td=1u, tr=tf=0, PW=1u, Period = 2




# Transient Simulation

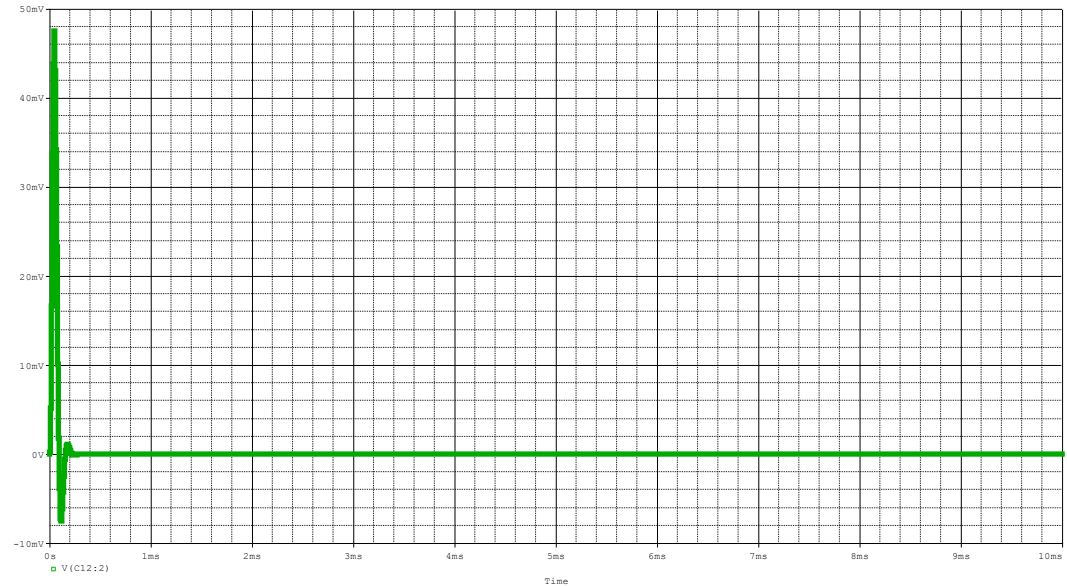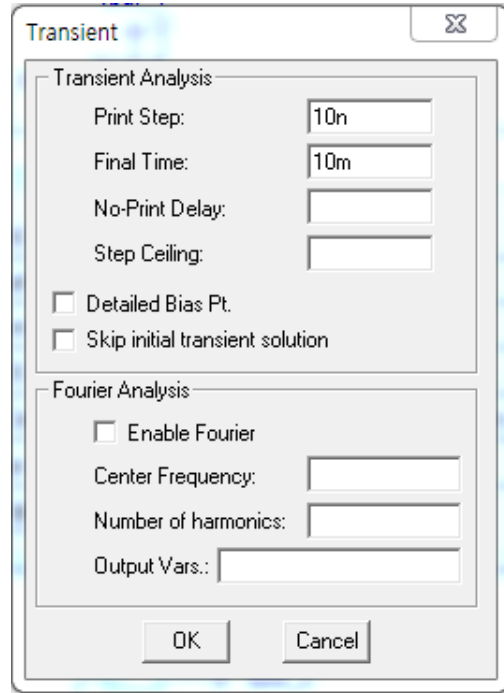



Put 20n~30n in step ceiling for higher resolution

<Output result>

Need FFT!

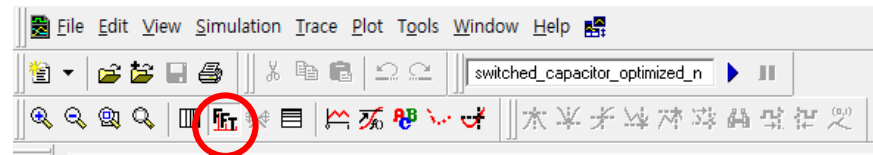

# Result Example

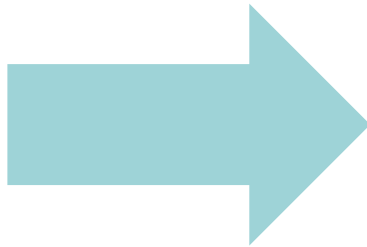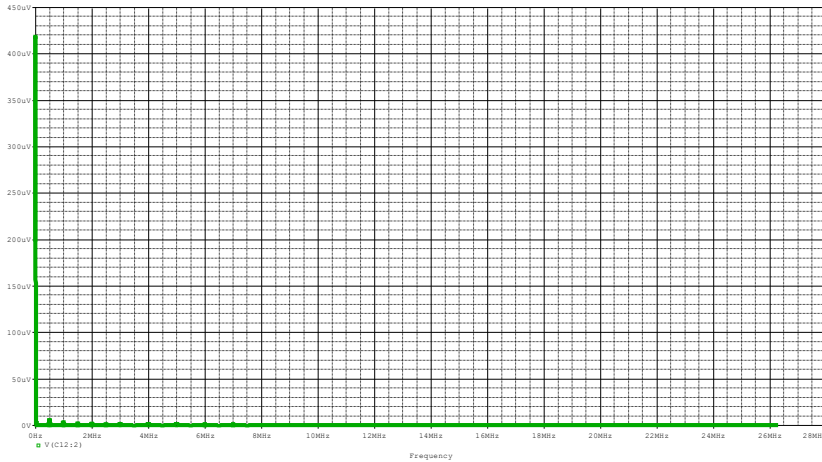

1. Scale(100Hz to 30kHz)
2. x-axis Log scale
3. Place Vdb marker

Maximum 0.4dB peaking  
is allowed



**Do not worry about DC gain value!**  
**Please mark important points in graph**

# Grading Policy

- MATLAB[10], Active RC filter[30], Switched-capacitor filter[40], Report[20]
- List R,C values with reasonable explanation and mark important points in graph.
- For switched-capacitor filter, design with smaller total capacitance will get more points. Grade policy is followed in table.

<b>Grade A ( 5 teams )</b>	<b>10 points</b>
<b>Grade B ( 5 teams )</b>	<b>8 points</b>
<b>Grade C ( 5 teams )</b>	<b>6 points</b>
<b>Grade D ( 4 teams )</b>	<b>4 points</b>
<b>Grade E ( 4 teams )</b>	<b>2 points</b>

- Three best designs will be selected and their designers will be given opportunities to present their results in class in English for extra 5 points.
- Deadline : 6:00 PM , 24 May. 2015 @ B629(Hardcopy)