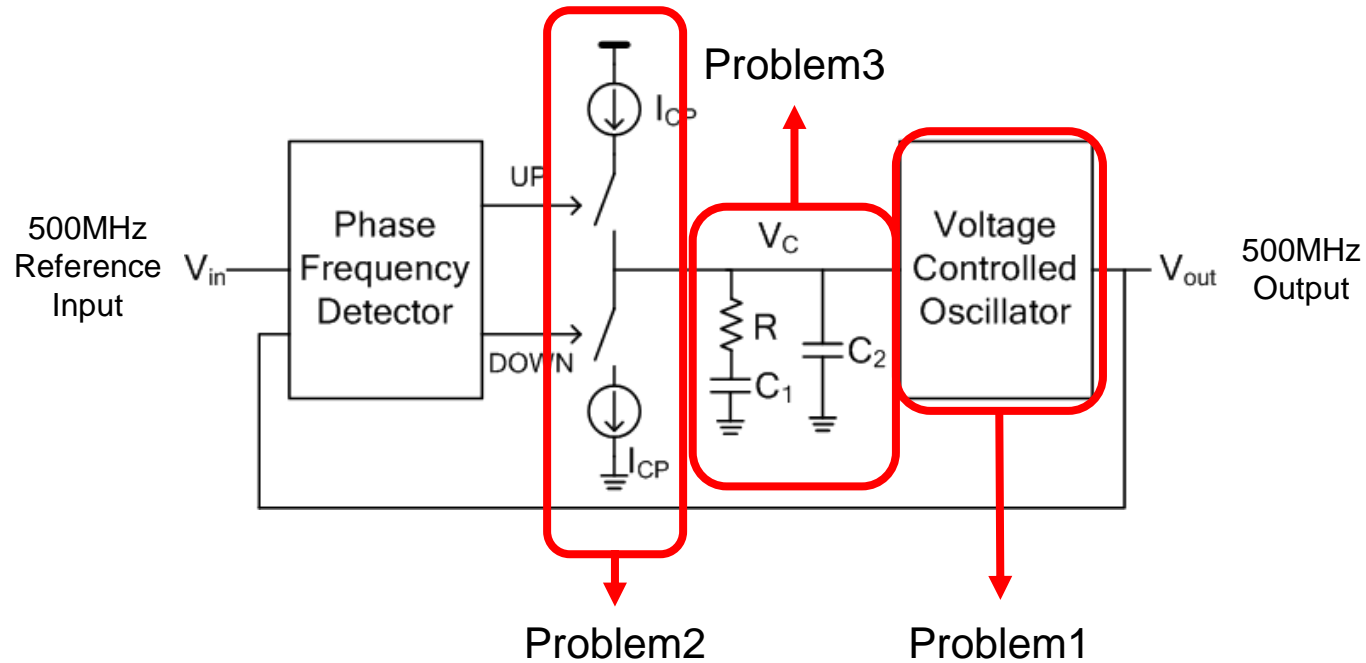


The background features a large, light blue watermark of the Yonsei University seal. The seal is circular with the text 'YONSEI UNIVERSITY' around the top and 'YONSEI' at the bottom. Inside the seal is a shield with a central circle, a book on the left, a torch on the right, and the year '1885' at the bottom.

# **Project 3 Design Guide**

**High-Speed Circuits & Systems Lab.  
Dept. of Electrical and Electronic Engineering  
Yonsei University**

# Goal




## Phase Locked Loop

- ✓ Output clock frequency : 500MHz
- ✓ 2.5V supply voltage
- ✓  $V_{cont}$  : 0.75~2.25V

# Problem 1
 
## I. Ring-type Voltage Controlled Oscillator(VCO) Design[20]



### Design Goals


Parameter	Value
Target Oscillation Frequency	500MHz
Average VCO gain	100MHz/V~150MHz/V
$V_{cont}$	0.75~2.25V




# Simulation Result
 
## Transient simulation

- ✓ Print step : 0.1ns
- ✓ Final time : 200ns



FFT

 


Find point which has maximum value

Determine  $V_{\text{cont}}$  whose oscillation frequency is 500MHz

→  $V_{\text{cont}}$  should be within 0.75V~2.25V

# Simulation Result

$V_{cont}$  parametric sweep(0.75~2.25V)

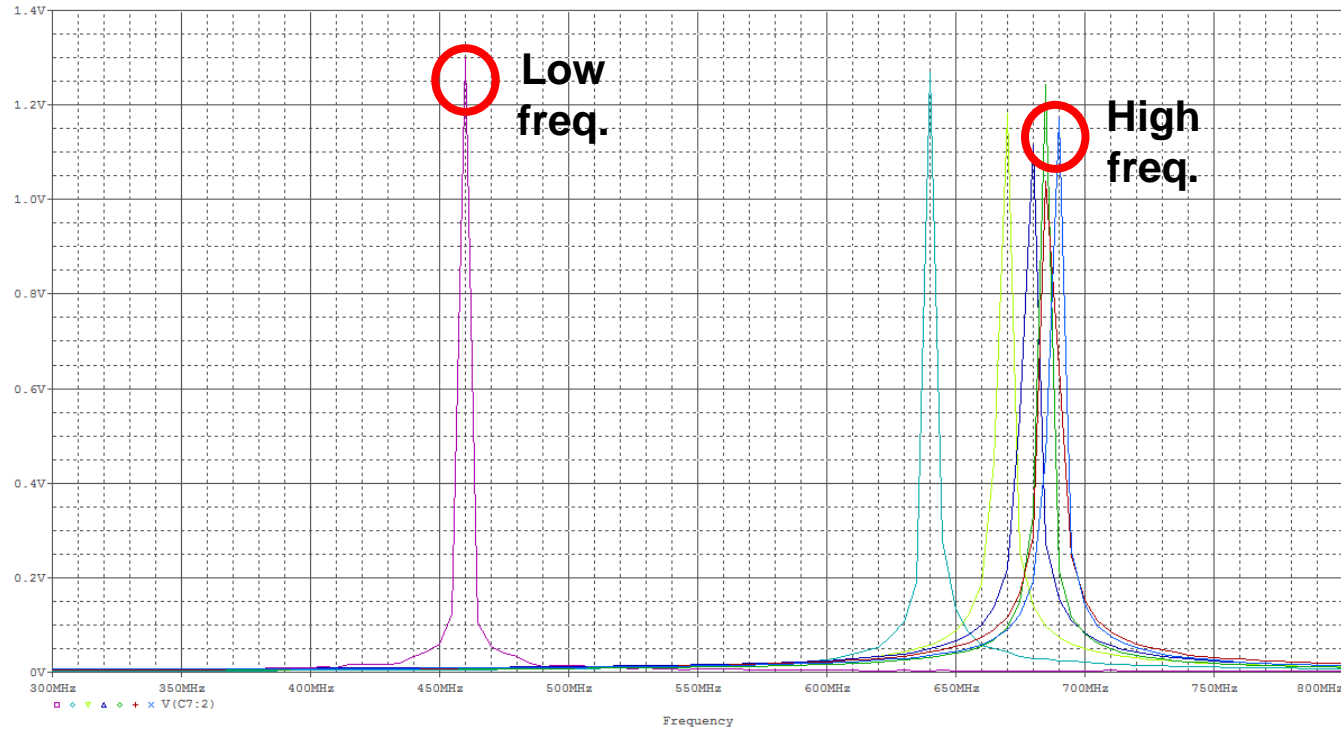


Average VCO gain : (High freq.-Low freq.)/1.5

→Average VCO gain should be within 100~150MHz/V

→Plot  $V_{cont}$  vs frequency


# Problem 2

## II. Charge Pump Design[20]

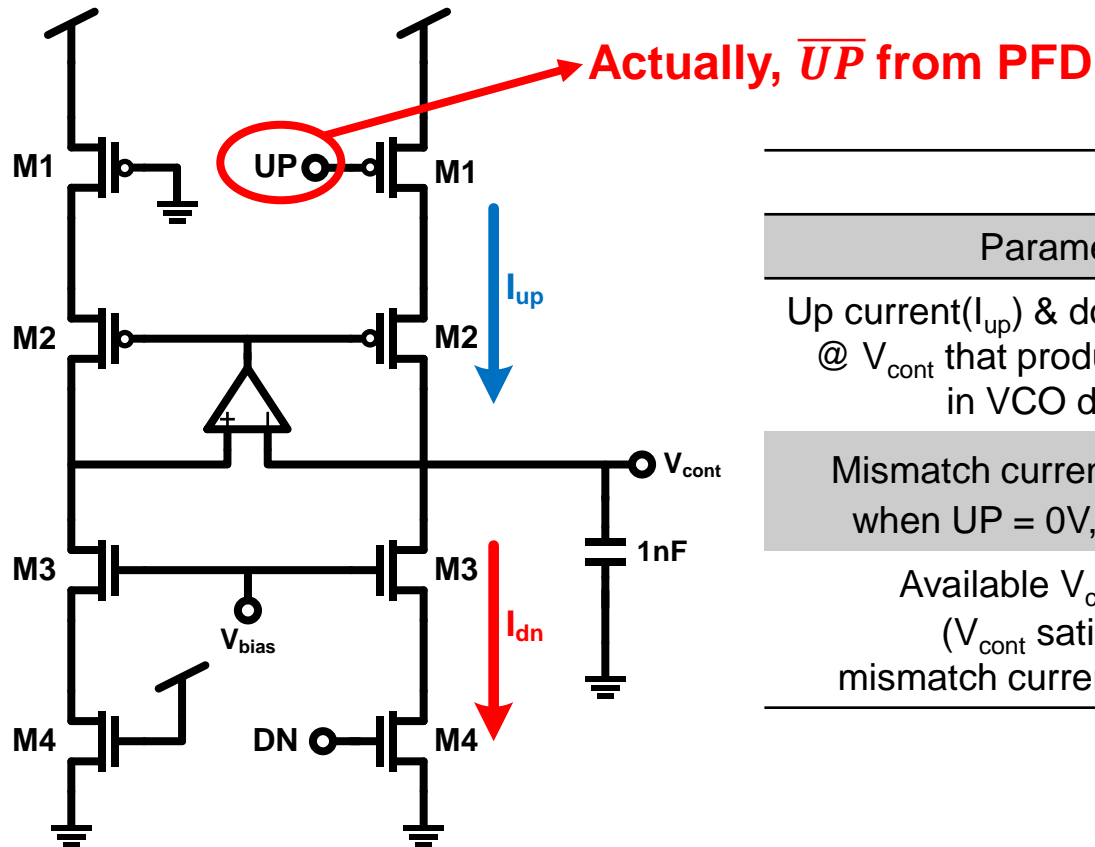

Design Goals	
Parameter	Value
Up current( $I_{up}$ ) & down current( $I_{dn}$ ) @ $V_{cont}$ that produces 500MHz in VCO design	4~6mA
Mismatch current, $ I_{up} - I_{dn} $ when $UP = 0V$ , $DN = 2.5V$	$< 50 \mu A$
Available $V_{cont}$ range ( $V_{cont}$ satisfying mismatch current condition)	$>1.45V$


# Charge Pump Design

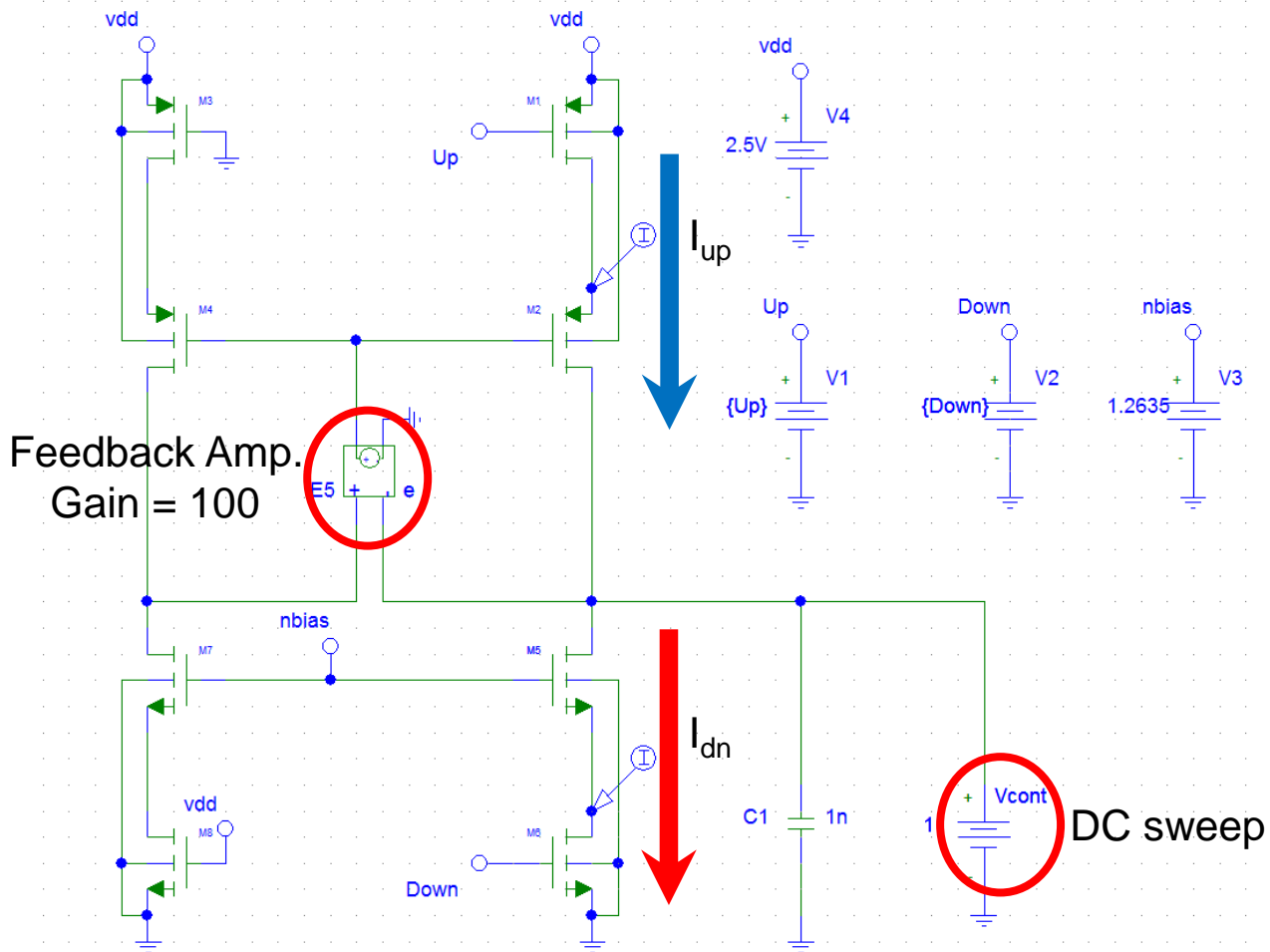




# Simulation Result


$V_{cont}$  DC sweep(0~2.5V)

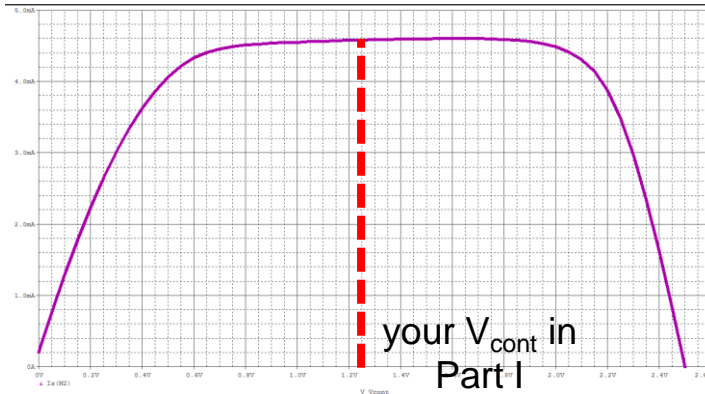

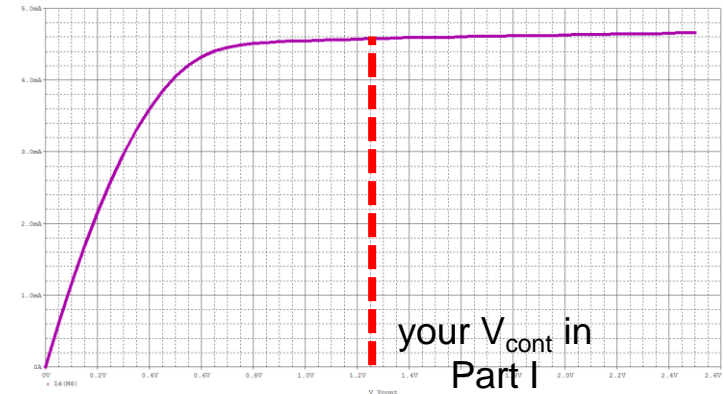$\langle V_{cont} \text{ vs } I_{up} \rangle$



 $\langle V_{cont} \text{ vs } I_{dn} \rangle$




$\langle V_{cont} \text{ vs } I_{up} - I_{dn} \rangle$

1.  $I_{up}$  &  $I_{dn}$  @ your  $V_{cont}$  should be within 4~6mA
2. Mismatch current  $< 50\mu A$
3. Available  $V_{cont}$  range  $> 1.45V$

# Problem 3
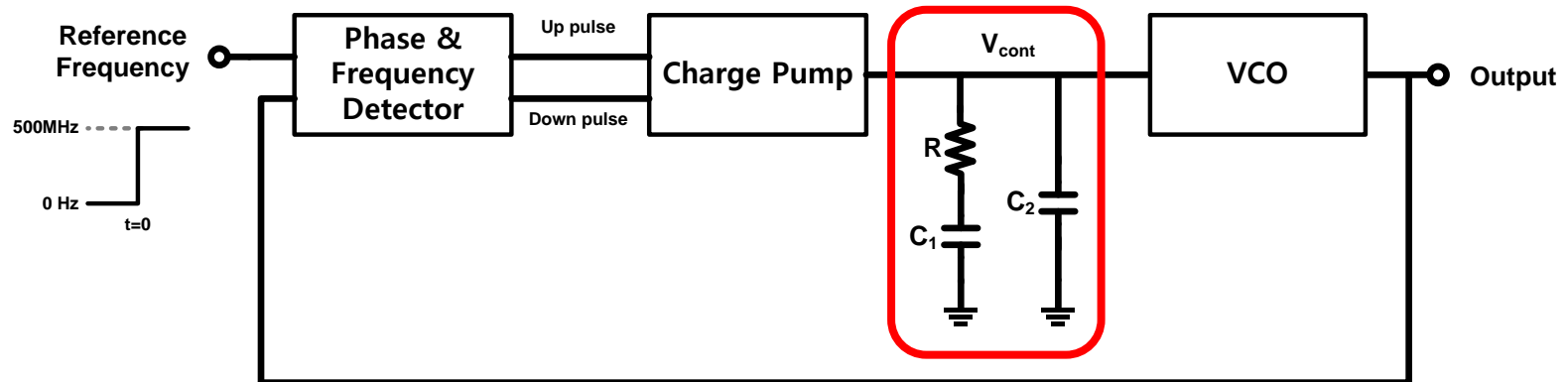
## III. PLL Design[50] – MATLAB simulation



✓ Determine the values for  $R$  &  $C_1$  with given conditions following:

✓ Resonance frequency( $f_0$ ) = 25MHz,  $C_2=C_1/10$ ,  $580\Omega \leq R \leq 600\Omega$ ,  $\omega_0 = \sqrt{\frac{I_{cp}K_{VCO}}{2\pi C_1}}$

✓ Use design parameters( $I_{cp}$  &  $K_{VCO}$ ) determined in Part I&II

<Problem 3(a), frequency response>

<Problem 3(b), step response(time)>

### Design Goals

Parameter	Value
Phase margin for open-loop transfer function	> 50 deg
Max. peaking for closed-loop transfer function	< 2dB


### Design Goals

Parameter	Value
Settling time (Locking time)	As low as possible

# Simulation Result


## Problem 3(a) – MATLAB simulation

Open-loop transfer function

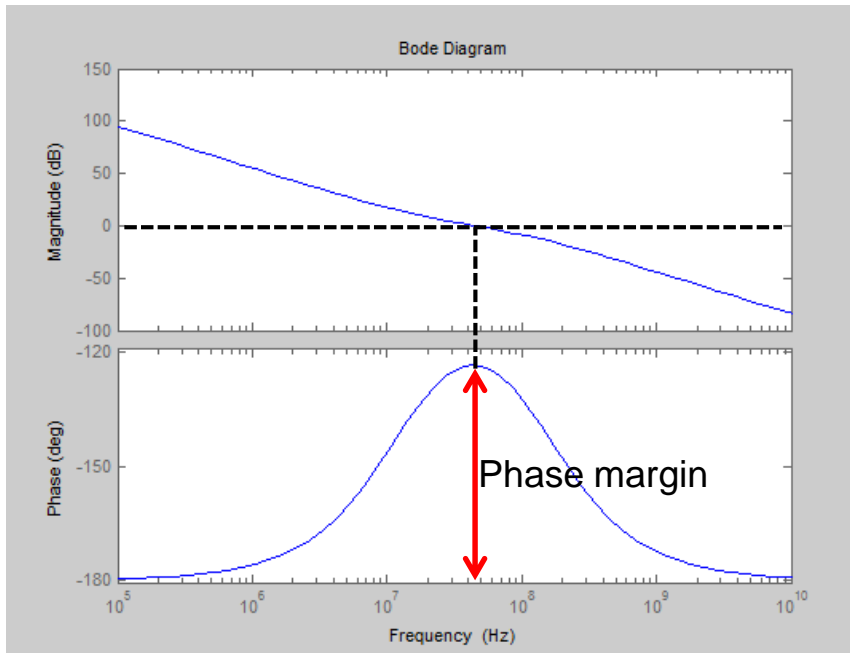

✓ Phase margin > 50deg



Closed-loop transfer function

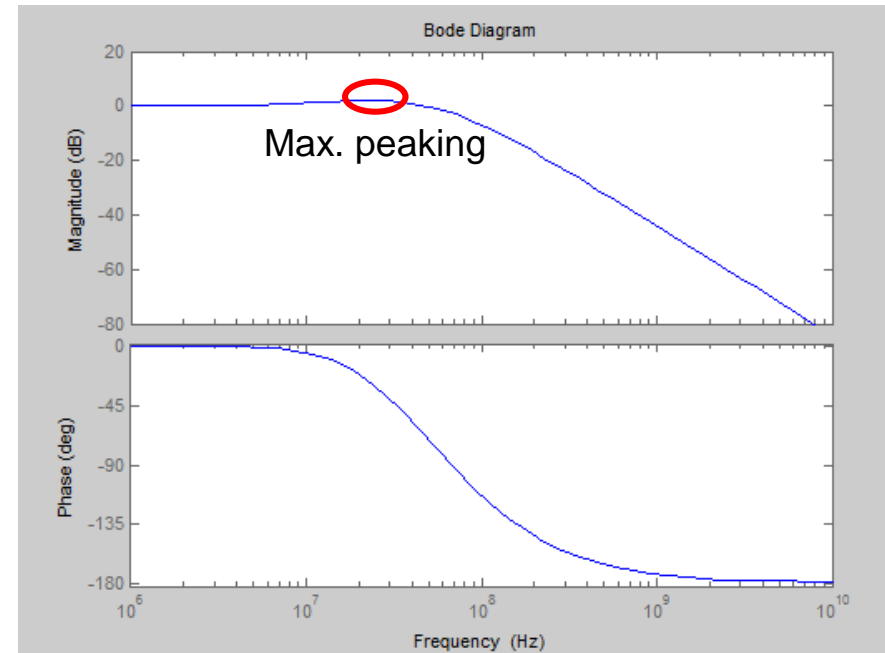


✓ Max. peaking < 2dB

# Simulation Setup

 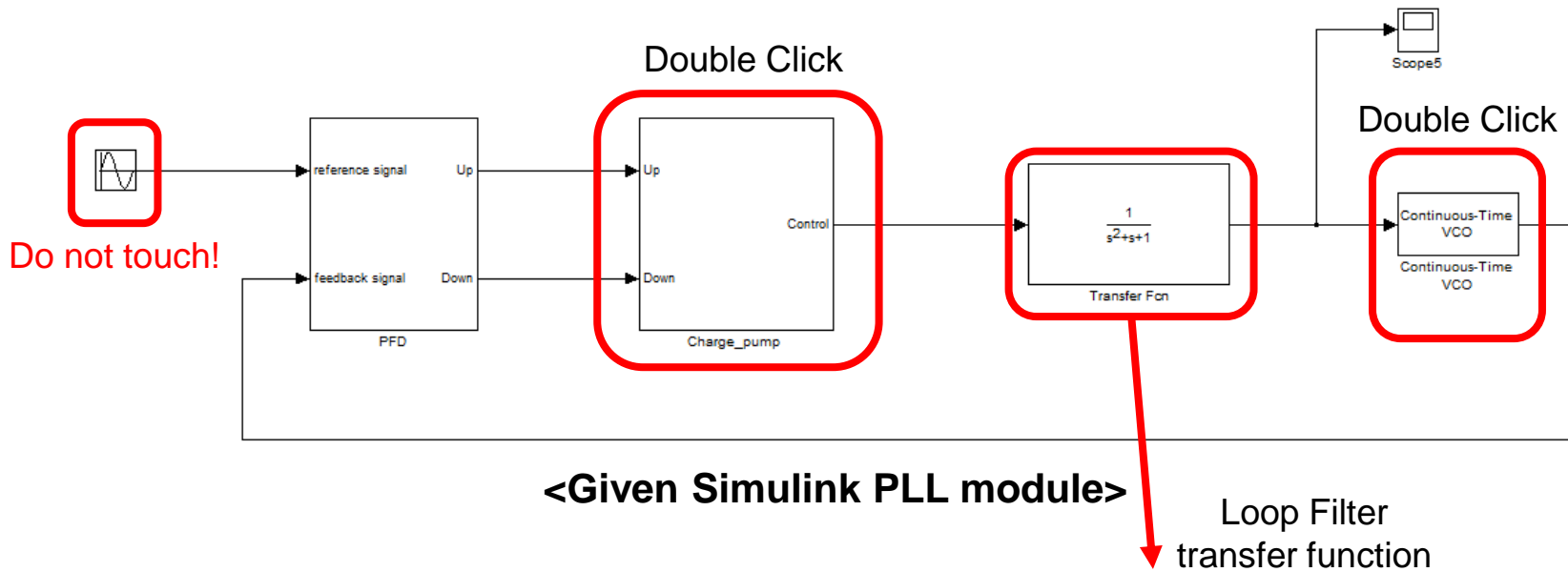
## Problem 3(b) – MATLAB Simulink simulation



# Simulation Setup

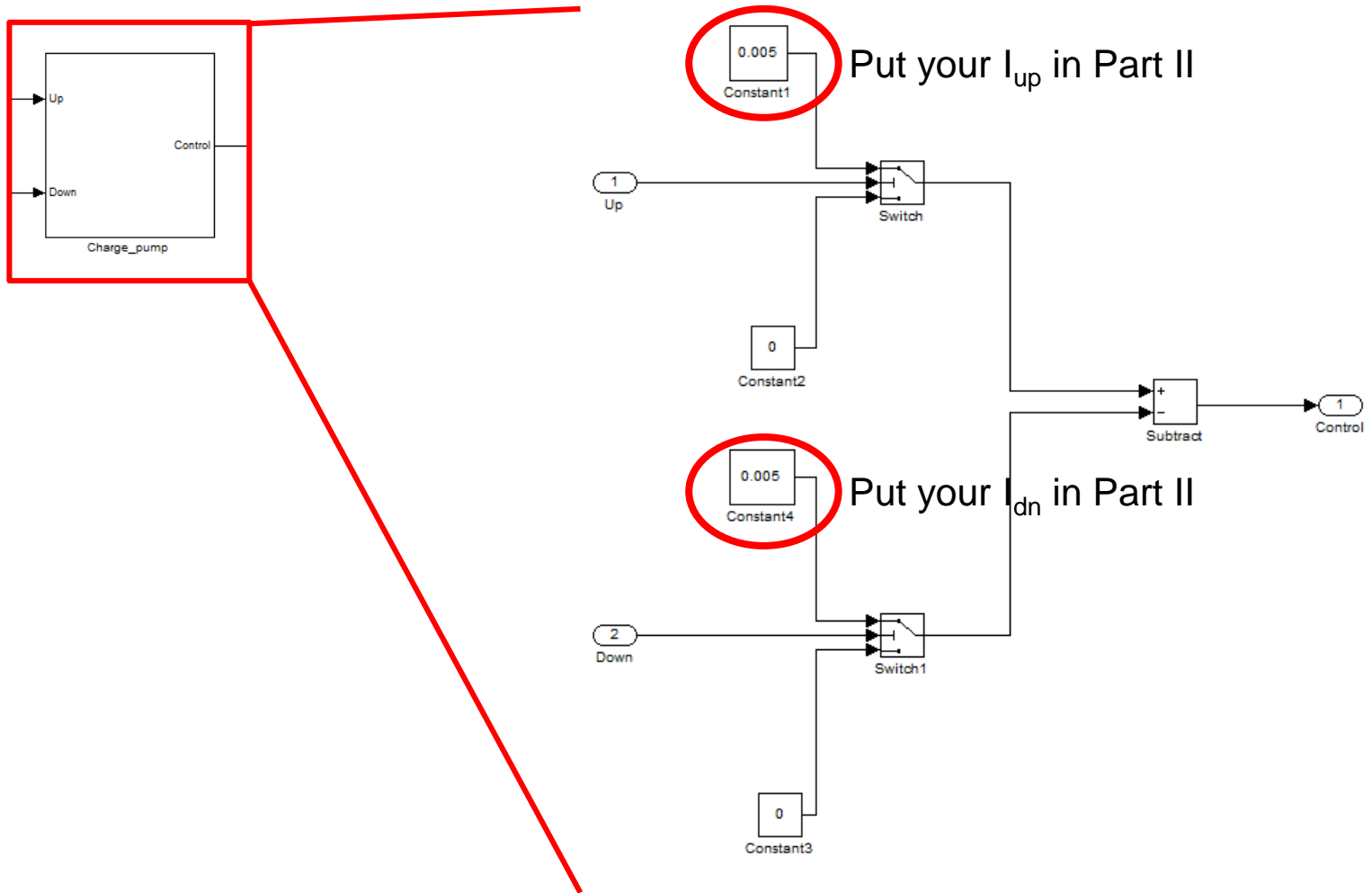

# Simulation Setup

 

Function Block Parameters: Continuous-Time VCO

Continuous-Time VCO (mask) (link)

Generate a continuous-time output signal whose frequency changes in response to the amplitude variations of the input signal. The input signal must be a sample-based scalar.

Parameters

Output amplitude (V):  
1      500e6-(Average VCO gain x your  $V_{cont}$ )

Quiescent frequency (Hz):  
200e6

Input sensitivity (Hz/V):  
100e6      Your average VCO gain


Initial phase (rad):  
0

OK    Cancel    Help    Apply

$$f_{out} = f_0 + gain \times V_{cont}$$

Quiescent frequency =  $f_0$

# Simulation Result


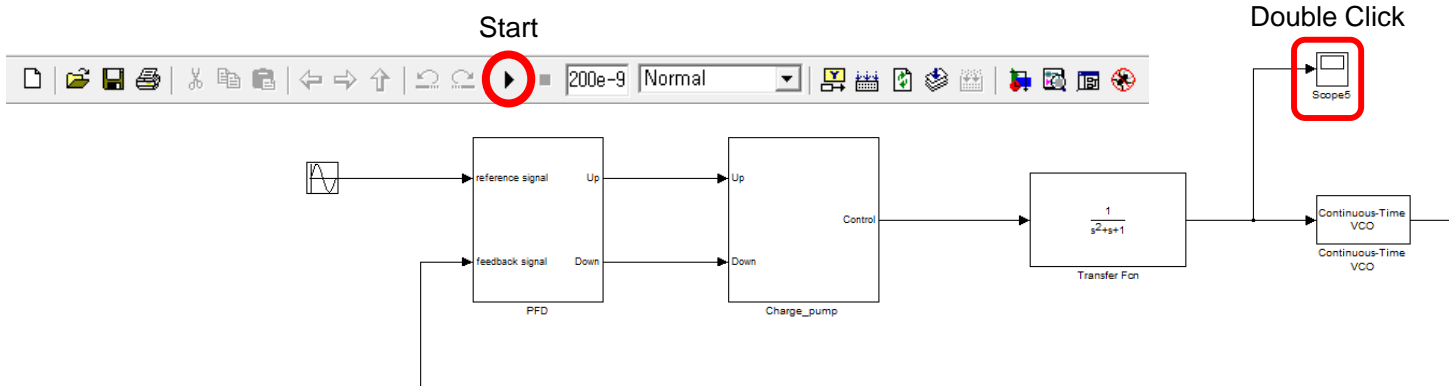


<Given Simulink PLL module>

Setting time

your  $V_{cont} - 0.005 < \text{Ripple} < \text{your } V_{cont} + 0.005$

ex) your  $V_{cont} = 1.7V$

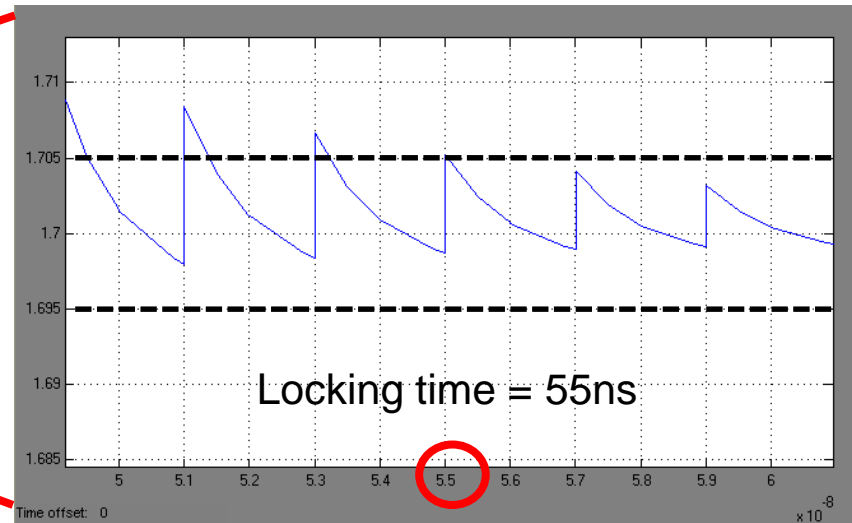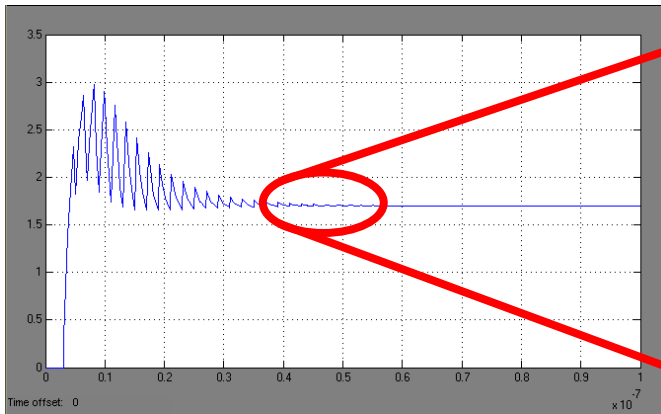

# Simulation Tip

✓ MATLAB transfer function

-Sample code for  $H(s) = \frac{s+1}{s^2+s+1}$

```
1  
2 - s=tf('s'); %define s-domain  
3 - transfer_function=(s+1)/(s^2+s+1); %put your transfer function  
4 - bode(transfer_function); % bode plot
```



# Grading Policy

---

- VCO design[20], Charge pump design[20], PLL design[50], Report[10]
- Describe how you get result with reasonable values in detail
- You will get more points for lower settling(locking time)
- Deadline : 6:00 PM , 22 June 2015 @ B629(Hardcopy)