

Test #2

June 8, 2015

Electronic Circuits (II)


Prof. Woo-Young Choi

Dept. of Electrical and Electronic Engineering

Yonsei University

Prob.1(30)

 
Consider the differential amplifier shown below. Assume M1 and M2 are identical, in saturation, have transconductance g_m . The channel length modulation can be ignored for this problem.



 
- (5) Redraw the circuit that contains all the capacitive elements of a MOS transistor, C_{GS} , C_{GD} , C_{SB} , C_{DB} .
- (5) How many poles does the amplifier transfer function, $[V_{out+}(s) - V_{out-}(s)] / [V_{in+}(s) - V_{in-}(s)]$, have? What are the pole angular frequencies? Use the Miller's theorem for this problem.
- (10) Determine the 3-dB bandwidth in Hz of the amplifier from the results obtained in (b). Assume resistance values for R_s and R_D are compatible, and capacitance values for are compatible C_{GS} , C_{GD} , C_{SB} , C_{DB} .
- (10) Determine f_t , the unit-gain frequency in Hz of this amplifier using the Miller's theorem.

Prob.2 (30)

Consider a filter having the following pole-zero diagram ($Q > 1/2$)



 - (5) Determine the filter transfer function $T(s)$. Normalize the transfer function so that $T(s=0)=1$.
- (5) Sketch the magnitude Bode plot of this filter. In your sketch, clearly indicate the locations and the values of any peaks.
- (10) Design this filter using passive components such as R , L , C . Specify conditions that R, L, C have to satisfy in terms of ω_0 and Q .
- (10) Design this filter using the Tow-Thomas biquad shown below. Redraw your Tow-Thomas filter including only the necessary components and specify the conditions that necessary components have to satisfy in terms of ω_0 and Q . You may satisfy only the magnitude of the filter.



Prob. 3 (20)


Give the transistor-level CMOS logic circuit for each of the following logic functions. You may use only NMOS and PMOS transistors in your answer.

(a) (10) $Y = ABC + D$

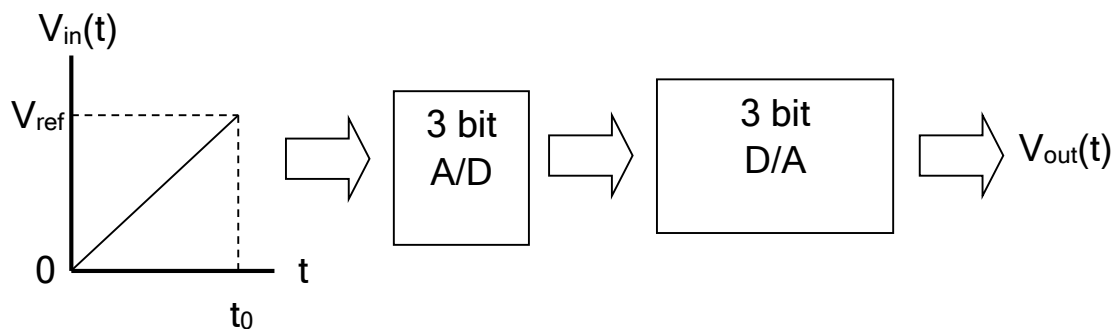
(b) (10) $Y = A \oplus B$ (A XOR B)

Prob. 4 (20)

We want convert $V_{in}(t)$ into binary codes and then back into analog signals using 3-bit A/D and 3-bit D/A as shown below. Assume the operation voltage ranges for A/D and D/A converters are from 0 to V_{ref} .



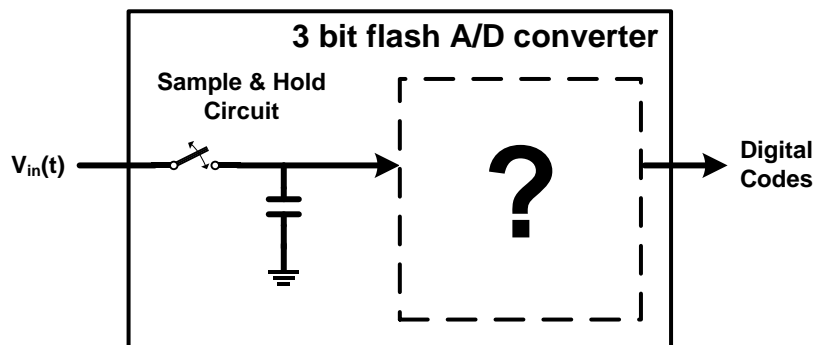(a) (5) Complete the block diagram of a 3-bit flash A/D converter shown below.



- (b) (5) Show the output binary code of the A/D converter as function of time.
- (c) (5) Show the block diagram of 3-bit D/A converter based on R-2R ladder. Clearly indicate how the A/D output (b1, b2, b3 with b1 MSB) is connected to the D/A converter.
- (d) (5) Plot the output of the D/A converter as function of time