
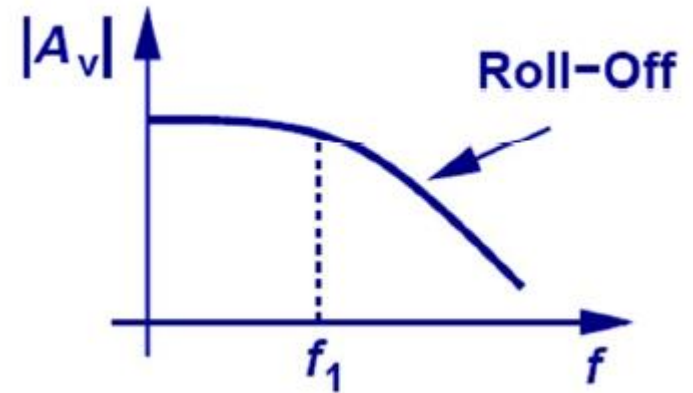



Lect. 10: Pole, Zero, Bode Plot

(Razavi 12.8.1)

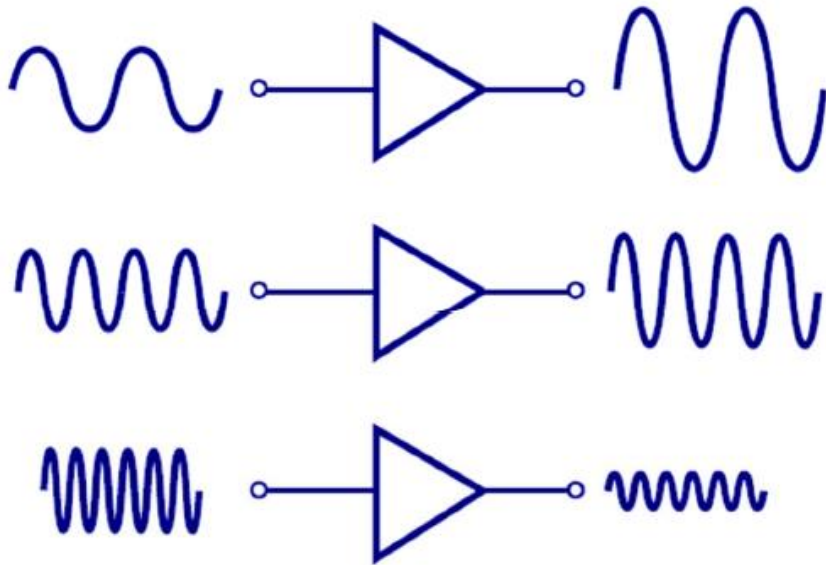


Lect. 10: Pole, Zero, Bode Plot

- Examples of Frequency Roll-off

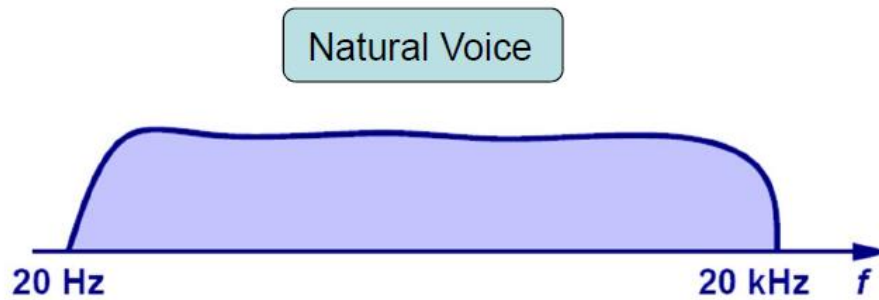

E

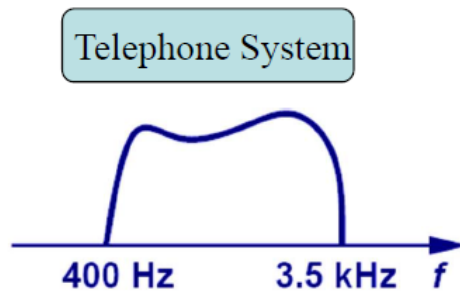


E

Lect. 10: Pole, Zero, Bode Plot


- How do we express frequency-domain characteristics of circuits?

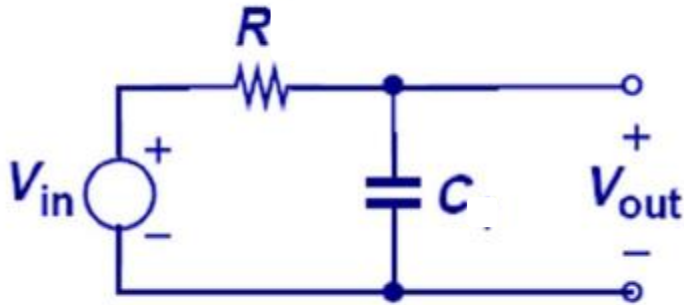→ Transfer functions in s-domain (Laplace Transform)



$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{1/sC}{1/sC + R} = \frac{1}{1 + sRC}$$

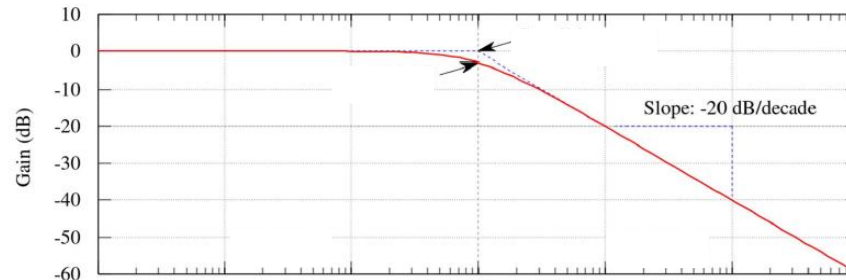- How do magnitude and phase of $H(s)$ change as frequency changes?



$$H(j\omega) = \frac{1}{1 + j\omega RC}$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$



Magnitude Bode Plot: $20 \log_{10} |H(j\omega)|$ (dB) vs $\log \omega$

Low-frequency limit? High-frequency limit?

At $\omega = \frac{1}{RC}$? → Pole at $s = -1/RC$

Lect. 10: Pole, Zero, Bode Plot

- Phase Bode Plot (One-pole system)

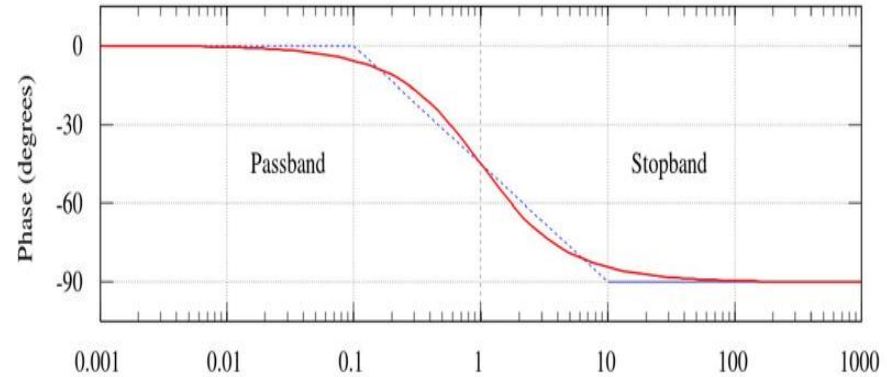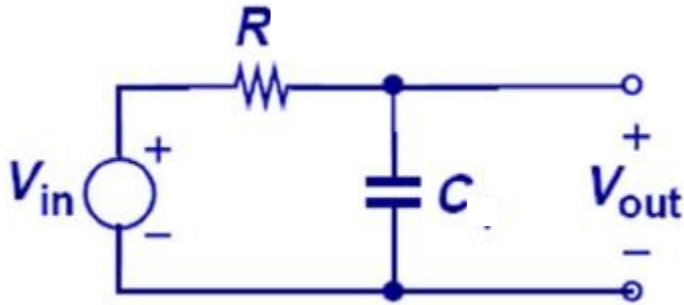

$$H(j\omega) = \frac{1}{1 + j\omega RC}$$

$$\angle H(j\omega) = -\tan^{-1}(\omega RC)$$

Low-frequency limit?

High-frequency limit?

At $\omega = \frac{1}{RC}$?



Lect. 10: Pole, Zero, Bode Plot

- How about $H(s)=1+sRC$?

$$H(j\omega)=1+j\omega RC$$

$$|H(j\omega)|=\sqrt{1+(\omega RC)^2}$$

$$\angle H(j\omega)=\tan^{-1}(\omega RC)$$

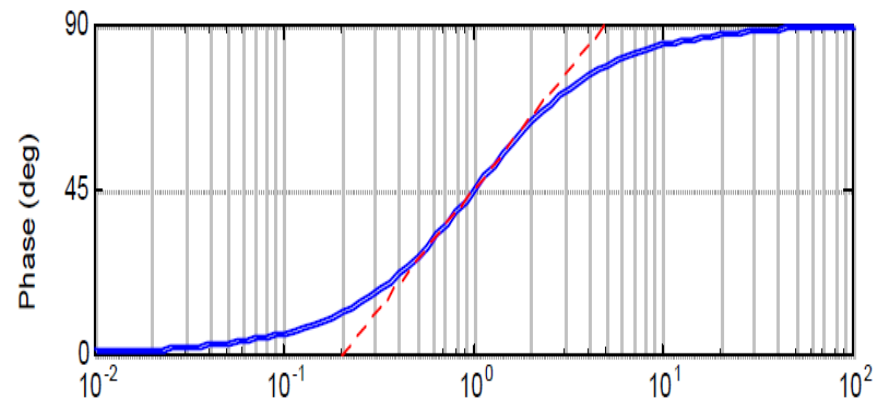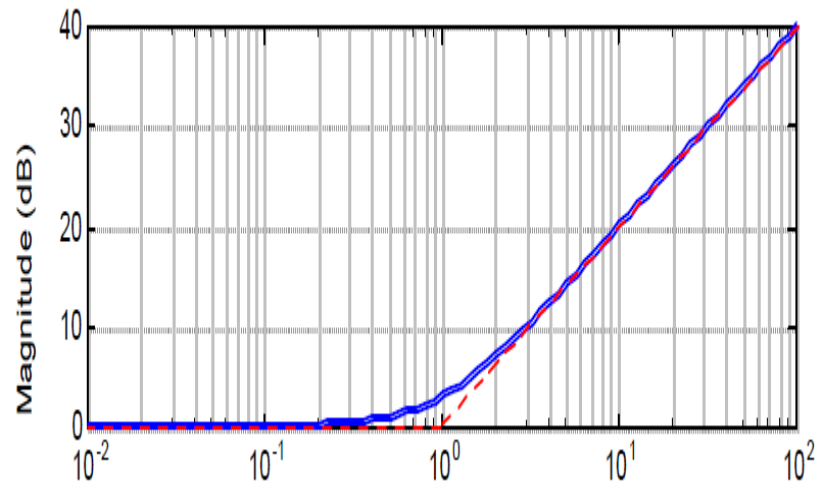


Lect. 10: Pole, Zero, Bode Plot

In general, electronic circuits have multiple poles and zeros

$$H(s) = A_0 \frac{\left(1 + \frac{s}{\omega_{z1}}\right) \left(1 + \frac{s}{\omega_{z2}}\right) L}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right) L}$$



(Assuming poles and zeros are all real)

→ Frequency response can be determined by pole, zero identification and 'addition' of each pole and zero response

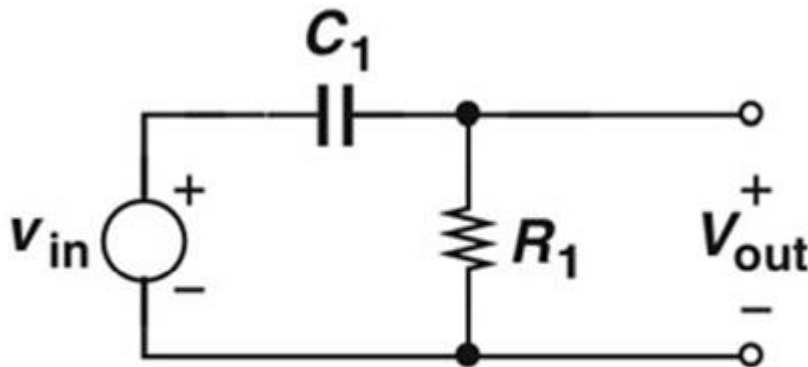


Lect. 10: Pole, Zero, Bode Plot

- Magnitude Bode Plot for MOS circuit
(Ignoring MOS frequency response, $\lambda = 0$)

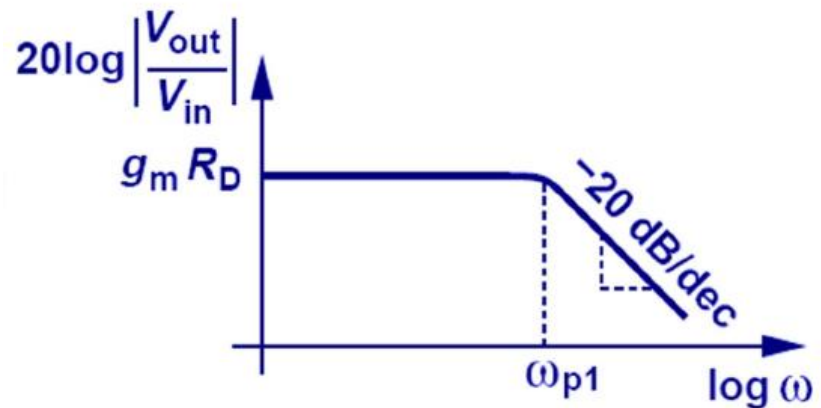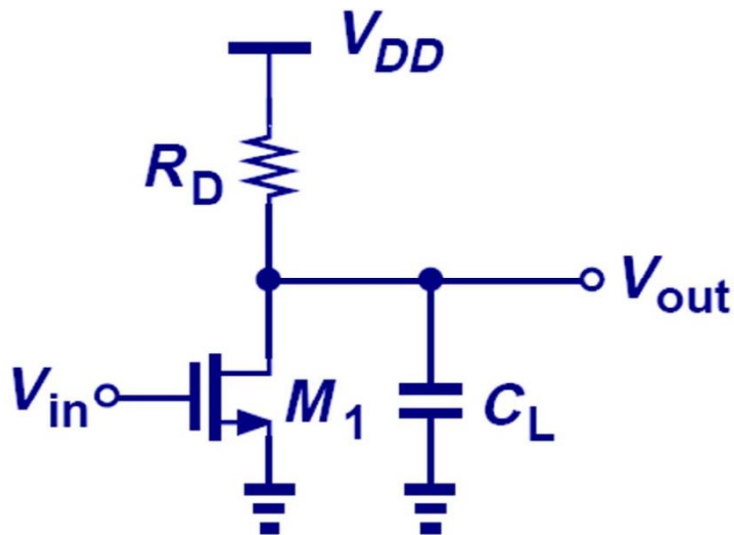


Lect. 10: Pole, Zero, Bode Plot

- Magnitude Bode Plot for MOS circuit
(Ignoring MOS frequency response, $\lambda = 0$)

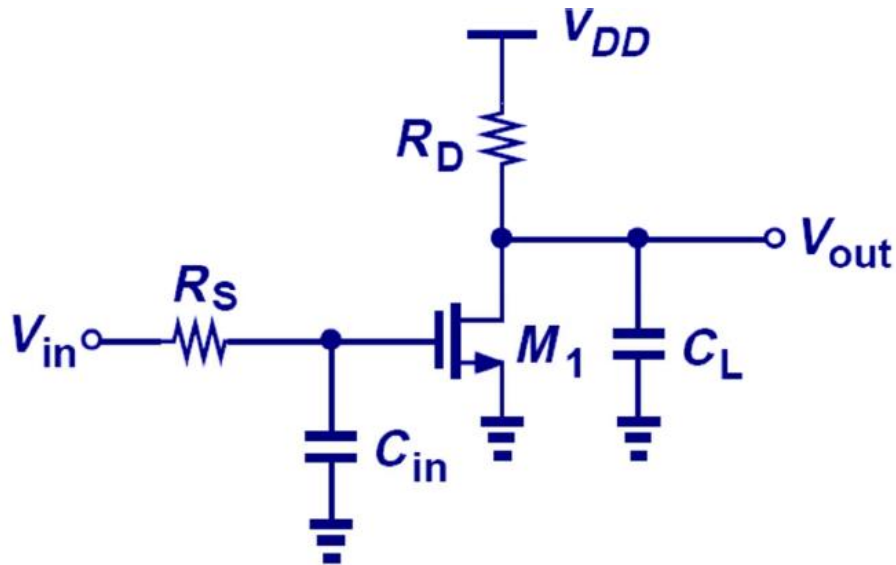

Lect. 10: Pole, Zero, Bode Plot

- Magnitude Bode Plot
(Ignoring MOS frequency response, $\lambda = 0$)

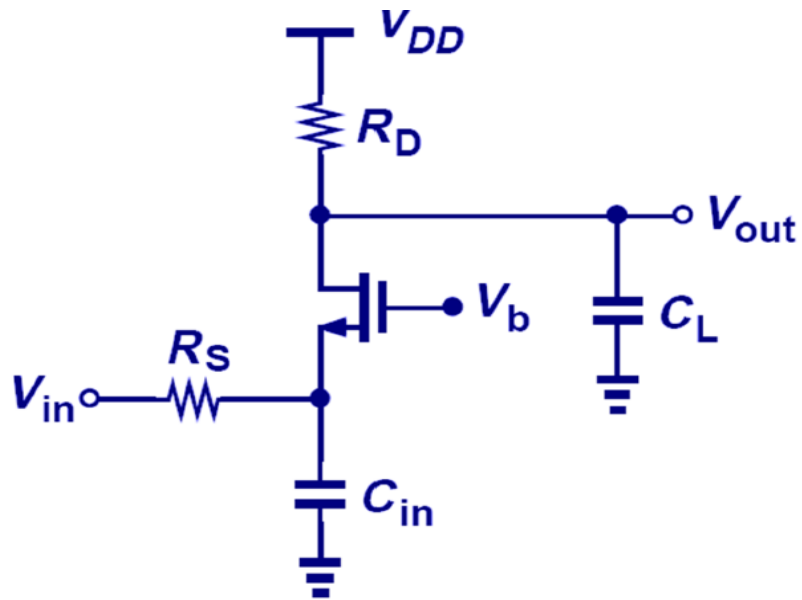

Lect. 10: Pole, Zero, Bode Plot

- Homework: Determine magnitude Bode plot for V_{out}/V_{in}
(Ignoring MOS frequency response, $\lambda = 0$.
Assume input pole frequency is lower than output pole, zero frequency)

