
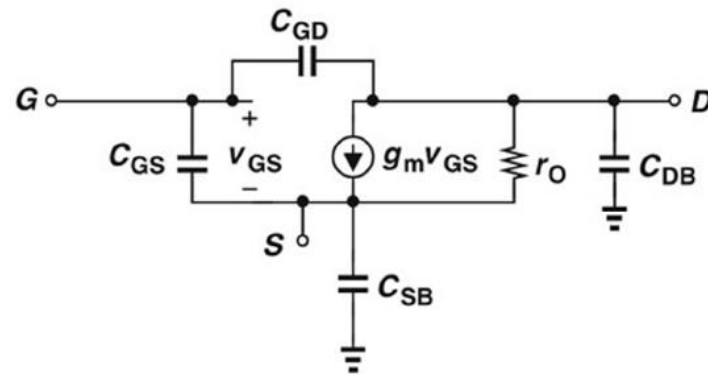
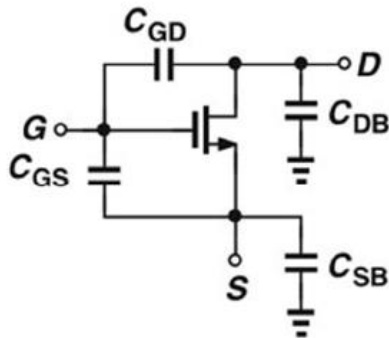


# Lect. 11: High-Frequency Response of MOS Transistors



(Razavi 11.2)

- MOSFET has many capacitive elements

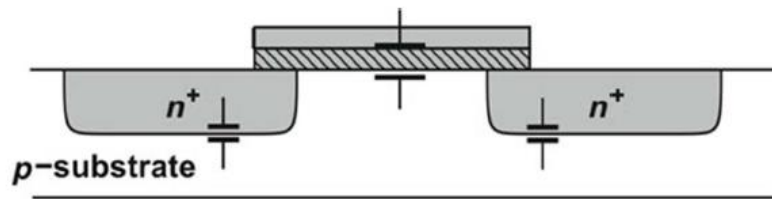

# Lect. 11: High-Frequency Response of MOS Transistors

- Circuit with capacitors

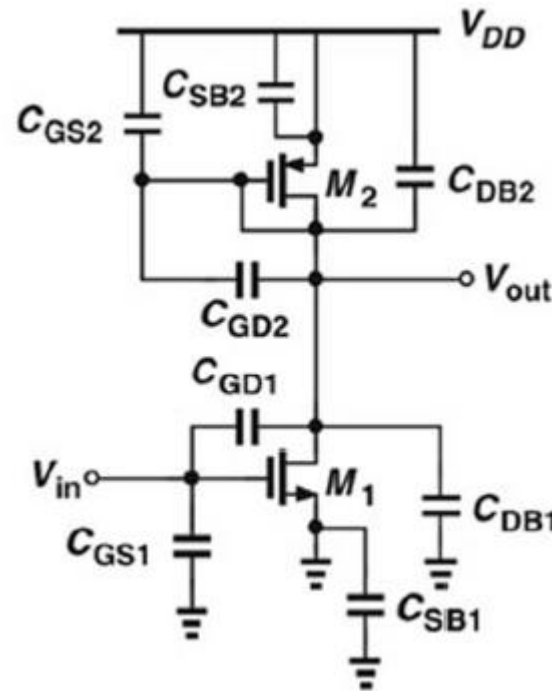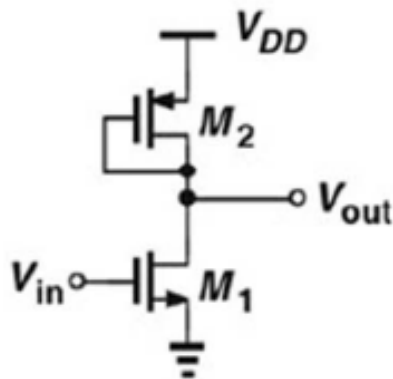



- Can be simplified somewhat but still requires very complex analysis  
→ Simulation

# Lect. 11: High-Frequency Response of MOS Transistors


- How fast can a MOSFET transistor operate?
- What determines this?

Unit-Gain Frequency ( $f_t$ ):

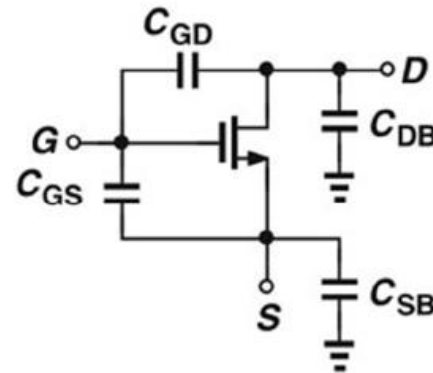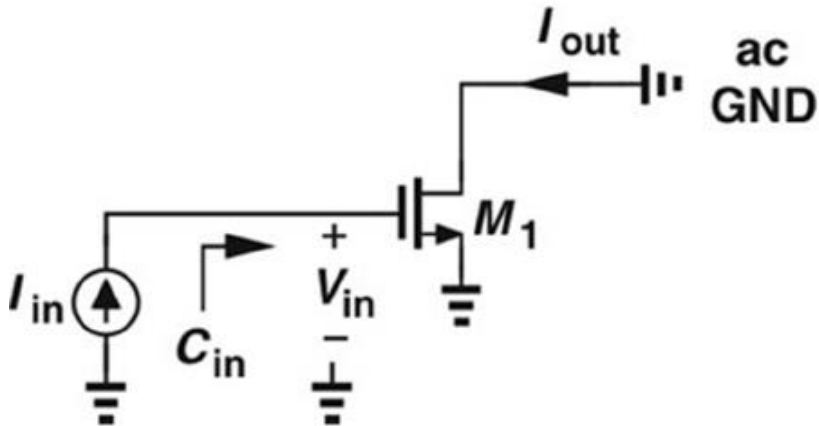Frequency at which magnitude of the short-circuit current gain of CS configuration becomes 1


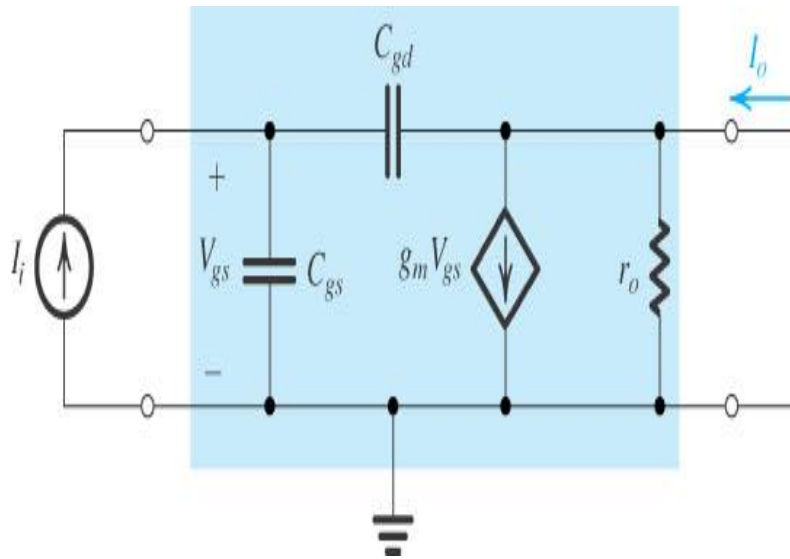
# Lect. 11: High-Frequency Response of MOS Transistors



$\frac{I_o}{I_i}$  in frequency ( $\omega$ ) domain?

$$I_o = g_m V_{gs} - \frac{V_{gs}}{1/j\omega C_{gd}} = g_m V_{gs} - j\omega C_{gd} V_{gs}$$

$$\sim g_m V_{gs} \quad (\text{assuming } g_m \gg \omega C_{gd})$$


$$V_{gs} = I_i \cdot \left( \frac{1}{j\omega C_{gd}} \parallel \frac{1}{j\omega C_{gs}} \right) = I_i \cdot \frac{1}{j\omega(C_{gd} + C_{gs})}$$

$$\therefore \frac{I_o}{I_i} = \frac{g_m}{j\omega(C_{gd} + C_{gs})}$$
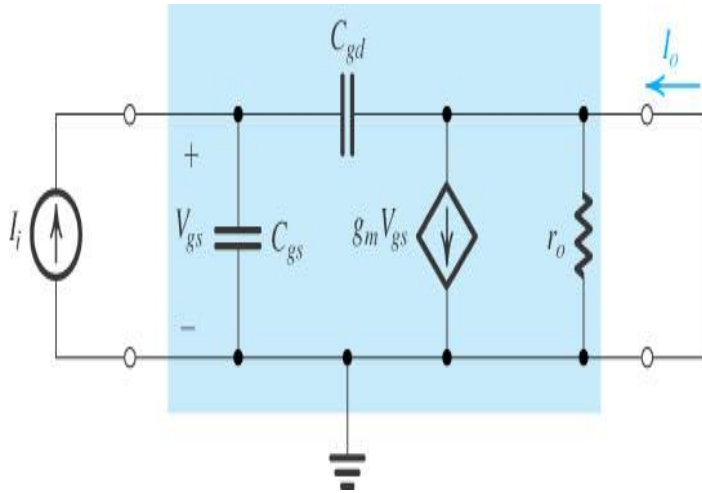
# Lect. 11: High-Frequency Response of MOS Transistors

Unit-Gain Frequency ( $f_t$ ):

Frequency at which magnitude of the short-circuit current gain of CS configuration becomes 1



$$\frac{I_o}{I_i} = \frac{g_m}{j\omega(C_{gd} + C_{gs})}$$

$$\text{For } \left| \frac{I_o}{I_i} \right| = 1, \quad \omega = \frac{g_m}{C_{gd} + C_{gs}}$$

$$f_T = \frac{g_m}{2\pi(C_{gd} + C_{gs})}$$

How to make MOSFET faster?

Which is faster, NMOS or PMOS?

$$g_m = \sqrt{2\mu C_{ox} \cdot \frac{W}{L} \cdot I_D}$$

# Lect. 11: High-Frequency Response of MOS Transistors

$$f_T = \frac{g_m}{2\pi * (C_{gd} + C_{gs})}$$

Confirm above with our PSPICE model

( $L=0.25\mu\text{m}$  ,  $W=10\mu\text{m}$  ,  $V_{DS}=2\text{V}$  ,  $V_{GS}=1.5\text{V}$ )

$$C_{gs} = 1.51 * 10^{-14} [F]$$


$$C_{gd} = 4.59 * 10^{-15} [F]$$

$$g_m = 0.00304 [A/V]$$

$$f_T = \frac{0.00304}{2\pi * (1.968 * 10^{-14})} = 24.5\text{GHz}$$

```
MODEL orbit2L2N NMOS ( LEVEL = 7
+TNOM = 27 TOX = 5.6E-9
+XJ = 1E-7 NCH = 2.3549E17 VTH0 = 0.3654765
+K1 = 0.4732214 K2 = 7.994532E-4 K3 = 1E-3
+K3B = 3.0713494 W0 = 1E-7 NLX = 1.617898E-7
+DVT0W = 0 DVT1W = 0 DVT2W = 0
+DVT0 = 0.455178 DVT1 = 0.6258687 DVT2 = -0.5
+U0 = 280.4589023 UA = -1.607126E-9 UB = 2.806549E-18
+UC = 3.290051E-11 VSAT = 1.07496E5 A0 = 1.8770435
+AGS = 0.3310181 B0 = -3.173524E-8 B1 = -1E-7
+KETA = -8.69841E-3 A1 = 8.317145E-5 A2 = 0.6592347
+RDSW = 200 PRWG = 0.4477477 PRWB = 0.0208175
+WR = 1 WINT = 0 LINT = 1.392558E-10
+DWG = -2.28419E-8
+DWB = -6.95781E-10 VOFF = -0.0910963 NFACTOR = 1.202941
+CIT = 0 CDSC = 2.4E-4 CDSCD = 0
+CDSCB = 0 ETA0 = 5.0732E-3 ETAB = 6.262008E-5
+DSUB = 0.0310034 PCLM = 1.5101091 PDIBLC1 = 0.897659
+PDIBLC2 = 2.924029E-3 PDIBLCB = 0.0651312 DROUT = 1
+PSCBE1 = 7.017738E8 PSCBE2 = 2.271109E-4 PVAG = 8.531511E-3
+DELTA = 0.01 RSH = 4.6 MOBMOD = 1
+PRT = 0 UTE = -1.5 KT1 = -0.11
+KT1L = 0 KT2 = 0.022 UA1 = 4.31E-9
+UB1 = -7.61E-18 UC1 = -5.6E-11 AT = 3.3E4
+WL = 0 WLN = 1 WW = 0
+WWN = 1 WWL = 0 LL = 0
+LLN = 1 LW = 0 LWN = 1
+LWL = 0 CAPMOD = 2 XPART = 0.5
+CGDO = 4.59E-10 CGSO = 4.59E-10 CGBO = 5E-10
+CJ = 1.78338E-3 PB = 0.99 MJ = 0.4661295
+CJSW = 4.154041E-10 PBSW = 0.9563049 MJSW = 0.3162462
+CF = 0 PVTH0 = -9.648921E-3 PRDSW = -10
+PK2 = 3.534961E-3 WKETA = 0.0120981 LKETA = -3.31688E-3 )
```
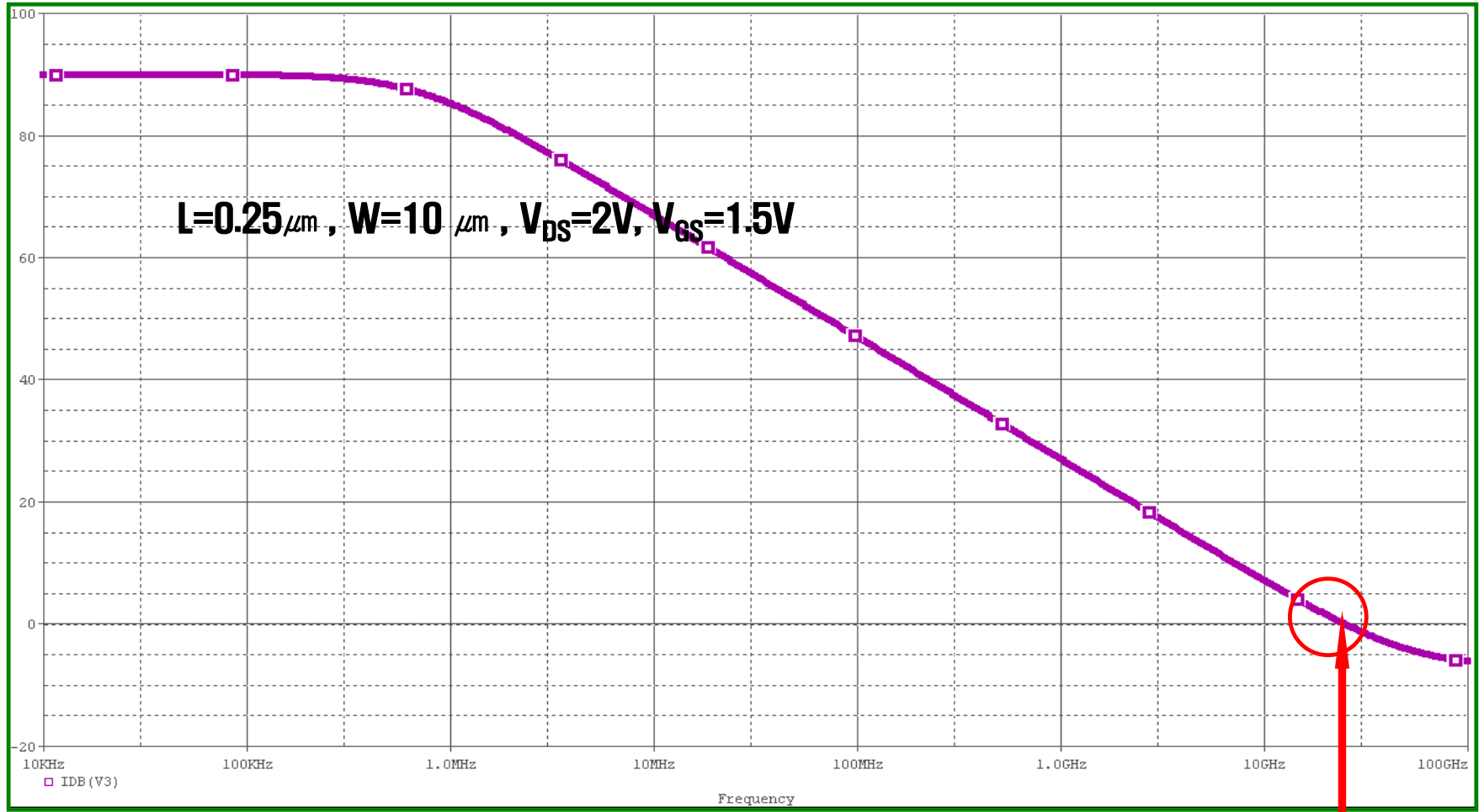
# Lect. 11: High-Frequency Response of MOS Transistors



24.9GHz

# Lect. 11: High-Frequency Response of MOS Transistors

## Homework

-Determine by simulation how  $f_T$  changes as a function of  $V_{GS}$  (from 1V to 2V) and  $V_{DS}$  (from 1V to 2V) for our NMOS transistor with  $L=0.25\mu m$ ,  $W=10\mu m$ .

