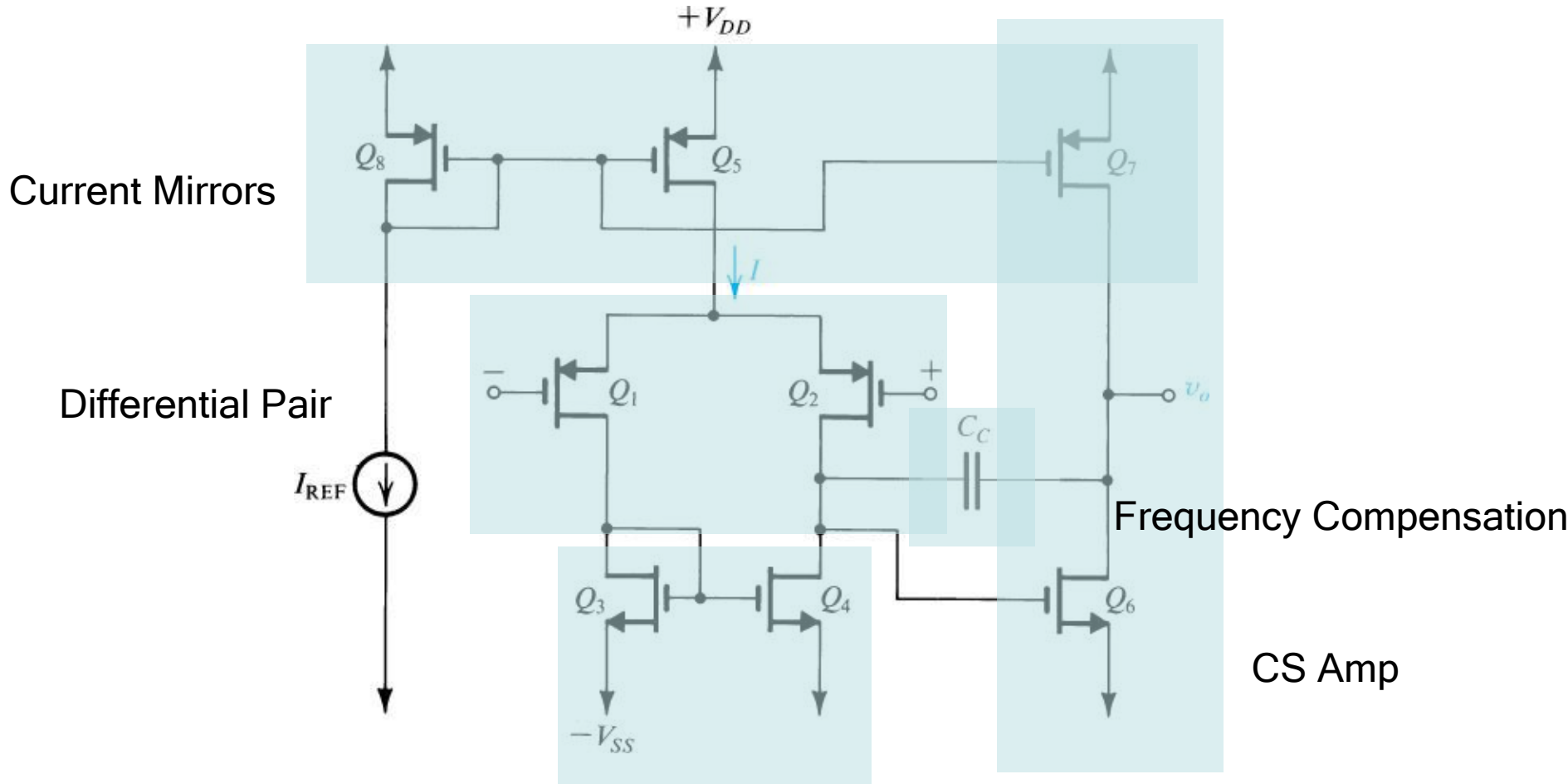



Lect. 15: Two-Stage Amplifier



Analysis of Two-Stage Transconductance Amplifier: Qualitative Understanding

Lect. 15: Two-Stage Amplifier

Input Common-Mode Range

 

Large $I \rightarrow$ Large V_{SG5} , V_{SG1} , V_{GS3}
 \rightarrow Small input CM range

For $V_{ICM,min}$, Q_1 , Q_2 should be in saturation

$$V_{SD1} > V_{SG1} - |V_{tp}|$$

$$V_{S1} - V_{D1} > V_{S1} - V_{ICM} - |V_{tp}|$$

$$V_{ICM} > V_{D1} - |V_{tp}|$$

$$V_{ICM,min} = -V_{ss} + V_{GS3} - |V_{tp}|$$

For $V_{ICM,max}$, Q_5 should be in saturation

$$V_{SD5} > V_{SG5} - |V_{tp}|$$


$$V_{S5} - V_{D5} > V_{S5} - V_{G5} - |V_{tp}|$$

$$V_{D5} < V_{G5} + |V_{tp}| = V_{DD} - V_{SG5} + |V_{tp}|$$

$$V_{ICM} + V_{SG1} < V_{DD} - V_{SG5} + |V_{tp}|$$

$$V_{ICM,max} = V_{DD} - V_{SG5} - V_{SG1} + |V_{tp}|$$

Lect. 15: Two-Stage Amplifier

 

Voltage Gain (DC)

Two CS amps in cascade

$$G_{m1} =$$

$$R_1 =$$

$$A_{V1} =$$

$$G_{m2} =$$

$$R_2 =$$


$$A_{V2} =$$

$$A_V =$$


$$R_{in} =$$

$$R_{out} =$$

Small Signal Model

 


Lect. 15: Two-Stage Amplifier

 


Frequency Response


For simplicity, assume all the capacitive elements are lumped together as C_1 and C_2 .

 

Lect. 15: Two-Stage Amplifier

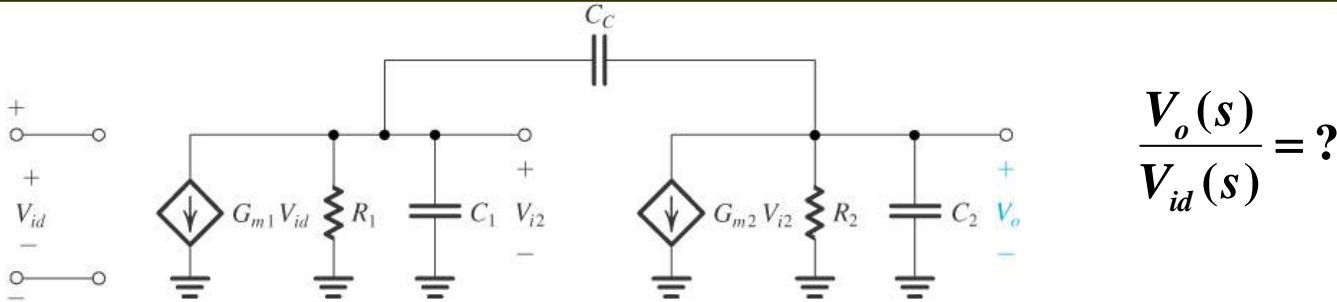

In Lect. 14,

 


$$\frac{V_o}{V_i} = \frac{(g_m - sC_{gd})R_2}{1 + s[C_{gs}R_1 + C_2R_2 + C_{gd}(g_mR_1R_2 + R_1 + R_2)] + s^2[C_{gs}C_2 + C_{gd}(C_{gs} + C_2)]R_1R_2}$$

Since $V_i = -G_{m1}V_{id}R_1$, $\frac{V_o(s)}{V_{id}(s)} = -G_{m1}R_1 \frac{V_o(s)}{V_i(s)}$ Same pole zero characteristics!


With corresponding parameter changes

Lect. 15: Two-Stage Amplifier

In Lect. 14,

 

 
$$\omega_{P1} \sim \frac{1}{C_{gd} g_m R_2 R_1} \quad \omega_{P2} \sim \frac{g_m C_{gd}}{C_{gs} C_2 + C_{gd} (C_{gs} + C_2)}$$



$$\omega_{P1} \sim \frac{1}{C_C G_{m2} R_2 R_1} \quad \omega_{P2} \sim \frac{G_{m2} C_C}{C_1 C_2 + C_C (C_1 + C_2)}$$

Can be used for initial design of the amp for the desired bandwidth and phase margin


Lect. 15: Two-Stage Amplifier

 

Where is zero?

- Zero in the right half-plane decreases the phase margin
- Move the zero to the left half-plane!

Lect. 15: Two-Stage Amplifier

 

- Move the zero to the left half-plane!

$$\text{With } V_o = 0 \quad V_{i2} = G_{m2} V_{i2} \left(R + \frac{1}{sC_c} \right)$$


$$\text{Zero at } s = \frac{1}{C_c \left(\frac{1}{G_{m2}} - R \right)}$$

When $R > 1/G_{m2}$, the zero moves to the left-half plane!

→ Good for phase margin!

Lect. 15: Two-Stage Amplifier

Mirrored OTA for Design Project #1

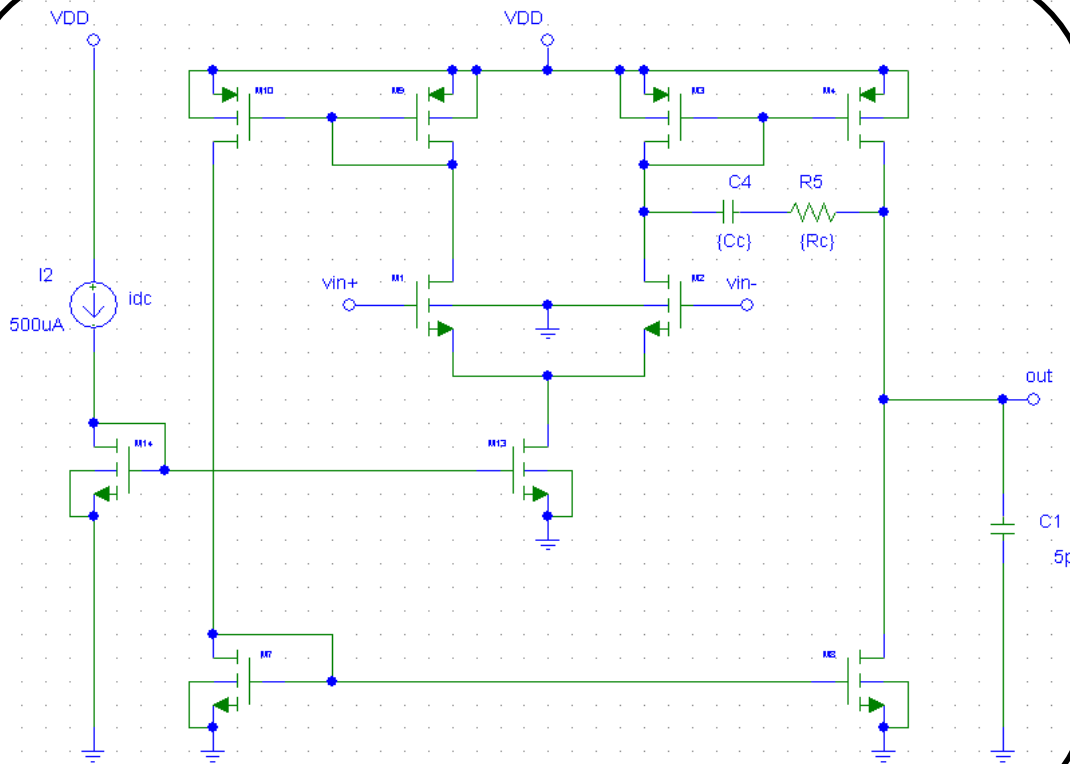


- Mirrored OTA Specifications

Parameter	Value
A_V	> 56dB
Bandwidth	> 60KHz
Phase Margin	> 65°
V_{p-p}	> 1.5V
Slew Rate	> 13MV/s
CMRR	> 85dB
Power Consumption	< 2.5mW


Lect. 15: Two-Stage Amplifier

Slew Rate

 

Apply step input at $v^+ \rightarrow v_o(t)=?$


$$\text{Slew Rate: } \left. \frac{dv_o(t)}{dt} \right|_{\max}$$

 

With step input

Q_2 off \rightarrow I through $Q_1, Q_3 \rightarrow$ I through C_C

$$v_o(t) = \frac{I}{C_C} t$$

 

$$\left. \frac{dv_o}{dt} \right|_{\max} = \frac{I}{C_C}$$