
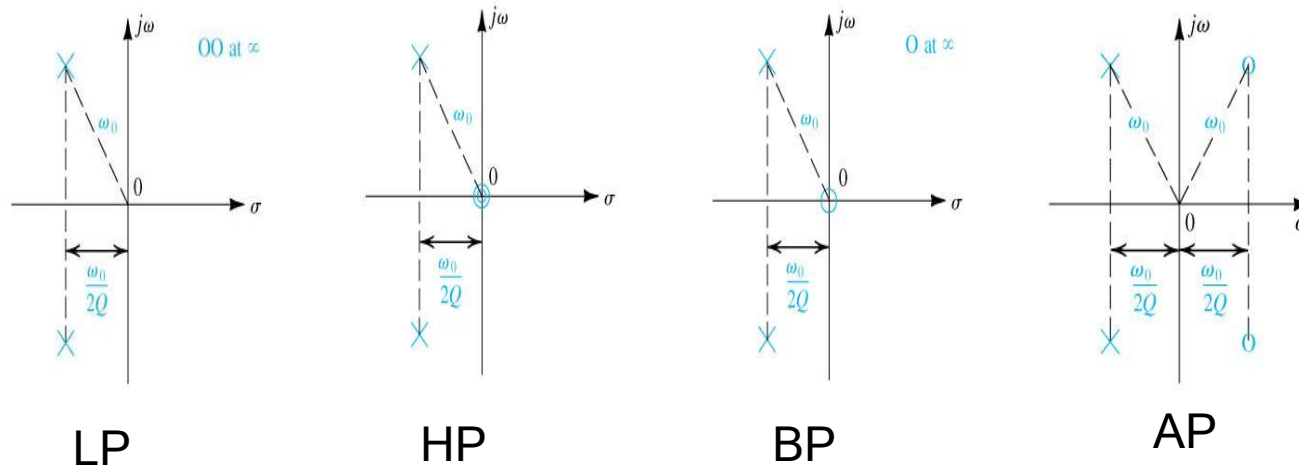


# Lect. 19: Second-Order Active Filters (Razavi 14.4)

## 2nd-order filters

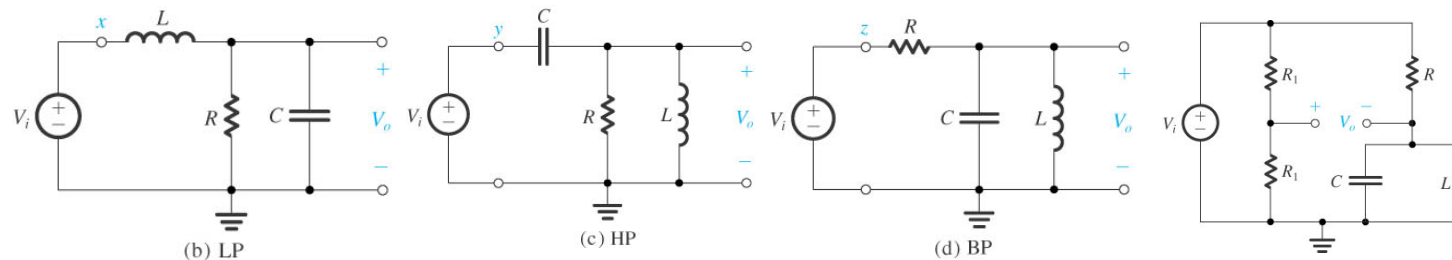

## Passive Realization




# Lect. 19: Second-Order Active Filters (Razavi 14.4)

---

Inductor:  $v = L \frac{di}{dt}$



Inductor on chip

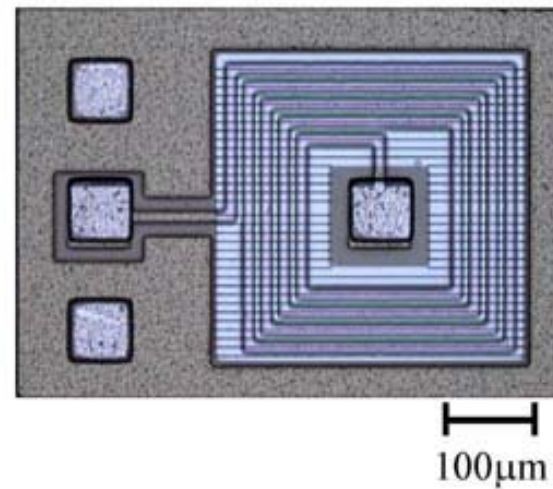


For IC implementation, inductors can be very large

Realization of inductive component by active circuits?


# Lect. 19: Second-Order Active Filters
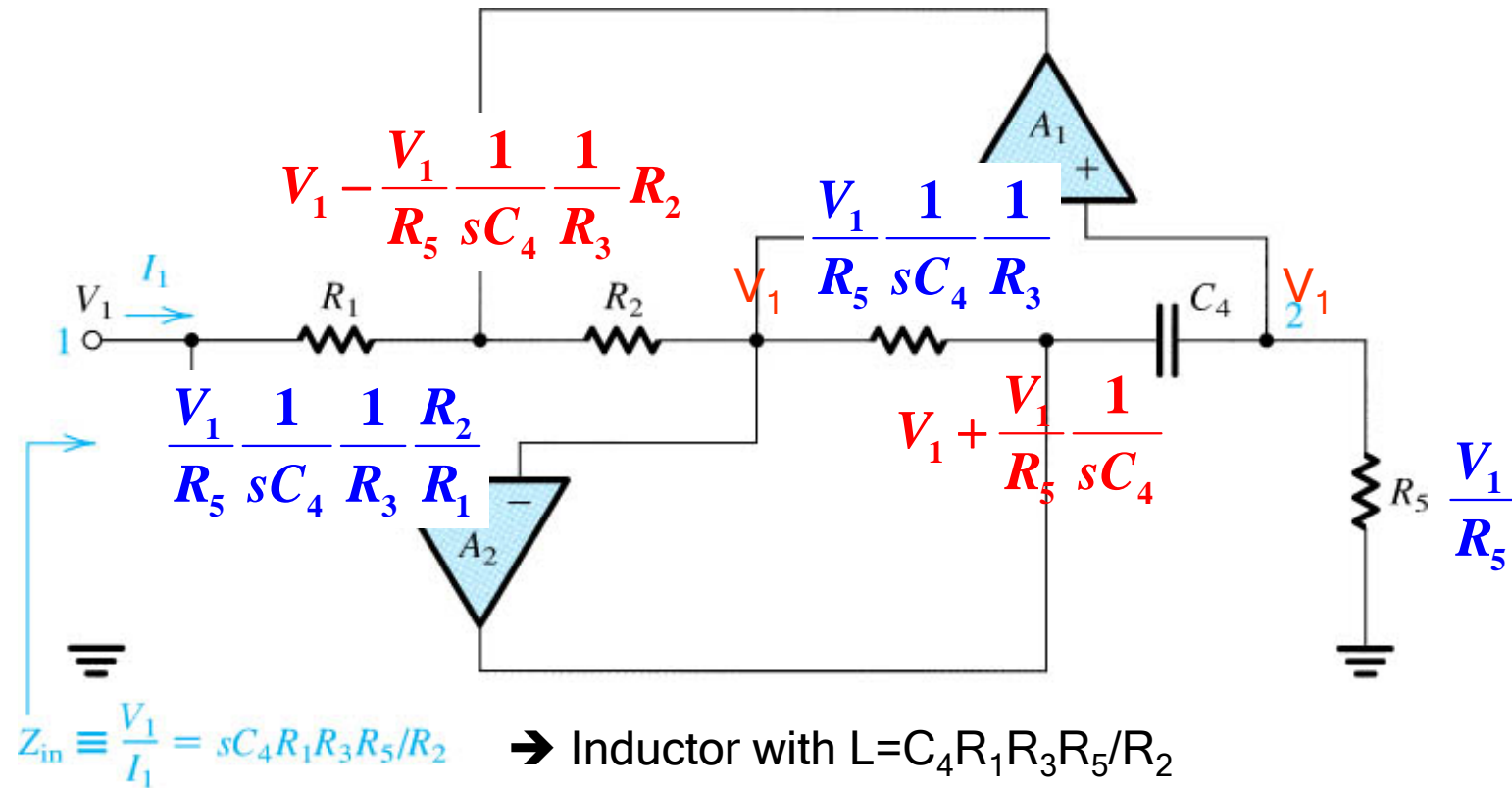
## Antoniou Inductance-Simulation Circuit




(a)

# Lect. 19: Second-Order Active Filters

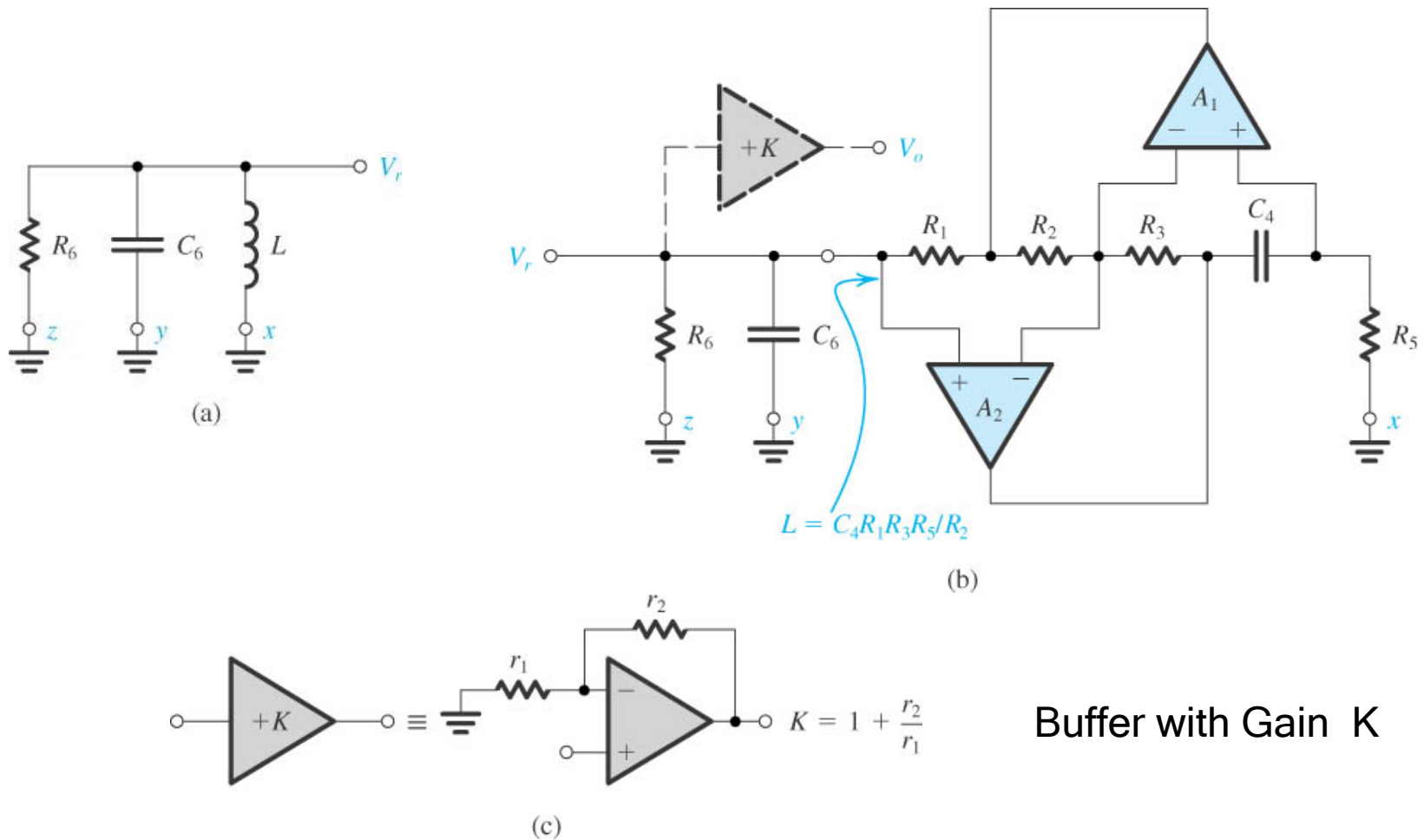


# Lect. 19: Second-Order Active Filters

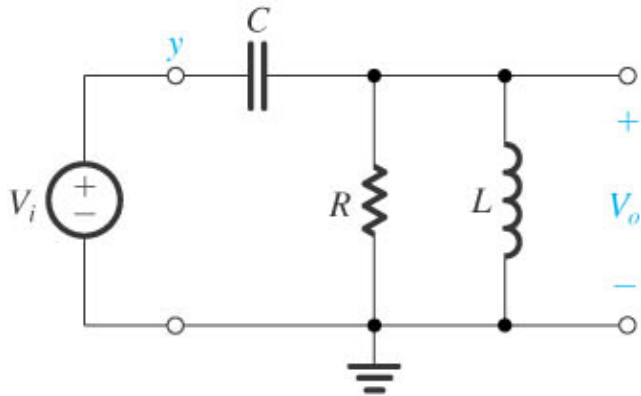

$$T(s) = \frac{s^2}{s^2 + s(1/RC) + (1/LC)}$$
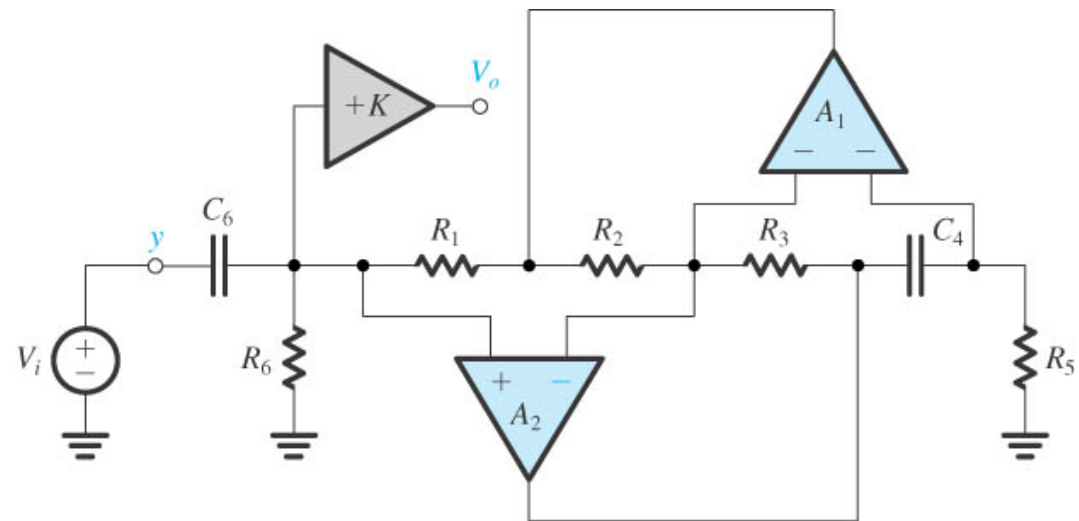
$$\omega_0 = \frac{1}{\sqrt{LC}} \quad Q = \sqrt{\frac{C}{L}}R$$




→ Replace L with  $C_4 R_1 R_3 R_5 / R_2$

Multiply K


# Lect. 19: Second-Order Active Filters

---

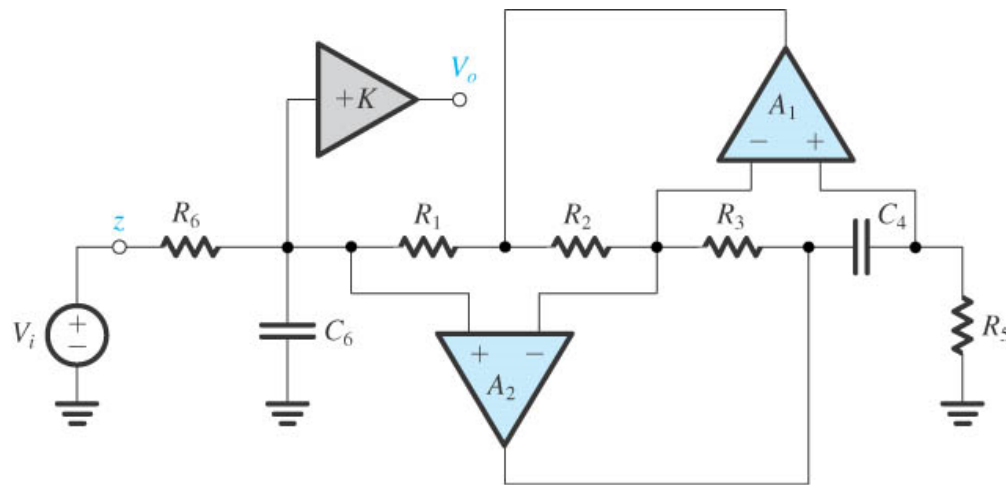

# Lect. 19: Second-Order Active Filters


## Second-Order All-Pass Filter

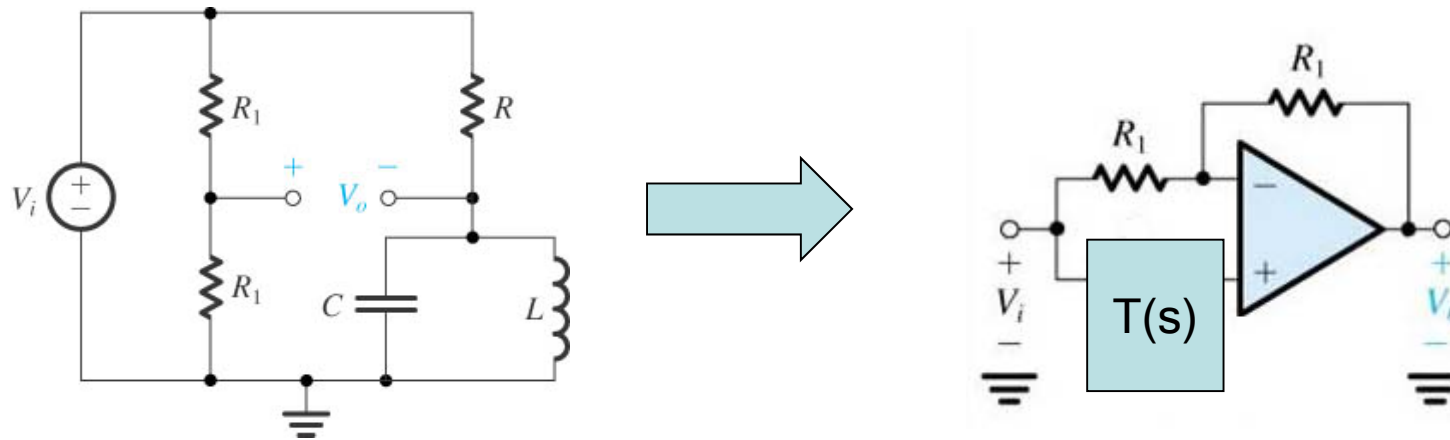


$$\begin{aligned}
 T(s) &= \frac{s^2 - s(\omega_0 / Q) + \omega_0^2}{s^2 + s(\omega_0 / Q) + \omega_0^2} \\
 &= 1 - \frac{2s(\omega_0 / Q)}{s^2 + s(\omega_0 / Q) + \omega_0^2} \\
 &= 2 \left( \frac{1}{2} - \frac{s(\omega_0 / Q)}{s^2 + s(\omega_0 / Q) + \omega_0^2} \right)
 \end{aligned}$$

T(s): Bandpass Filter

# Lect. 19: Second-Order Active Filters

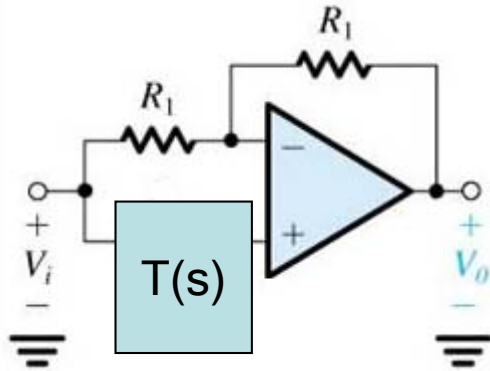

$T(s)$ : Bandpass Filter

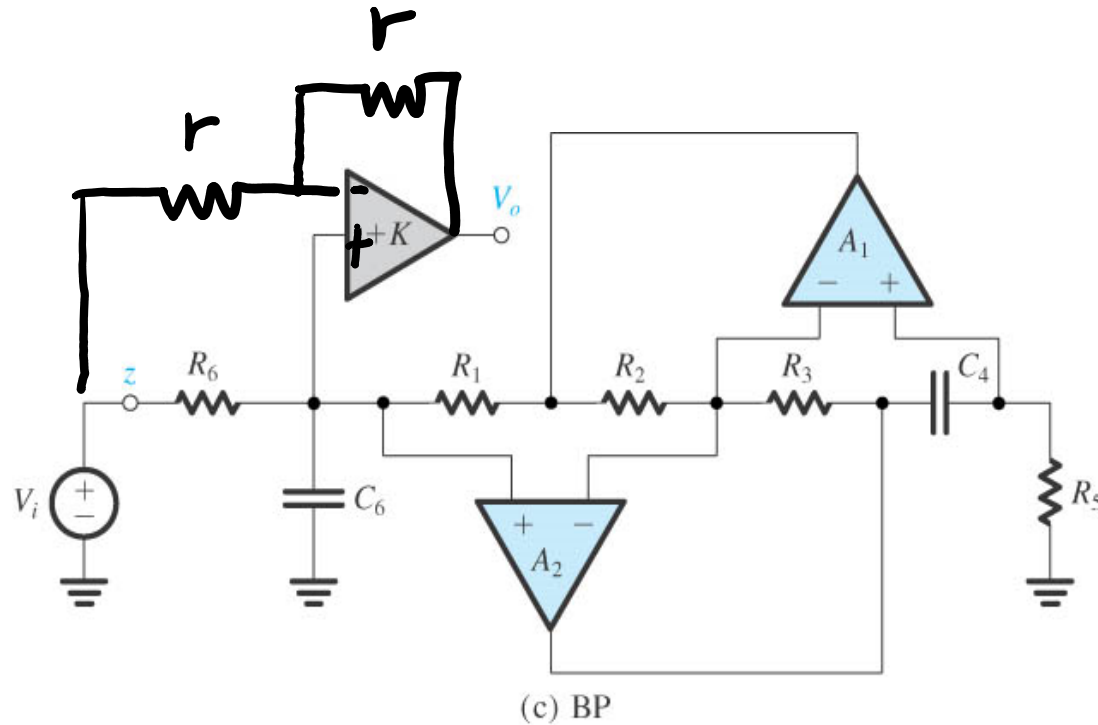


Second-order Bandpass Filter

→ Second-Order All-Pass Filter



# Lect. 19: Second-Order Active Filters


2nd-order LP filter

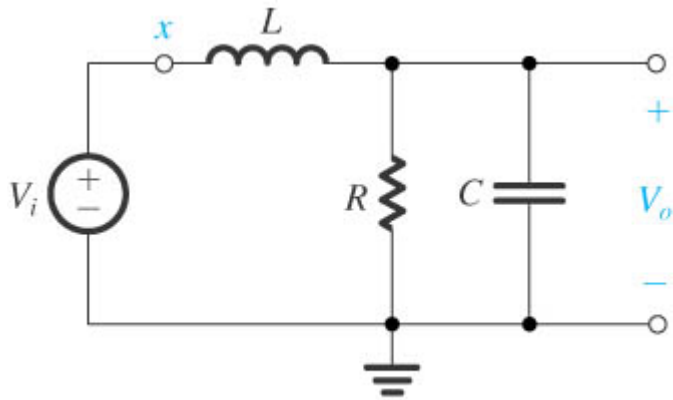

$$T(s) = \frac{\omega_0^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$


$$\omega_0 = \frac{1}{\sqrt{LC}} \quad Q = \sqrt{\frac{C}{L}}R$$

Antoniou Inductance-Simulation Circuit

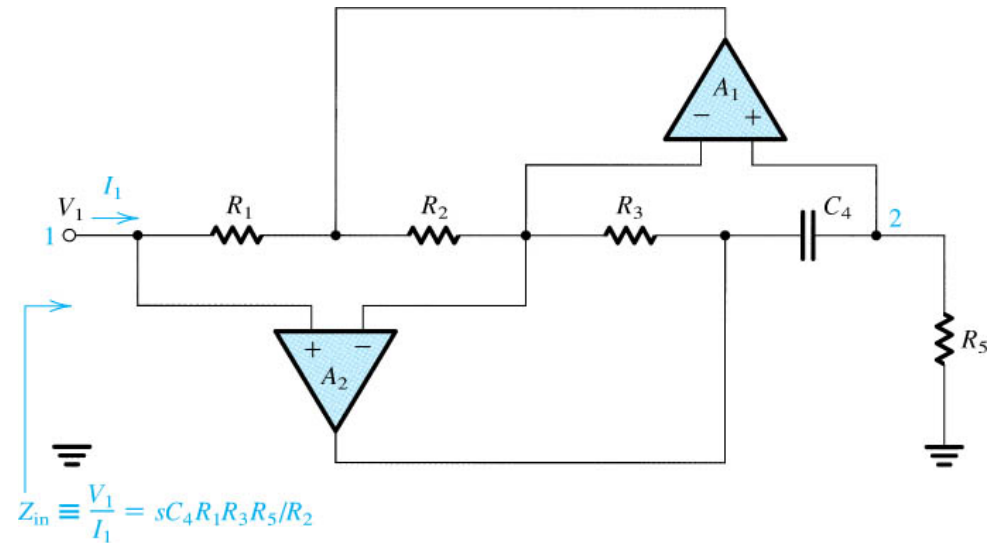

(a)

# Lect. 19: Second-Order Active Filters

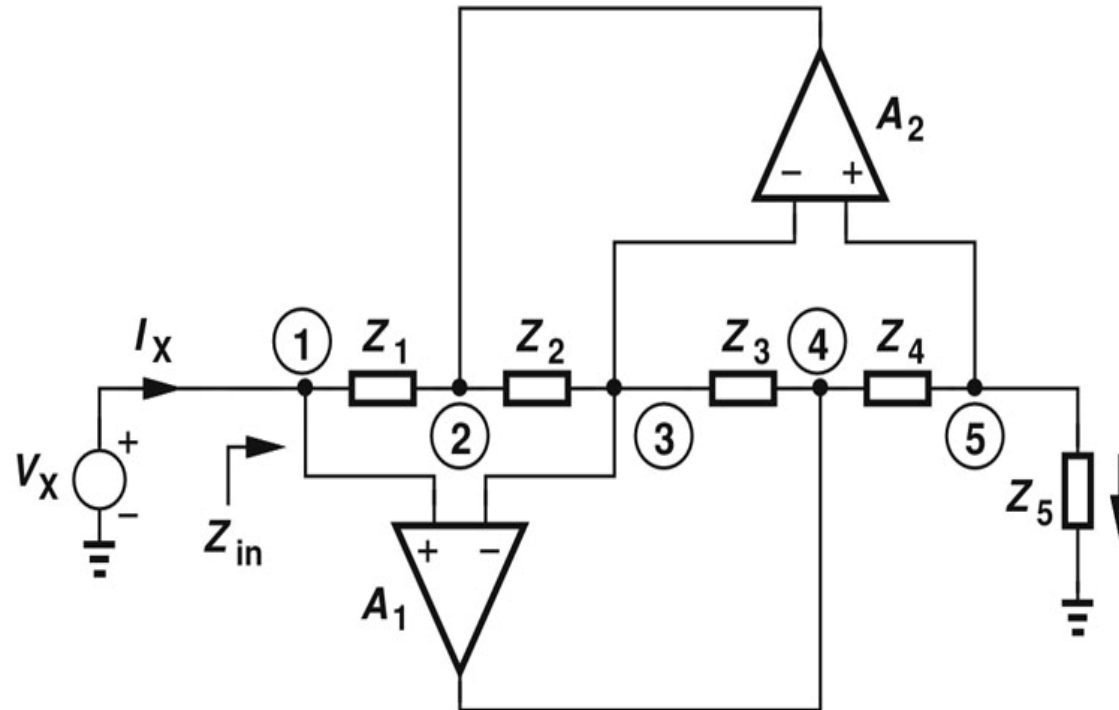

$$Z_{in} = \frac{Z_1 Z_3}{Z_2 Z_4} Z_5 \quad \text{Impedance converter}$$

# Lect. 19: Second-Order Active Filters

Homework:

Determine  $V_{out}(s)/V_{in}(s)$  for the circuit shown below. What type of filter is this?

