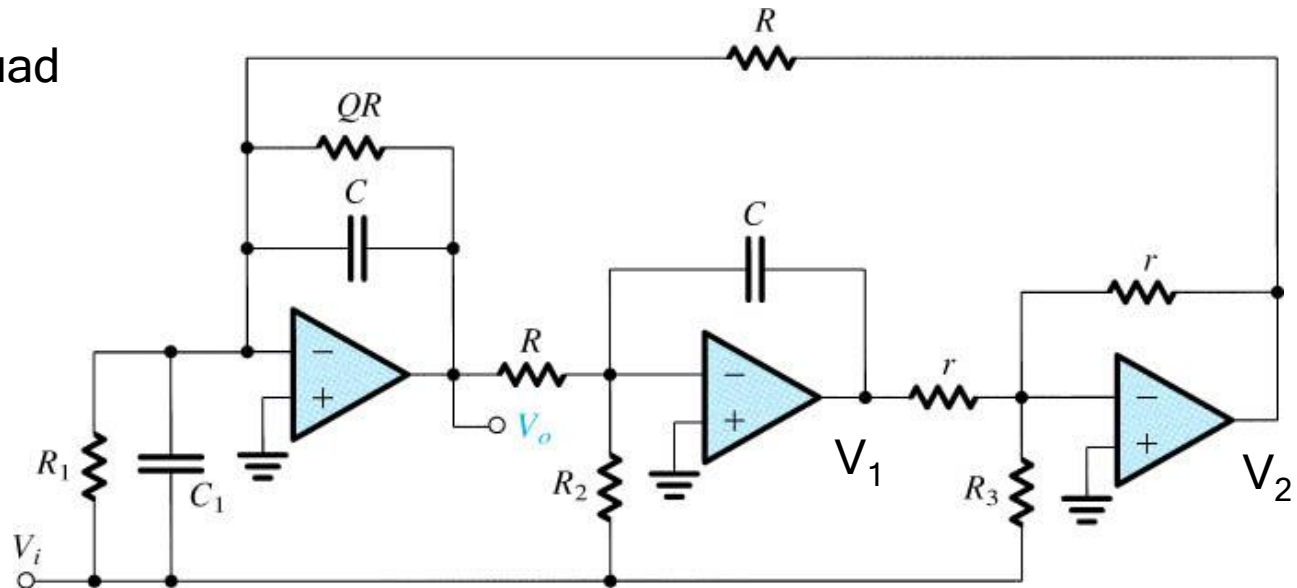


Lect. 22: Switched Capacitor Filters

Biquad can be used as a universal filter structure

Tow-Thomas biquad
(Lect. 20)



$$\frac{V_o}{V_i} = - \frac{s^2 \left(\frac{C_1}{C} \right) + s \frac{1}{C} \left(\frac{1}{R_1} - \frac{r}{RR_3} \right) + \frac{1}{C^2 RR_2}}{s^2 + s \frac{1}{QCR} + \frac{1}{C^2 R^2}}$$

Many R's are required


Lect. 22: Switched Capacitor Filters

Using many resistors are NOT desirable in IC design



- Large area
- Accurate control of R difficult

Circuit technique to solve the problem

→ Replace resistors with capacitors: Switched capacitor

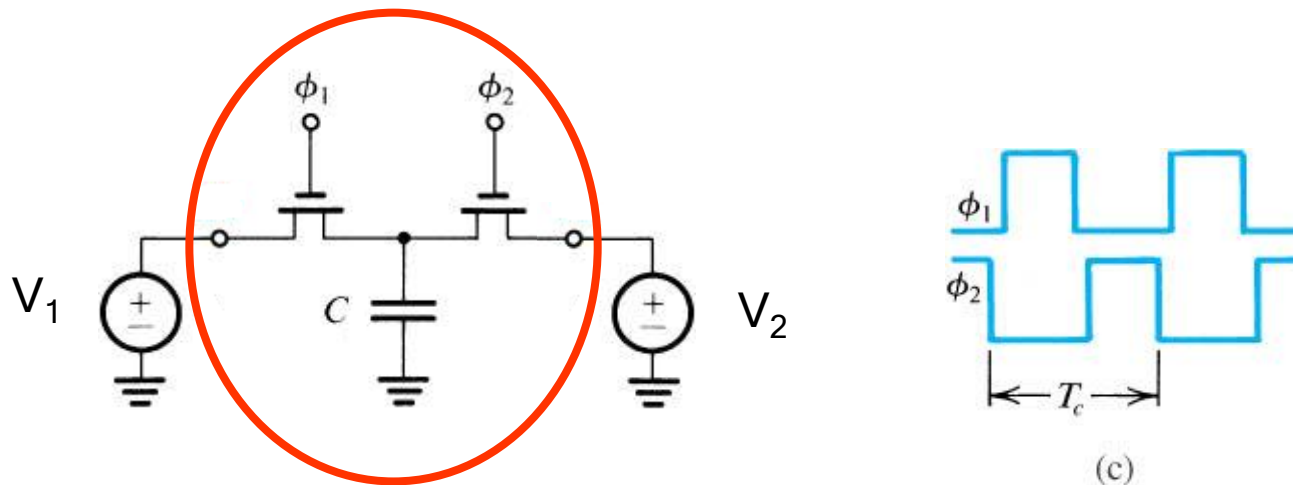

Lect. 22: Switched Capacitor Filters

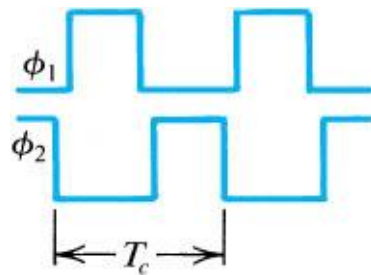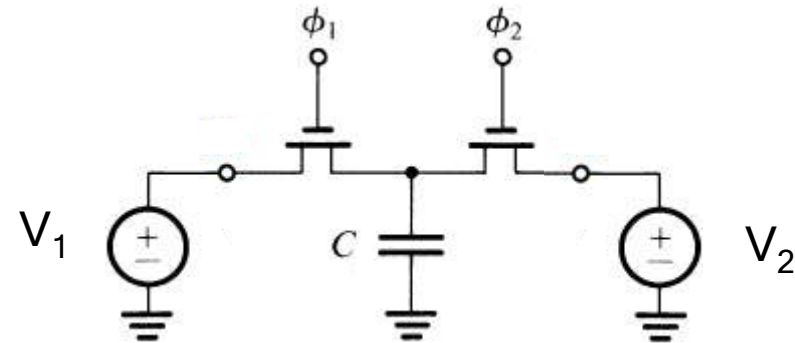

(c)

Assume initially ϕ_2 ON, ϕ_1 OFF and $V_1 > V_2$

$$Q = CV_2$$

When ϕ_2 is OFF and ϕ_1 is ON

$$Q = CV_1$$

$$\Delta Q = C(V_1 - V_2) \text{ supplied by } V_1$$

When ϕ_1 is OFF and ϕ_2 is ON

$$Q = CV_2$$

$$\Delta Q = C(V_1 - V_2) \text{ supplied to } V_2$$


➔ Switched capacitor delivers charges from V_1 to V_2

$$\Delta Q = C(V_1 - V_2) \text{ during } T_c$$

$$i_{\text{av}} = \frac{C(V_1 - V_2)}{T_c}$$

$$\frac{V_1 - V_2}{i_{\text{av}}} = \frac{T_c}{C} = R_{\text{eq}} \text{ Controlled by } C \text{ and } T_c$$

Lect. 22: Switched Capacitor Filters

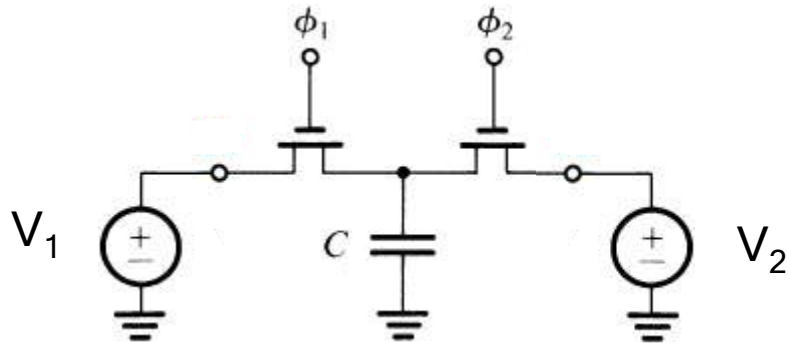


$$R_{eq} = \frac{T_c}{C}$$



Switches can be easily realized with MOS transistors

If $1/T_c \gg$ frequency of interests,
Switched capacitor is acting as a resistor.


→ Discrete time domain processing

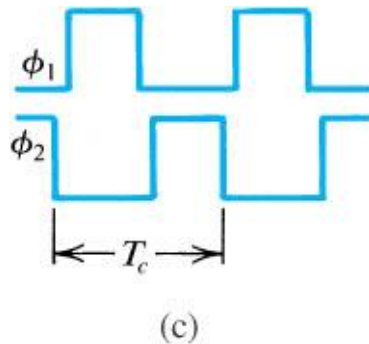

Lect. 22: Switched Capacitor Filters

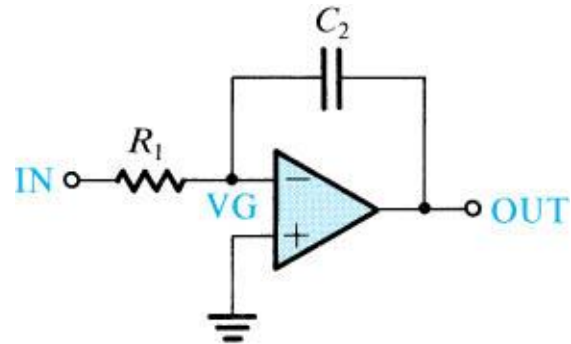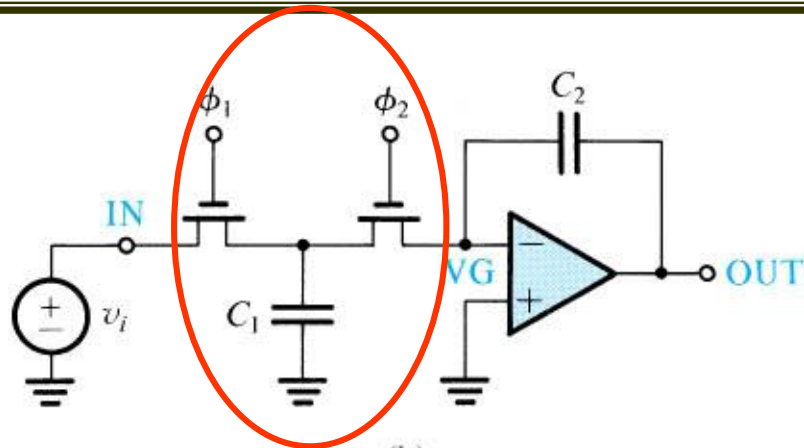

Integrator

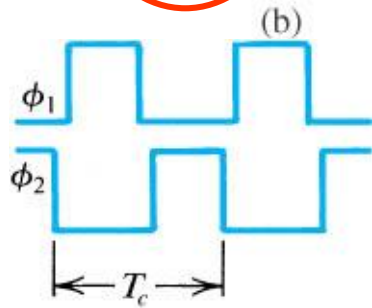




(c)

$$v_o(t) - v_o(t=0) = -\frac{1}{R_1 C_2} \int_0^t v_i(t) dt$$


With switched capacitor

$$R_1 C_2 \rightarrow \left(\frac{T_c}{C_1} \right) C_2$$

Lect. 22: Switched Capacitor Filters

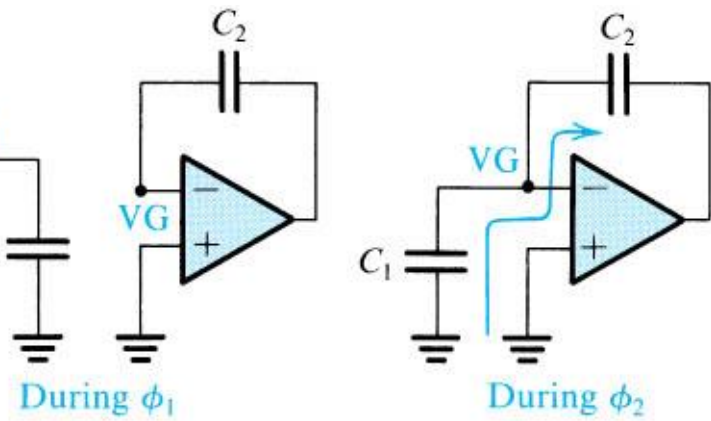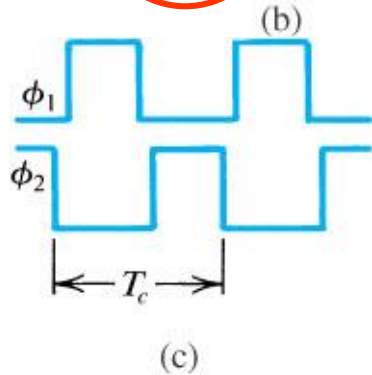
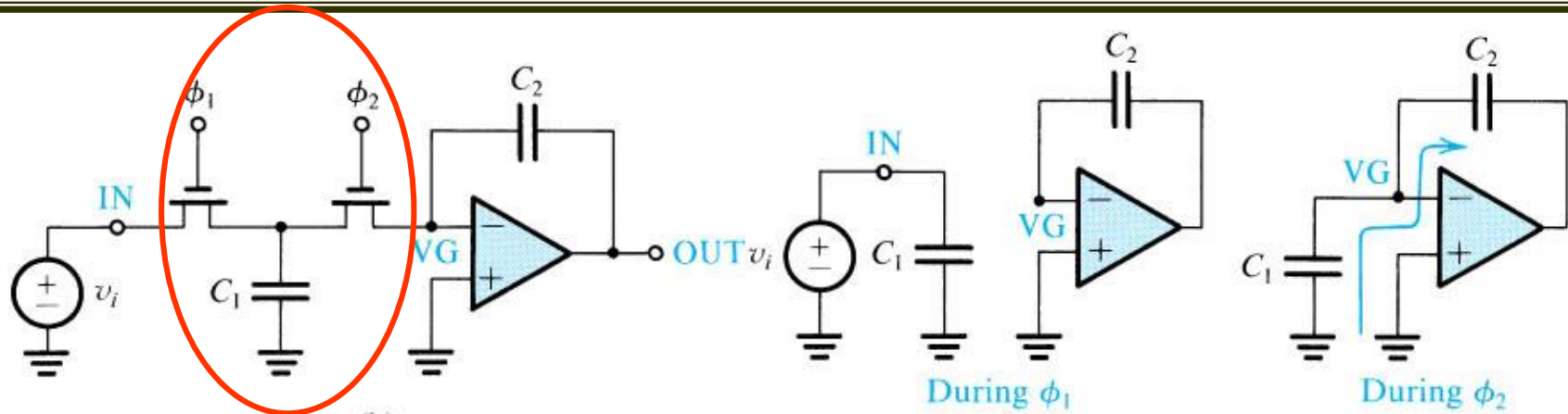


sample (d) update

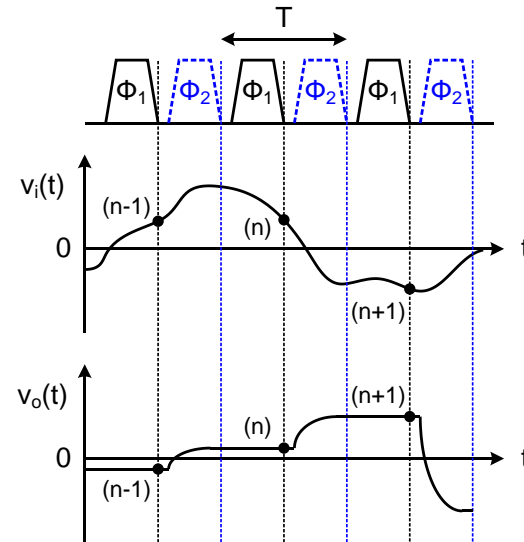


Lect. 22: Switched Capacitor Filters

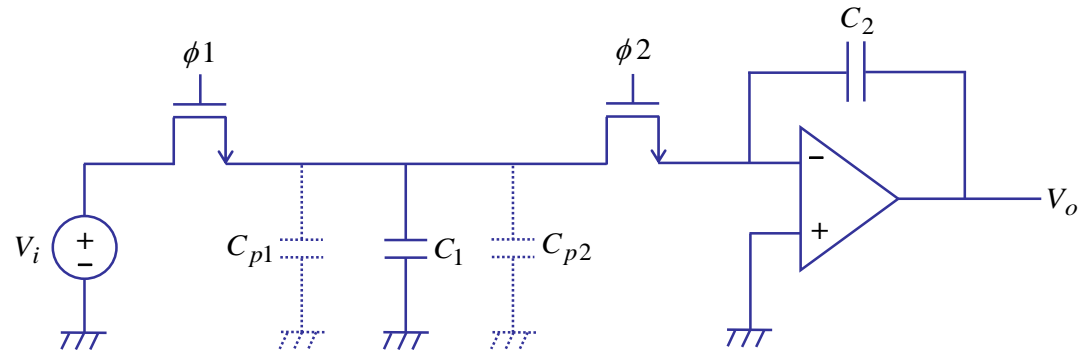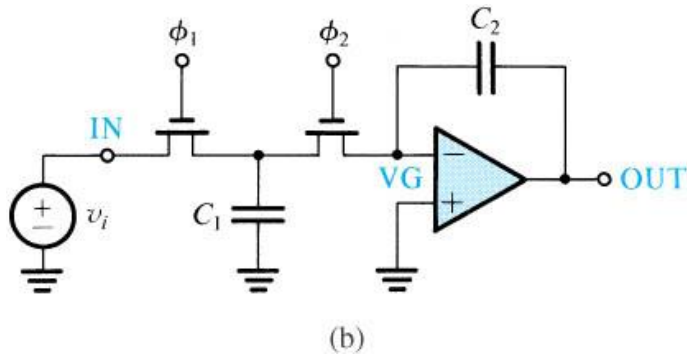Influence of parasitic capacitances due to source/drain capacitance of MOS transistors




Better Configuration

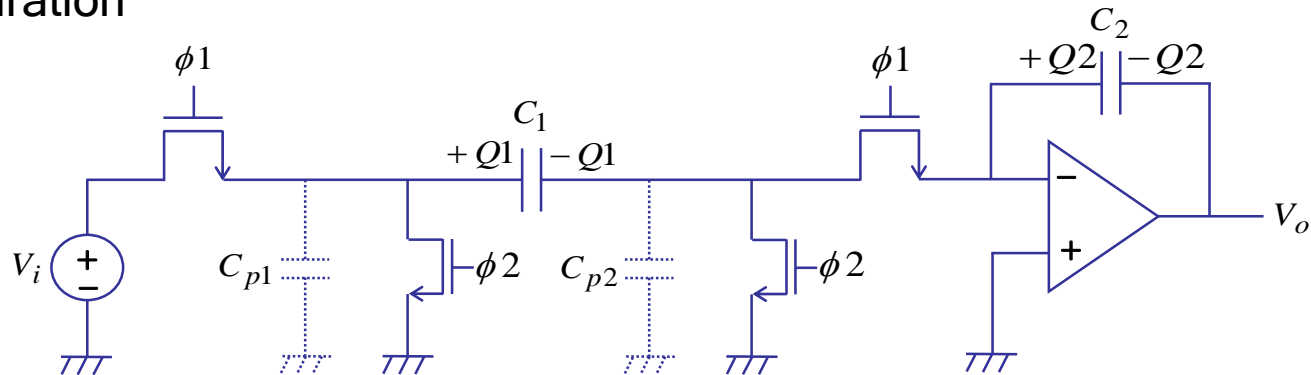

Sampling and updating during ϕ_1


Refreshing during ϕ_2

Lect. 22: Switched Capacitor Filters

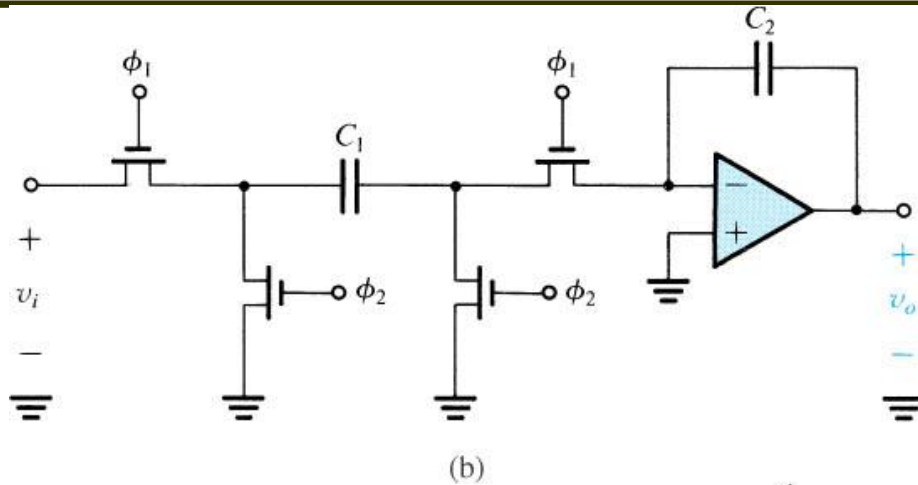

Inverting



Non-Inverting

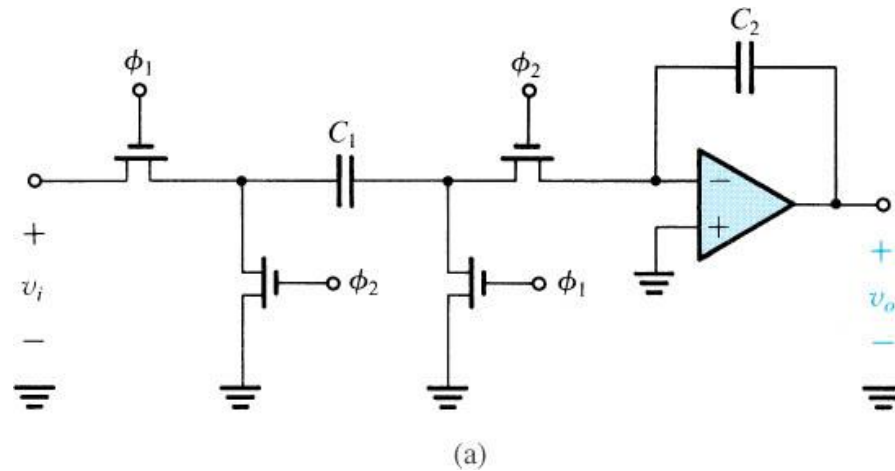

Effectively, $R_{eq} = -\frac{T_c}{C}$

Lect. 22: Switched Capacitor Filters

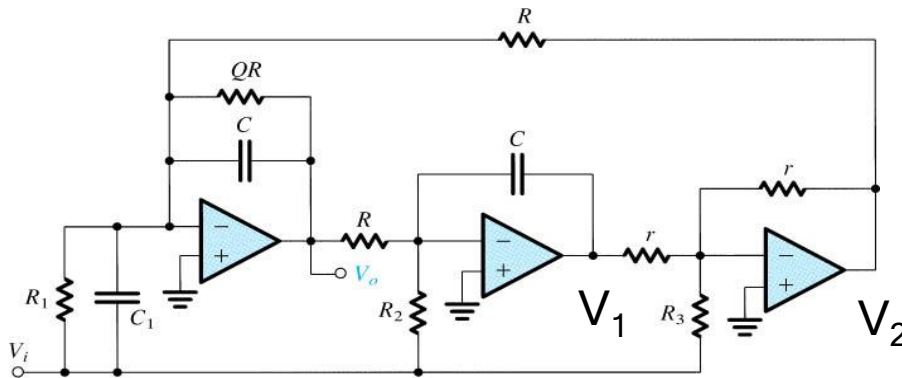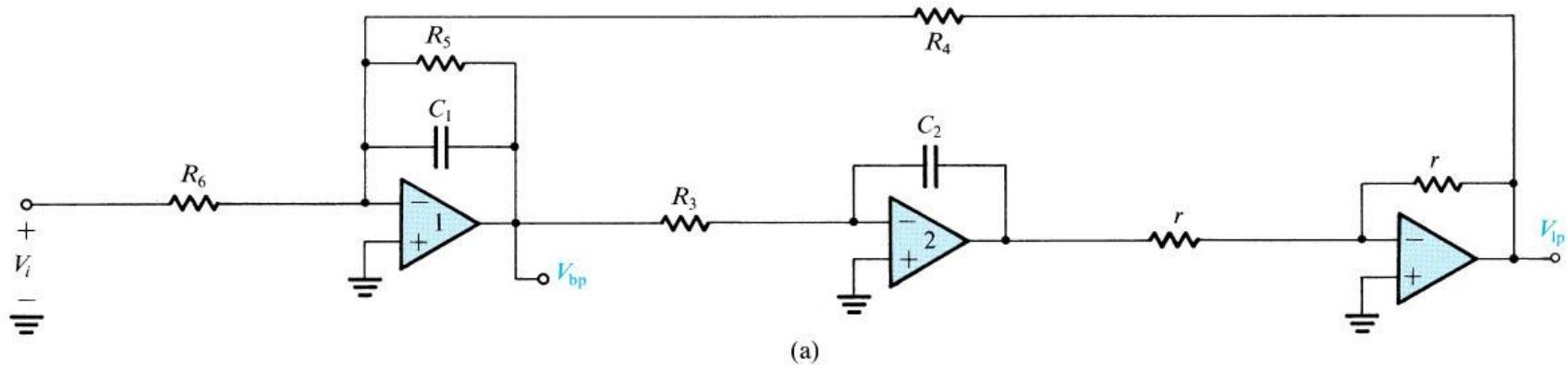
Realize following Tow-Thomas biquad by SC



$$\frac{V_o}{V_i} = - \frac{s^2 \left(\frac{C_1}{C} \right) + s \frac{1}{C} \left(\frac{1}{R_1} - \frac{r}{RR_3} \right) + \frac{1}{C^2 RR_2}}{s^2 + s \frac{1}{QCR} + \frac{1}{C^2 R^2}}$$

Lect. 22: Switched Capacitor Filters

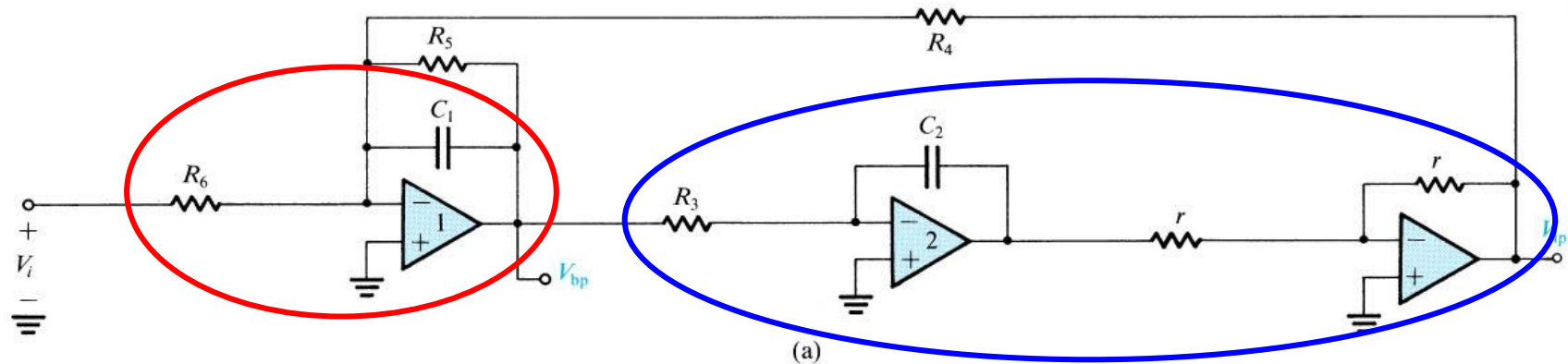Realize following Tow-Thomas biquad by SC





- Inverting Integrator

- Non-inverting Integrator

- Replace resistors with switched capacitors with proper switching time

Lect. 22: Switched Capacitor Filters

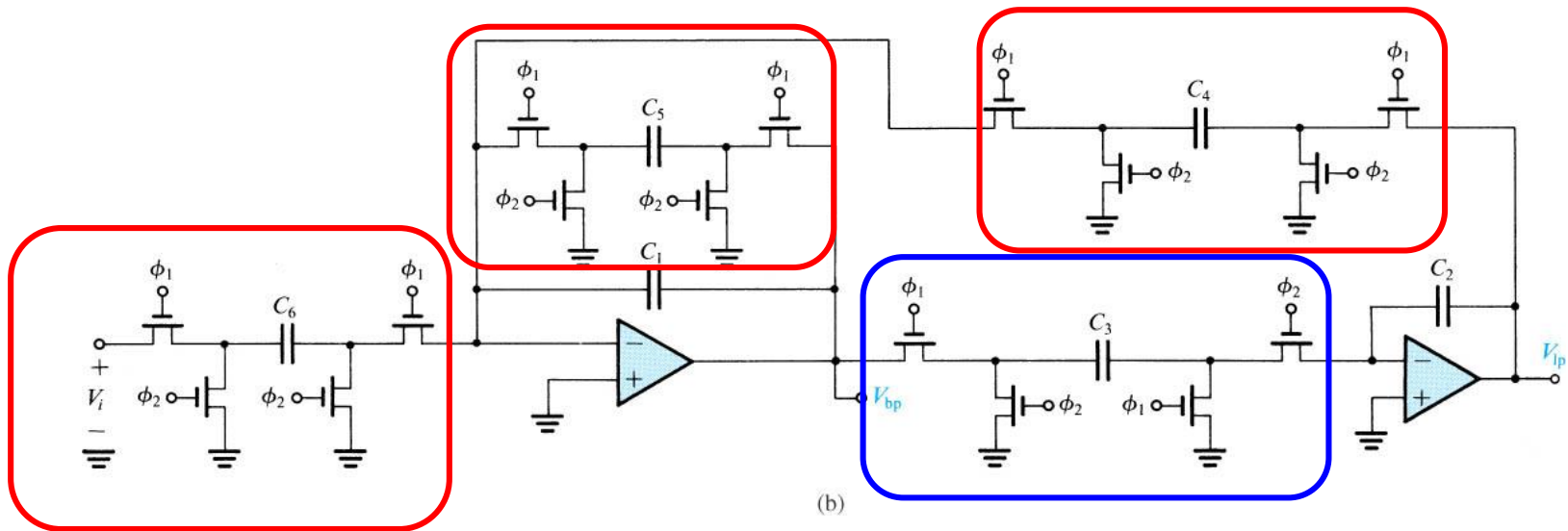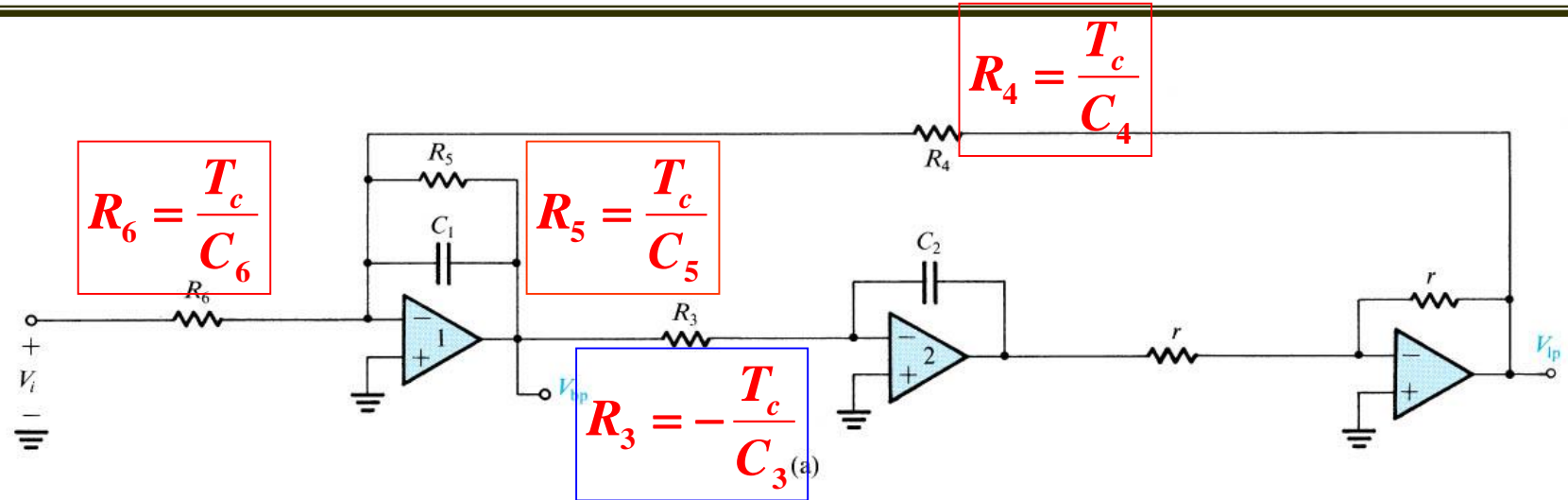

Lect. 22: Switched Capacitor Filters

Any active RC filter (such as biquad) can be replaced with equivalent SC filter → Project #2

SC filters perform discrete time domain signal processing

s-domain analysis for continuous time signal processing

→ z-domain analysis for discrete time signal processing

SC circuits are widely used for filters and data converters but has speed limitations