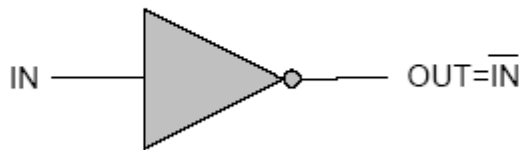


Lect. 23: Inverters (Razavi 15.1, 2, 3)

Digital Electronics


How to implement logic circuits?

→ Inverters are the basic building block!






IN	OUT
0	1
1	0

Ideally,

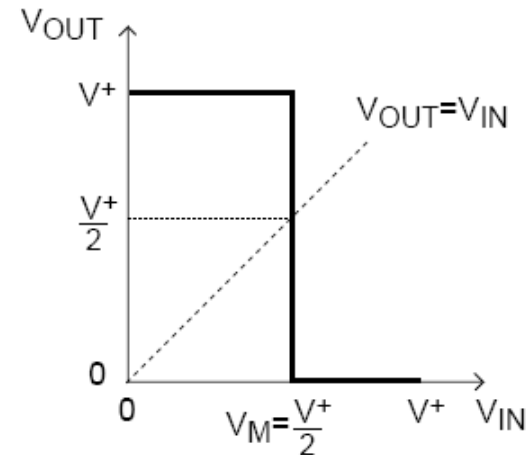

Lect. 23: Inverters

Real inverters

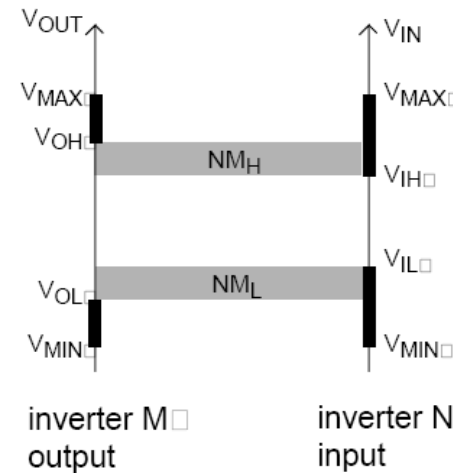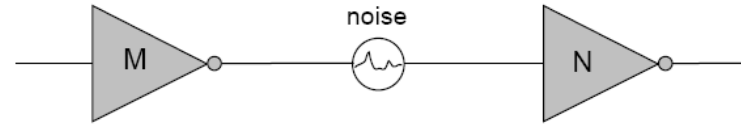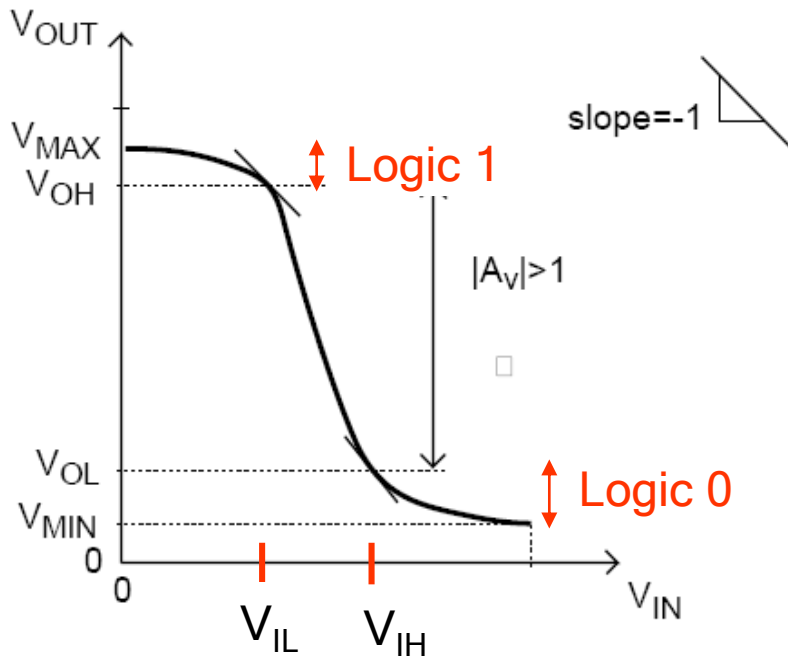


$$NM_H = V_{OH} - V_{IH}$$

$$NM_L = V_{IL} - V_{OL}$$

Larger noise margin \rightarrow smaller V_{IH} , larger V_{IL} \rightarrow Larger $|A_v|$





Lect. 23: Inverters

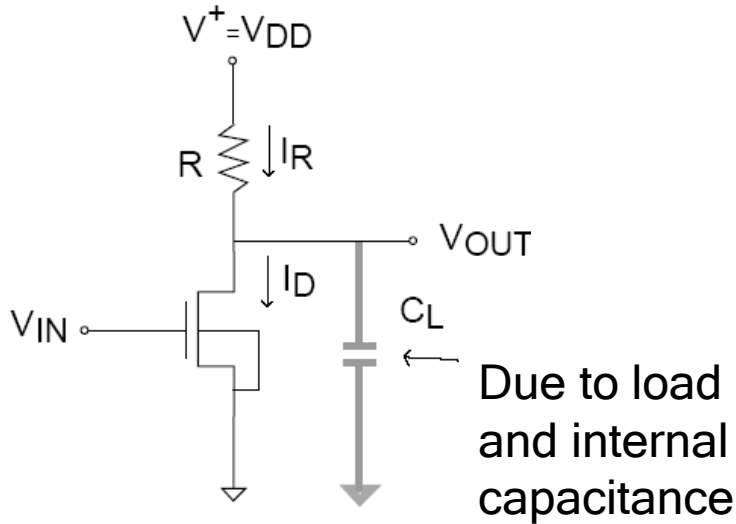How to implement an inverter? CS amplifier configuration




V_{OUT} vs V_{IN} ?

Load line analysis

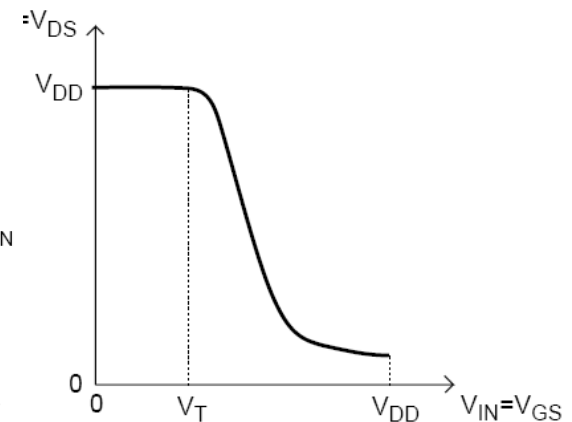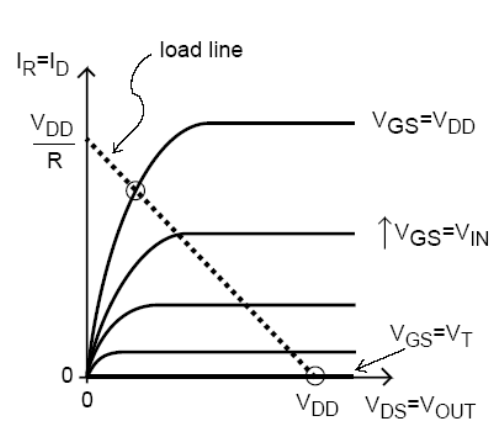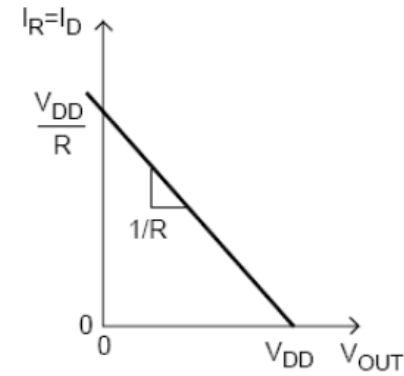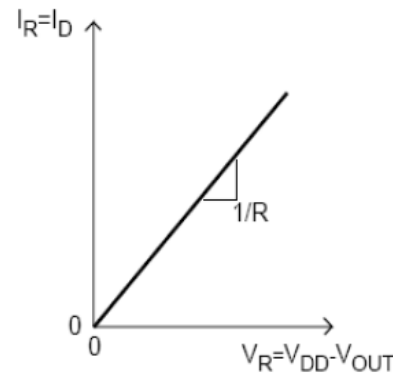

Lect. 23: Inverters

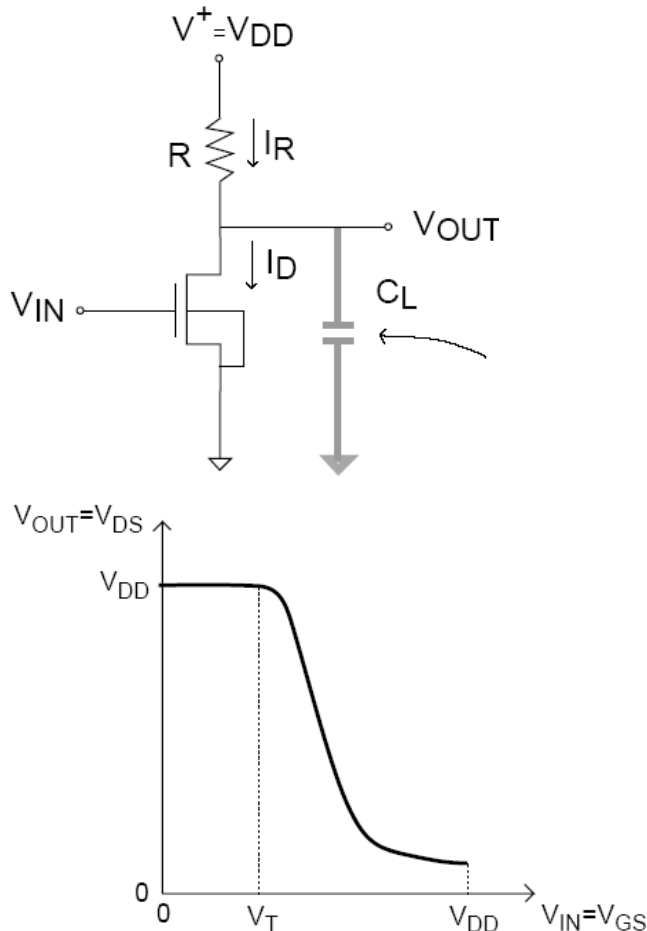

For V_{MIN} , MOSFET in triode

$$I_D = \frac{W}{L} \mu_n C_{ox} \left(V_{GS} - \frac{1}{2} V_{DS} - V_T \right) V_{DS}$$

$$I_D = \frac{W}{L} \mu_n C_{ox} \left(V_{DD} - \frac{V_{MIN}}{2} - V_T \right) V_{MIN}$$

$$= I_R = \frac{V_{DD} - V_{MIN}}{R}$$



$$V_{MIN} \approx - \frac{V_{DD}}{1 + \mu_n C_{ox} \frac{W}{L} R (V_{DD} - V_T)}$$

$A_V = ?$

Large R preferred

Lect. 23: Inverters

Dynamics

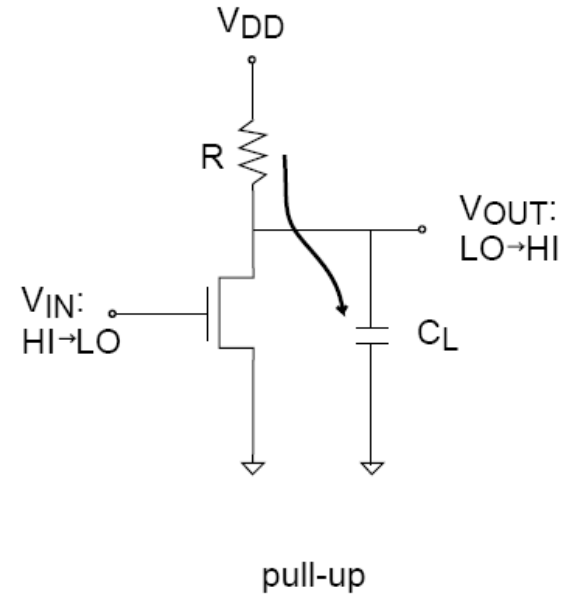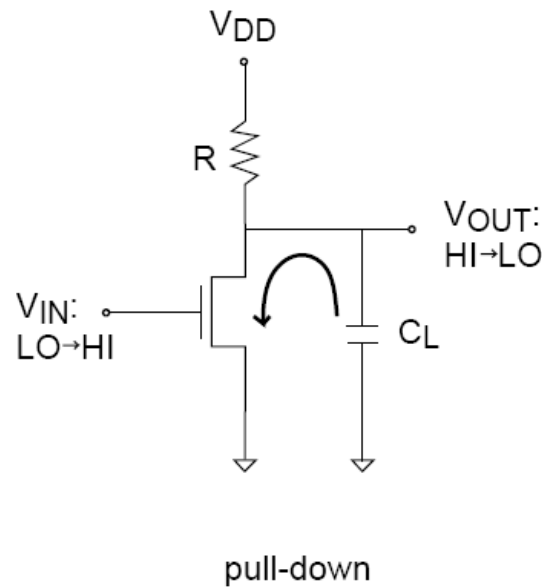


RC time constant for pull-down and pull-up operation

Small R preferred for fast operation





→ Better way of implementing inverters?

Lect. 23: Inverters


Replace R with PMOS current source

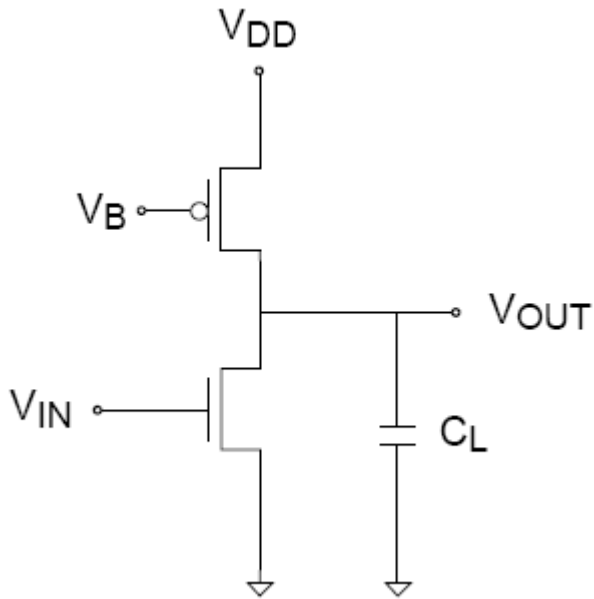

$A_v = ?$

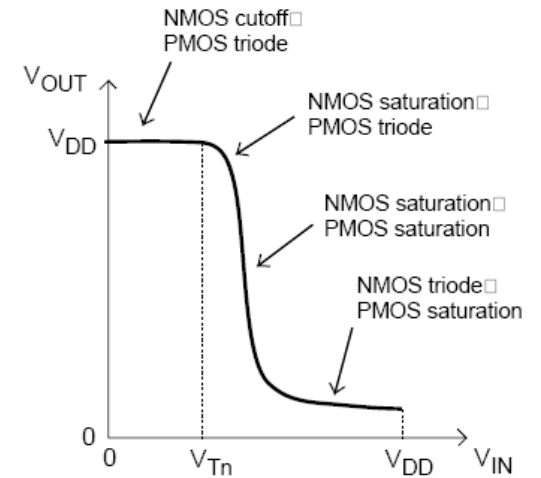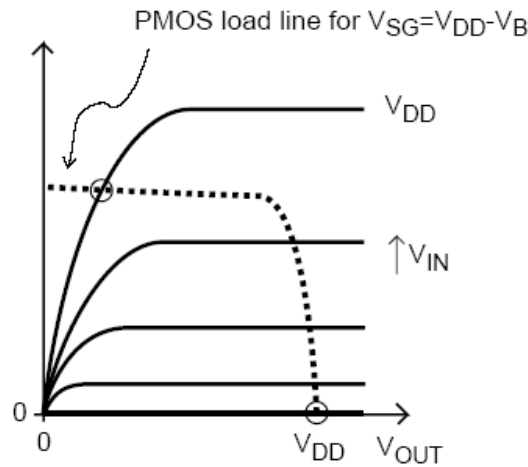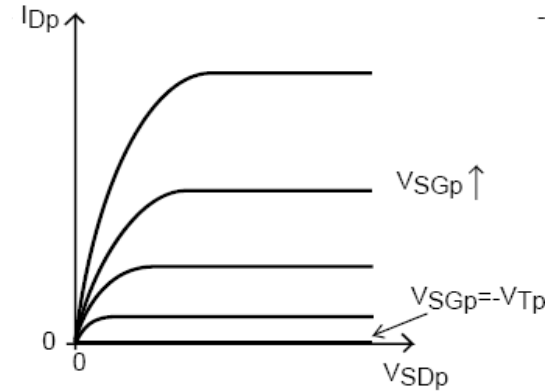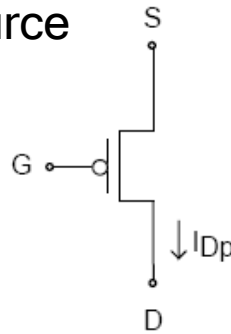

Lect. 23: Inverters

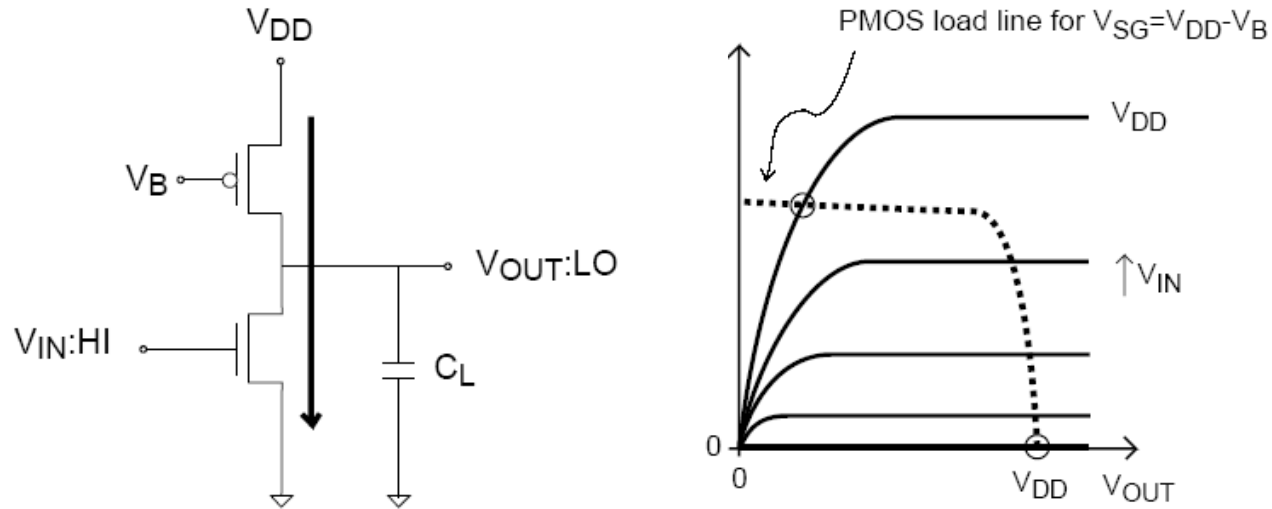


Direct current path when V_{IN} is high

Static power consumption!

→ How can we shut it off when input is high?

Lect. 23: Inverters

Complementary MOS (CMOS) Inverter

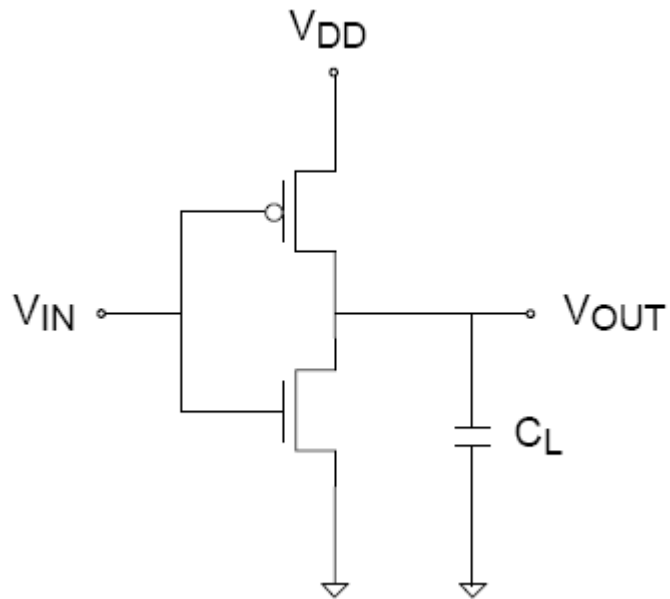

$$V_{IN} = V_{DD}$$

NMOS ON, PMOS OFF

$$\rightarrow V_{OUT} = 0$$




$$V_{IN} = 0$$

NMOS OFF, PMOS ON

$$\rightarrow V_{OUT} = V_{DD}$$

→ The most popular building block for today's digital electronics!


Lect. 23: Inverters

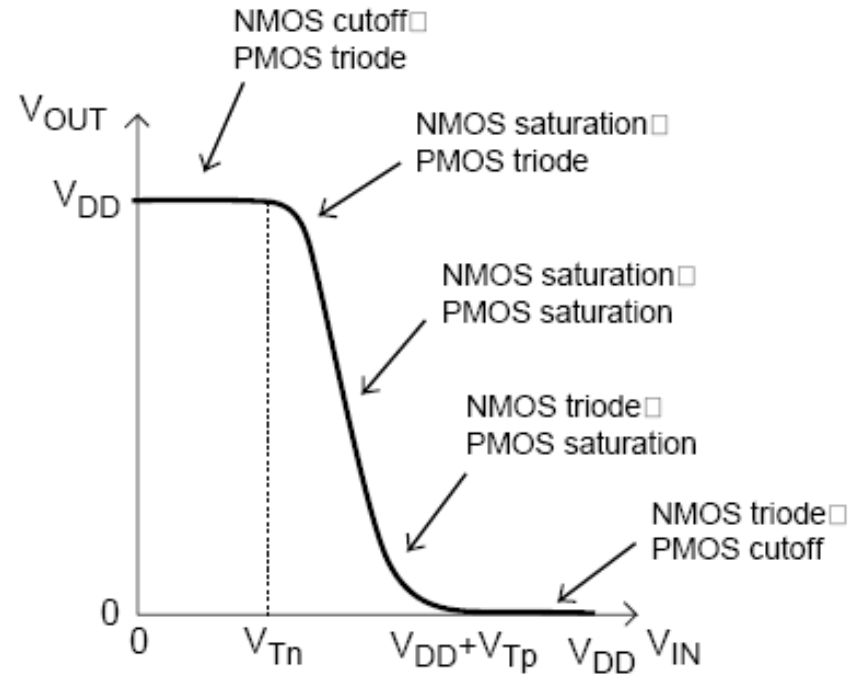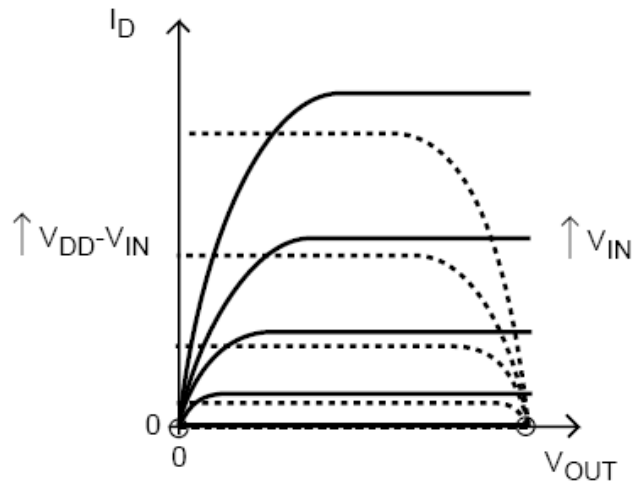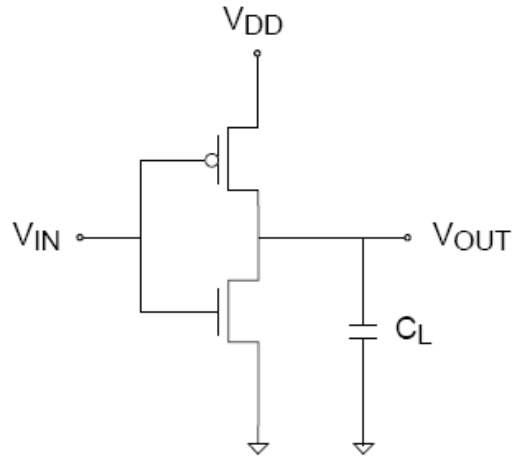

Rail-to-Rail logic

Lect. 23: Inverters

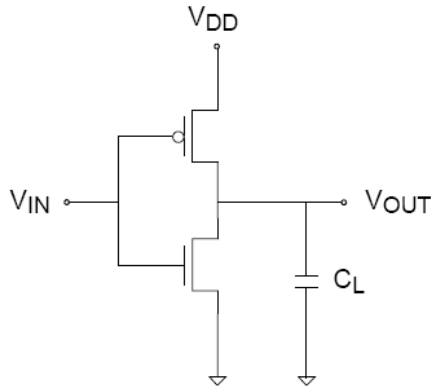Estimation of important parameters for CMOS inverter: V_M , $A_V(V_M)$, NM_L , NM_H



For V_M ($V_{IN} = V_{OUT} = V_M$)

$$\frac{1}{2} \frac{W_n}{L_n} \mu_n C_{ox} (V_M - V_{Tn})^2 = \frac{1}{2} \frac{W_p}{L_p} \mu_p C_{ox} (V_{DD} - V_M + V_{Tp})^2$$


Using $k_n = \frac{W_n}{L_n} \mu_n C_{ox}$, $k_p = \frac{W_p}{L_p} \mu_p C_{ox}$

$$V_M = \frac{V_{Tn} + \sqrt{\frac{k_p}{k_n}} (V_{DD} + V_{Tp})}{1 + \sqrt{\frac{k_p}{k_n}}}$$

V_M can be engineered with controlling k_p/k_n


If $V_{Tn} = -V_{Tp}$ and $k_p = k_n$, $V_M = V_{DD}/2$

$$(W_p \sim 3W_n)$$



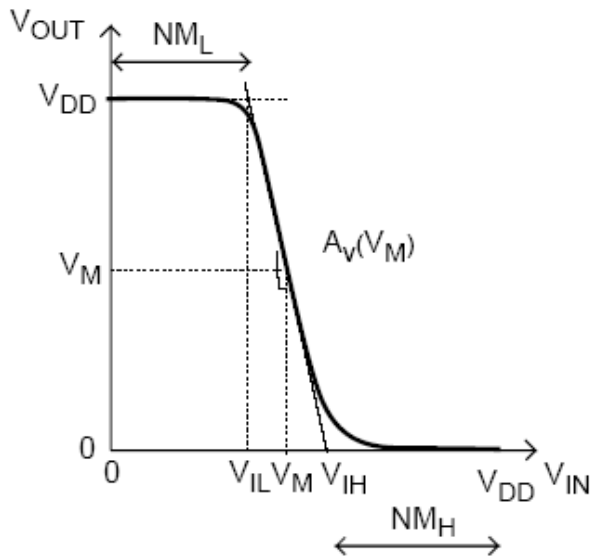


Lect. 23: Inverters

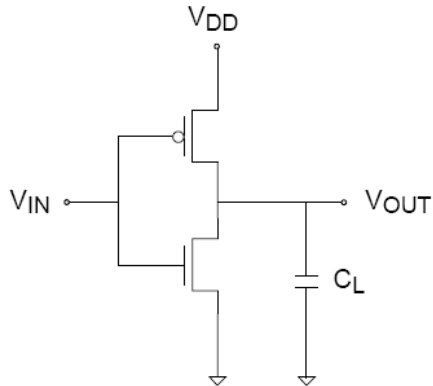Estimation of important parameters for CMOS inverter: V_M , $A_v(V_M)$, NM_L , NM_H




$A_v(V_M)$

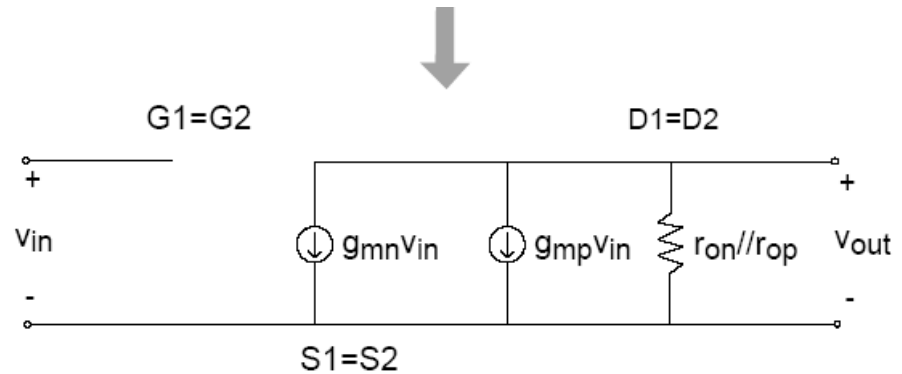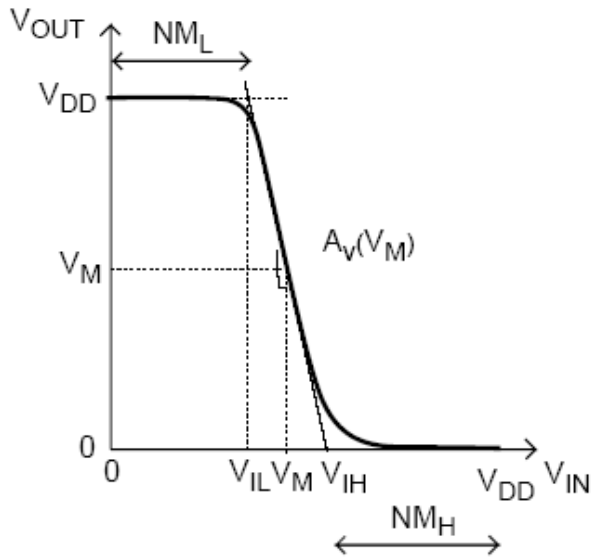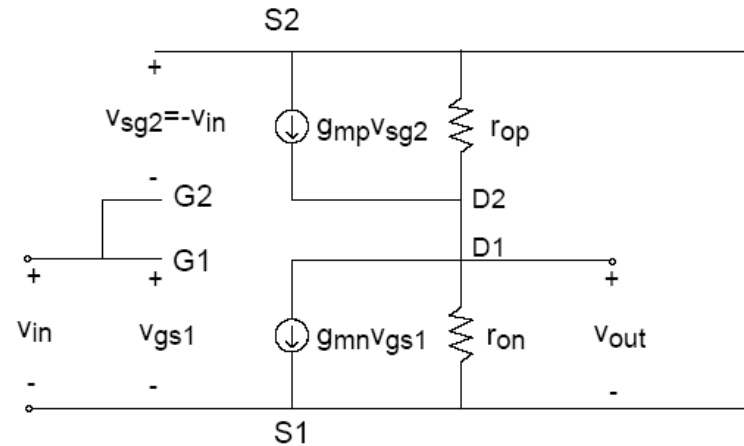

$$A_v = -(g_{mn} + g_{mp})(r_{on} // r_{op})$$

Lect. 23: Inverters

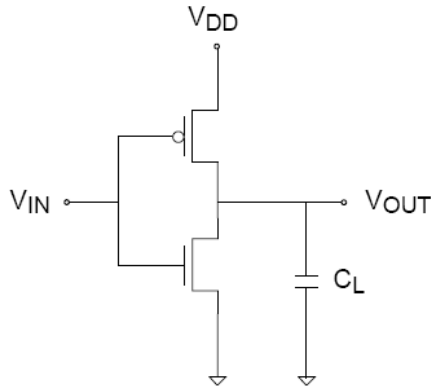
Estimation of important parameters for CMOS inverter: V_M , $A_v(V_M)$, NM_L , NM_H



Noise Margin Estimation:

$$NM_H = V_{OH} - V_{IH}$$

$$NM_L = V_{IL} - V_{OL}$$

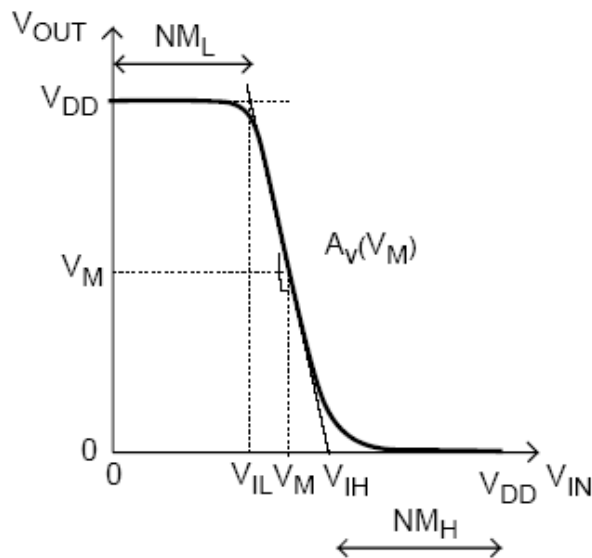


$$NM_H = V_{DD} - V_{IH} = V_{DD} - V_M \left(1 + \frac{1}{|A_v|}\right)$$

$$NM_L = V_{IL} - 0 = V_M - \frac{V_{DD} - V_M}{|A_v|}$$

$$\text{When } V_M = V_{DD}/2, \quad NM_H = NM_L$$

Lect. 23: Inverters

Estimation of propagation delay,

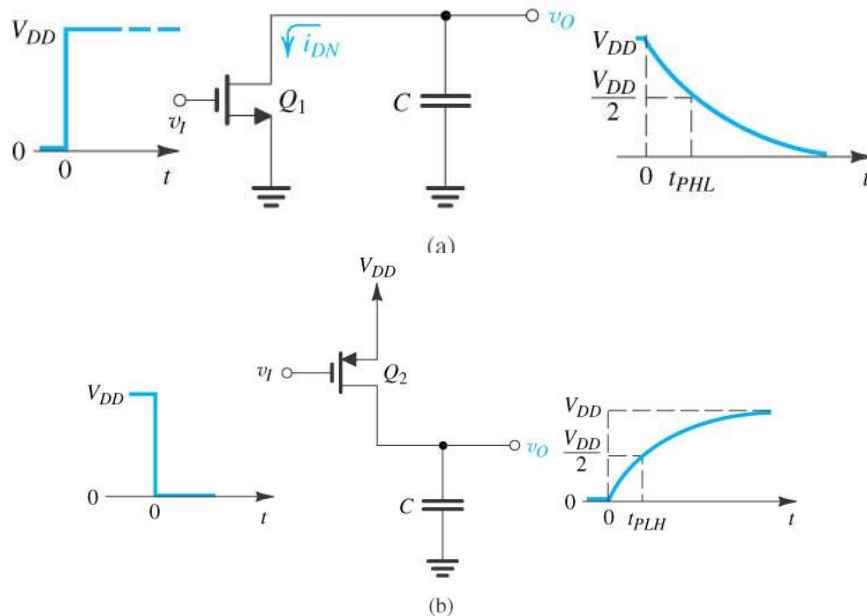

$$t_{P,HL} \sim \frac{1.7C}{k_n V_{DD}}$$

$$t_{P,LH} \sim \frac{1.7C}{k_p V_{DD}}$$

$$t_P = \frac{1}{2} (t_{PHL} + t_{PLH})$$

In each cycle, $Q = CV_{DD}$ is charged and discharged over V_{DD}

In each cycle, energy of CV_{DD}^2 is consumed

Power consumption: fCV_{DD}^2

➔ Make them smaller, smaller, smaller, smaller, smaller, smaller ...