


Lect. 24: CMOS Logic Gates

(Razavi 15.3)



CMOS inverter

Different transistor acting for pull-down and pull-up operation

- Pull-down: NMOS

 


- Pull-up: PMOS

 
 


Lect. 24: CMOS Logic Gates

CMOS Logic Gates

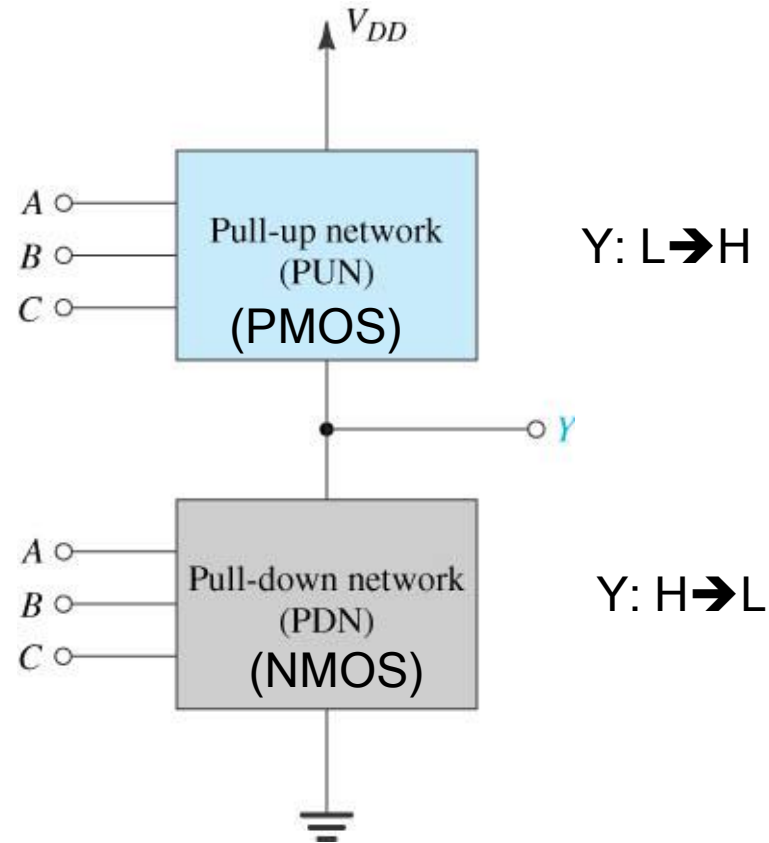

Lect. 24: CMOS Logic Gates

  

Y Pull-down,

Initially, Q_A OFF and Q_B OFF
(A LOW and B LOW)

Q_A ON or Q_B ON
(A HIGH or B HIGH)

$$\bar{Y} = A + B$$

NOR Gate

Y Pull-up,


Initially, Q_A OFF or Q_B OFF
(A HIGH or B HIGH)

Q_A ON and Q_B ON
(A LOW and B LOW)

$$Y = \bar{A}\bar{B}$$

Lect. 24: CMOS Logic Gates



CMOS NOR Gate

 

Structures of PUN and PDN have the duality property

Three input CMOS NOR Gate?

Lect. 24: CMOS Logic Gates

  

Y Pull-down,

Initially, Q_A OFF or Q_B OFF
(A LOW or B LOW)

Q_A ON and Q_B ON
(A HIGH and B HIGH)

$\bar{Y} = AB \rightarrow$ NAND Gate

Y Pull-up,


Initially, Q_A OFF and Q_B OFF
(A HIGH and B HIGH)

Q_A ON or Q_B ON
(A LOW or B LOW)

$Y = \bar{A} + \bar{B}$

Lect. 24: CMOS Logic Gates


CMOS NAND Gate

 



Three input CMOS NAND Gate?

Lect. 24: CMOS Logic Gates

Corresponding PUN?

 

Logic function?

  

Lect. 24: CMOS Logic Gates

CMOS XOR (Exclusive OR)




A: 0 1 0 1

B: 0 0 1 1

XOR: 0 1 1 0

PDN: $\bar{Y} = AB + \bar{A}\bar{B}$

PUN: $Y = A\bar{B} + \bar{A}B$

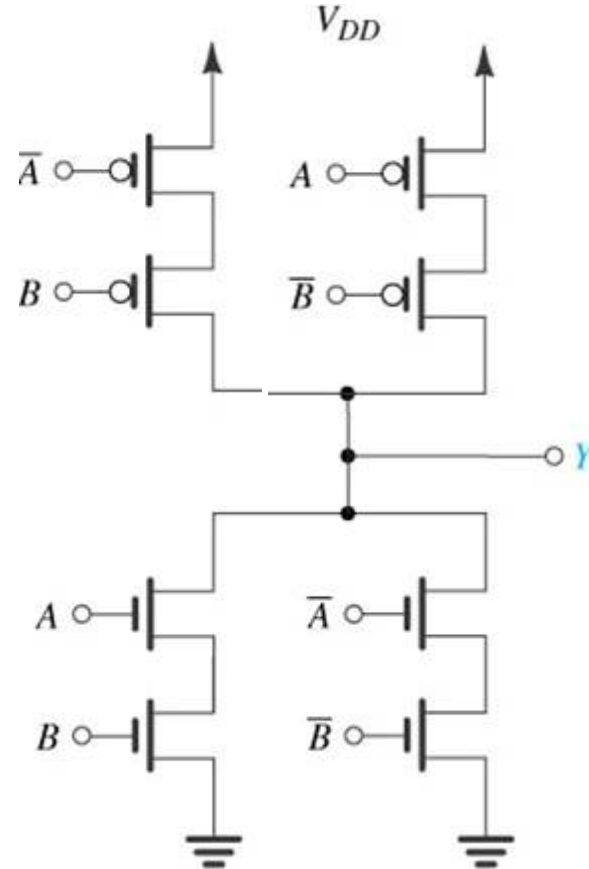

Complicated digital logic gates can be realized by CMOS logic gates!