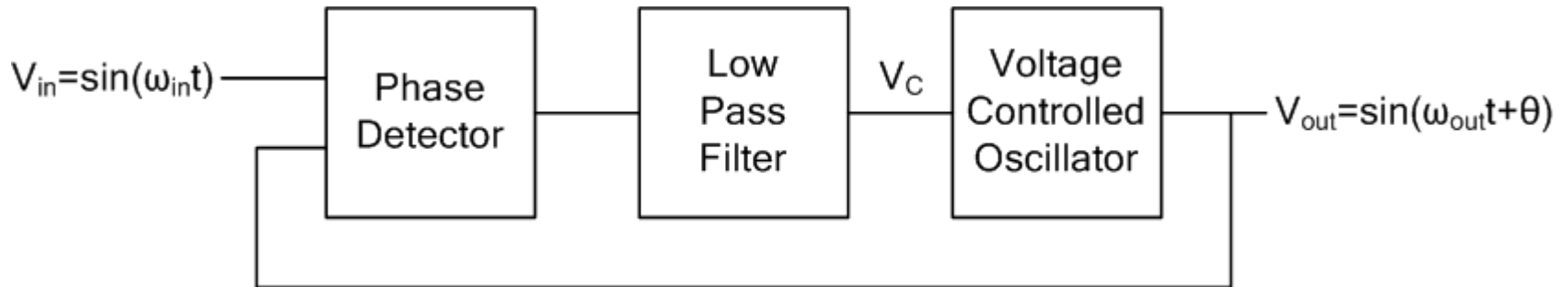



# Lect. 25: PLL

PLL (Phase-Locked Loop): A closed-loop feedback system that synchronizes output signal with input signal in frequency and phase




→ Frequency locking of input and output ( $\omega_{in} = \omega_{out}$ )  
with constant phase difference ( $\theta$ )

# Lect. 25: PLL

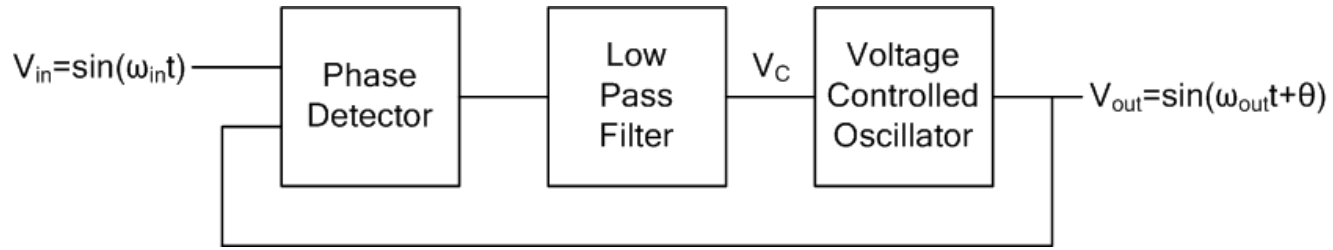

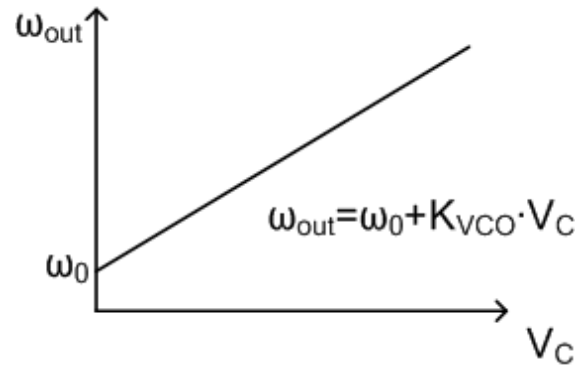VCO (Voltage Controlled Oscillator): Frequency-tunable oscillator  
→ Output frequency is a function of control voltage ( $V_C$ )



# Lect. 25: PLL

Electronic Oscillators (Chap. 13 in Razavi 2nd Edition)


- Crystal oscillator (Razavi 13.6): Piezoelectricity

Very accurate and stable oscillation frequency

But limited frequency range (typical up to tens of MHz)

Used as a master clock in many electronic systems




- LC oscillators (Razavi 13.3)

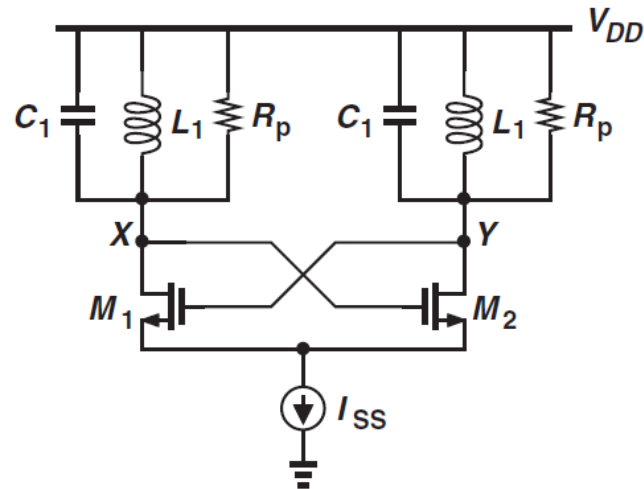


# Lect. 25: PLL

- Ring-oscillator: Odd-stage chain of inverters


Voltage control of oscillation frequency

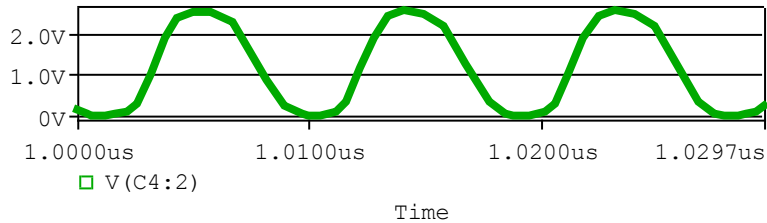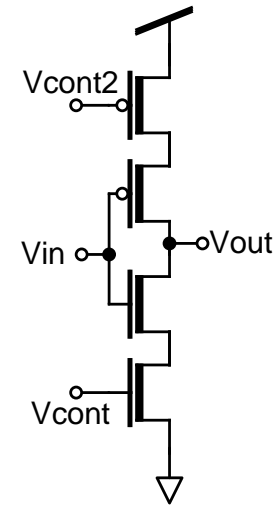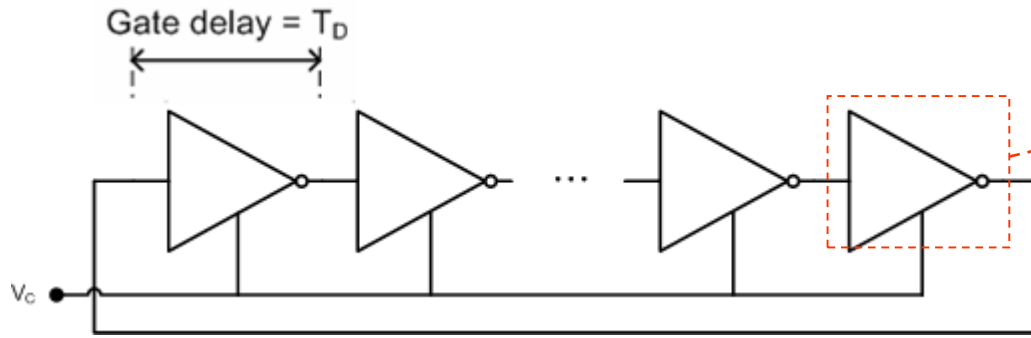
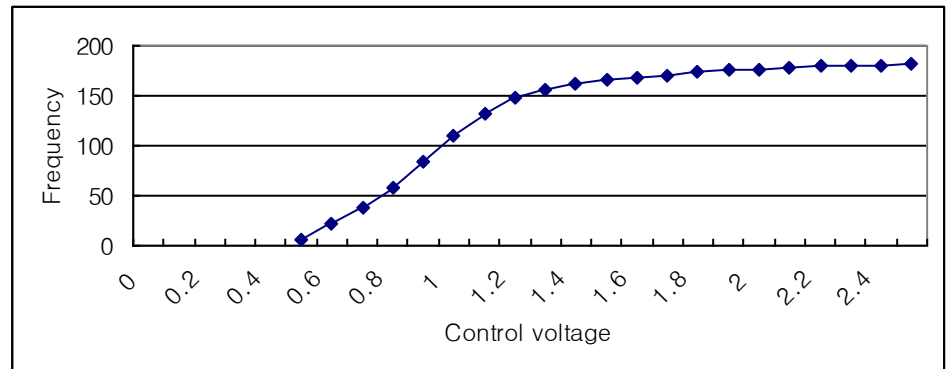
$$T = 2nT_D \quad f = \frac{1}{T} = \frac{1}{2nT_D}$$



# Lect. 25: PLL

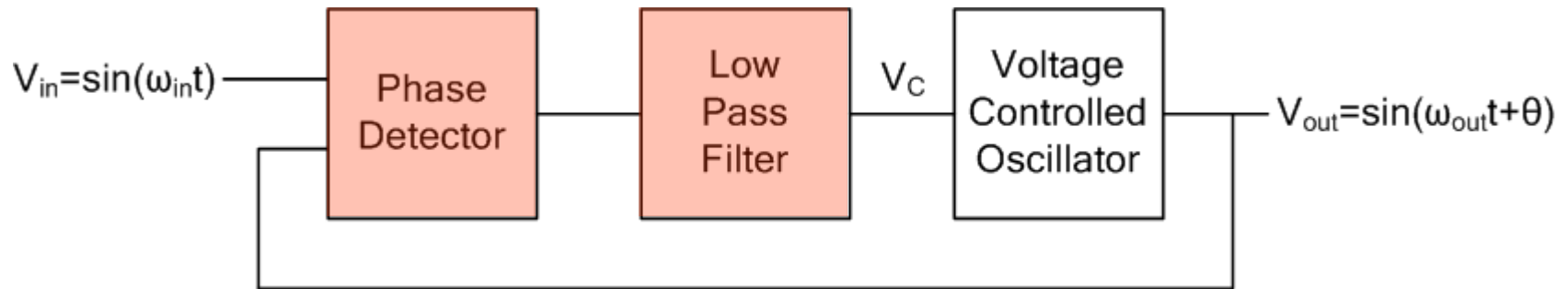


PD (Phase Detector): Compares phases of input and output signal and converts the phase difference to voltage signal

LPF (Low Pass Filter): Takes an average level of PD's output voltage signal

PD can be realized with a multiplier

$$\sin(\omega_{in} t) \sin(\omega_{out} t + \theta) = \frac{1}{2} \left\{ \cos[(\omega_{in} - \omega_{out})t - \theta] - \cos[(\omega_{in} + \omega_{out})t + \theta] \right\}$$

# Lect. 25: PLL


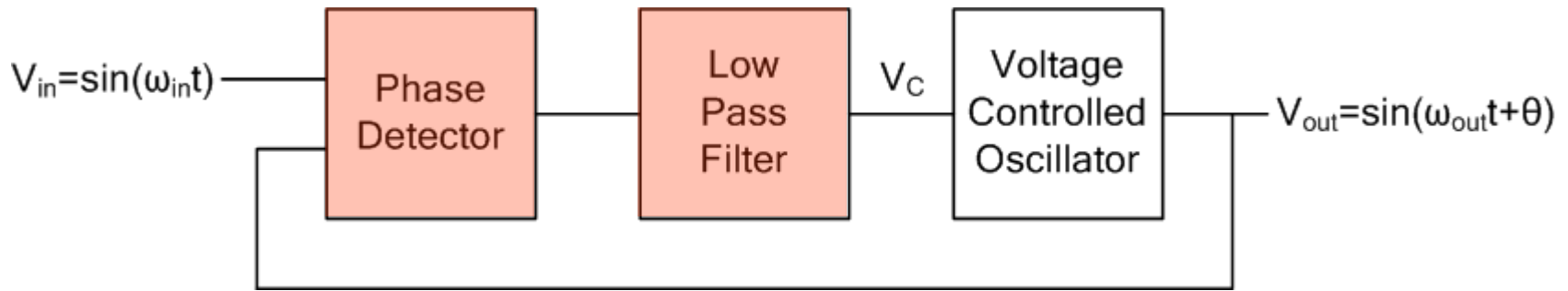


$$\sin(\omega_{in} t) \sin(\omega_{out} t + \theta) = \frac{1}{2} \left\{ \cos[(\omega_{in} - \omega_{out})t - \theta] - \cos[(\omega_{in} + \omega_{out})t + \theta] \right\}$$

Filtered out by LPF

Assuming  $\omega_{in} = \omega_{out}$

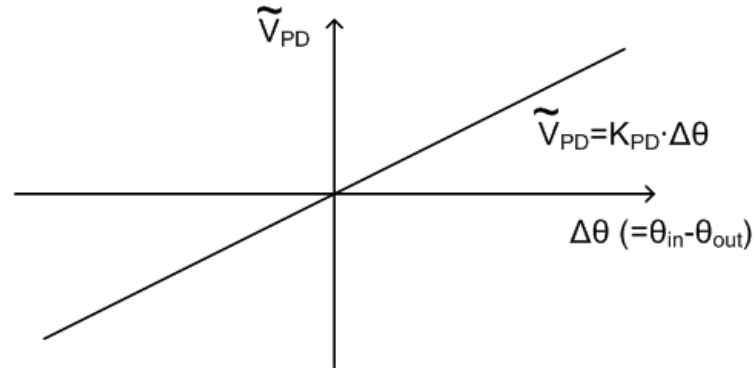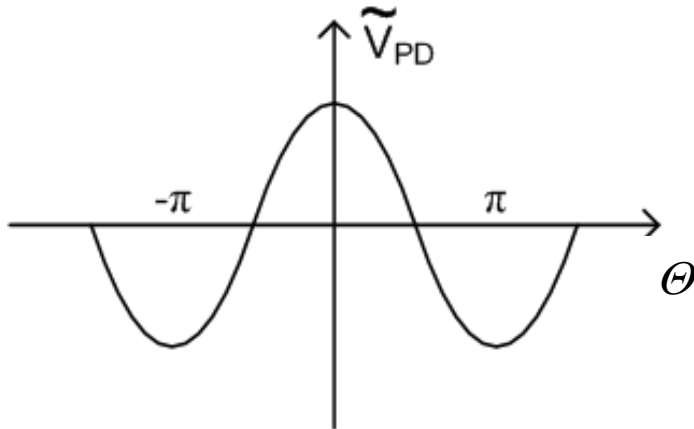
Approximately linear for  $\theta = -\pi/2$



# Lect. 25: PLL



## Phase tracking of PLL

$$\omega_{in} = \omega_{out}$$

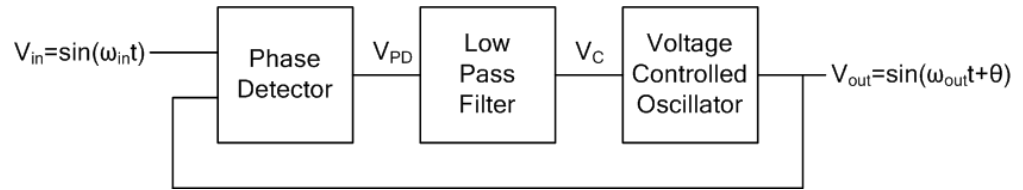

Initially,  $V_{out}$  is locked to  $V_{in}$   
With  $\theta = -\pi/2$


Phase jump in  $V_{in}$  here

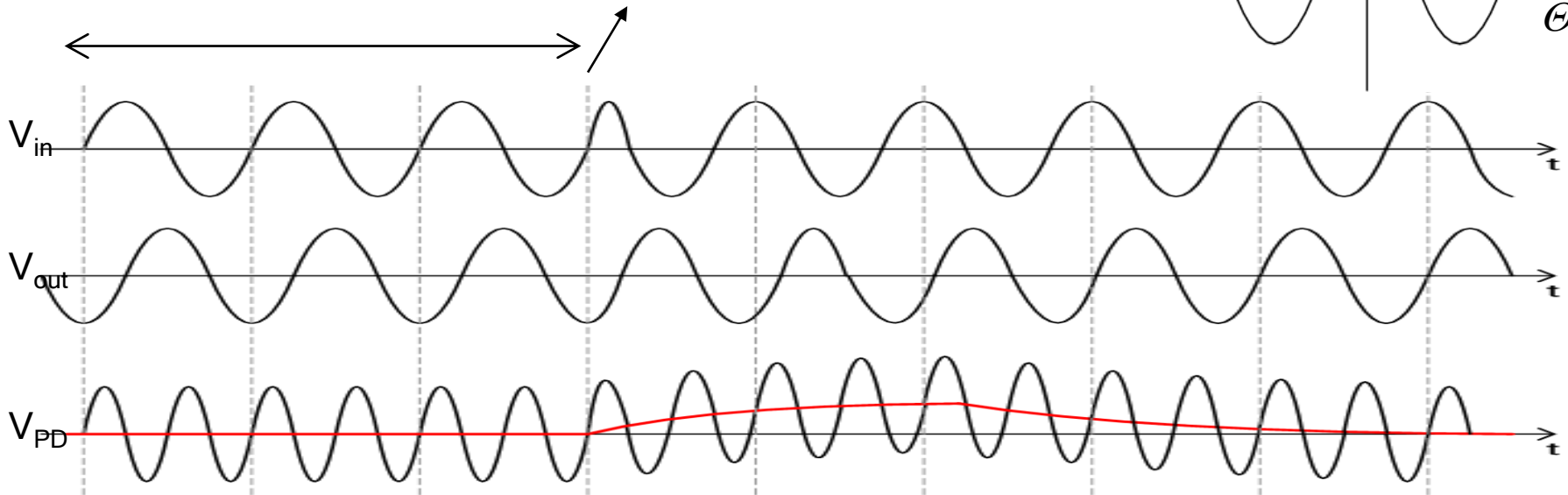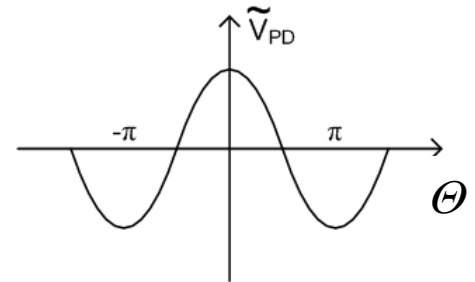

# Lect. 25: PLL



## Frequency tracking of PLL

$$\omega_{in} \neq \omega_{out}$$

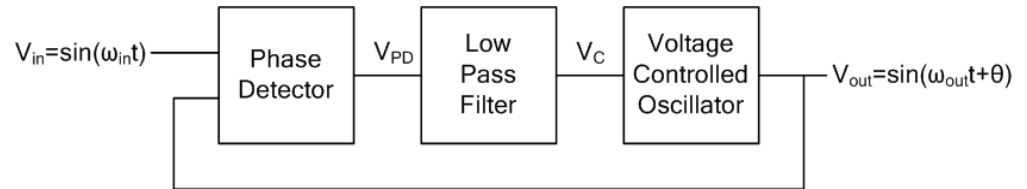

$V_{out}$  is locked to  $V_{in}$   
With  $\theta = -\pi/2$

Frequency jump in  $V_{in}$  here

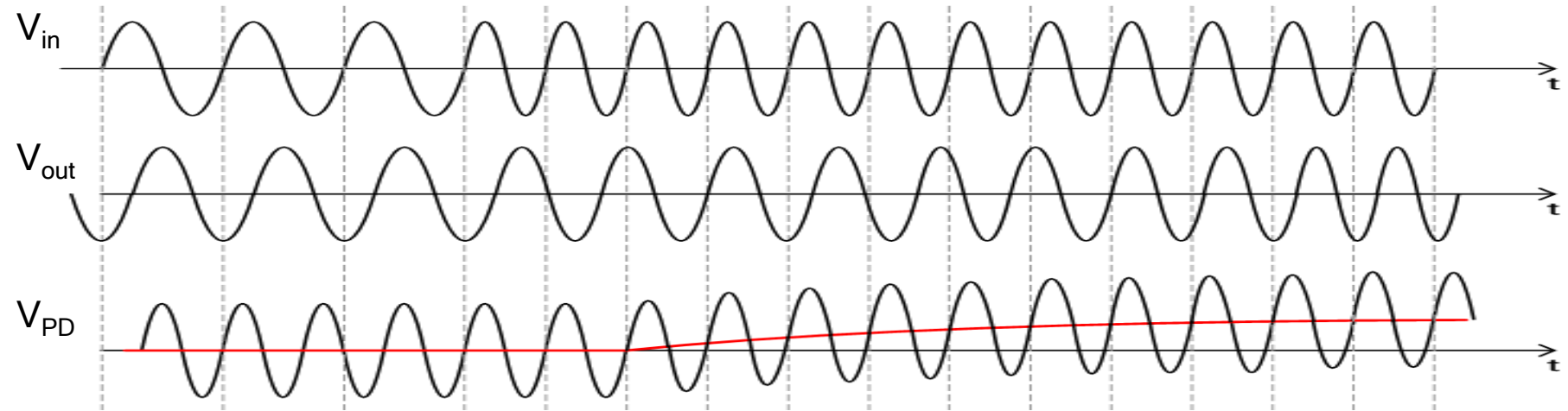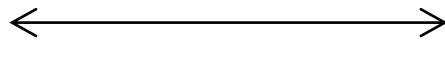




# Lect. 25: PLL


XOR gate can be used as PD for digital signals




A	B	V <sub>PD</sub>
0	0	0
0	1	1
1	0	1
1	1	0

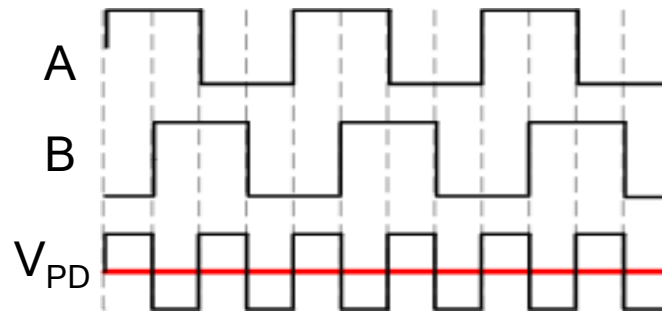

Locked  
( $\pi/2$  phase offset)

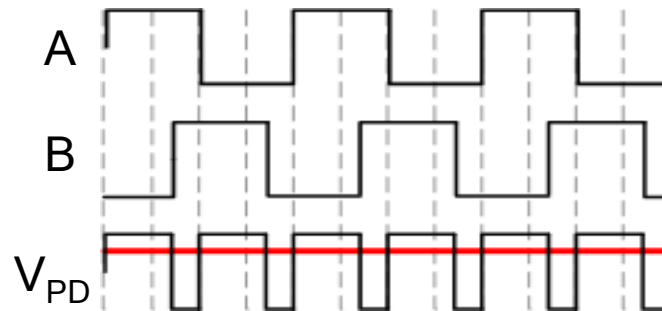

B later than A


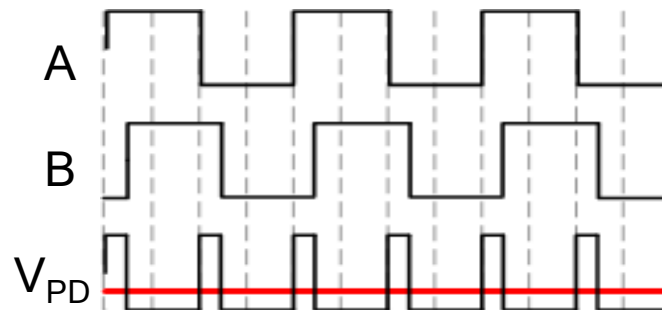


B earlier than A

# Lect. 25: PLL

## Phase tracking of PLL



$$\omega_{in} = \omega_{out}$$

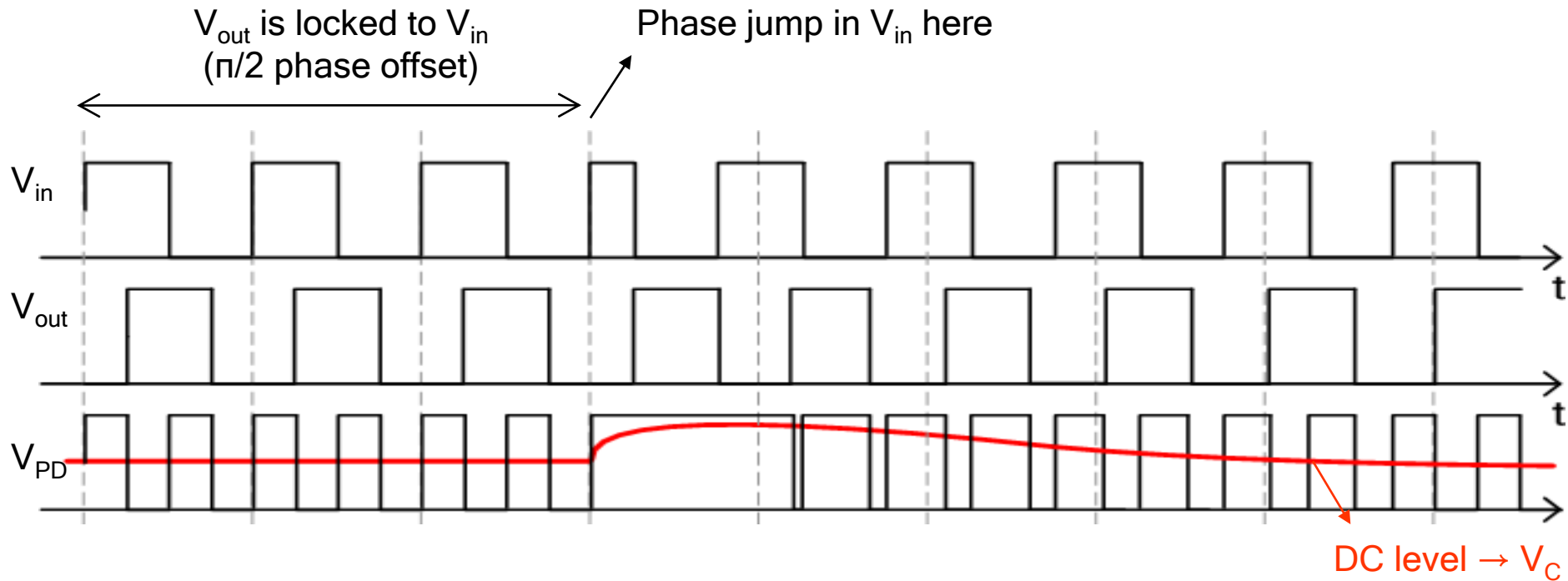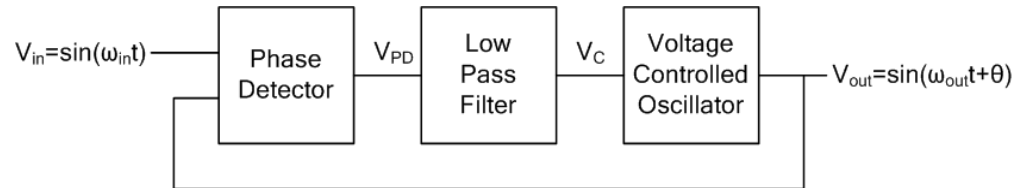

# Lect. 25: PLL


## Frequency tracking of PLL

$$\omega_{in} \neq \omega_{out}$$

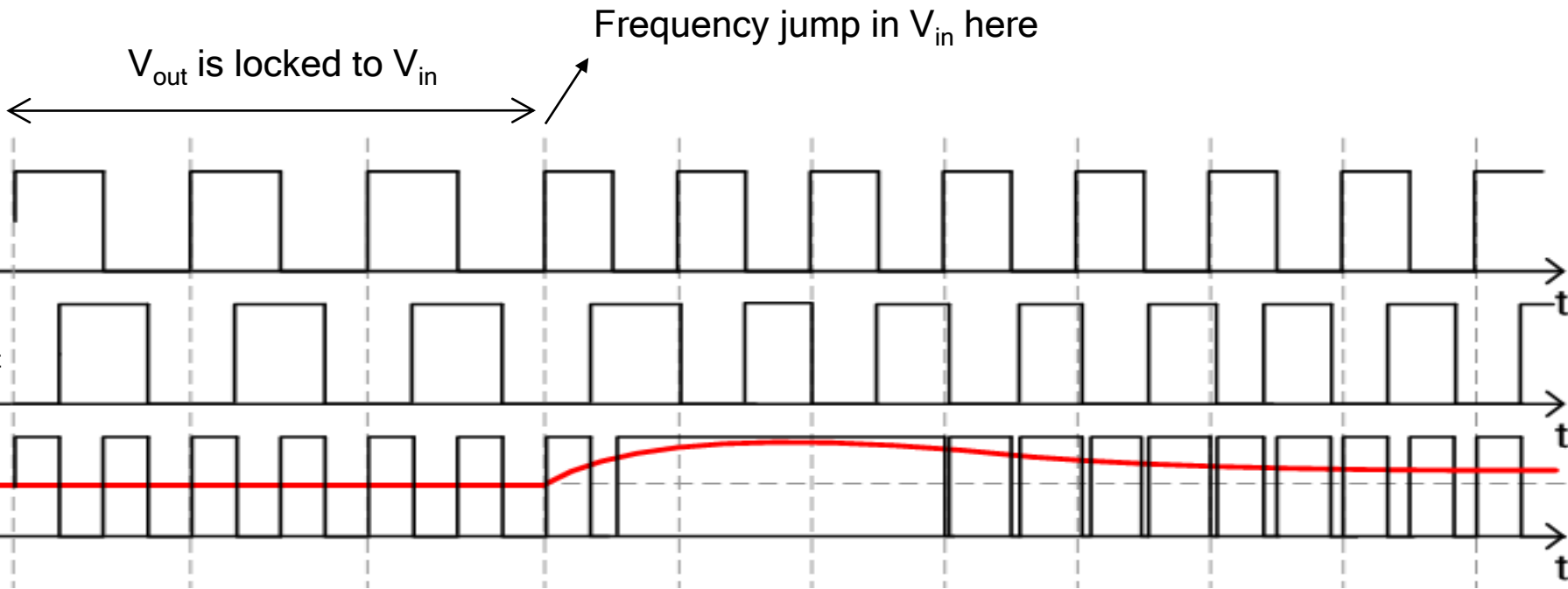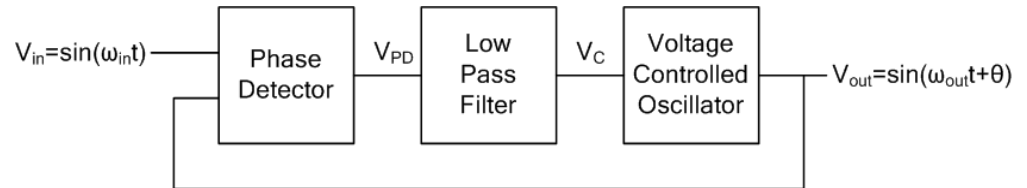


# Lect. 25: PLL
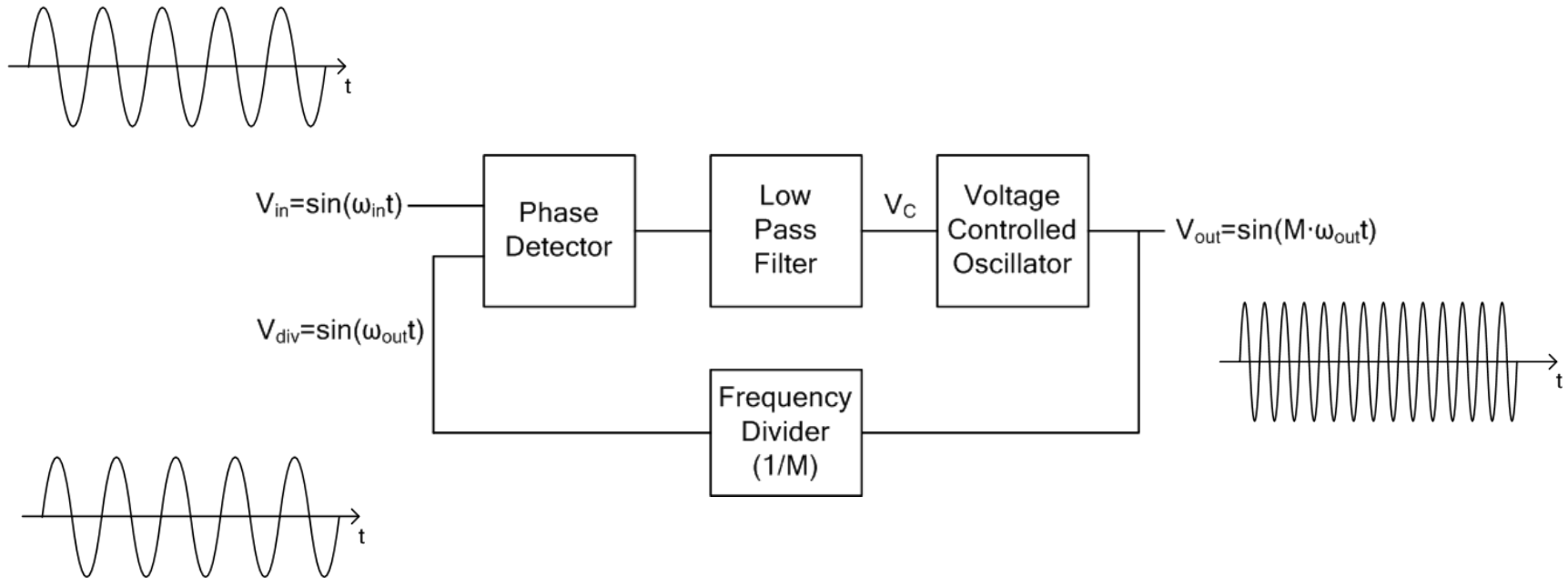
## Applications of PLL: Frequency Synthesis




# Lect. 25: PLL


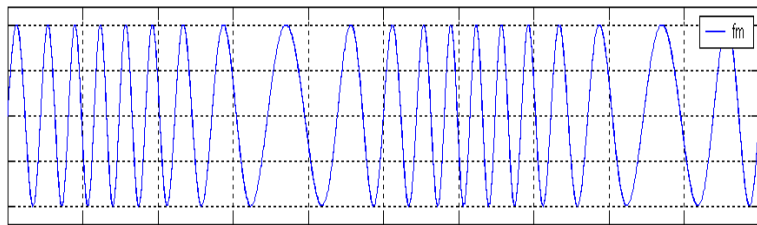
## Applications of PLL: Frequency Demodulation



(FM signal)

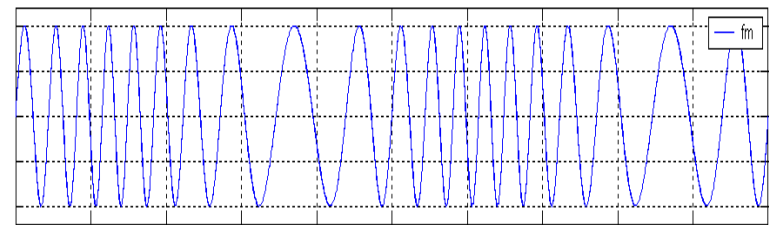

(PLL output)

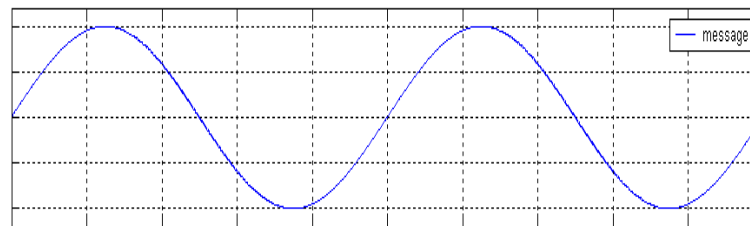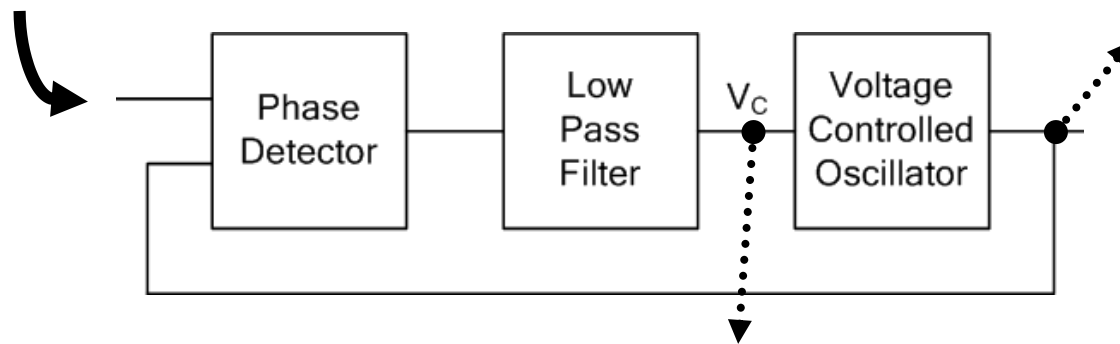

(Recovered message)

# Lect. 25: PLL

Applications of PLL: Clock signal recovery for digital signals

