

PLL Block Diagram

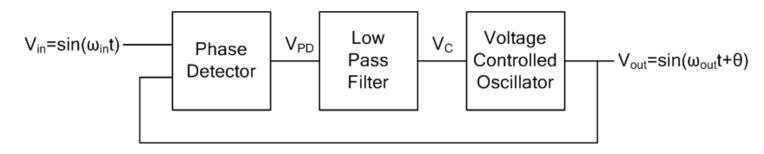

 $\varphi_{\text{out}} / \varphi_{\text{in}} \,$ in s-domain?

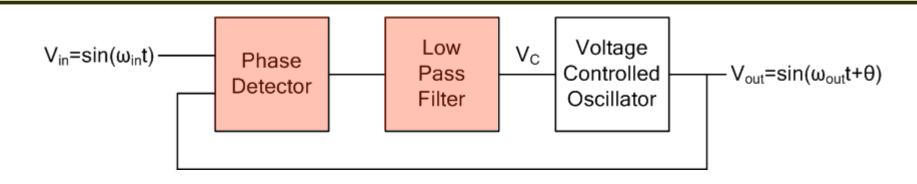
 $\omega_{\text{out}}/\omega_{\text{in}}\,$ in s-domain?





Linear approximation for PD characteristics

LPF: First order with pole at - ω_p

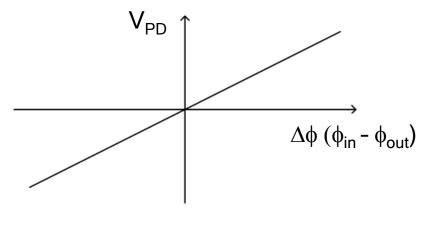


$$T(s) = \frac{\omega_p}{s + \omega_p}$$






W.-Y. Choi

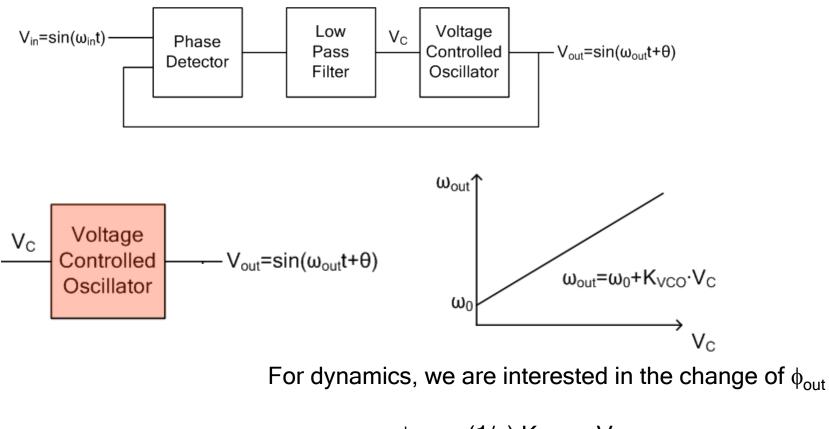

$$\phi_{out} = (1/s) K_{VCO} \times V_C$$




W.-Y. Choi

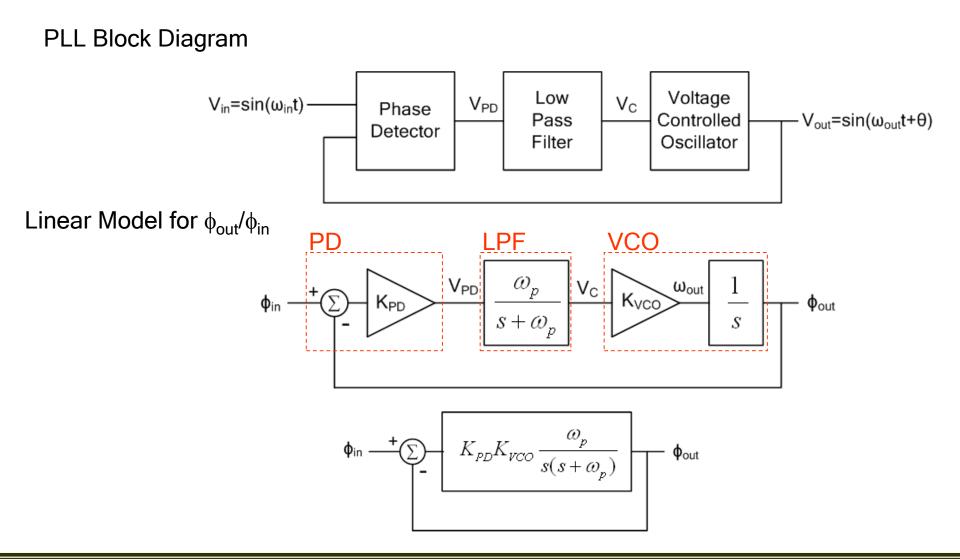

Electronic Circuits 2 (15/1)



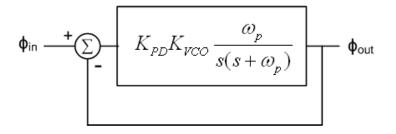

Open loop gain:

$$G(s) = K_{PD} K_{VCO} \frac{\omega_p}{s(s + \omega_p)}$$


Closed loop gain

$$H(s) = \frac{\phi_{out}}{\phi_{in}} = \frac{G(s)}{1 + G(s)} = \frac{K_{PD}K_{VCO}\frac{\omega_p}{s(s + \omega_p)}}{1 + K_{PD}K_{VCO}\frac{\omega_p}{s(s + \omega_p)}} = \frac{K_{PD}K_{VCO}\omega_p}{s^2 + \omega_p s + K_{PD}K_{VCO}\omega_p}$$

→ 2nd order LPF!



W.-Y. Choi

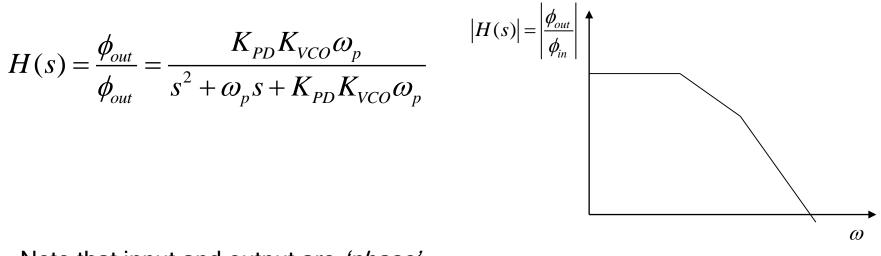


Note that input and output are 'phase'.

What does ω mean in x-axis?

(Assuming two real poles)


W.-Y. Choi



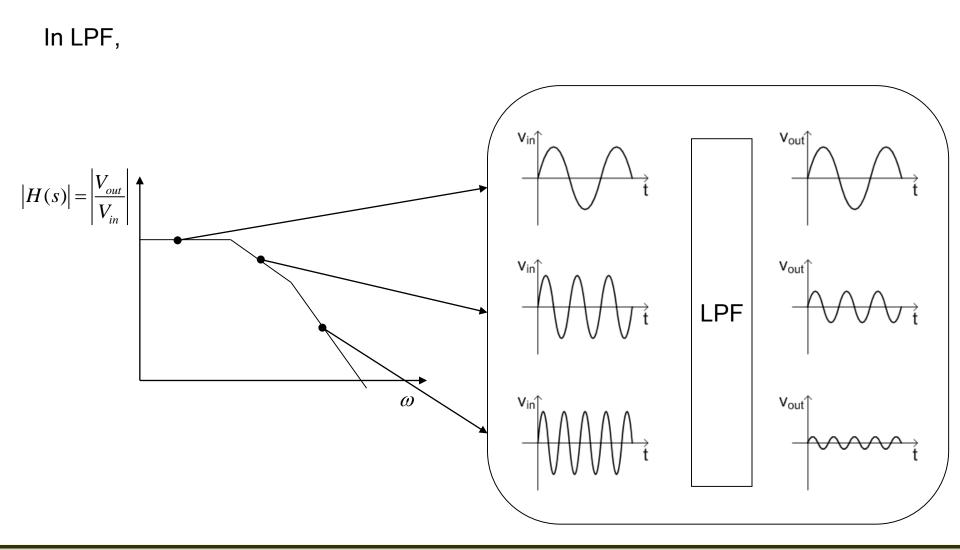

Electronic Circuits 2 (15/1)



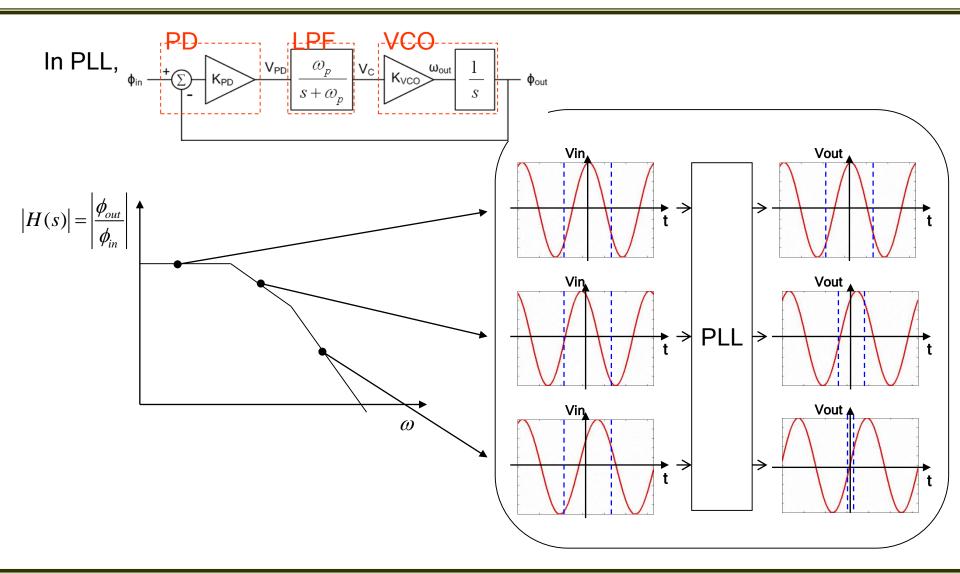

Electronic Circuits 2 (15/1)



$$H(s) = \frac{\phi_{out}}{\phi_{in}} = \frac{K_{PD}K_{VCO}\omega_p}{s^2 + \omega_p s + K_{PD}K_{VCO}\omega_p}$$

2nd order system
$$H(s) = \frac{a_0}{s^2 + (\omega_0 / Q)s + \omega_0^2}$$


$$\omega_0 = \sqrt{K_{PD} K_{VCO} \omega_P} \qquad Q = \sqrt{\frac{K_{PD} K_{VCO}}{\omega_P}} \qquad a_0 = \omega_0^2$$

$$\frac{\omega_{out}}{\omega_{in}} = \frac{s\phi_{out}}{s\phi_{in}} = \frac{\phi_{out}}{\phi_{in}} = \frac{\omega_0^2}{s^2 + (\omega_0 / Q)s + \omega_0^2}$$



W.-Y. Choi


 ω_o dependence

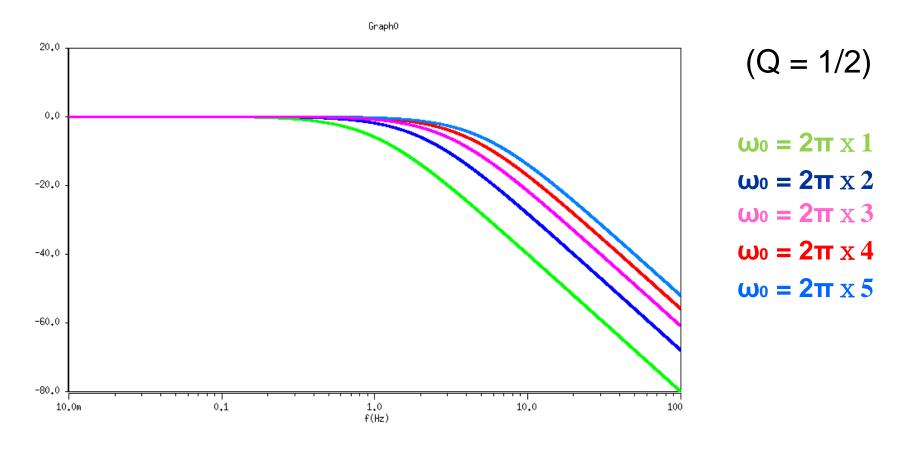





Q dependence

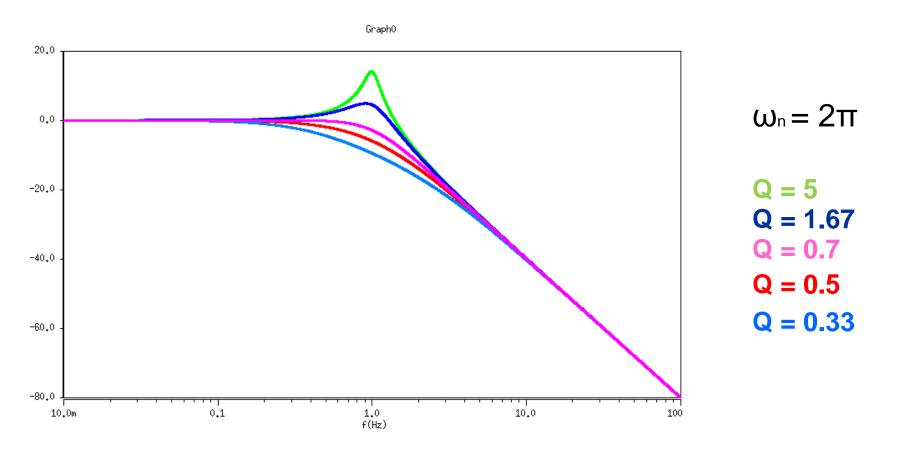





Step response

$$\omega_{in}(t) = \Delta \omega \cdot u(t) \qquad \exp\left[-\frac{\omega_0 t}{2Q}\right]$$


$$\omega_{in}(t) \qquad \Delta \omega \qquad t \qquad PLL \qquad \Rightarrow \qquad \omega_{out}(t) \qquad t$$

$$\omega_{out}(t) = \left\{1 - e^{-\frac{\omega_0}{2Q}t} \left[\cos(\omega_0 \sqrt{1 - \frac{1}{4Q^2}} \cdot t) + \frac{1}{\sqrt{4Q^2}} \sin(\omega_0 \sqrt{1 - \frac{1}{4Q^2}} \cdot t)\right]\right\} \Delta \omega \cdot u(t)$$



W.-Y. Choi

Step response: Q dependence:

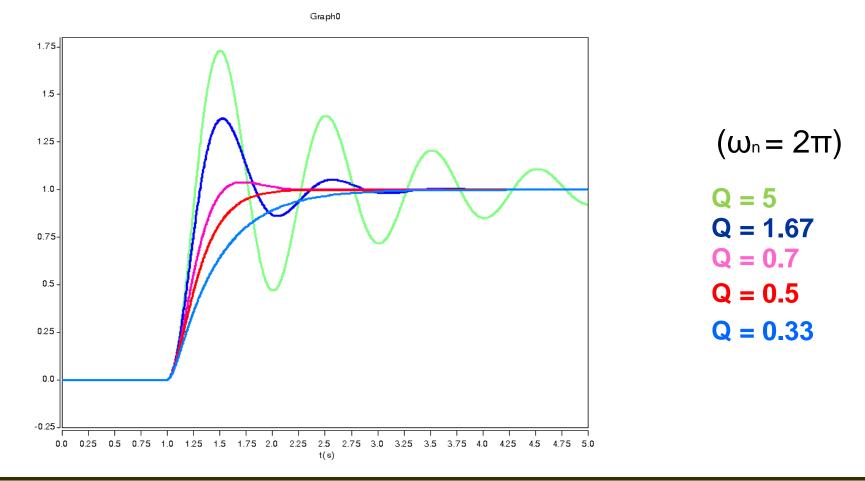

Electronic Circuits 2 (15/1)



Natural frequency dependence: Step Response

