


Lect. 28: Data Converters

Data Converters


- ADC: Analog to Digital Converter
- DAC: Digital to Analog Converter

Why data conversion?

- Digital is very powerful:
Computation/Signal Processing in digital domain is much more powerful than in analog domain
- Real world is made up of analog signals

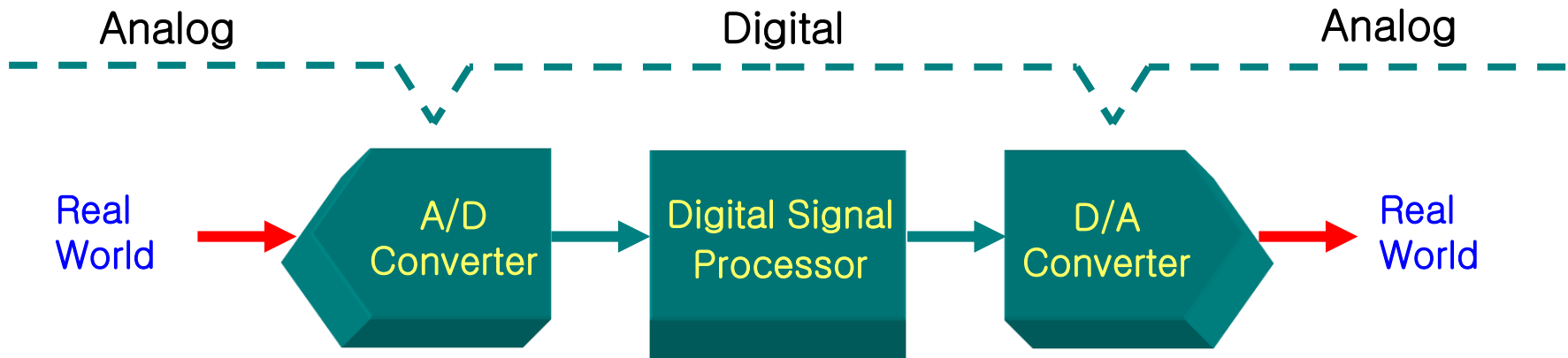


Lect. 28: Data Converters

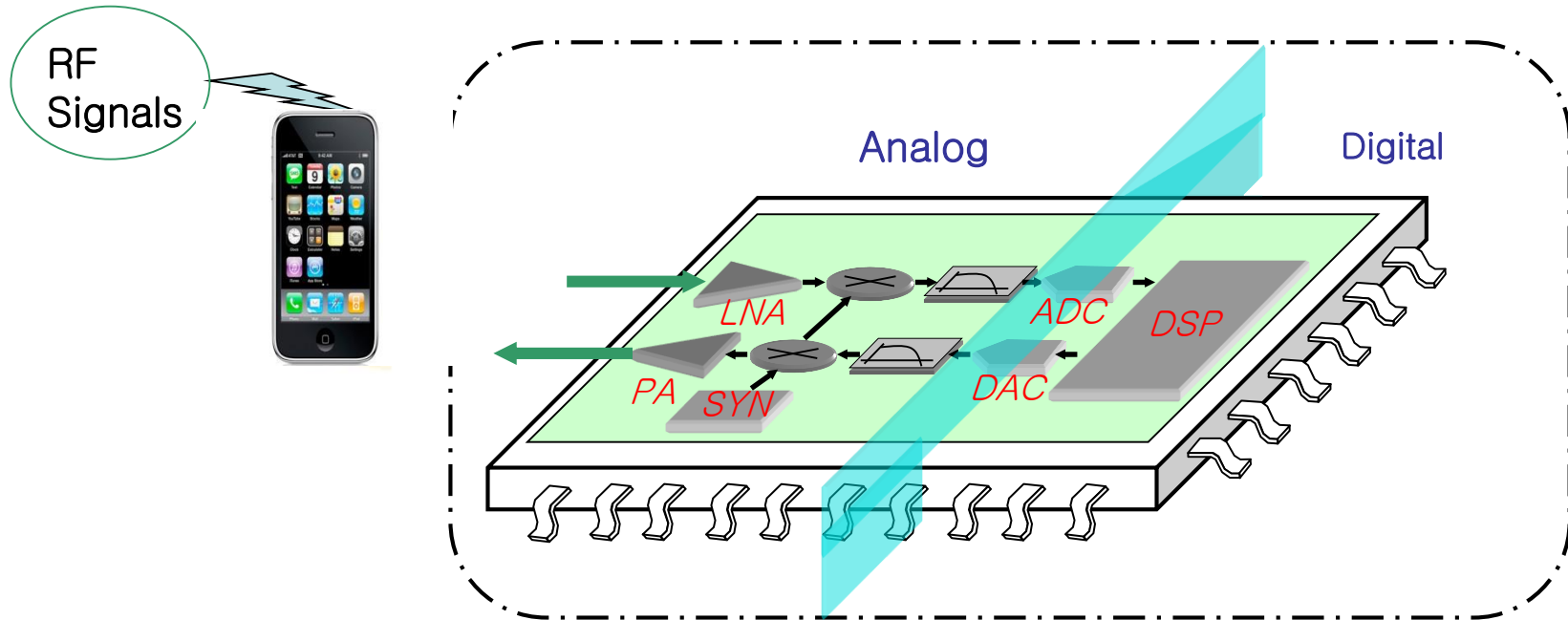


LNA: Low Noise Amplifier
PA: Power Amplifier
SYN: Frequency Synthesizer

Lect. 28: Data Converters

A/D Process

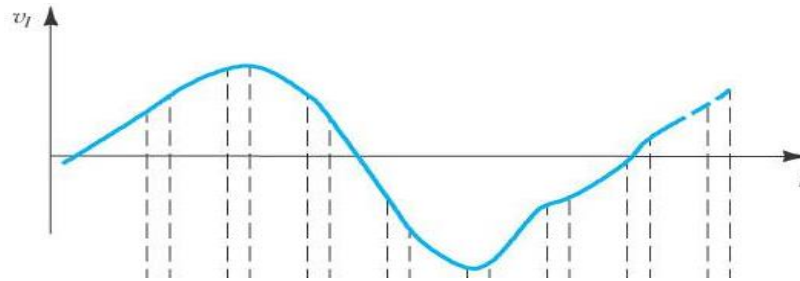


Input analog signal


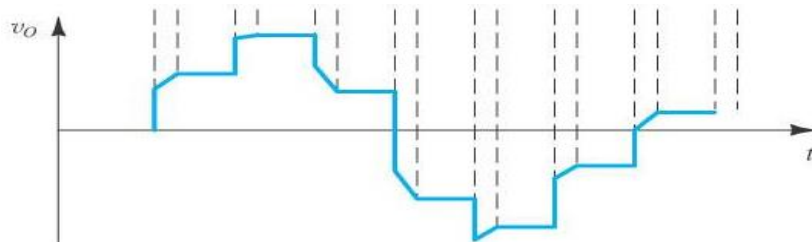


Sampled signal

Lect. 28: Data Converters

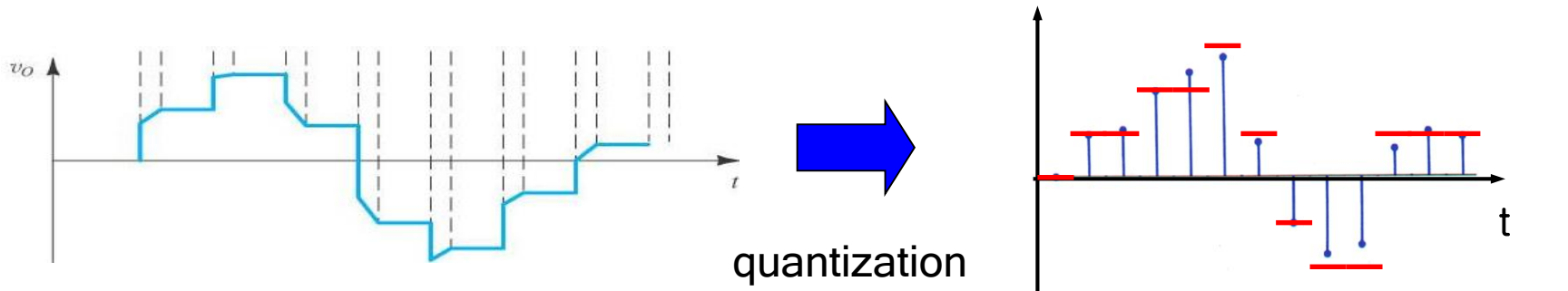

Output Code

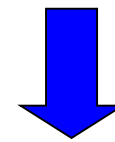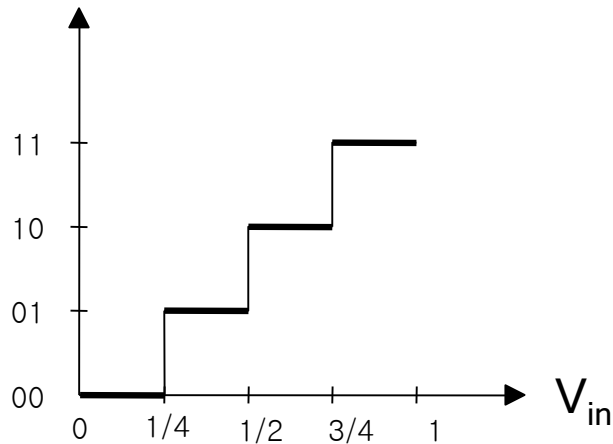



digital coding

... 01011 ...

Lect. 28: Data Converters

D/A Process

Digital input: ...01011 ...

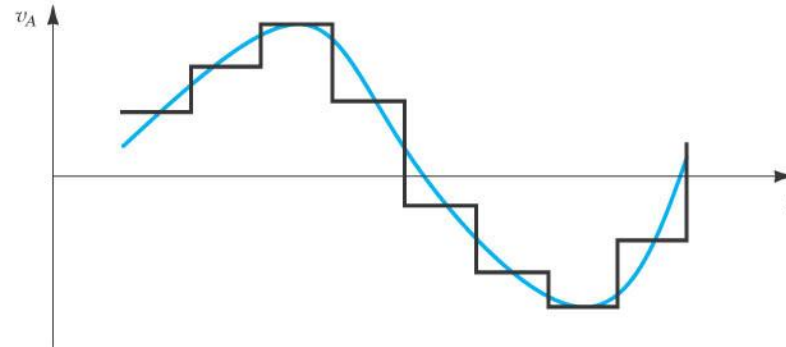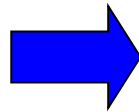


Key parameters: Resolution and bandwidth

Lect. 28: Data Converters

Hardware implementation of D/A Converter

Input: $b_1 b_2 b_3 \dots b_N$ (b_N : Least significant bit)


$$D = \frac{b_1}{2^1} + \frac{b_2}{2^2} + \dots + \frac{b_N}{2^N}$$

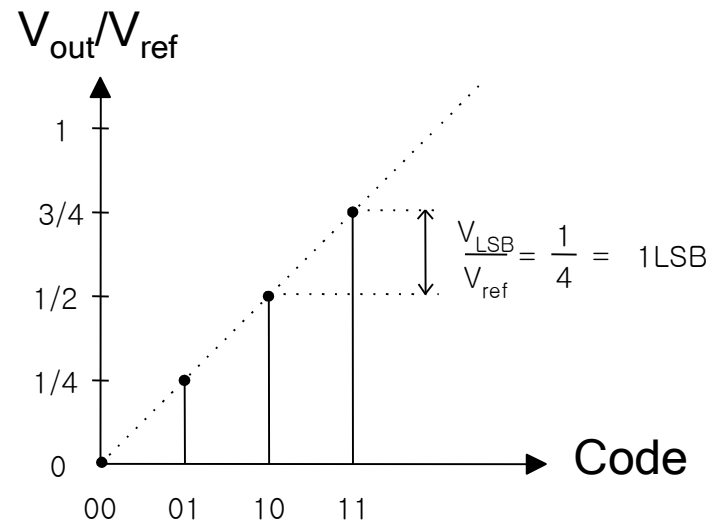

Lect. 28: Data Converters

N-bit D/A Converter
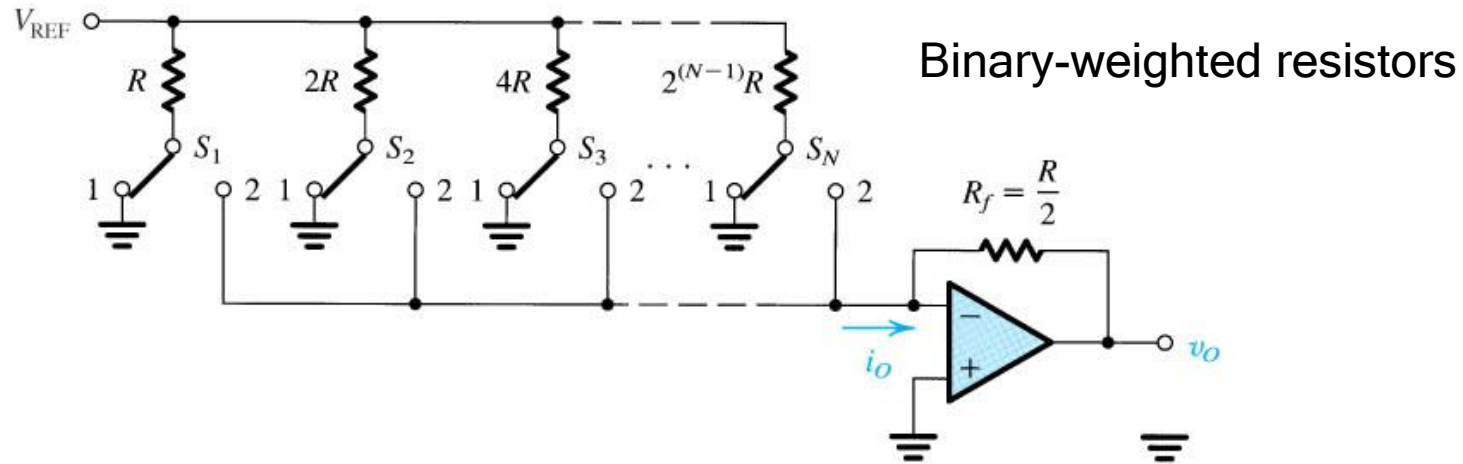
$$D = \frac{b_1}{2^1} + \frac{b_2}{2^2} + \dots + \frac{b_N}{2^N}$$




$$i_o = \frac{V_{REF}}{R} b_1 + \frac{V_{REF}}{2R} b_2 + \dots + \frac{V_{REF}}{2^{N-1}R} b_N = \frac{2V_{REF}}{R} \left(\frac{b_1}{2^1} + \frac{b_2}{2^2} + \dots + \frac{b_N}{2^N} \right)$$

$$v_o = -V_{REF} \left(\frac{b_1}{2^1} + \frac{b_2}{2^2} + \dots + \frac{b_N}{2^N} \right) = -V_{REF} D$$

Lect. 28: Data Converters

N-bit D/A Converter

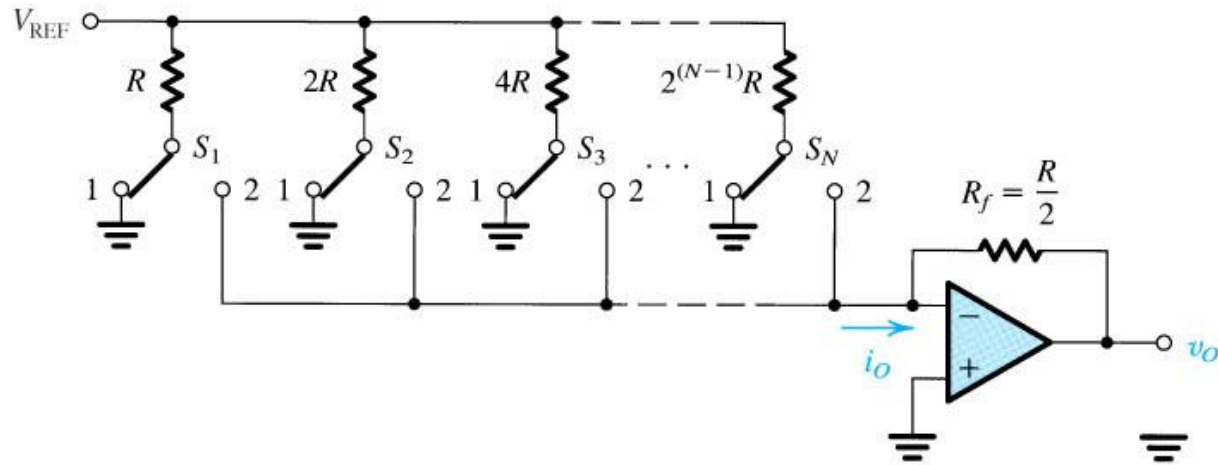



Accuracy of DAC: Precision of binary resistors

→ With binary weighted resistors, big differences in resistance values

Lect. 28: Data Converters

Flash ADC

Ex.) 3-bit Flash ADC

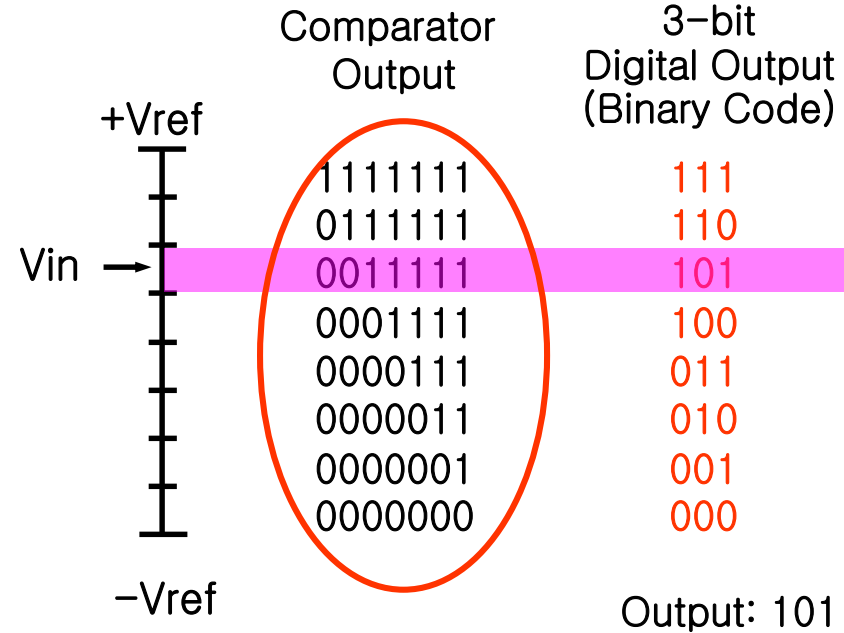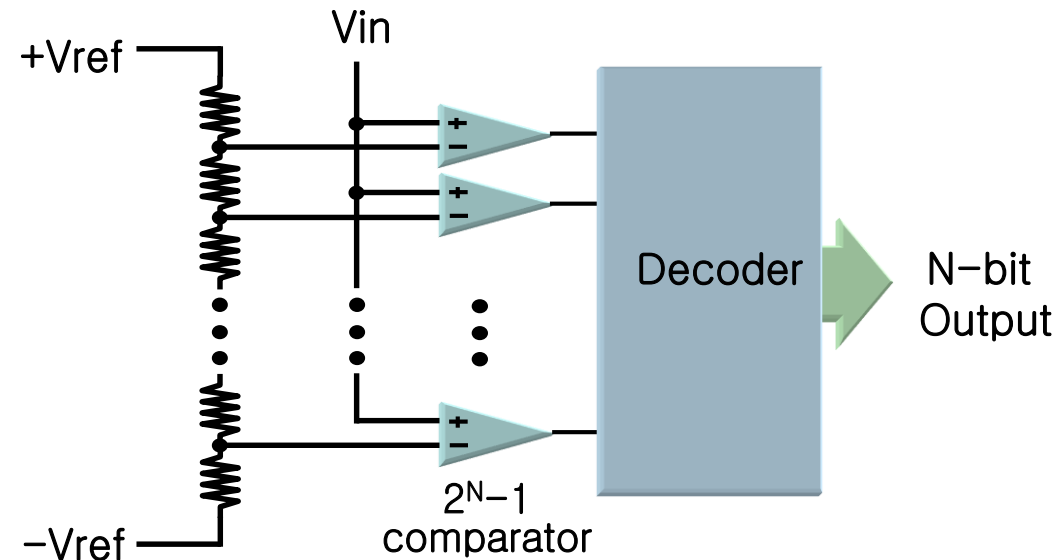

Output: 101



Thermometer Code

Fast because of parallel processing

R matching problem

Lect. 28: Data Converters

Dual-Slope ADC

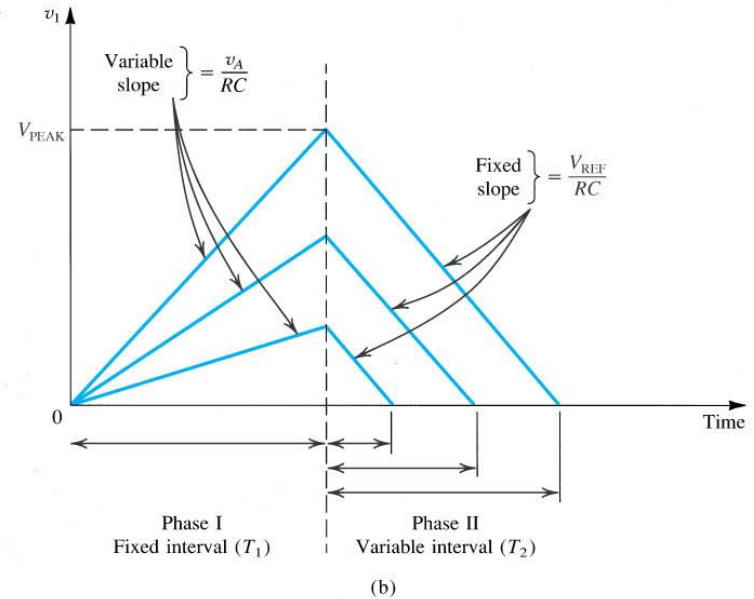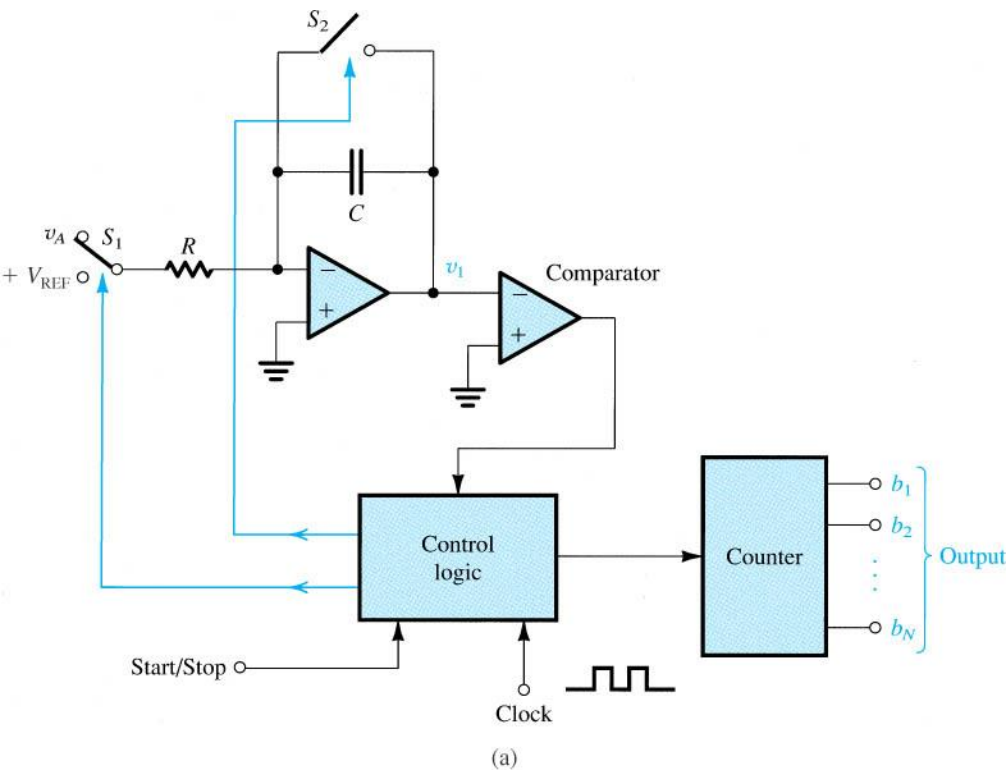



Charge up the integrator for T_1 with v_A

$$T_1 = \frac{V_{PEAK}}{|v_A| / RC}$$

Simultaneously count up the counter to 2^N

Lect. 28: Data Converters

Dual-Slope ADC

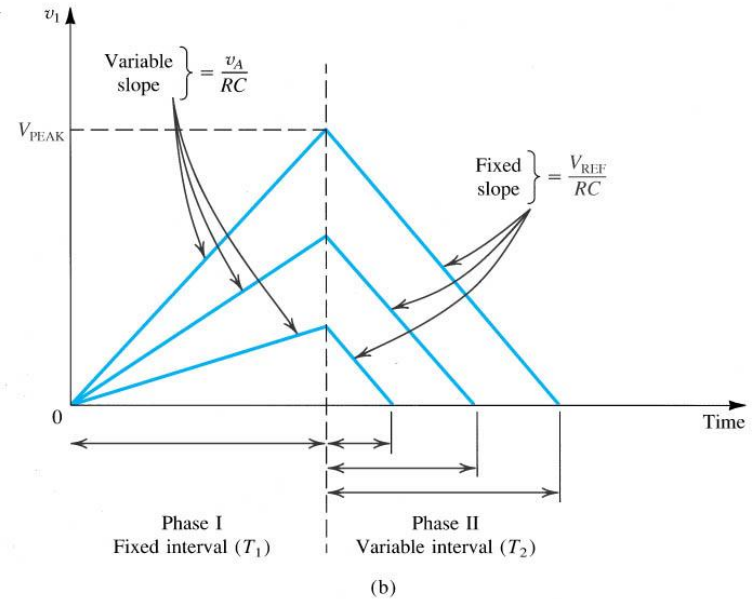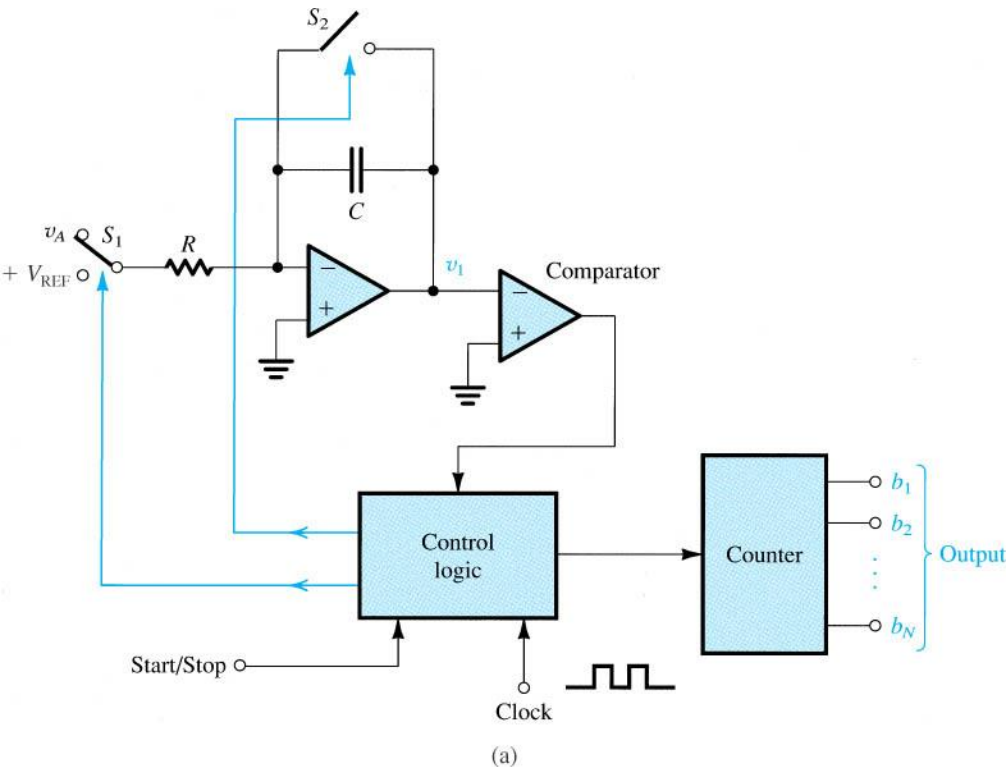


Discharge the integrator with V_{REF}
 Stop counting when v_1 reaches 0 at T_2

$$T_2 = \frac{V_{PEAK}}{V_{REF} / RC} \quad \frac{T_2}{T_1} = \frac{|v_A|}{V_{REF}}$$

Output bit sequence is the digital bit corresponding to $\frac{|v_A|}{V_{REF}}$

High accuracy: No direct dependence on R, C
 But slow

Lect. 28: Data Converters

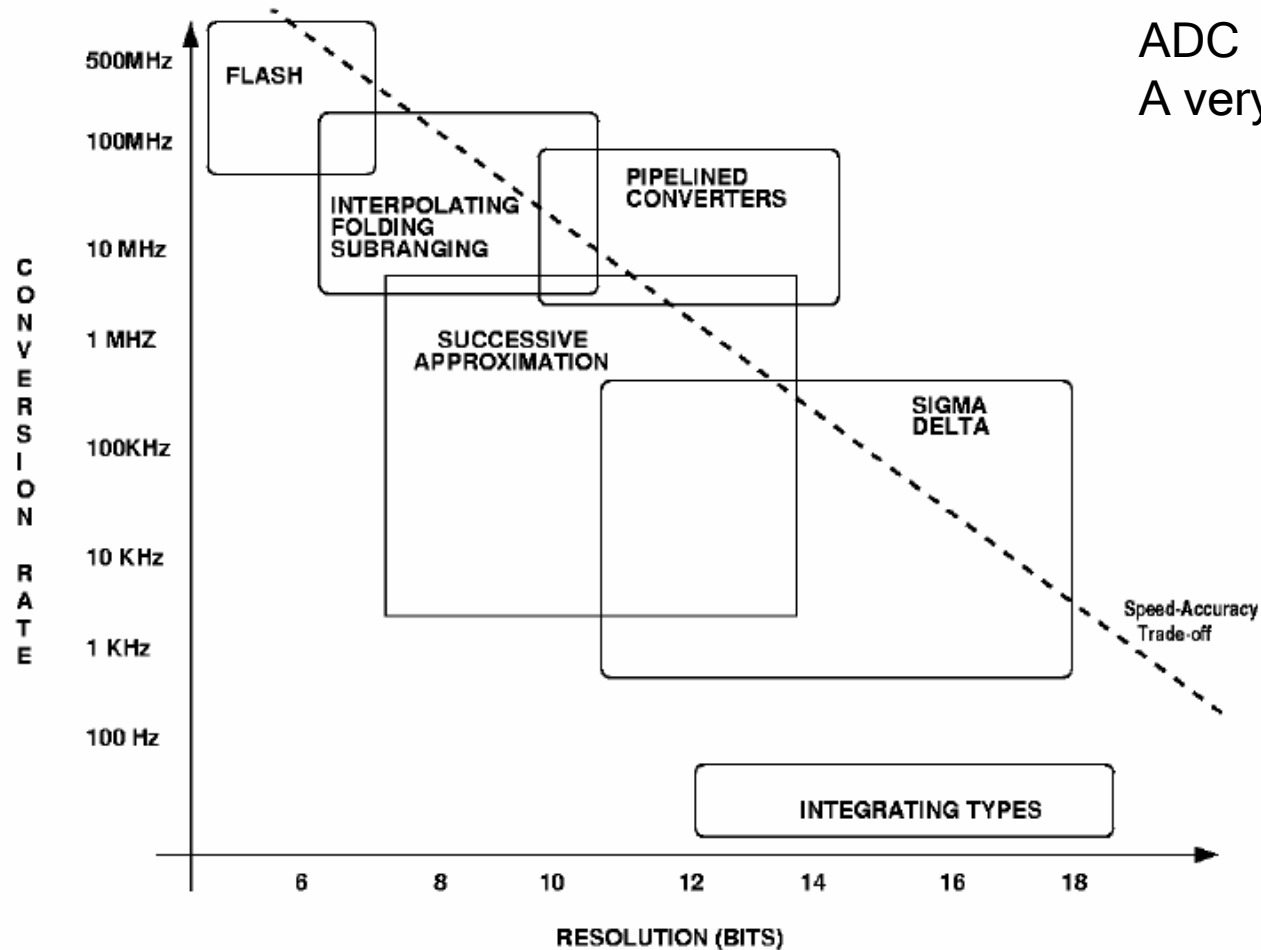

ADC
A very active research area