
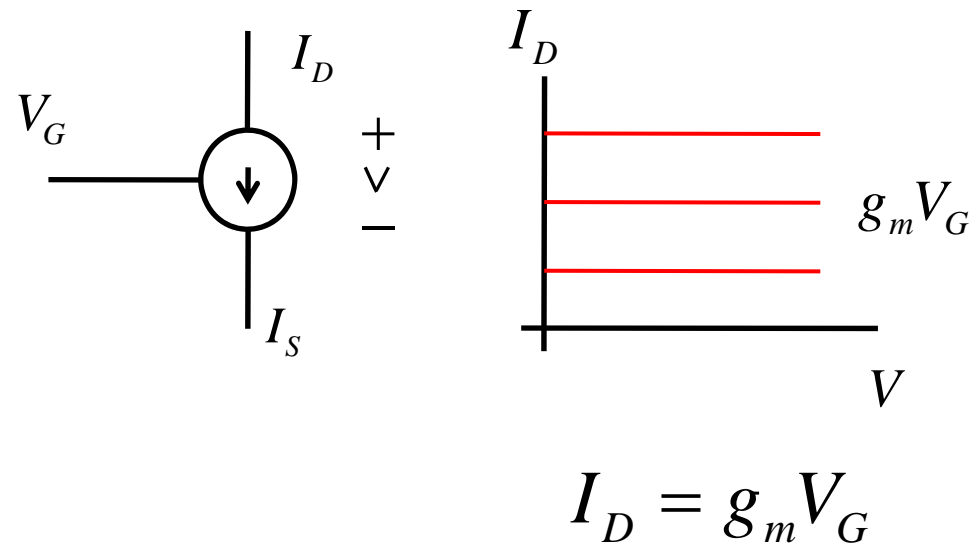


Lect. 4: MOS Transistors (3)

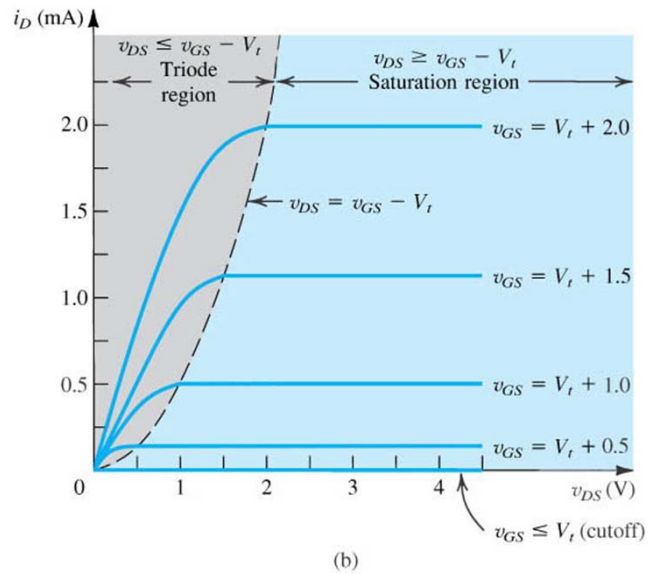
→ Voltage-controlled current source (In saturation)



What's special about this?

Lect. 4: MOS Transistors (3)

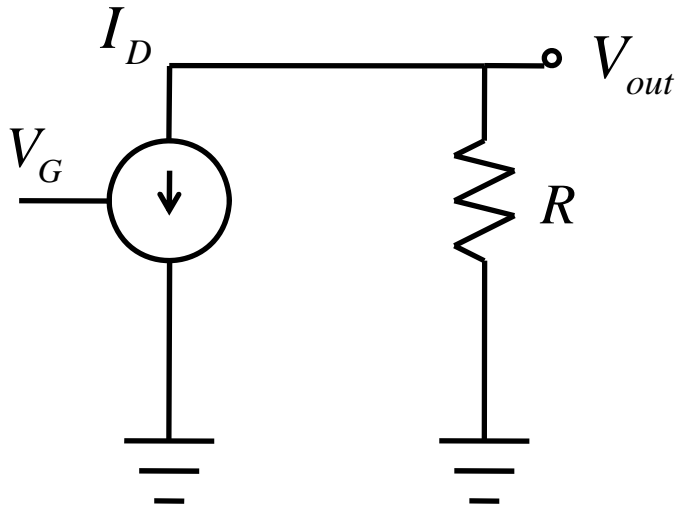Voltage-controlled current source: What can you do with it?



$$V_{out} = -I_D \cdot R$$


$$= -g_m V_G R$$

$$\frac{V_{out}}{V_G} = -g_m \cdot R$$


Voltage amplifier

Lect. 4: MOS Transistors (3)

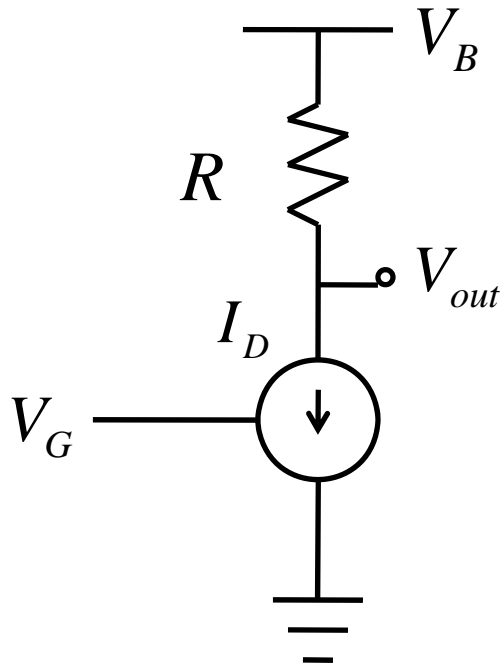Voltage-controlled current source: What can you do with it?


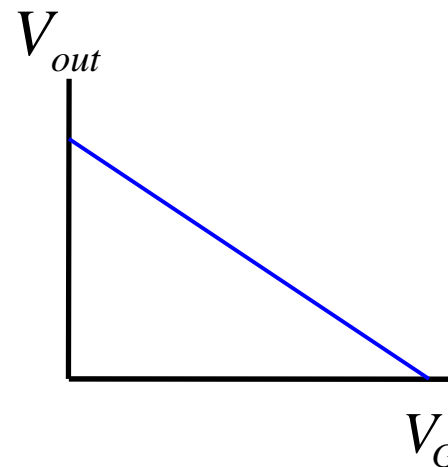
$$\begin{aligned} V_{out} &= V_B - I_D \cdot R \\ &= V_B - g_m V_G \cdot R \end{aligned}$$




Inverter

Lect. 4: MOS Transistors (3)

- Small-signal model for NMOS in saturation

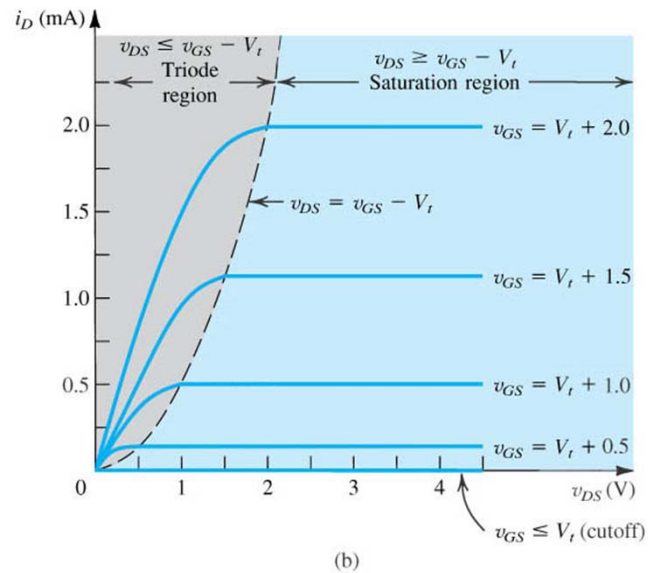- What happens when v_{GS} changes slightly?



$$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{GS} - V_{TH})^2$$


$$\Delta i_D \sim \frac{\partial i_D}{\partial v_{GS}} \cdot \Delta v_{GS} \quad \frac{\partial i_D}{\partial v_{GS}} = g_m \quad \text{Transconductance}$$

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})$$


$$= \frac{2I_D}{V_{GS} - V_{TH}}$$

$$= \sqrt{2\mu_n C_{ox} \cdot \frac{W}{L} \cdot I_D}$$

Lect. 4: MOS Transistors (3)

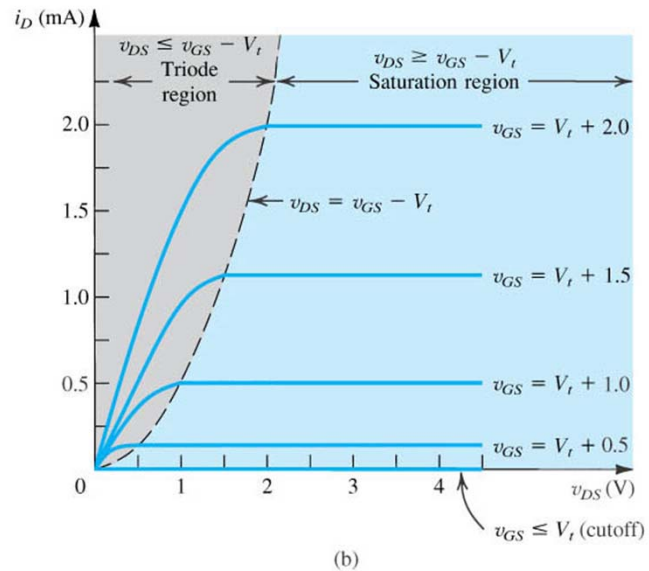

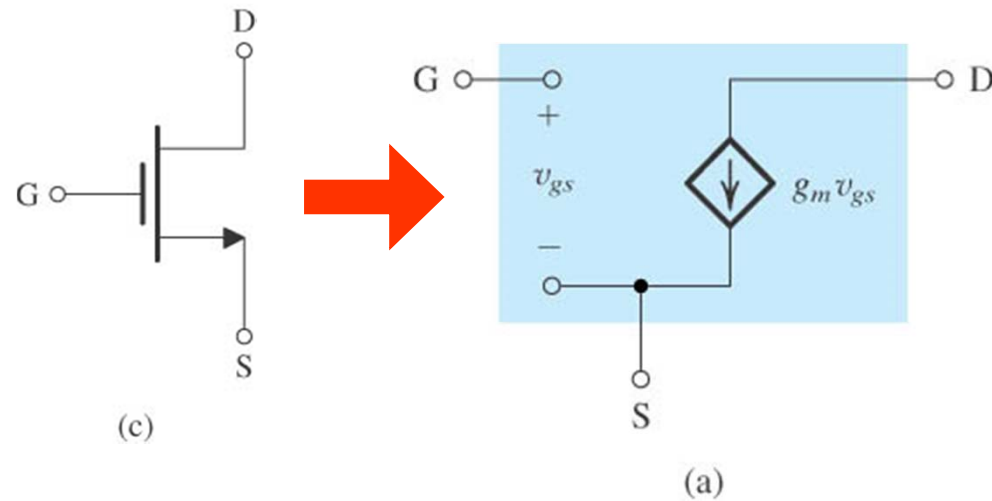
- Small-signal circuit model for NMOS in saturation




- Linearization of non-linear characteristics of transistors
- Depends on bias

Lect. 4: MOS Transistors (3)

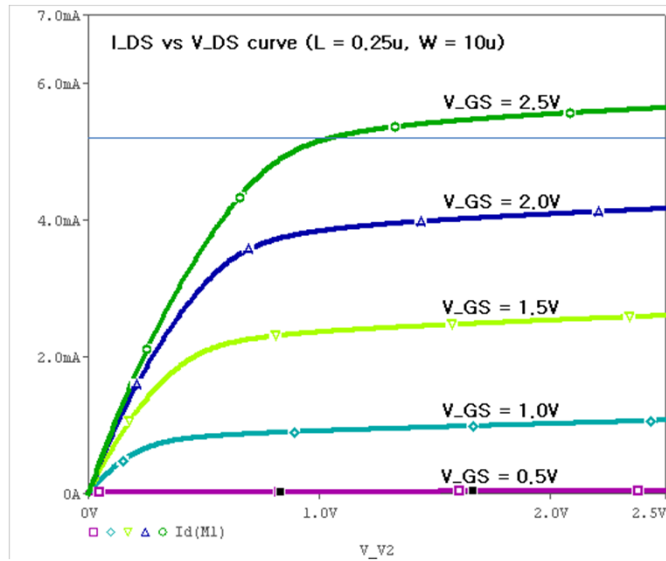- Small-signal model with channel length modulation


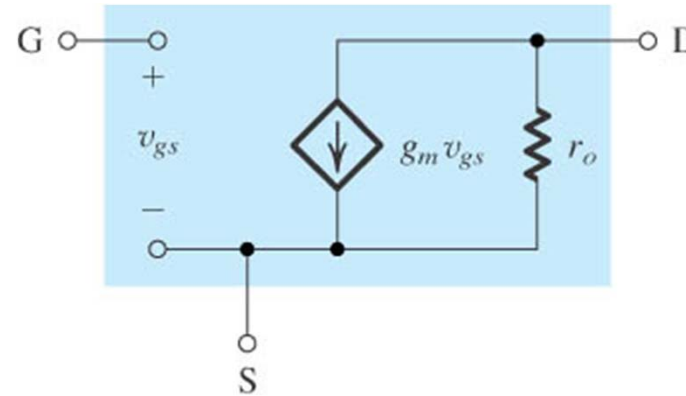
$$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{GS} - V_{TH})^2 (1 + \lambda \cdot v_{DS})$$




$$\frac{1}{r_0} = \frac{\partial i_D}{\partial v_{DS}} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{GS} - V_{TH})^2 \lambda$$


$$r_0 = \frac{1}{\lambda I_D}$$

Lect. 4: MOS Transistors (3)

Small-signal model including Body effect

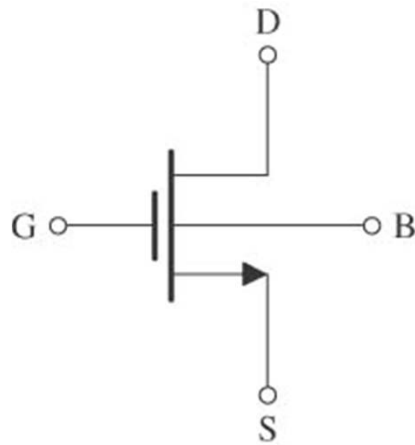

(a)

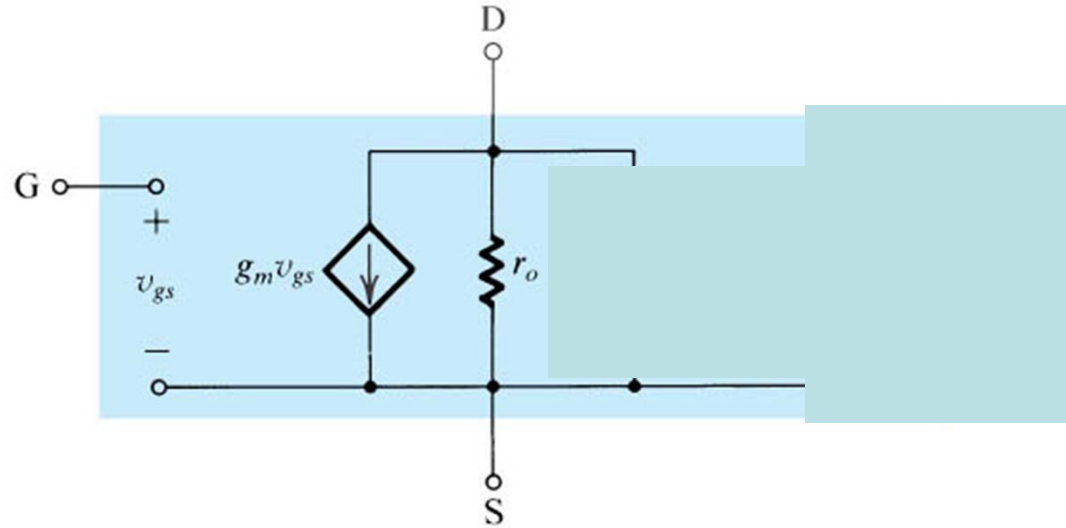

Practically, Body Effect
Is not easy to model analytically.

→ Simulation


$$g_{mb} \equiv \left. \frac{\partial i_D}{\partial v_{BS}} \right|_{\substack{v_{GS} = \text{constant} \\ v_{DS} = \text{constant}}}$$

$$g_{mb} \equiv \chi g_m \quad (\chi : 0.1 - 0.3)$$

Lect. 4: MOS Transistors (3)

- Small-signal model for PMOS in saturation? $i_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (v_{SG} - |V_{TH}|)^2$
- What happens when v_{SG} changes slightly?

$$g_m = \frac{\partial i_D}{\partial v_{SG}} = \mu_p C_{ox} \frac{W}{L} (v_{SG} - |V_{TH}|) = \frac{2I_D}{v_{SG} - |V_{TH}|} = \sqrt{2\mu_p C_{ox} \cdot \frac{W}{L} \cdot I_D}$$

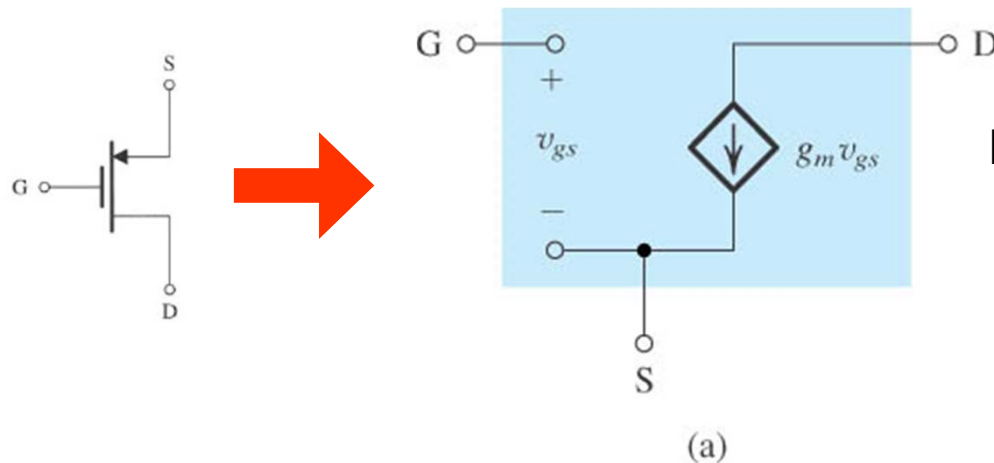

Identical to NMOS small-signal model

Lect. 4: MOS Transistors (3)

Homework

- Determine by simulation how g_m changes as a function of V_{GS} (for NMOS, from 1V to 2V) and V_{SG} (for PMOS, from 1V to 2V) for our MOS transistors.