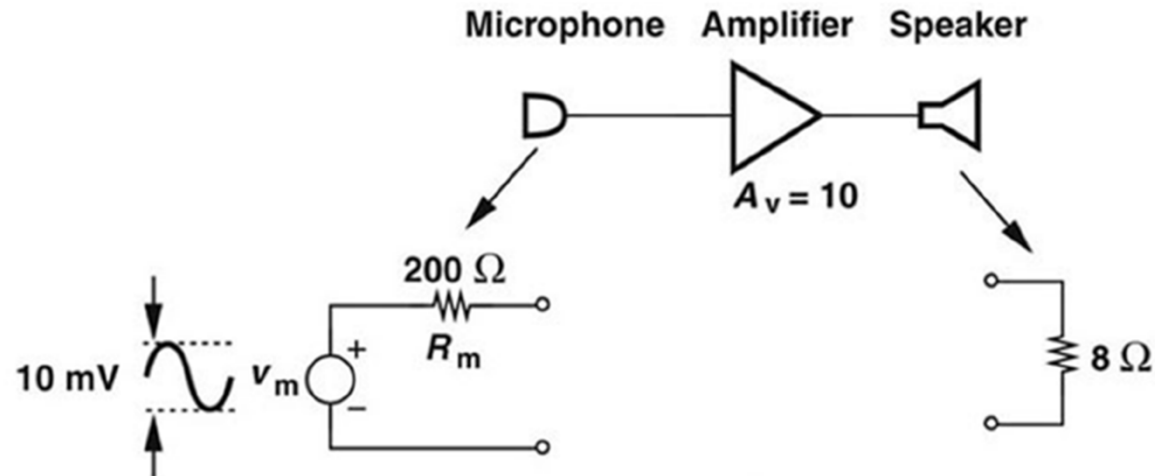


Lect. 5: CMOS Amplifiers (1) (Razavi 7)




- Amplifier output signal should be **faithful replica** of input signal with desired amount of amplification

→ Linear (Small-signal operation for MOS transistor)

- Key amplifier parameters:

Gain


R_{in} and R_{out}

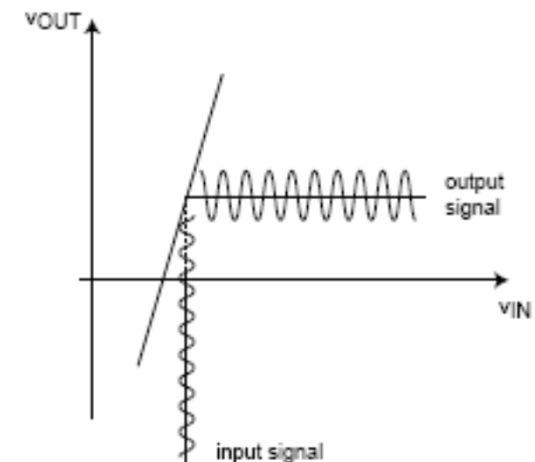

Lect. 5: CMOS Amplifiers (1) (Razavi 7)


How can make amplifiers with MOS transistors

Three basic configurations: CS, CG, CD (SF)

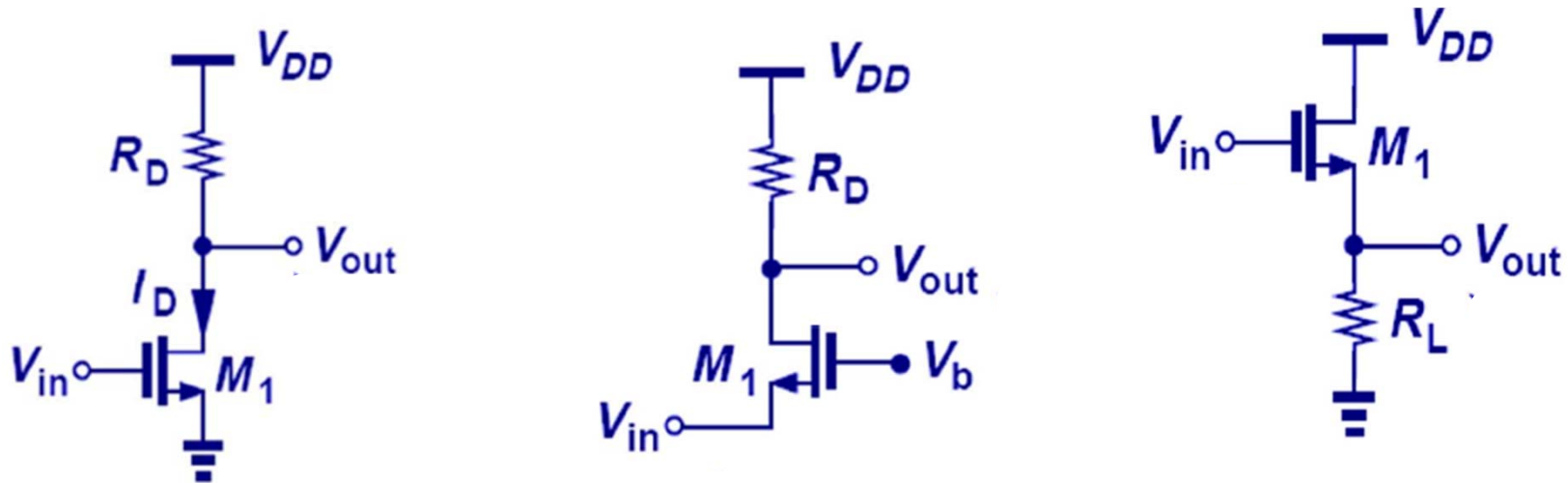

Lect. 5: CMOS Amplifiers (1) (Razavi 7)

- Common Source
- How does it work?

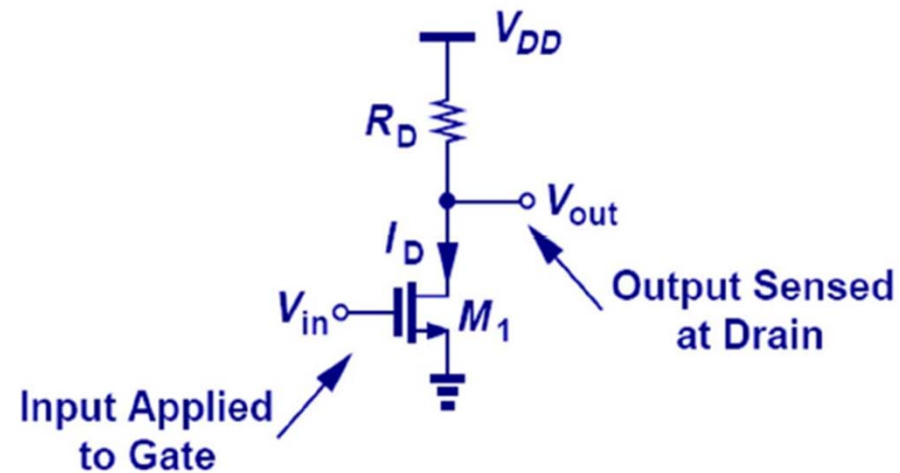


- Operation in saturation

$$R_D I_D < V_{DD} - (V_{GS} - V_{TH})$$



Lect. 5: CMOS Amplifiers (1) (Razavi 7)

- CS

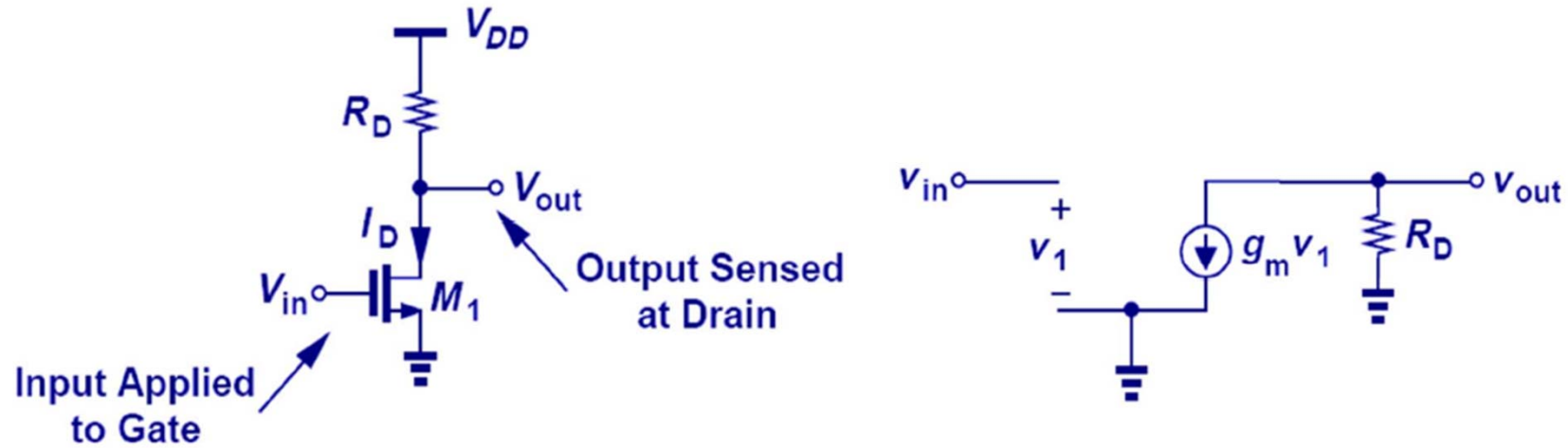

Lect. 5: CMOS Amplifiers (1) (Razavi 7)

- CS

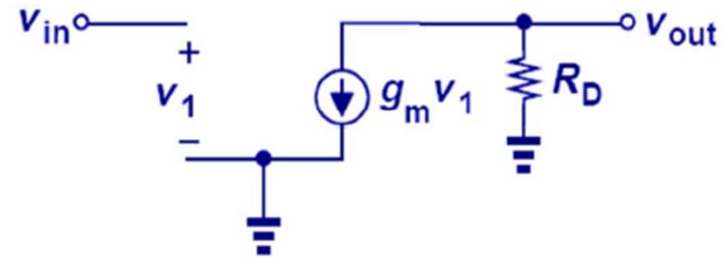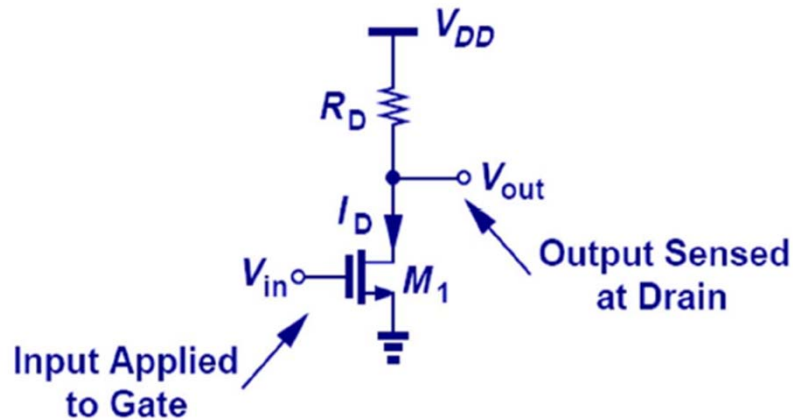


- With channel length modulation

- With a load (R_L)

Lect. 5: CMOS Amplifiers (1) (Razavi 7)



- CS with Current-Source Load

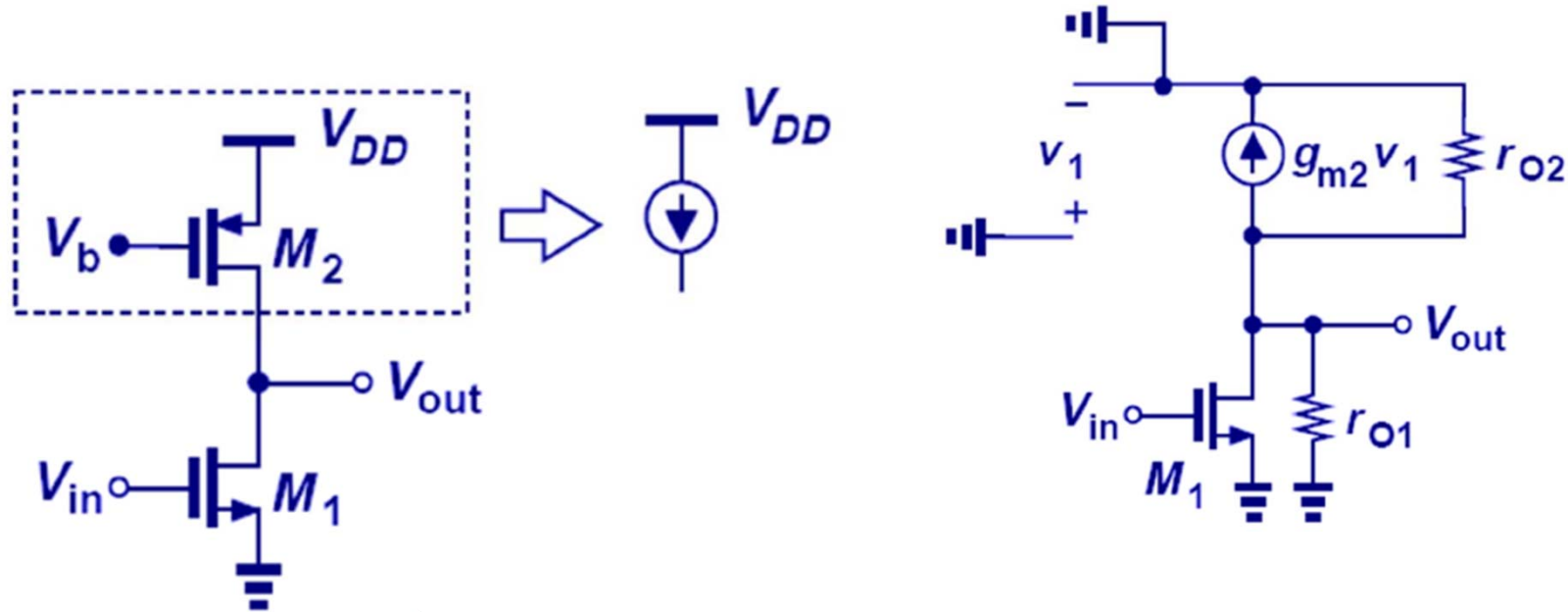

$$A_v = -g_{m1} (r_{O1} \parallel r_{O2})$$
$$R_{out} = r_{O1} \parallel r_{O2}$$

Lect. 5: CMOS Amplifiers (1) (Razavi 7)



- CS with Diode-Connected Load

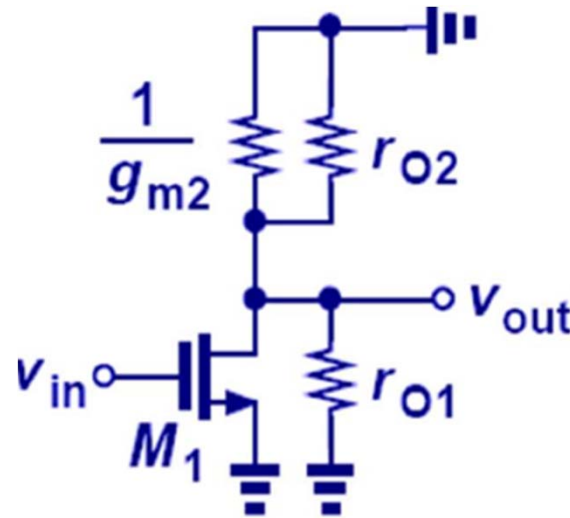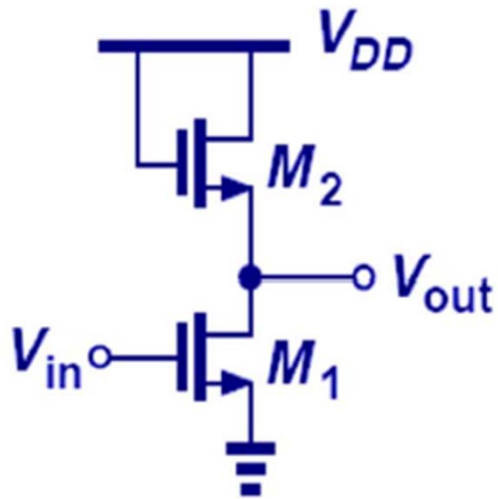

$$A_v = -g_{m1} \left(\frac{1}{g_{m2}} \parallel r_{o2} \parallel r_{o1} \right)$$

Lect. 5: CMOS Amplifiers (1) (Razavi 7)


- CS with Degeneration

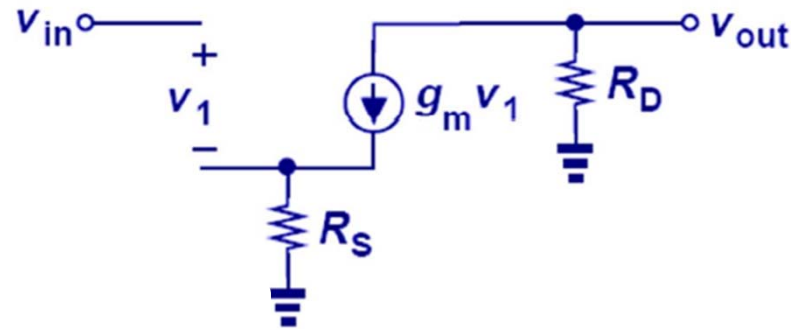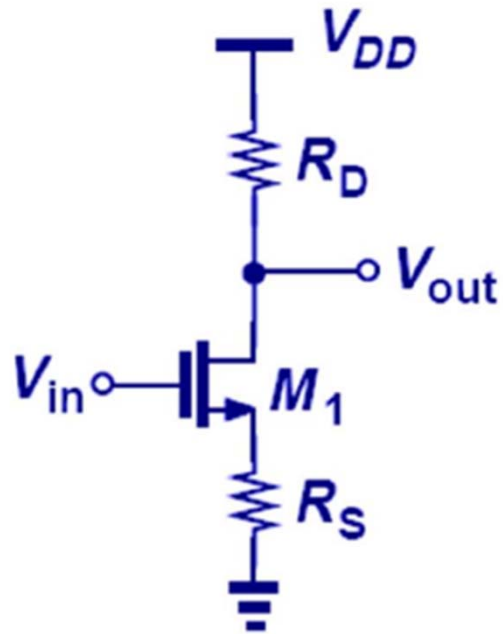

$$A_v = -\frac{R_D}{\frac{1}{g_m} + R_S}$$

Lect. 5: CMOS Amplifiers (1) (Razavi 7)

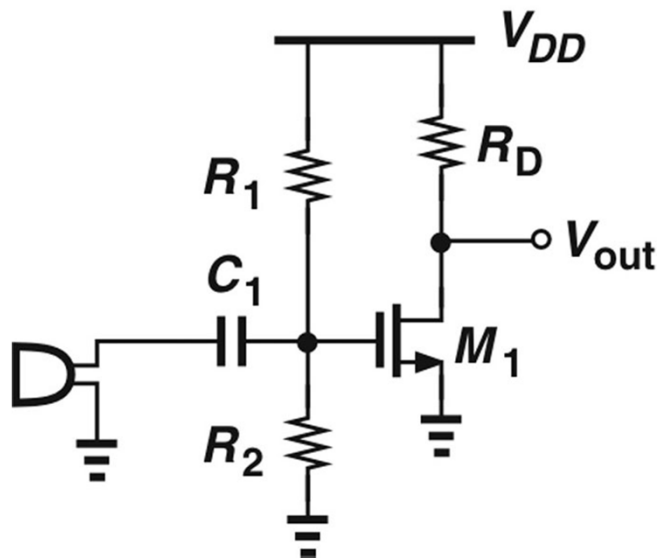
- Why source degeneration?
- Bias stabilization



- R_1, R_2 provide bias for M_1
- Why C_1 ?
- What happens if R_1, R_2 fluctuate?

Lect. 5: CMOS Amplifiers (1) (Razavi 7)



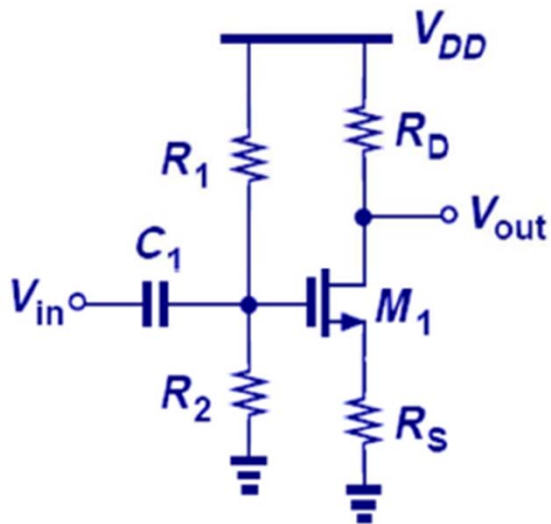
- Why source degeneration?
- Bias stabilization



- Any fluctuation in M_1 gate voltage is stabilized by R_S (Negative feedback)

Lect. 5: CMOS Amplifiers (1) (Razavi 7)

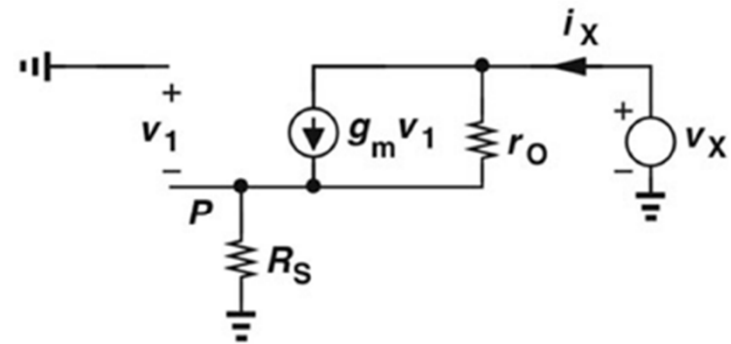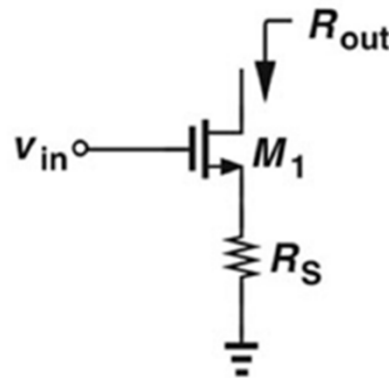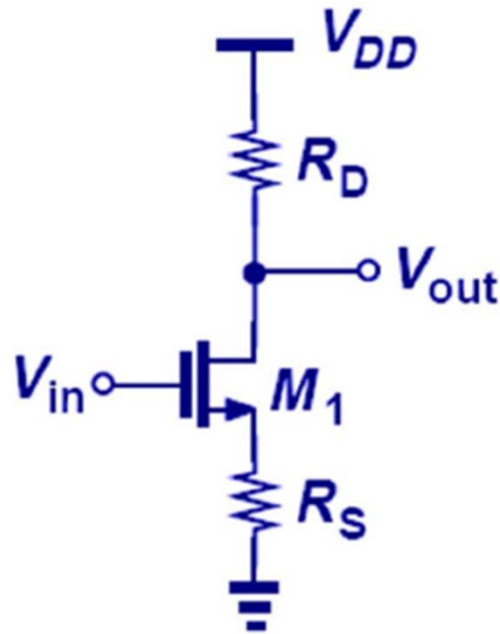- Output Impedance for CS with Degeneration



$$R_{out} = (1 + g_m r_o) R_S + r_o$$

$$\approx g_m r_o R_S$$

R_{out} for CS with Degeneration?

Lect. 5: CMOS Amplifiers (1) (Razavi 7)

- Homework

Prob. 7.17. 7.19 (Assume $\lambda = 0$) in Razavi