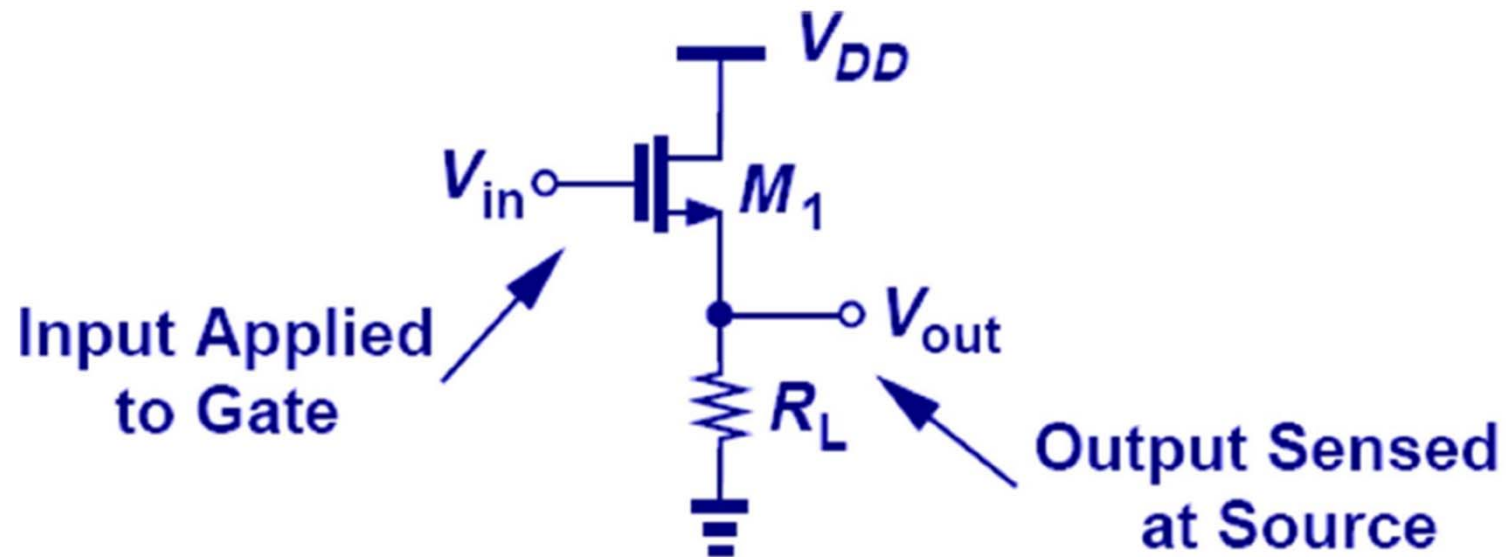




Lect. 6: CMOS Amplifiers (2)

- Source Follower (Common Drain)




Lect. 6: CMOS Amplifiers (2)

- Source Follower

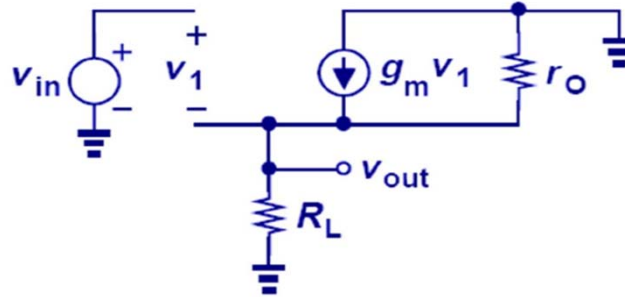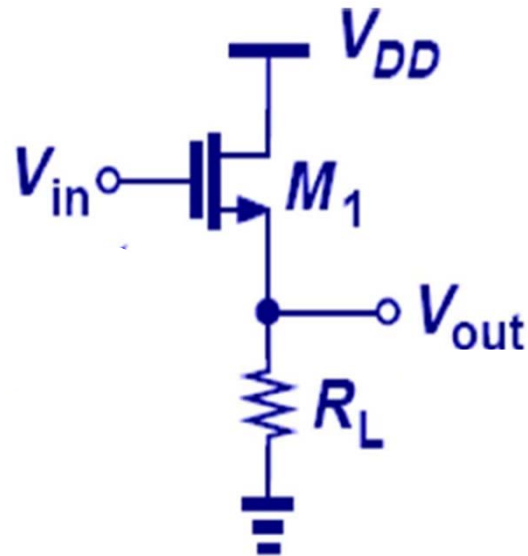


$$A_v = \frac{v_{out}}{v_{in}} = \frac{r_o \parallel R_L}{\frac{1}{g_m} + r_o \parallel R_L} < 1$$

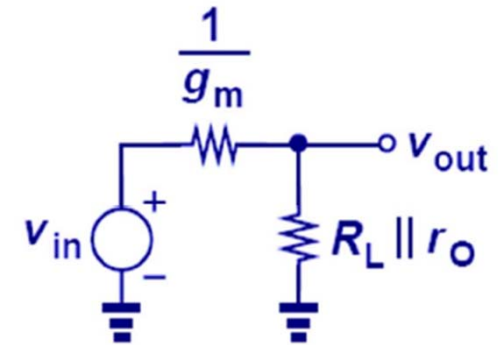


Lect. 6: CMOS Amplifiers (2)

- Source Follower

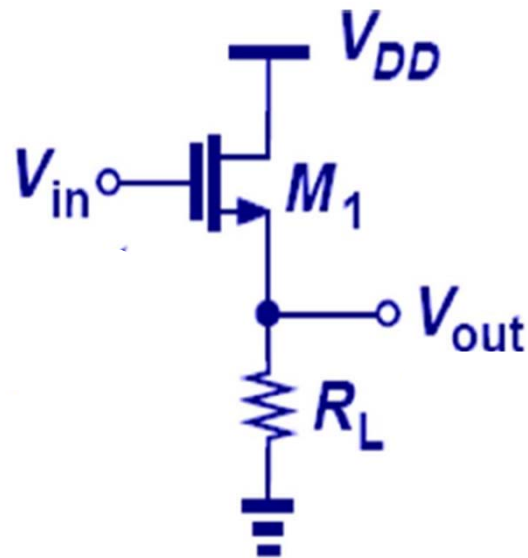

- R_{in} ?

- R_{out} ?

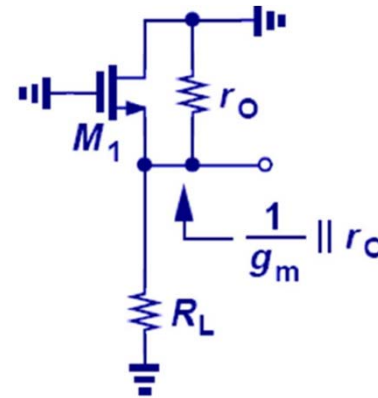


$$R_{out} = \frac{1}{g_m} \parallel r_o \parallel R_L$$

- Large R_{in} , small R_{out}

Is this good for voltage amplifier?

Lect. 6: CMOS Amplifiers (2)

- Model for voltage amplifier

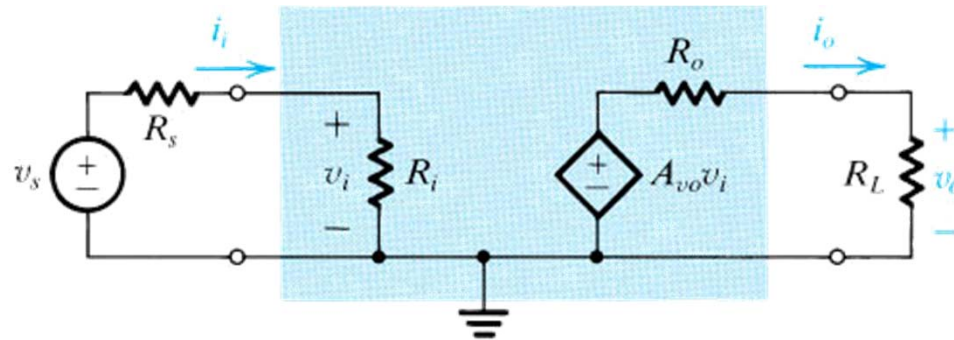


$$v_o = \frac{R_L}{R_L + R_o} A_{vo} v_i = \frac{R_L}{R_L + R_o} A_{vo} \frac{R_i}{R_i + R_s} v_s$$


Voltage amplifier needs large R_{in} and small R_{out}

Lect. 6: CMOS Amplifiers (2)

SF

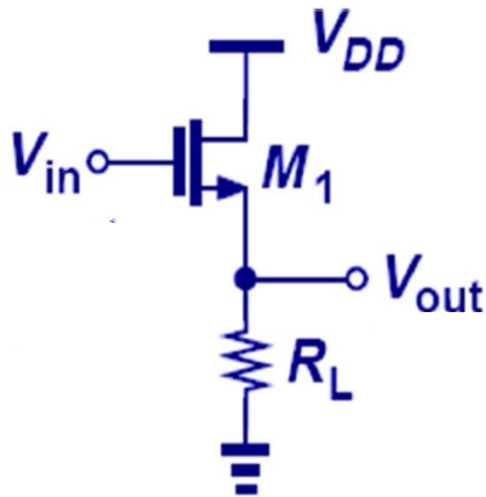

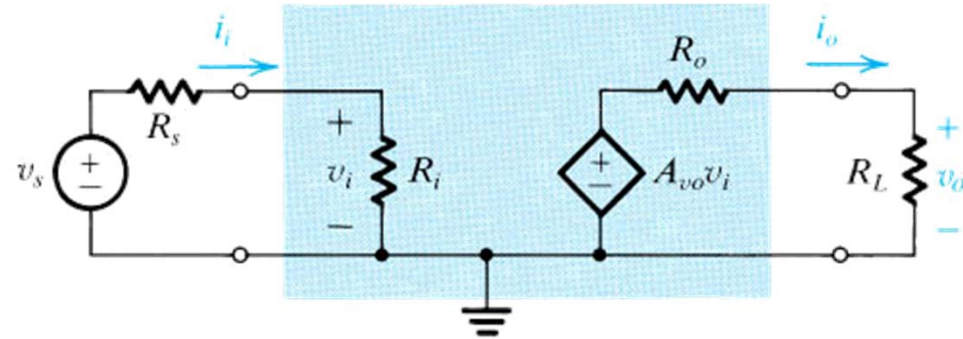$A_v < 1$
 R_{in} : Large
 R_{out} : Small




$$v_o = \frac{R_L}{R_L + R_o} A_{vo} v_i = \frac{R_L}{R_L + R_o} A_{vo} \frac{R_i}{R_i + R_s} v_s \sim v_s$$

Transform output impedance from R_s to R_o
 so that R_L loading can be avoided

→ Voltage buffer

Is this a good voltage amplifier?

Lect. 6: CMOS Amplifiers (2)

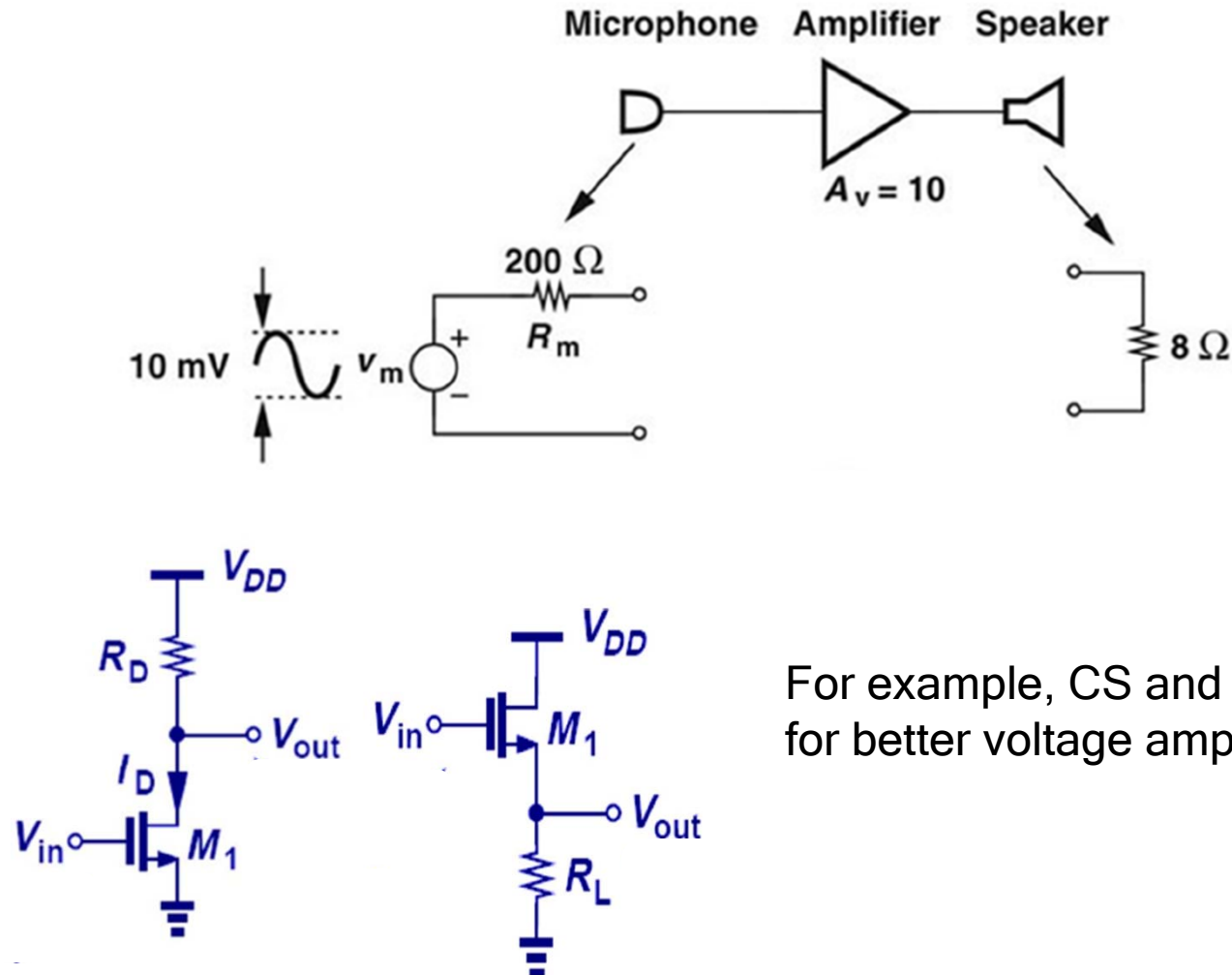

For example, CS and SF can be cascaded for better voltage amplifier performance

Lect. 6: CMOS Amplifiers (2)

- Homework: Prob. 7. 50 in Razavi