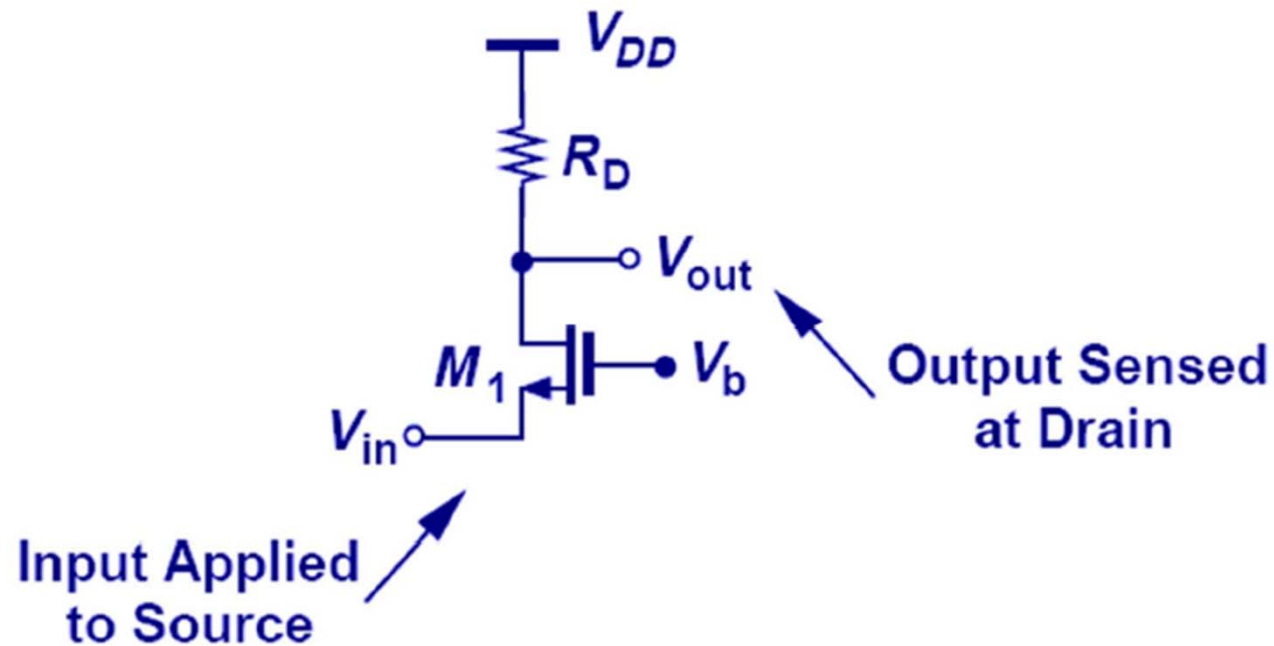



Lect. 7: CMOS Amplifiers (3) (Razavi 7)

- Common-Gate Amplifier




Lect. 7: CMOS Amplifiers (3)

- Common-Gate Amplifier

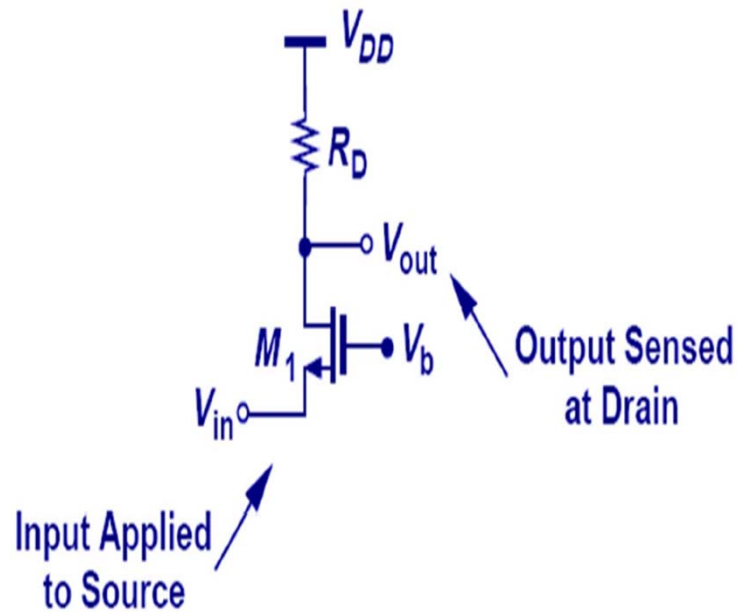

$R_{in} = ?$

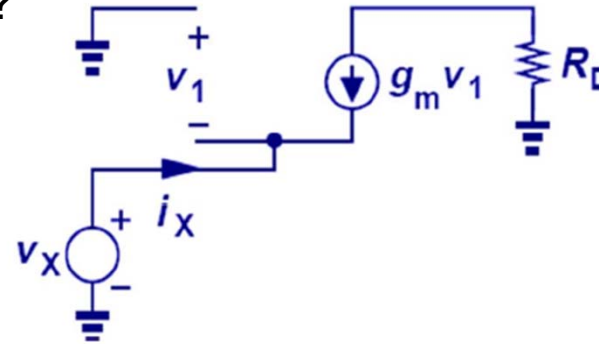


$$R_{in} = \frac{1}{g_m}$$

With r_o ?


$$R_{in} = (1 + R_D/r_o) / (g_m + 1/r_o)$$

Lect. 7: CMOS Amplifiers (3)

- Common-Gate Amplifier

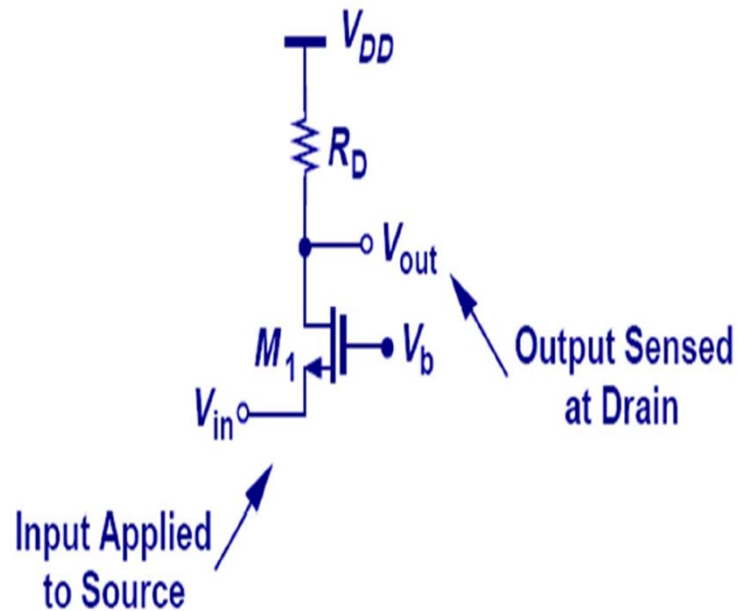

$R_{out} = ?$

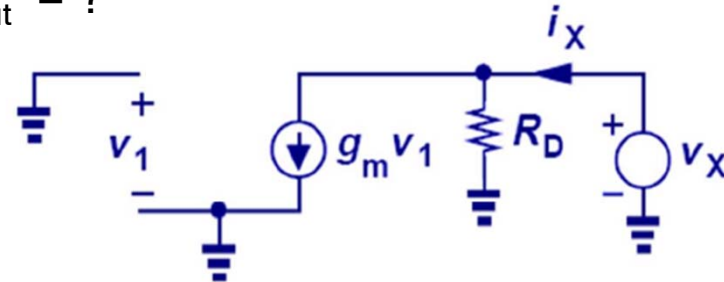

$$R_{out} = R_D$$

With r_o ?


Gain (without r_o)? $A_v = g_m R_D$

Gain (with r_o)?

$$A_v = (g_m R_D + R_D/r_o) / (1 + R_D/r_o)$$


Lect. 7: CMOS Amplifiers (3)

- Common-Gate Amplifier

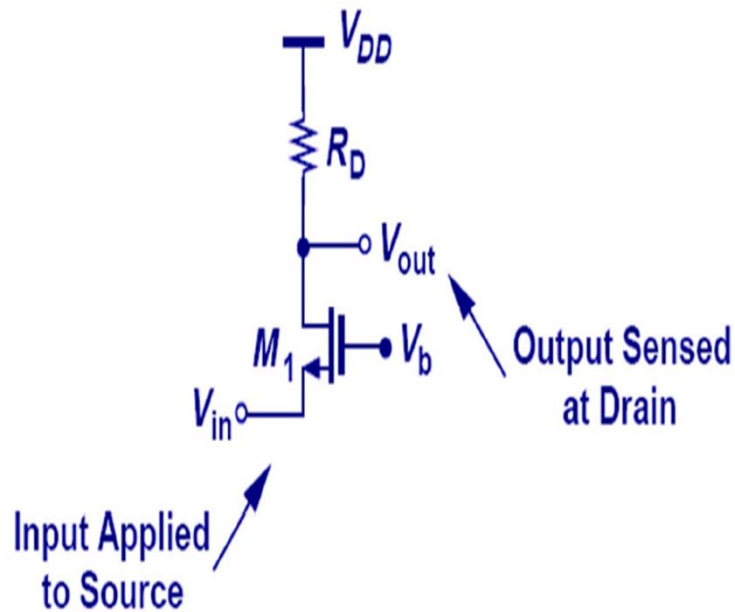


Small R_{in} , Large R_D , Large A_v

- Application for large A_v with small R_{in} ?
- High-frequency amplifiers required R_{in} of 50ohm for impedance matching

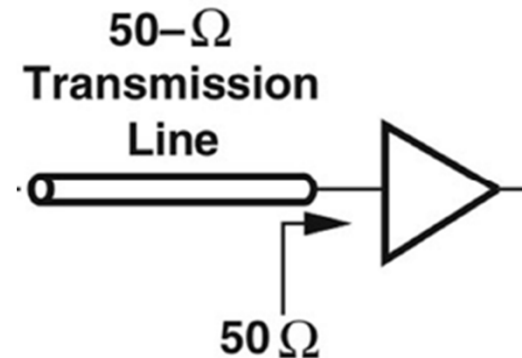


Lect. 7: CMOS Amplifiers (3)

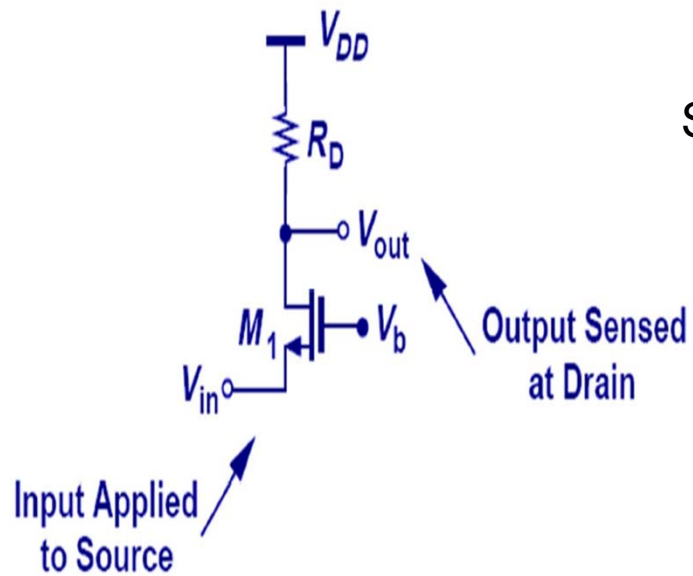

Small R_{in} , Large R_D , Large A_v

- CG as Current Amplifier

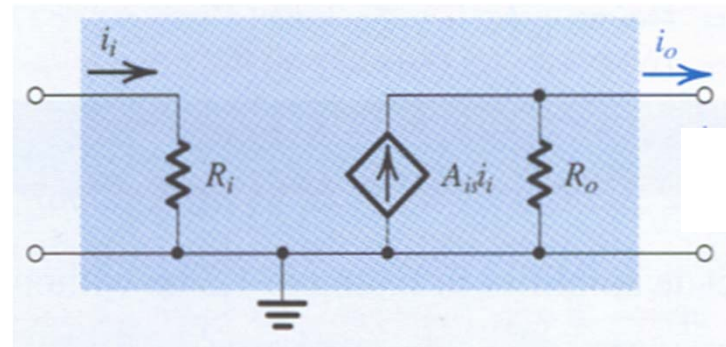Small R_i and large R_o desired for current amplifier





A_{is} : Short-circuit current gain

What is A_{is} for CG? → Current Buffer

Lect. 7: CMOS Amplifiers (3)

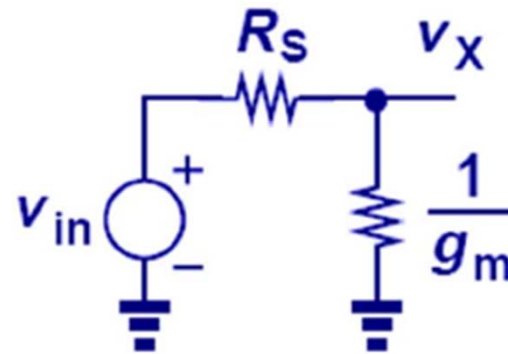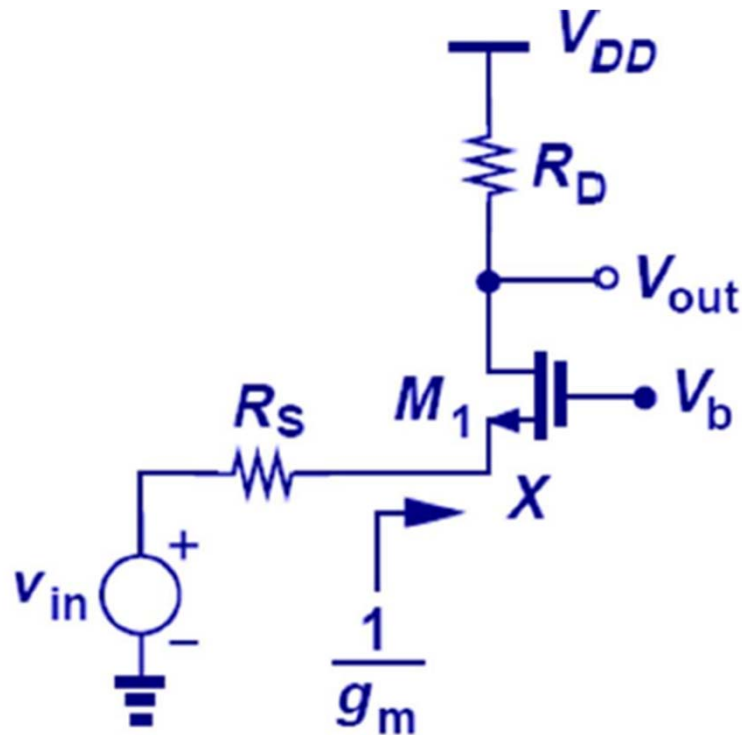- Common-Gate Amplifier with Source Resistance




$$A_v = \frac{R_D}{\frac{1}{g_m} + R_S}$$


- Gain reduction

Lect. 7: CMOS Amplifiers (3)

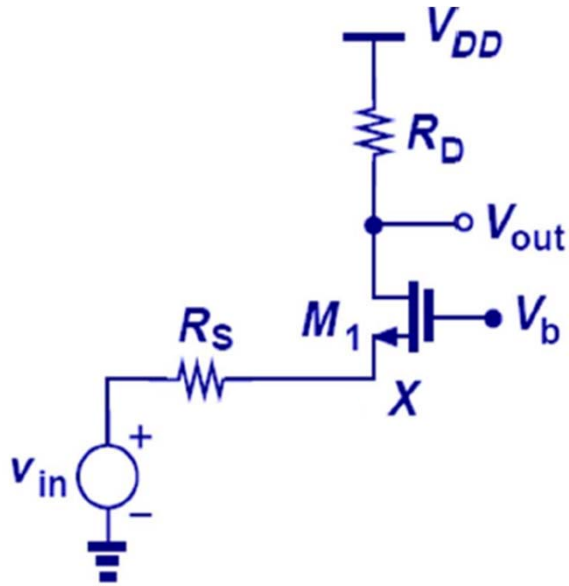- CG with Source Resistance vs CS with Degeneration



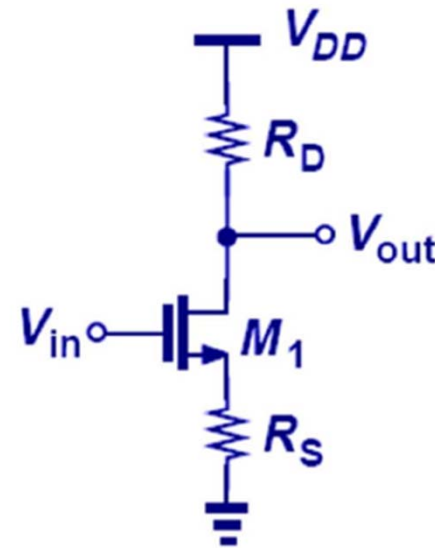
$$A_v = \frac{R_D}{\frac{1}{g_m} + R_S}$$



$$A_v = -\frac{R_D}{\frac{1}{g_m} + R_S}$$

Lect. 7: CMOS Amplifiers (3)


- R_{out} for CG with Source Resistance

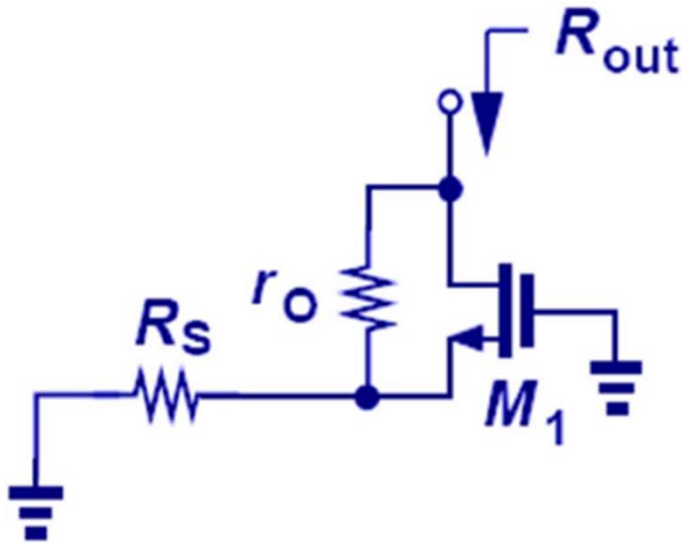

$$R_{out} = (1 + g_m r_o) R_s + r_o$$

Lect. 7: CMOS Amplifiers (3)

- CG with Diode-Connected MOS

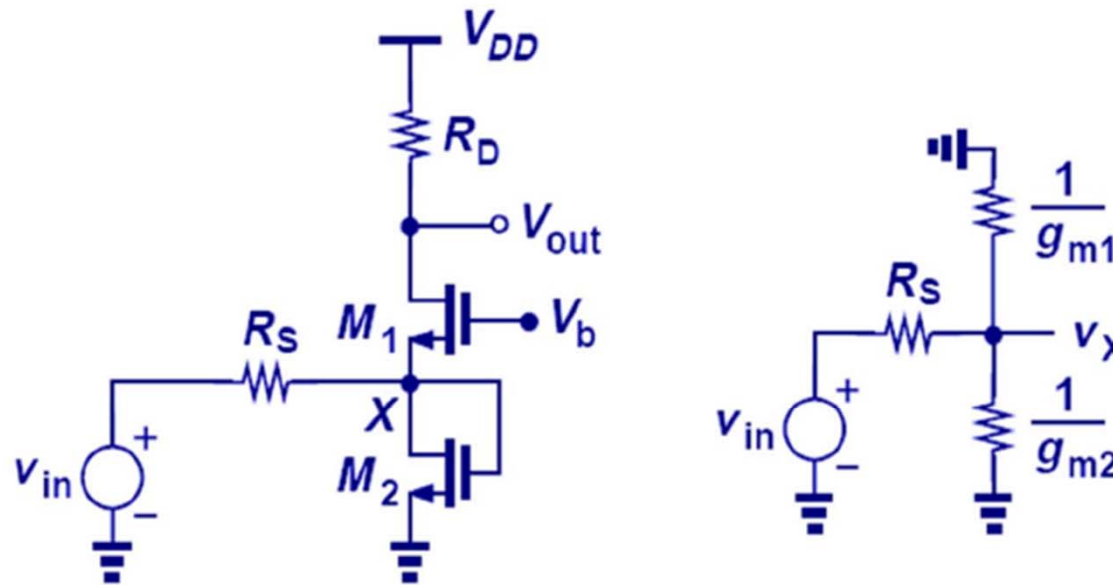

$$\frac{v_{out}}{v_{in}} = \frac{g_{m1} R_D}{1 + (g_{m1} + g_{m2}) R_S}$$

Lect. 7: CMOS Amplifiers (3)

Homework: Determine the voltage gain (assume $\lambda = 0$) and output impedance (assume λ is not zero) for following CG amp.

