
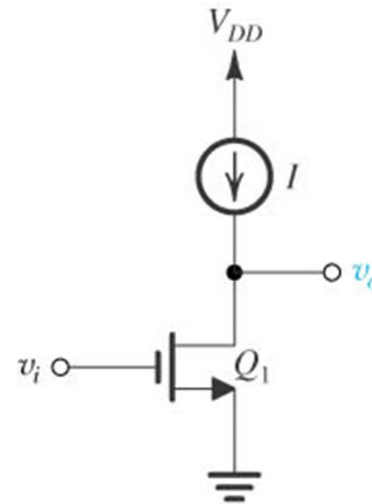


Lect. 8: Current Mirror and Cascode Amplifier

(Razavi 9.1, 9.2)


Various bias techniques for MOS circuits

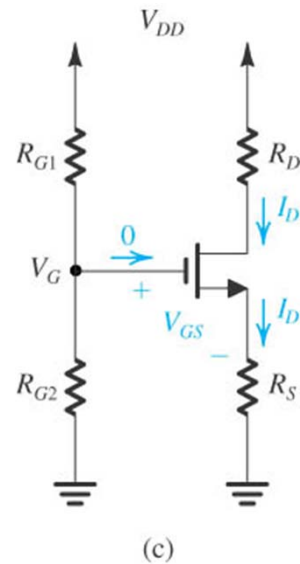

How can we make
a constant current source
with MOS?

Lect. 8: Current Mirror and Cascode Amplifier

Constant current source:

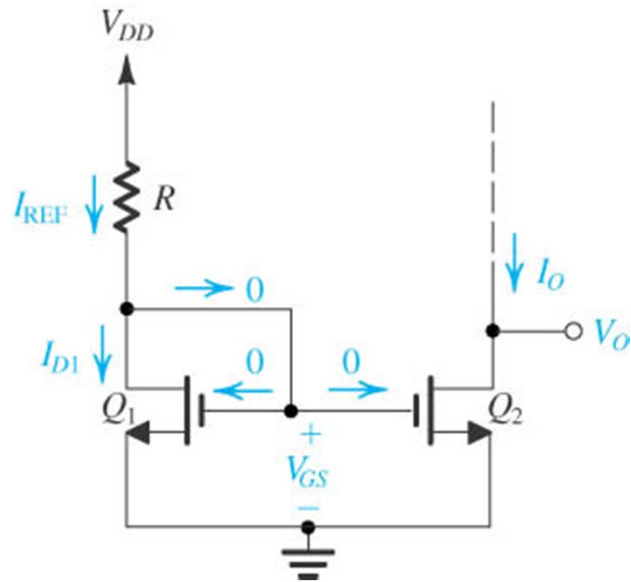

→ Current mirror

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{GS} - V_{TH})^2$$

$$I_{D1} = I_{REF} = \frac{V_{DD} - V_{GS}}{R}$$

$$I_O = I_{D2} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_2 (V_{GS} - V_{TH})^2$$



$$\frac{I_O}{I_{REF}} = \frac{(W/L)_2}{(W/L)_1}$$

Limitation on V_o ? $V_o \geq V_{GS} - V_{TH}$

Lect. 8: Current Mirror and Cascode Amplifier

Mismatches between I_{REF} and I_O

Due to channel-length modulation

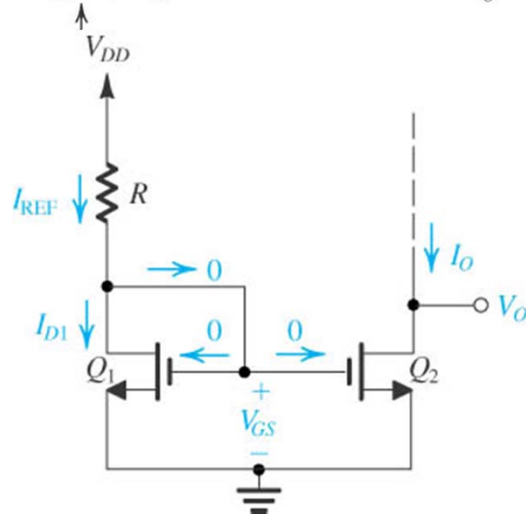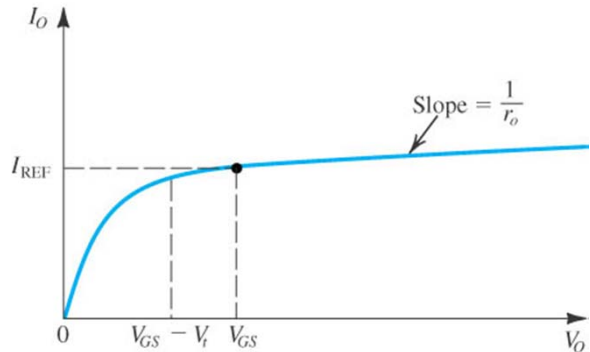

For Q_1 and Q_2


$$I_O = I_{REF} \text{ only if } V_{DS1} = V_{DS2} \rightarrow V_O = V_{GS}$$

As V_O increases, I_O increases from I_{REF}

$$I_O = I_{REF} + \frac{V_O - V_{GS}}{r_o}$$

Lect. 8: Current Mirror and Cascode Amplifier

(Without r_0 consideration)

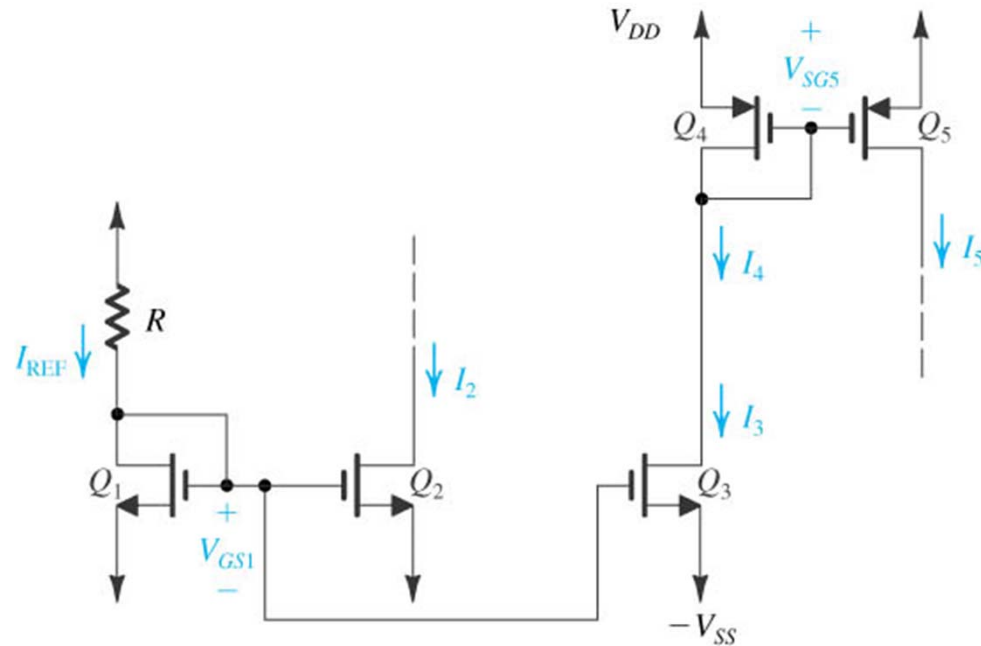

$$I_2 = I_{REF} \frac{(W/L)_2}{(W/L)_1}$$


$$I_3 = I_{REF} \frac{(W/L)_3}{(W/L)_1}$$

$$I_3 = I_4$$

$$I_5 = I_4 \frac{(W/L)_5}{(W/L)_4}$$

Lect. 8: Current Mirror and Cascode Amplifier

CS with Current Source as an active load

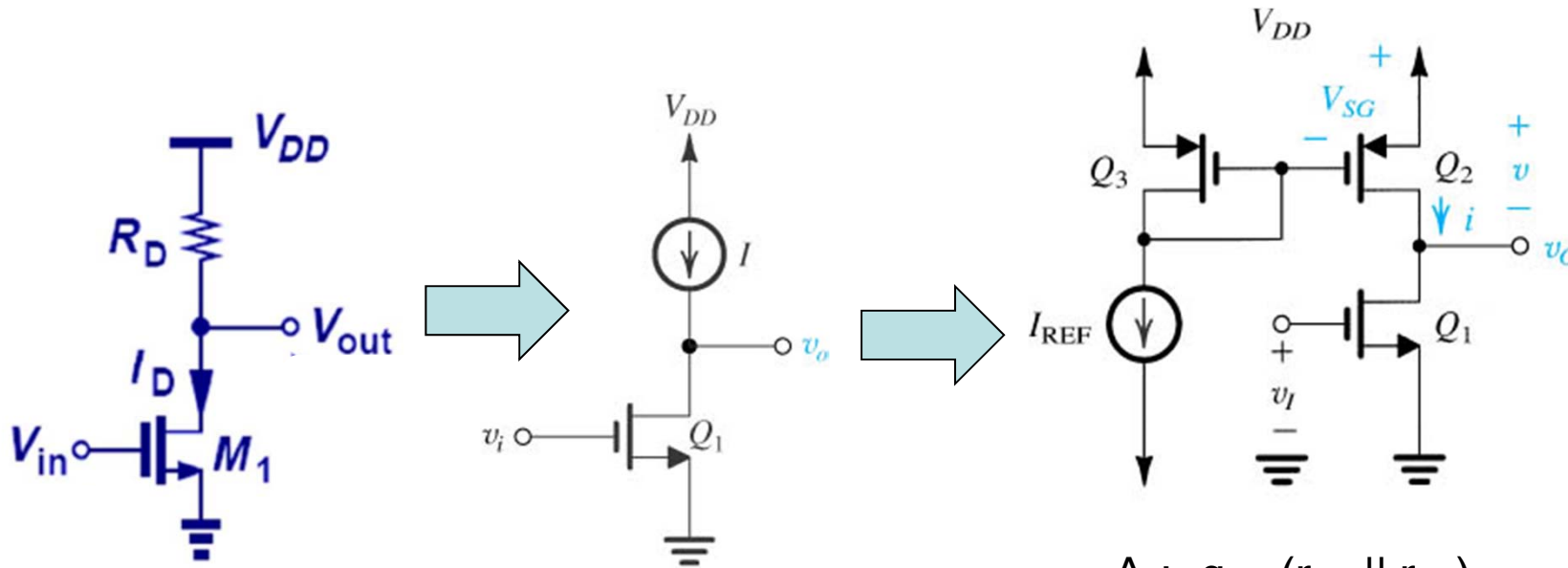


$$A_v: -g_{m1} (r_{O1} \parallel r_{O2})$$

PMOS current mirror provides bias and large resistance (Active Load) as well as bias current!


→ Good for IC!

Lect. 8: Current Mirror and Cascode Amplifier

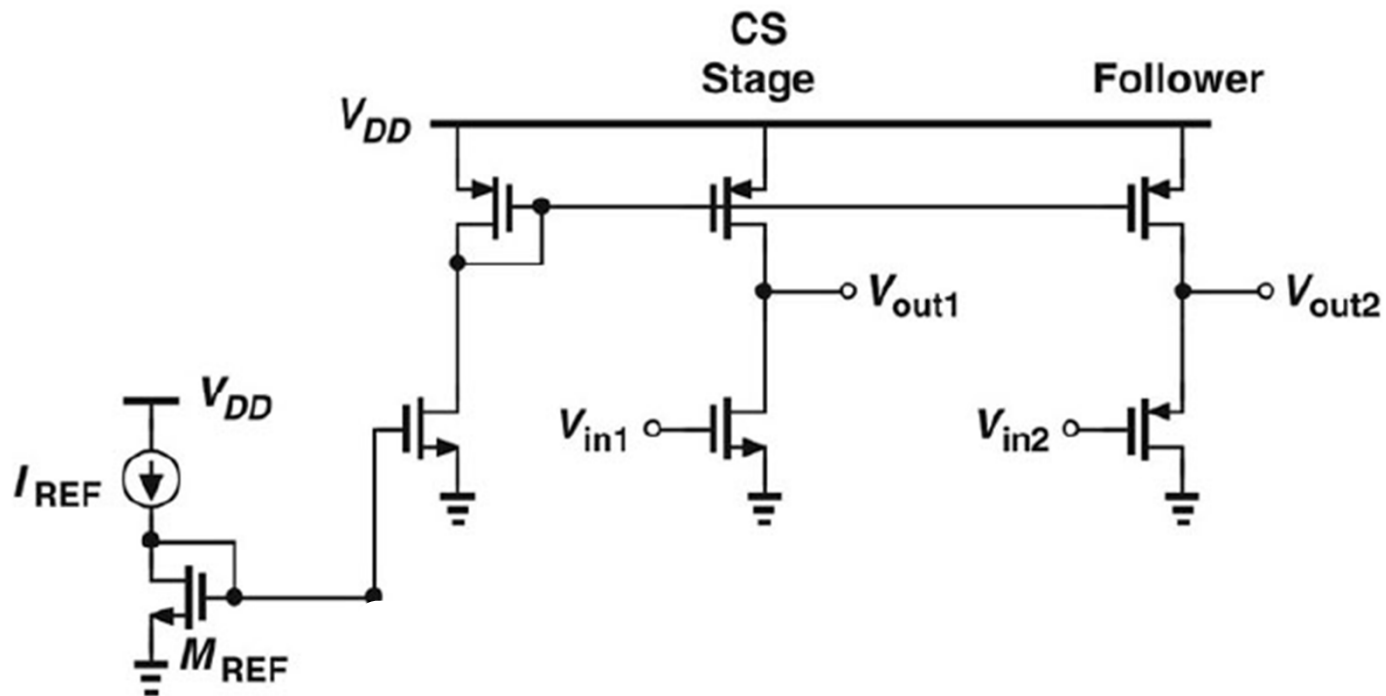

Lect. 8: Current Mirror and Cascode Amplifier


Cascode Amplifier

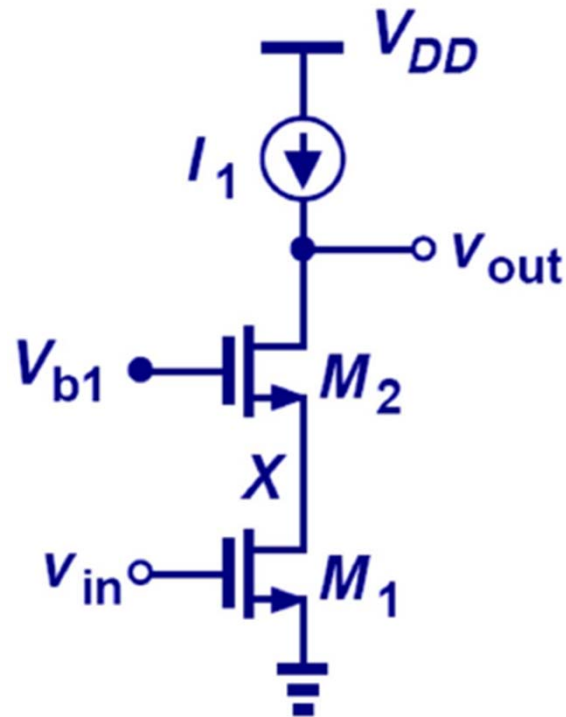

Assume ideal current source for simplicity

- R_{in} ?

- R_{out} ?

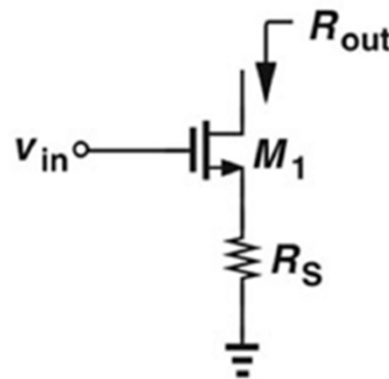

(From CS with Degeneration in Lect 5)

$$R_{out}: (1 + g_m r_O) R_s + r_O$$


$$\rightarrow g_m r_O R_s$$

- R_{out} for cascode: $g_{m2} r_{O2} r_{O1}$


Cascoding MOS transistors enhances impedance by factor of $g_m r_O$

Lect. 8: Current Mirror and Cascode Amplifier

A_v for Cascode Amplifier

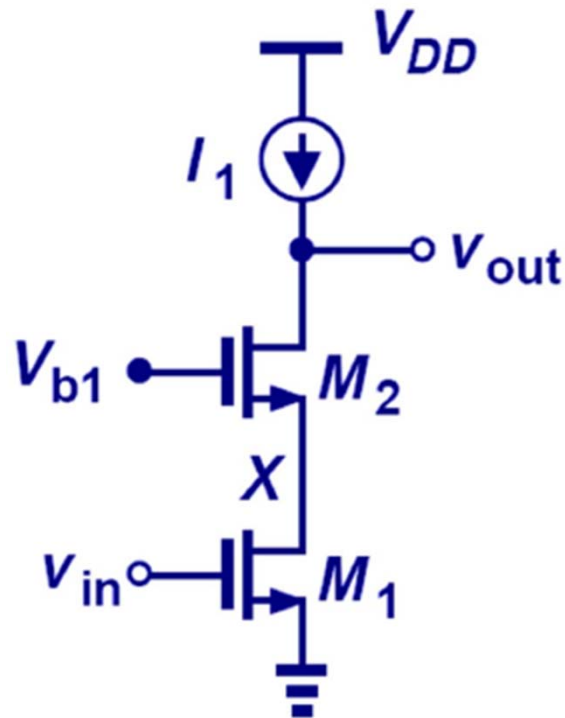

- Can be viewed as CS+CG

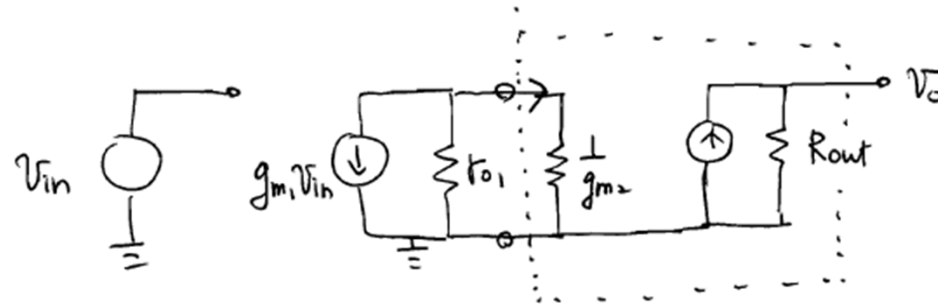

$$A_v : - g_{m1} g_{m2} r_{O2} r_{O1}$$


→ Effectively CS amplifier with $R_{out} = g_{m2} r_{O2} r_{O1}$

Larger gain or faster for the same gain

Less V_{out} range

Lect. 8: Current Mirror and Cascode Amplifier

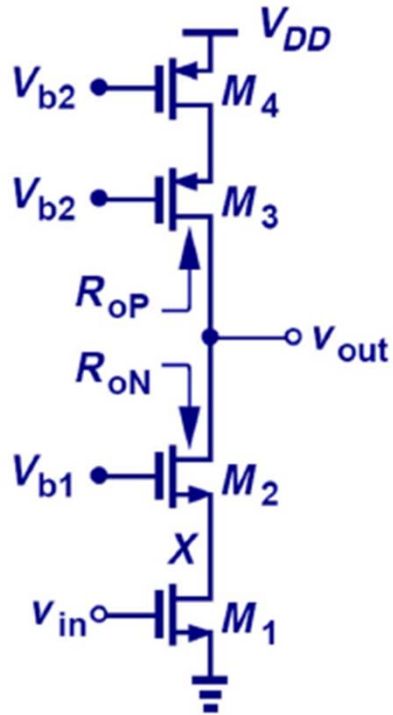With cascoded PMOS transistors for the current source



$$R_{on} \approx g_{m2} r_{O2} r_{O1}$$


$$R_{op} \approx g_{m3} r_{O3} r_{O4}$$

$$A_V : - g_{m1} (g_{m2} r_{O2} r_{O1} \parallel g_{m3} r_{O3} r_{O4})$$


Lect. 8: Current Mirror and Cascode Amplifier

Homework(1)

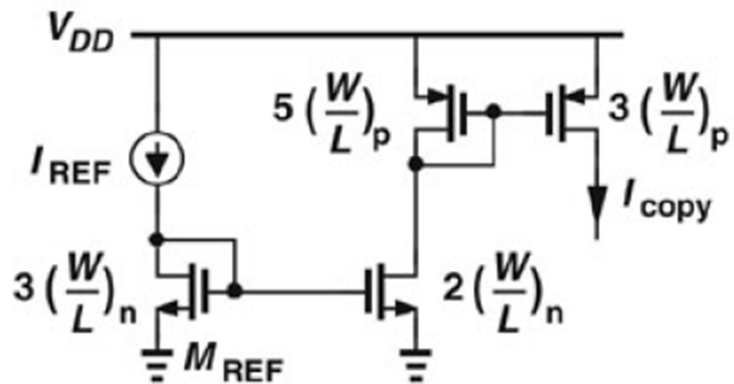Determine I_{copy} in following circuits. Assume all MOS transistors are in saturation and the influence of r_0 can be ignored.



(a)

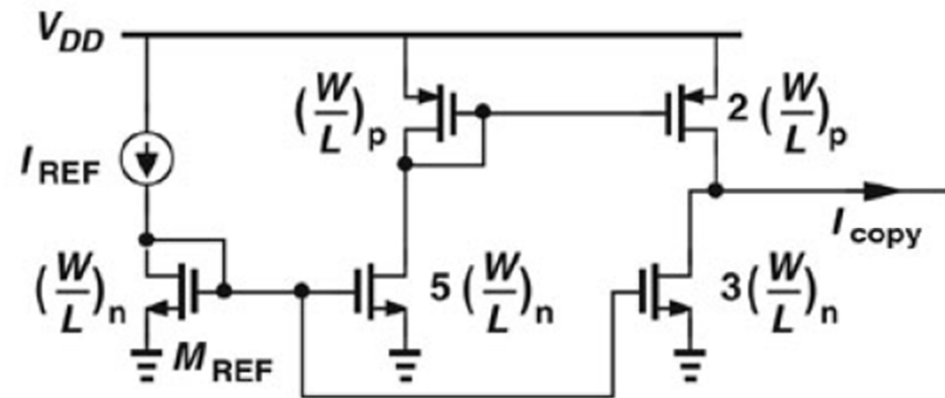

(b)

Lect. 8: Current Mirror and Cascode Amplifier

Homework(2)

Determine the output impedance of circuits shown below. All transistors are in saturation and $g_m r_O \gg 1$

